

## Boost Converter Operated in CCM

Christophe Basso - Switch Mode Power Supplies: SPICE Simulations and Practical Designs  
Second Edition - January 2014

### 1) Input data

$$V_{in} := 2.7 \text{ V} \quad L_1 := 5 \text{ } \mu\text{H} \quad T_{sw} := 1 \text{ } \mu\text{s} \quad R_{load} := 5 \text{ } \Omega \quad V_{out} := 5 \text{ V} \quad \eta := 100\%$$

### 2) Calculations

$$F_{sw} := \frac{1}{T_{sw}} = 1 \text{ MHz}$$

Beyond this load value, the converter operates in DCM:  $R_{crit} := \frac{2 \cdot L_1 \cdot F_{sw} \cdot V_{out}^2}{\left(1 - \frac{V_{in}}{V_{out}}\right) \cdot V_{in}^2} = 74.551 \text{ } \Omega$

$$P_{out} := \frac{V_{out}^2}{\eta \cdot R_{load}} = 5 \text{ W} \quad D_{boost} := \frac{V_{out} - V_{in}}{V_{out}} = 0.46$$

$$I_{outboost} := \frac{P_{out}}{V_{out}} = 1 \text{ A} \quad R_{loadboost} := \frac{V_{out}^2}{P_{out}} = 5 \text{ } \Omega \quad M_{boost} := \frac{V_{out}}{V_{in}} = 1.852$$

$$I_{pboost} := \frac{P_{out}}{V_{in}} + \frac{V_{in}}{2 \cdot L_1} \cdot D_{boost} \cdot T_{sw} = 1.976 \text{ A}$$

$$I_{vpboost} := \frac{P_{out}}{V_{in}} - \frac{V_{in}}{2 \cdot L_1} \cdot D_{boost} \cdot T_{sw} = 1.728 \text{ A}$$

$$\Delta I_{Lboost} := \frac{V_{in}}{L_1} \cdot D_{boost} \cdot T_{sw} = 0.248 \text{ A}$$

$$\tau_L := \frac{L_1}{R_{loadboost} \cdot T_{sw}} = 1$$

### 2.1) Inductor rms current

$$I_{LCCM} := \sqrt{\frac{P_{out}^2}{V_{in}^2} + \frac{\Delta I_{Lboost}^2}{12}} = 1.853 \text{ A}$$

$$\sqrt{\frac{P_{out}^2}{V_{in}^2} + \left(\frac{D_{boost} \cdot T_{sw} \cdot V_{in}}{L_1}\right)^2 \cdot \frac{1}{12}} = 1.853 \text{ A}$$

$$I_{outboost} \cdot \sqrt{\frac{1}{(1-D_{boost})^2} + \frac{D_{boost}^2 \cdot (1-D_{boost})^2 \cdot R_{loadboost}^2}{12 \cdot F_{sw}^2 \cdot L_1^2}} = 1.853 \text{ A}$$

$$\frac{V_{out}}{R_{loadboost}} \cdot \sqrt{\frac{1}{(1-D_{boost})^2} + \frac{1}{3} \cdot \left(\frac{1}{2 \cdot \tau_L}\right)^2 \cdot (D_{boost}^2 \cdot (1-D_{boost})^3)} = 1.853 \text{ A}$$

## 2.2) Switch rms current

$$I_{SWCCM} := \sqrt{D_{boost} \cdot \left(\frac{P_{out}^2}{V_{in}^2} + \frac{\Delta I_{Lboost}^2}{12}\right)} = 1.257 \text{ A}$$

$$\frac{\sqrt{\frac{D_{boost}^3 \cdot T_{sw}^2 \cdot V_{in}^4 + 12 \cdot D_{boost} \cdot L_1^2 \cdot P_{out}^2}{L_1^2 \cdot V_{in}^2}}}{2 \cdot \sqrt{3}} = 1.257 \text{ A}$$

$$I_{outboost} \cdot \sqrt{\frac{D_{boost}}{(1-D_{boost})^2} + \frac{D_{boost}^3 \cdot (1-D_{boost})^2 \cdot R_{loadboost}^2}{12 \cdot F_{sw}^2 \cdot L_1^2}} = 1.257 \text{ A}$$

$$\frac{V_{out}}{R_{loadboost}} \cdot \sqrt{\frac{D_{boost}}{(1-D_{boost})^2} + \frac{1}{3} \cdot \left(\frac{1}{2 \cdot \tau_L}\right)^2 \cdot (D_{boost}^2 \cdot (1-D_{boost})^3)} = 1.257 \text{ A}$$

## 2.3) Diode rms current

$$I_{DCCM} := \sqrt{(1-D_{boost}) \cdot \left(\frac{P_{out}^2}{V_{in}^2} + \frac{\Delta I_{Lboost}^2}{12}\right)} = 1.362 \text{ A}$$

$$\frac{\sqrt{(1-D_{boost}) \cdot (D_{boost}^2 \cdot T_{sw}^2 \cdot V_{in}^4 + 12 \cdot L_1^2 \cdot P_{out}^2)}}{L_1^2 \cdot V_{in}^2}}{2 \cdot \sqrt{3}} = 1.362 \text{ A}$$

$$I_{outboost} \cdot \sqrt{\frac{1}{(1-D_{boost})} + \frac{D_{boost}^2 \cdot (1-D_{boost})^3 \cdot R_{loadboost}^2}{12 \cdot F_{sw}^2 \cdot L_1^2}} = 1.362 \text{ A}$$

$$\frac{V_{out}}{R_{loadboost}} \cdot \sqrt{\frac{1}{(1-D_{boost})} + \frac{1}{3} \cdot \left(\frac{1}{2 \cdot \tau_L}\right)^2 \cdot (D_{boost}^2 \cdot (1-D_{boost})^3)} = 1.362 \text{ A}$$

## 2.4) Output capacitor rms current

$$I_{CCM} := \sqrt{(1 - D_{boost}) \cdot \left( \frac{P_{out}^2}{V_{in}^2} + \frac{\Delta I_{L_{boost}}^2}{12} \right) - I_{outboost}^2} = 0.924 \text{ A}$$

$$\sqrt{\frac{(1 - D_{boost}) \cdot (D_{boost}^2 \cdot T_{sw}^2 \cdot V_{in}^4 + 12 \cdot L_1^2 \cdot P_{out}^2)}{12 \cdot L_1^2 \cdot V_{in}^2} - I_{outboost}^2} = 0.924 \text{ A}$$

$$I_{outboost} \cdot \sqrt{\frac{D_{boost}}{1 - D_{boost}} + \frac{D_{boost}^2 \cdot (1 - D_{boost})^3 \cdot R_{loadboost}^2}{12 \cdot F_{sw}^2 \cdot L_1^2}} = 0.924 \text{ A}$$

$$\frac{V_{out}}{R_{loadboost}} \cdot \sqrt{\frac{D_{boost}}{1 - D_{boost}} + \frac{D_{boost}^2 \cdot (1 - D_{boost})}{12} \cdot \left( \frac{1 - D_{boost}}{\tau_L} \right)^2} = 0.924 \text{ A}$$

## 2.5) Input capacitor rms current

$$I_{CinRMS} := \sqrt{I_{LCCM}^2 - (M_{boost} \cdot I_{outboost})^2} = 71.707 \text{ mA}$$

## Boost Converter Operated in DCM

Christophe Basso - Switch Mode Power Supplies: SPICE Simulations and Practical Designs  
Second Edition - January 2014

### 3) Input data

$$V_{in} := 10 \text{ V} \quad L_1 := 2.8 \text{ } \mu\text{H} \quad T_{sw} := 10 \text{ } \mu\text{s} \quad R_{loadboostDCM} := 6 \text{ } \Omega \quad V_{outbDCM} := 12 \text{ V} \quad \eta := 100\%$$

### 4) Calculations

$$F_{sw} := \frac{1}{T_{sw}} = 100 \text{ kHz}$$

Below this load value, the converter operates in DCM:  $R_{crit} := \frac{2 \cdot L_1 \cdot F_{sw} \cdot V_{outbDCM}^2}{\left(1 - \frac{V_{in}}{V_{outbDCM}}\right) \cdot V_{in}^2} = 4.838 \text{ } \Omega$

$$P_{outbDCM} := \frac{V_{outbDCM}^2}{\eta \cdot R_{loadboostDCM}} = 24 \text{ W}$$

$$I_{outboostDCM} := \frac{V_{outbDCM}}{R_{loadboostDCM}} = 2 \text{ A}$$

$$\tau_L := \frac{L_1}{R_{loadboostDCM} \cdot T_{sw}} = 0.047$$

$$M_{dcm} := \frac{V_{outbDCM}}{V_{in}} = 1.2$$

$$I_{pboostDCM} := \frac{T_{sw} \cdot (V_{outbDCM} - V_{in}) \cdot \sqrt{\frac{2 \cdot L_1 \cdot P_{outbDCM} \cdot V_{outbDCM}}{T_{sw} \cdot (V_{outbDCM} - V_{in})}}}{L_1 \cdot V_{outbDCM}} = 5.345 \text{ A}$$

$$D_1 := \frac{(V_{outbDCM} - V_{in}) \cdot \sqrt{\frac{2 \cdot L_1 \cdot P_{outbDCM} \cdot V_{outbDCM}}{T_{sw} \cdot (V_{outbDCM} - V_{in})}}}{V_{in} \cdot V_{outbDCM}} = 0.15 \quad \text{then } t_{on} := D_1 \cdot T_{sw} = 1.497 \text{ } \mu\text{s}$$

$$D_2 := \frac{\sqrt{\frac{2 \cdot L_1 \cdot P_{outbDCM} \cdot V_{outbDCM}}{T_{sw} \cdot (V_{outbDCM} - V_{in})}}}{V_{outbDCM}} = 0.748 \quad \text{then } t_{off} := D_2 \cdot T_{sw} = 7.483 \text{ } \mu\text{s}$$

$$D_3 := \frac{V_{in} - \sqrt{\frac{2 \cdot L_1 \cdot P_{outbDCM} \cdot V_{outbDCM}}{T_{sw} \cdot (V_{outbDCM} - V_{in})}}}{V_{in}} = 0.102 \quad \text{then } DT := D_3 \cdot T_{sw} = 1.02 \text{ } \mu\text{s}$$

We verify  $D_1 + D_2 + D_3 = 1$

#### 4.1) Inductor rms current

$$I_{Lrms} := I_{pboostDCM} \cdot \sqrt{\frac{1 - D_3}{3}} = 2.924 \text{ A}$$

$$I_{LboostDCMRMS} := \sqrt{\frac{2 \cdot P_{outbDCM} \cdot T_{sw} \cdot (V_{outbDCM} - V_{in}) \cdot \sqrt{\frac{2 \cdot L_1 \cdot P_{outbDCM} \cdot V_{outbDCM}}{T_{sw} \cdot (V_{outbDCM} - V_{in})}}}{3 \cdot L_1 \cdot V_{in} \cdot V_{outbDCM}}} = 2.924 \text{ A}$$

$$I_{LboostDCMRMS2} := I_{outboostDCM} \cdot \sqrt{\frac{2 \cdot D_1 \cdot R_{loadboostDCM}}{3 \cdot F_{sw} \cdot L_1}} = 2.924 \text{ A}$$

$$\frac{V_{outbDCM}}{R_{loadboostDCM}} \cdot \sqrt{\frac{2 \cdot D_1}{3 \cdot \tau_L}} = 2.924 \text{ A}$$

#### 4.2) Switch rms current

$$I_{SWboostDCMRMS} := I_{pboostDCM} \cdot \sqrt{\frac{D_1}{3}} = 1.194 \text{ A}$$

$$I_{SWboostDCMRMS2} := \frac{(V_{outbDCM} - V_{in})}{V_{outbDCM}} \cdot \sqrt{\frac{2 \cdot P_{outbDCM} \cdot T_{sw} \cdot \sqrt{\frac{2 \cdot L_1 \cdot P_{outbDCM} \cdot V_{outbDCM}}{T_{sw} \cdot (V_{outbDCM} - V_{in})}}}{3 \cdot L_1 \cdot V_{in}}} = 1.194 \text{ A}$$

$$I_{SWboostDCMRMS3} := I_{outboostDCM} \cdot \frac{1}{\sqrt{3 \cdot D_1}} \cdot \left( \sqrt{1 + \frac{2 \cdot D_1^2 \cdot R_{loadboostDCM}}{L_1 \cdot F_{sw}}} - 1 \right) = 1.194 \text{ A}$$

$$\frac{V_{outbDCM}}{R_{loadboostDCM}} \cdot \frac{\sqrt{1 + \frac{2 \cdot D_1^2}{\tau_L}} - 1}{\sqrt{3 \cdot D_1}} = 1.194 \text{ A}$$

$$I_{SWboostDCMRMS4} := I_{Lrms} \cdot \sqrt{\frac{D_1}{1 - D_3}} = 1.194 \text{ A}$$

### 4.3) Diode rms current

$$I_{diodeboostDCMRMS} := I_{pboostDCM} \cdot \sqrt{\frac{D_2}{3}} = 2.67 \text{ A}$$

$$I_{diodeboostDCMRMS2} := \frac{1}{V_{outbDCM}} \cdot \sqrt{\frac{2 \cdot P_{outbDCM} \cdot T_{sw} \cdot (V_{outbDCM} - V_{in}) \cdot \sqrt{\frac{2 \cdot L_1 \cdot P_{outbDCM} \cdot V_{outbDCM}}{T_{sw} \cdot (V_{outbDCM} - V_{in})}}}{3 \cdot L_1}} = 2.67 \text{ A}$$

$$I_{diodeboostDCMRMS3} := I_{outboostDCM} \cdot \sqrt{\frac{2}{3 \cdot D_1}} \cdot \left( \sqrt{1 + \frac{2 \cdot D_1^2 \cdot R_{loadboostDCM}}{L_1 \cdot F_{sw}}} - 1 \right) = 2.67 \text{ A}$$

$$I_{diodeboostDCMRMS4} := I_{outboostDCM} \cdot \left( \sqrt{\frac{2}{3} \cdot \frac{\left( \sqrt{1 + \frac{2 \cdot D_1^2}{\tau_L}} - 1 \right)}{D_1}} \right) = 2.67 \text{ A}$$

$$I_{diodeboostDCMRMS5} := I_{Lrms} \cdot \sqrt{\frac{D_2}{1 - D_3}} = 2.67 \text{ A}$$

### 4.4) Output capacitor rms current

$$I_{CoutRMS1} := \sqrt{\left( \frac{2 \cdot P_{outbDCM} \cdot T_{sw} \cdot (V_{outbDCM} - V_{in}) \cdot \sqrt{\frac{2 \cdot L_1 \cdot P_{outbDCM} \cdot V_{outbDCM}}{T_{sw} \cdot (V_{outbDCM} - V_{in})}}}{3 \cdot L_1 \cdot V_{outbDCM}^2} \right) - I_{outboostDCM}^2} = 1.768 \text{ A}$$

$$I_{CoutRMS2} := I_{outboostDCM} \cdot \sqrt{\frac{2}{3 \cdot D_1} \cdot \left( \sqrt{1 + \frac{2 \cdot D_1^2 \cdot R_{loadboostDCM}}{L_1 \cdot F_{sw}}} - 1 \right) - 1} = 1.768 \text{ A}$$

$$I_{outboostDCM} \cdot \left( \sqrt{\frac{2}{3} \cdot \frac{\left( \sqrt{1 + \frac{2 \cdot D_1^2}{\tau_L}} - 1 \right)}{D_1}} - 1 \right) = 1.768 \text{ A}$$

**4.5) Input capacitor rms current**

$$I_{CinRMS} := \sqrt{I_{LboostDCMRMS}^2 - (M_{dcm} \cdot I_{outboostDCM})^2} = 1.671 \text{ A}$$