

Borderline PFC Small-Signal Parameters Calculations

Christophe Basso - Switch Mode Power Supplies: SPICE Simulations and Practical Designs
Second Edition - January 2014

1) Input data

$$G_{PWM} := 6.8 \frac{\mu s}{V} \quad V_{ac} := 100 V \quad V_{err} := 1.647 V \quad L_1 := 350 \mu H \quad V_{out} := 400 V$$

$$t_{on} := V_{err} \cdot G_{PWM} = 11.2 \mu s \quad P_{out} := \frac{V_{ac}^2}{2 \cdot L_1} \cdot G_{PWM} \cdot V_{err} = 159.994 W \quad C_{out} := 180 \mu F$$

$$k_{div} := 0.0078 \quad k_{mul} := 0.6 \frac{1}{V} \quad R_i := 0.24 \Omega \quad R_{load} := \frac{V_{out}^2}{P_{out}} = 1 k\Omega \quad P_{in} := P_{out}$$

From José Cappilla

$$Start_Freq_{log} := -2$$

$$Stop_Freq_{log} := 3$$

$$Points_per_decade := 200$$

$$Number_of_decades := Stop_Freq_{log} - Start_Freq_{log} = 5$$

$$Number_of_points := Number_of_decades \cdot Points_per_decade + 1 = 1001$$

$$k := 0 .. Number_of_points$$

$$f_k := 10^{Start_Freq_{log} + k \cdot \frac{Number_of_decades}{Number_of_points}} \cdot Hz \quad \omega_k := 2 \cdot \pi \cdot f_k$$

2) Voltage mode

$$\frac{d}{dV_{out}} \left(\frac{V_{ac}^2}{2 \cdot L_1} \cdot \frac{G_{PWM} \cdot V_{err}}{V_{out}} \right) \rightarrow -\frac{0.00099996428571428571431 \cdot \mu s}{\mu H} = -10 \cdot 10^{-4} \frac{1}{\Omega}$$

$$\frac{d}{dV_{err}} \left(\frac{V_{ac}^2}{2 \cdot L_1} \cdot \frac{G_{PWM} \cdot V_{err}}{V_{out}} \right) \rightarrow \frac{0.24285714285714285714 \cdot \mu s}{\mu H} = 0.243 \frac{1}{\Omega}$$

$$\text{Gain dc: } H_{0VM} := \frac{R_{load} \cdot G_{PWM} \cdot V_{ac}^2}{4 \cdot L_1 \cdot V_{out}} = 121.433$$

$$\text{Gain dc in dB: } H_{0VMdB} := 20 \cdot \log \left(\frac{R_{load} \cdot G_{PWM} \cdot V_{ac}^2}{4 \cdot L_1 \cdot V_{out}} \right) = 41.687$$

$$f_{p1} := \frac{1}{\pi \cdot R_{load} \cdot C_{out}} = 1.768 Hz$$

$$f_{po} := \frac{G_{PWM} \cdot V_{ac}^2}{2 \cdot L_1 \cdot V_{out}} \cdot \frac{1}{2 \cdot \pi \cdot C_{out}} = 214.733 Hz$$



Borderline PFC Small-Signal Parameters Calculations

$$t_{on} := \frac{P_{in}}{V_{ac}^2} \cdot 2 \cdot L_1 = 11.2 \mu s$$

$$I_{peak} := \frac{V_{ac} \cdot \sqrt{2}}{L_1} \cdot t_{on} = 4.525 A$$

Resistive loading: $H_1(s) := H_{OVM} \cdot \frac{1}{1 + \frac{s}{2 \cdot \pi \cdot f_{p1}}}$

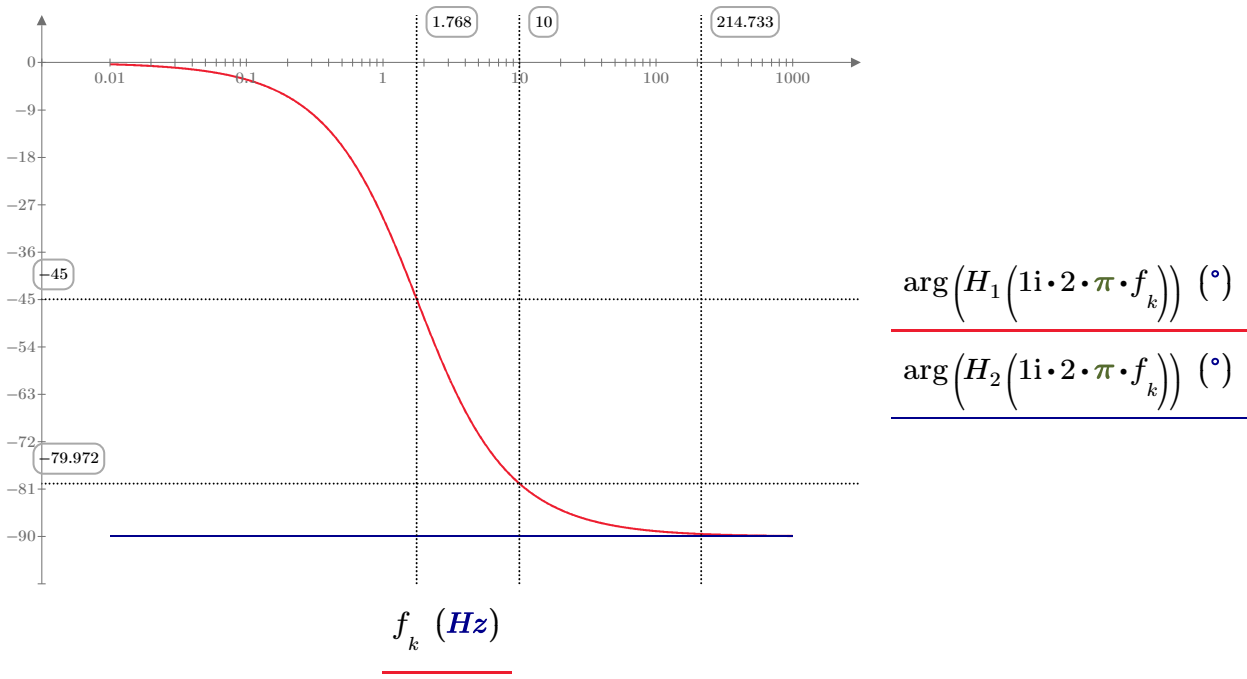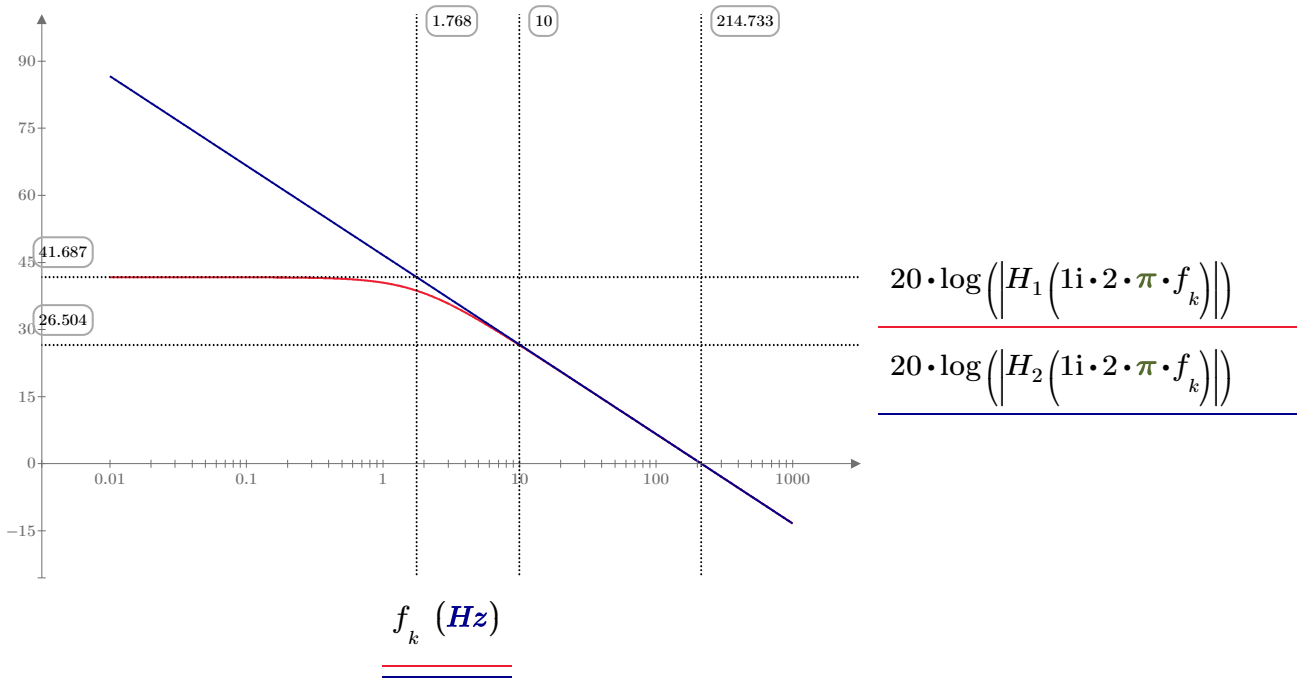SMPS loading: $H_2(s) := \frac{1}{\frac{s}{f_{po} \cdot 2 \cdot \pi}}$



selected crossover frequency: $f_c := 10 \text{ Hz}$

$$20 \cdot \log(|H_1(1i \cdot 2 \cdot \pi \cdot f_c)|) = 26.504 \quad \arg(H_1(1i \cdot 2 \cdot \pi \cdot f_c)) = -79.972^\circ$$

$$20 \cdot \log\left(\frac{H_{0VM}}{\sqrt{1 + \left(\frac{f_c}{f_{p1}}\right)^2}}\right) = 26.504 \quad -\text{atan}\left(\frac{f_c}{f_{p1}}\right) = -79.972^\circ$$

$$20 \cdot \log(|H_2(1i \cdot 2 \cdot \pi \cdot f_c)|) = 26.638 \quad \arg(H_2(1i \cdot 2 \cdot \pi \cdot f_c)) = -90^\circ$$

$$20 \cdot \log\left(\frac{f_{po}}{f_c}\right) = 26.638$$

$$f_{po} := f_{p1} \cdot \sqrt{H_{0VM} - 1} \cdot \sqrt{H_{0VM} + 1} = 214.726 \text{ Hz}$$

3) Current mode

$$\frac{d}{dV_{out}} \left(\frac{V_{ac}^2}{2} \cdot \frac{k_{div} \cdot k_{mul} \cdot V_{err}}{R_i \cdot V_{out}} \right) \rightarrow \frac{0.001003640625}{\Omega} = -0.001 \frac{1}{\Omega}$$

$$\frac{d}{dV_{err}} \left(\frac{V_{ac}^2}{2} \cdot \frac{k_{div} \cdot k_{mul} \cdot V_{err}}{R_i \cdot V_{out}} \right) \rightarrow \frac{0.24375}{\Omega} = 0.244 \frac{1}{\Omega}$$

$$G_{0CM} := \frac{V_{ac}^2 \cdot k_{div} \cdot k_{mul} \cdot R_{load}}{4 \cdot R_i \cdot V_{out}} = 121.879$$

$$G_{0CMdb} := 20 \cdot \log\left(\frac{V_{ac}^2 \cdot k_{div} \cdot k_{mul} \cdot R_{load}}{4 \cdot R_i \cdot V_{out}}\right) = 41.719$$

$$I_{peak} := \frac{k_{mul} \cdot k_{div} \cdot \sqrt{2} \cdot V_{ac} \cdot V_{err}}{R_i} = 4.542 \text{ A}$$

$$\frac{L_1 \cdot k_{div} \cdot k_{mul}}{R_i} \cdot V_{err} = 11.241 \mu\text{s}$$

$$P_{out} := \frac{V_{ac}^2}{2 \cdot L_1} \cdot \frac{L_1 \cdot k_{div} \cdot k_{mul}}{R_i} \cdot V_{err} = 160.583 \text{ W}$$



$$f_{p1} = 1.768 \text{ Hz}$$

$$f_{poCM} := \frac{V_{ac}^2 \cdot k_{div} \cdot k_{mul}}{4 \cdot \pi \cdot R_i \cdot V_{out}} \cdot \frac{1}{C_{out}} = 215.522 \text{ Hz}$$

$$\text{Resistive loading: } H_3(s) := G_{0CM} \cdot \frac{1}{1 + \frac{s}{2 \cdot \pi \cdot f_{p1}}}$$

Borderline PFC Small-Signal Parameters Calculations

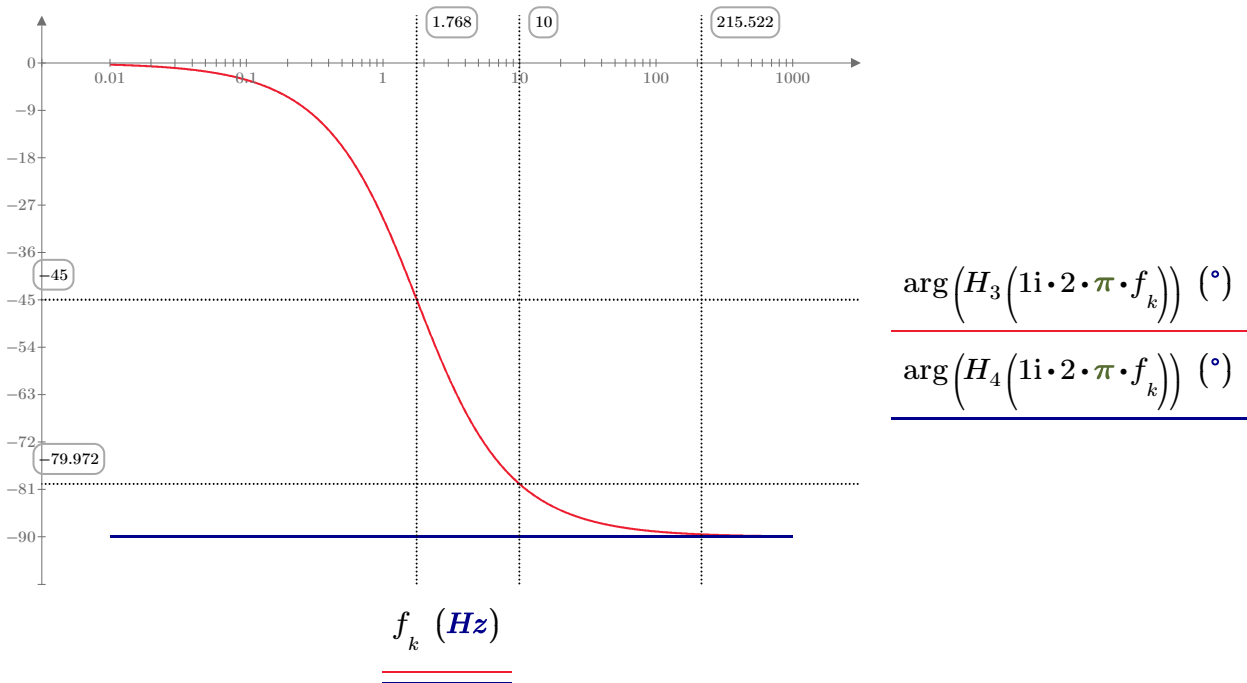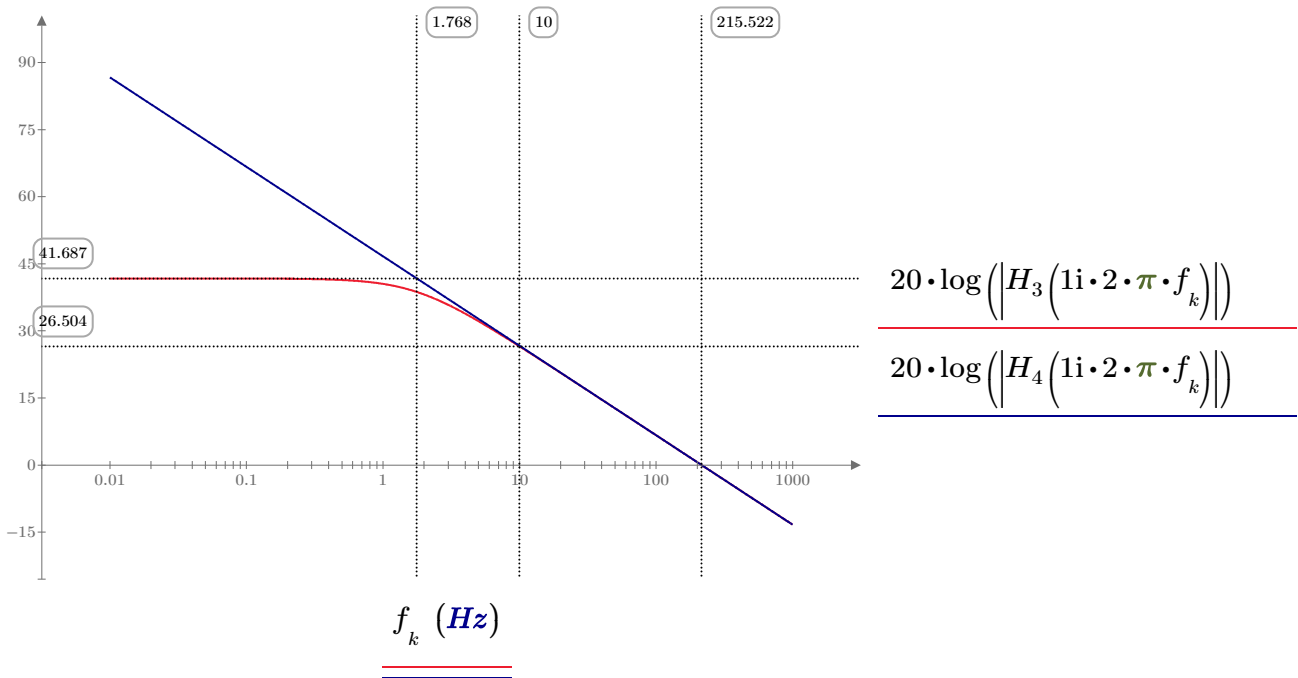SMPS loading: $H_4(s) := \frac{1}{s \cdot f_{poCM} \cdot 2 \cdot \pi}$



$$20 \cdot \log \left(\left| H_4 \left(1i \cdot 2 \cdot \pi \cdot f_c \right) \right| \right) = 26.67$$

$$\arg \left(H_4 \left(1i \cdot 2 \cdot \pi \cdot f_c \right) \right) = -90^\circ$$