



ON Semiconductor®

Closing the Feedback Loop through Simulation and Analysis

Christophe Basso – Technical Fellow
IEEE Senior Member



Course Agenda

- Blocks in a Switching Converter
- Introduction to Small-Signal Modeling
- Analytical Analysis of an Output Stage
- Simulation Models - Averaged or Switched?
- Crossover Frequency and Phase Margin
- Compensation Strategy
- Experiments on Prototypes
- Conclusion




Course Agenda

- Blocks in a Switching Converter**
- Introduction to Small-Signal Modeling
- Analytical Analysis of an Output Stage
- Simulation Models - Averaged or Switched?
- Crossover Frequency and Phase Margin
- Compensation Strategy
- Experiments on Prototypes
- Conclusion




What is a Control System?

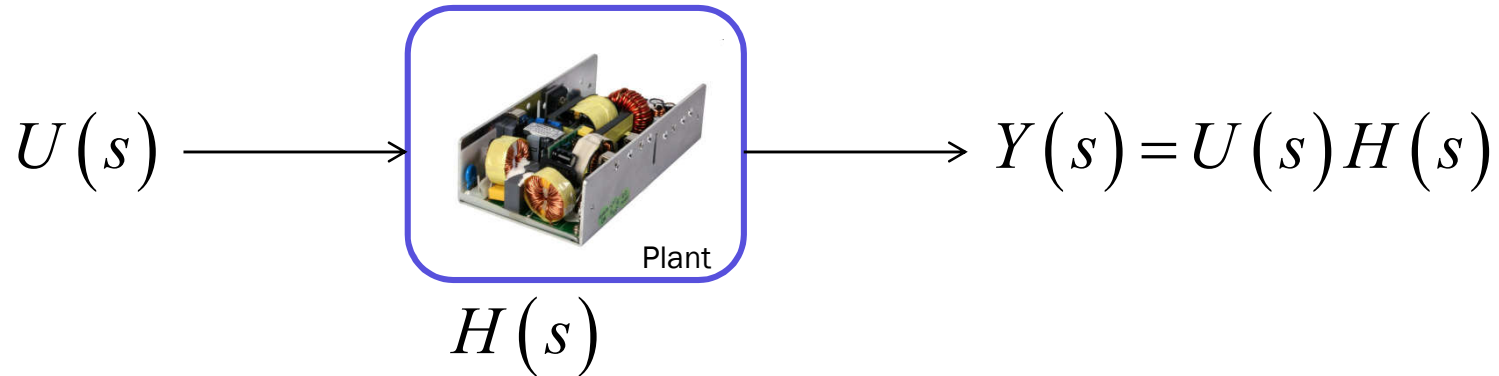- An *open-loop* system links the output to the control variable





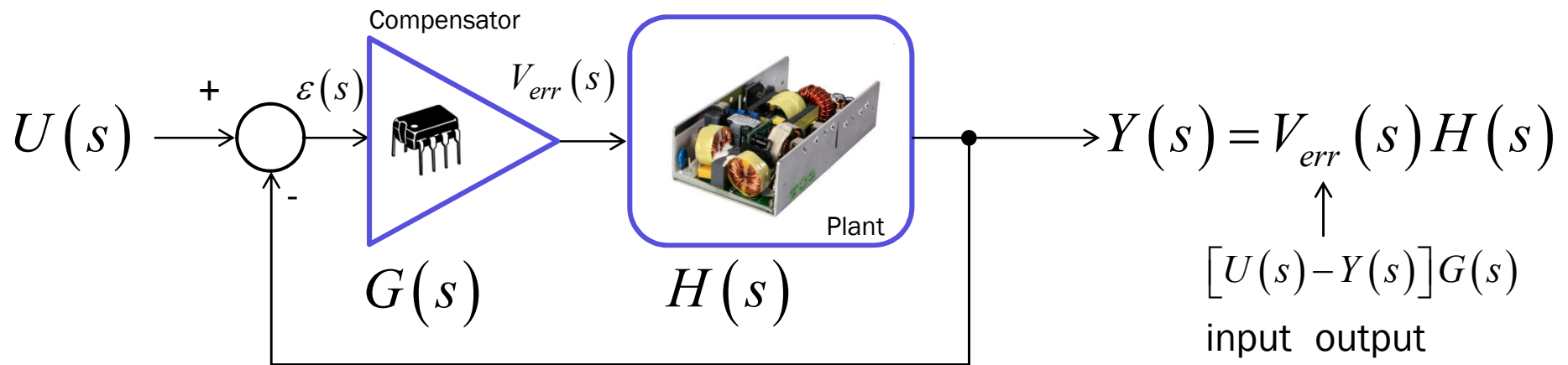- A *control system* observes the output and minimizes errors



Elements Found in a Switching Converter

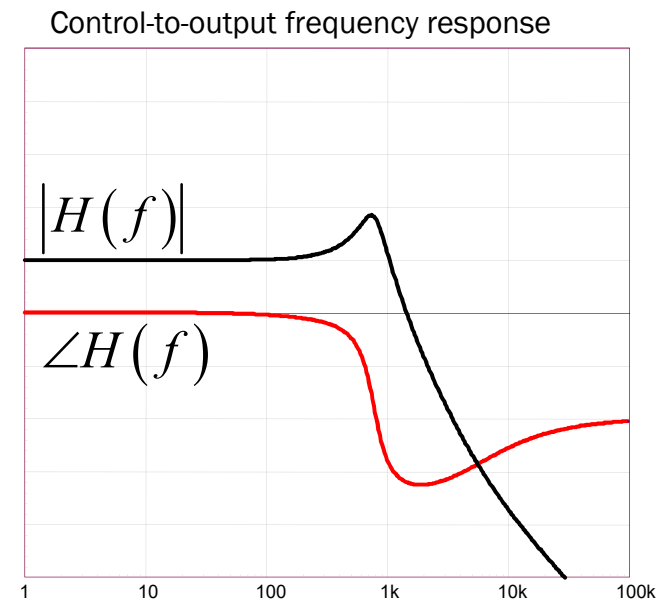
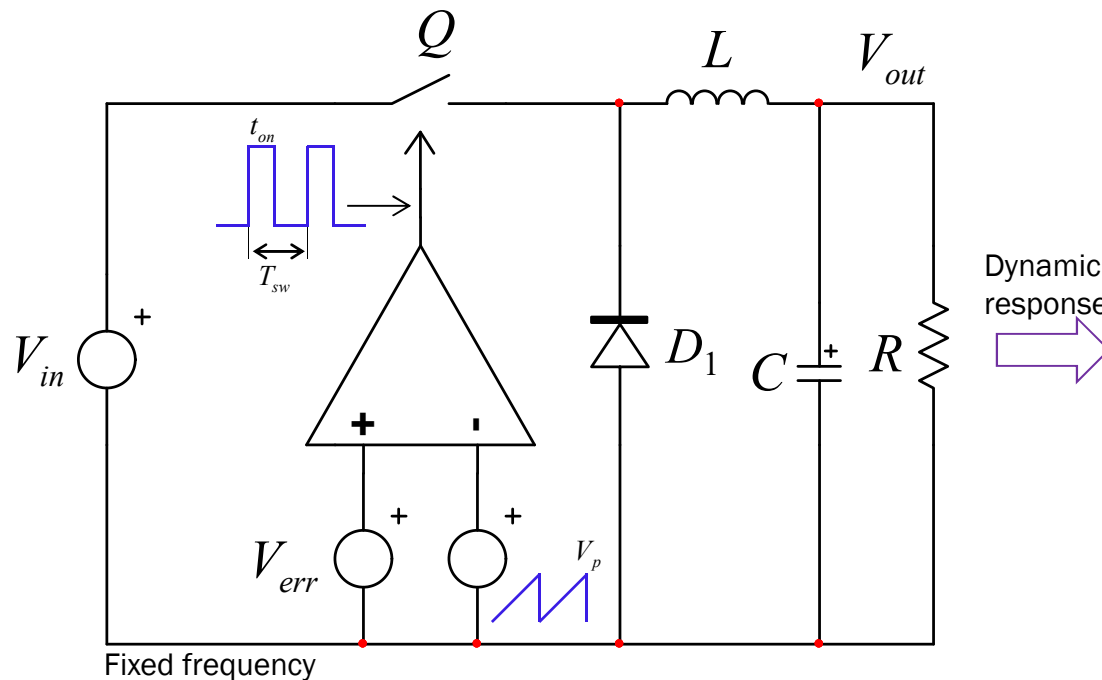
- ❑ The control system – your converter – is made of various blocks
 - The plant is the power stage of the buck, boost, LLC etc.
 - The control variable is D , the duty ratio, the response is V_{out} or I_{out}



- ❑ You need the control-to-output response of the plant beforehand

The Compensator – Shaping the Loop

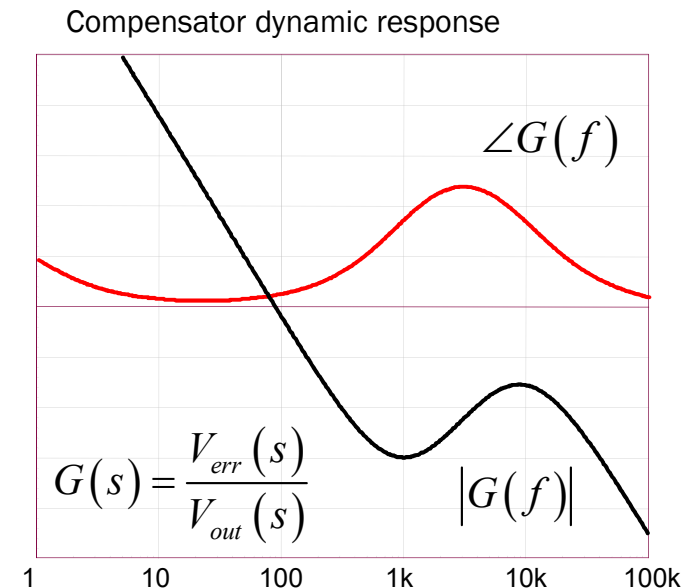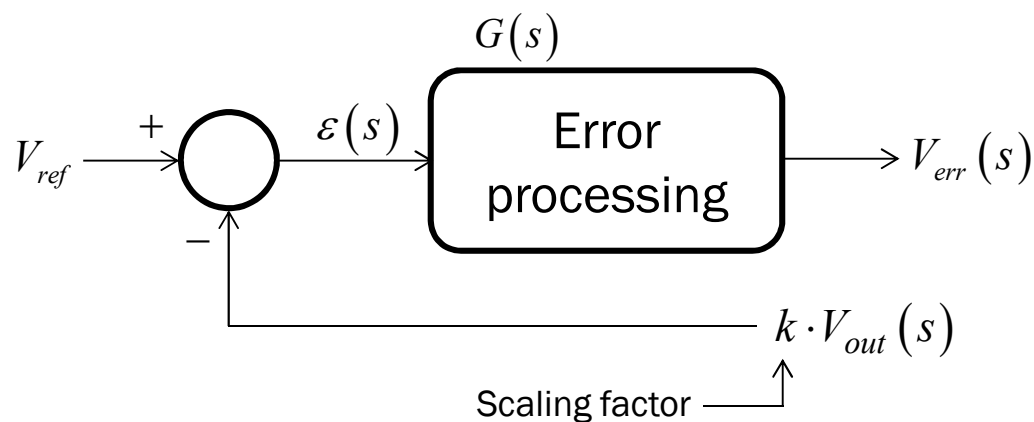- ❑ The compensator builds the error variable and ensures stability
 - Insert poles and zeros to build the compensation strategy
 - Choose how to cross over at f_c with phase and gain margins




- ❑ The block amplifies and shapes the error ε between V_{ref} and V_{out}
 - Minimize the error between the setpoint and the output


For a comprehensive analysis see APEC 2012 seminar: *The Dark Side of Loop Control Theory*

Amplifiers for the Compensator


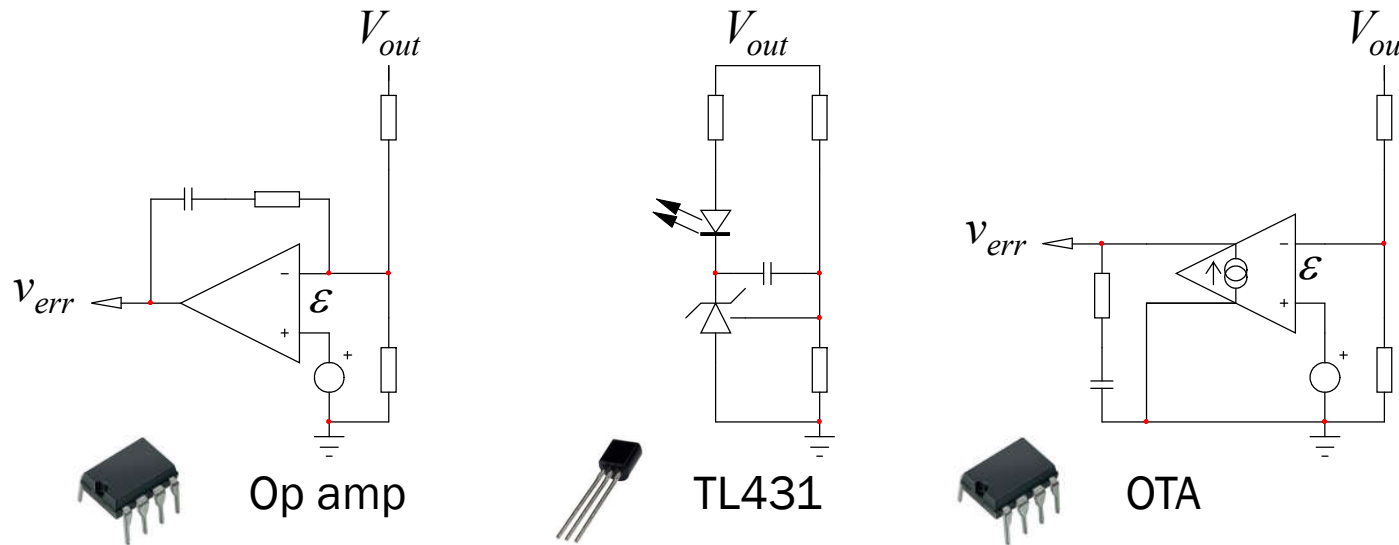
- ❑ The compensator is implemented with an error amplifier



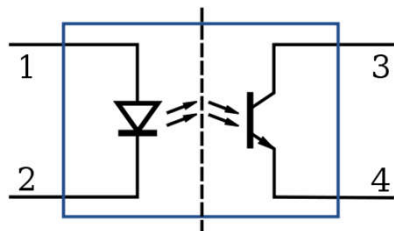- ❑ It is often associated with an optocoupler for isolation




Adds its own response

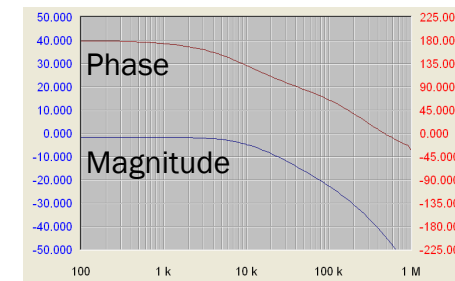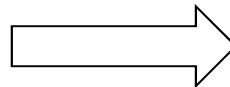


Shaping the Compensator Response

- Choose the closed-loop response by placing poles, zeros and gains

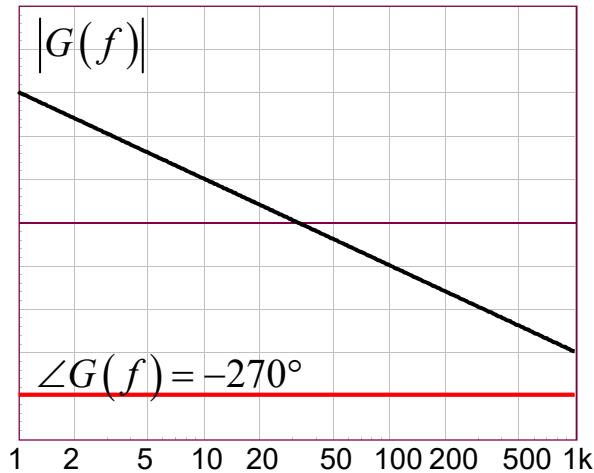


Type 1 – no boost

$$G_1(s) = -\frac{1}{\frac{s}{\omega_{po}}}$$

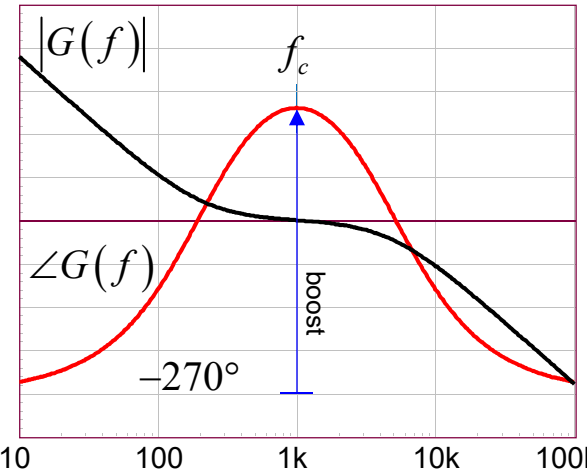

Type 2 – up to 90°

$$G_2(s) = -G_0 \frac{1 + \frac{s}{s_{z_1}}}{1 + \frac{s}{s_{p_1}}}$$

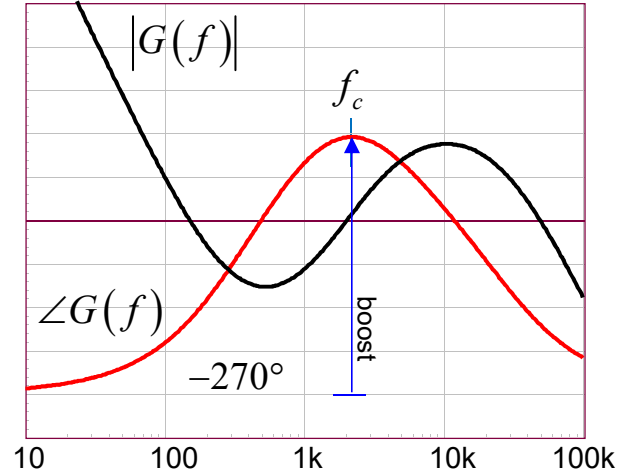


Type 3 – up to 180°


$$G_3(s) = -G_0 \frac{\left(1 + \frac{s}{s_{z_1}}\right) \left(1 + \frac{s}{s_{z_2}}\right)}{\left(1 + \frac{s}{s_{p_1}}\right) \left(1 + \frac{s}{s_{p_2}}\right)}$$

Controlling the Duty Ratio

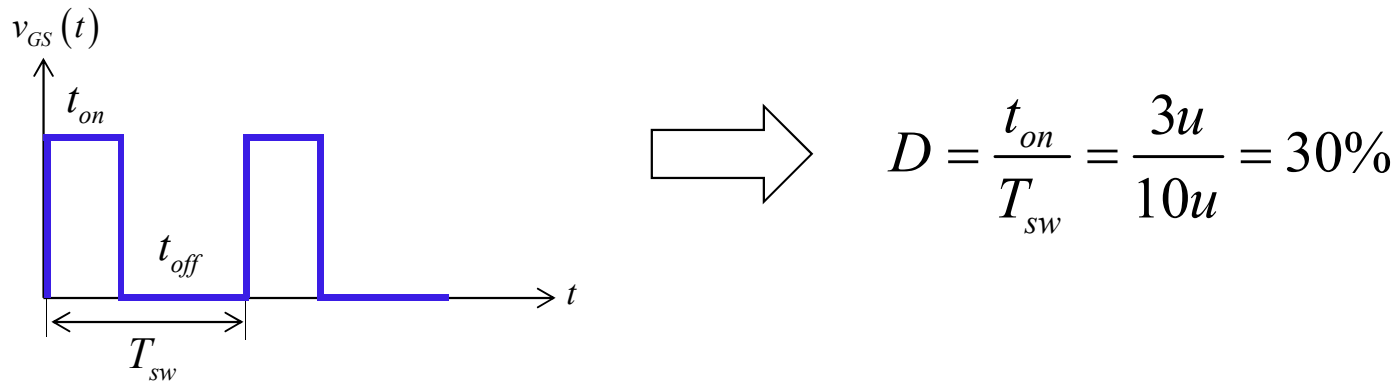- The power stage is controlled via the duty ratio D




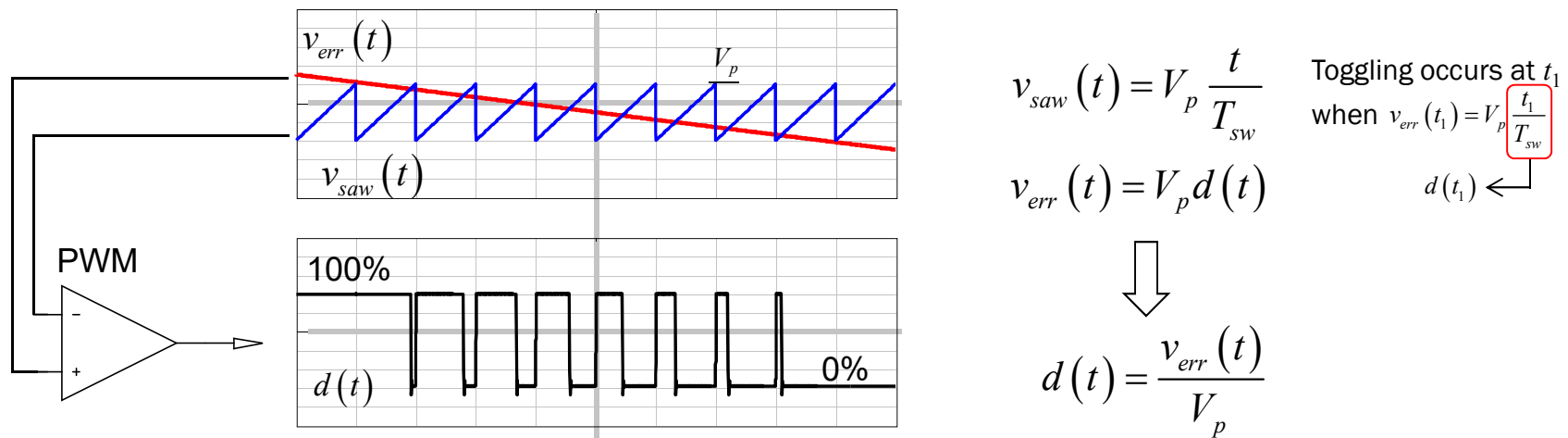- The pulse width modulator or PWM links D to V_{err}



Different Types of Modulators

Trailing edge

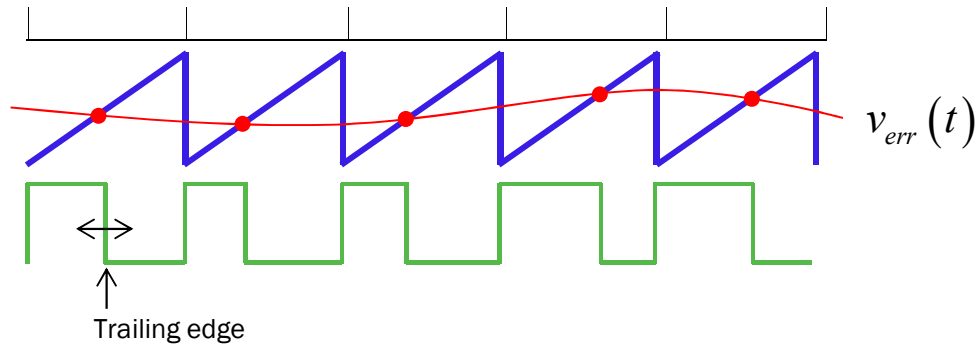


Clocked turn-on
Fast turn-off
Delayed turn-on



Conventional ac-dc, dc-dc

Leading edge

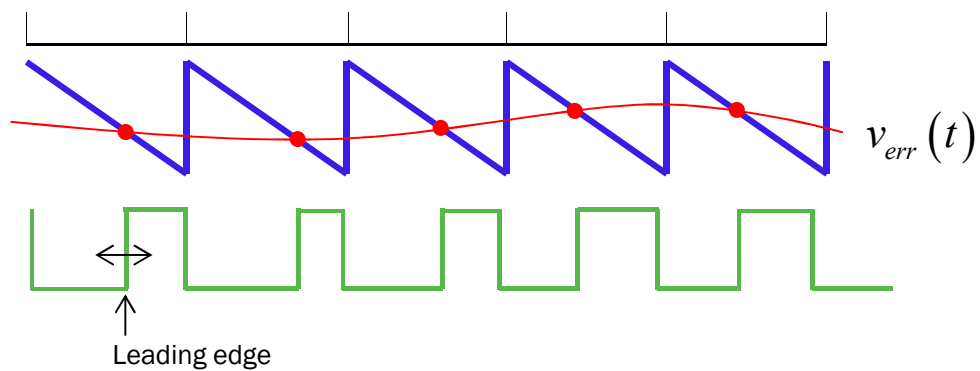


Clocked turn-off
Fast turn-on
Delayed turn-off



Post regulators

Dual edge

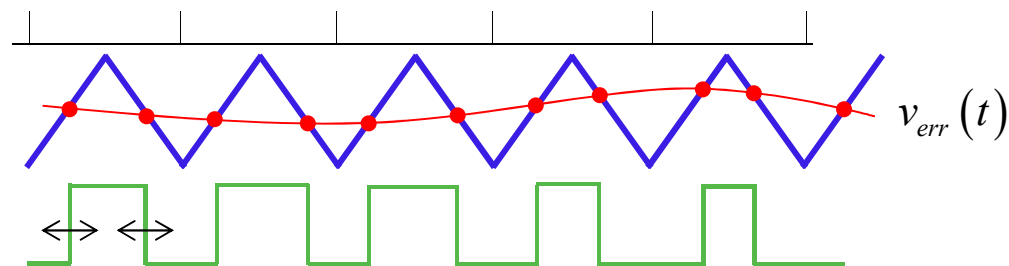

Fast turn-on
Fast turn-off





High-speed dc-dc




The Complete Picture

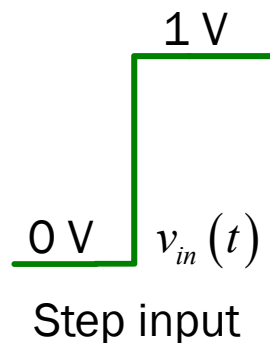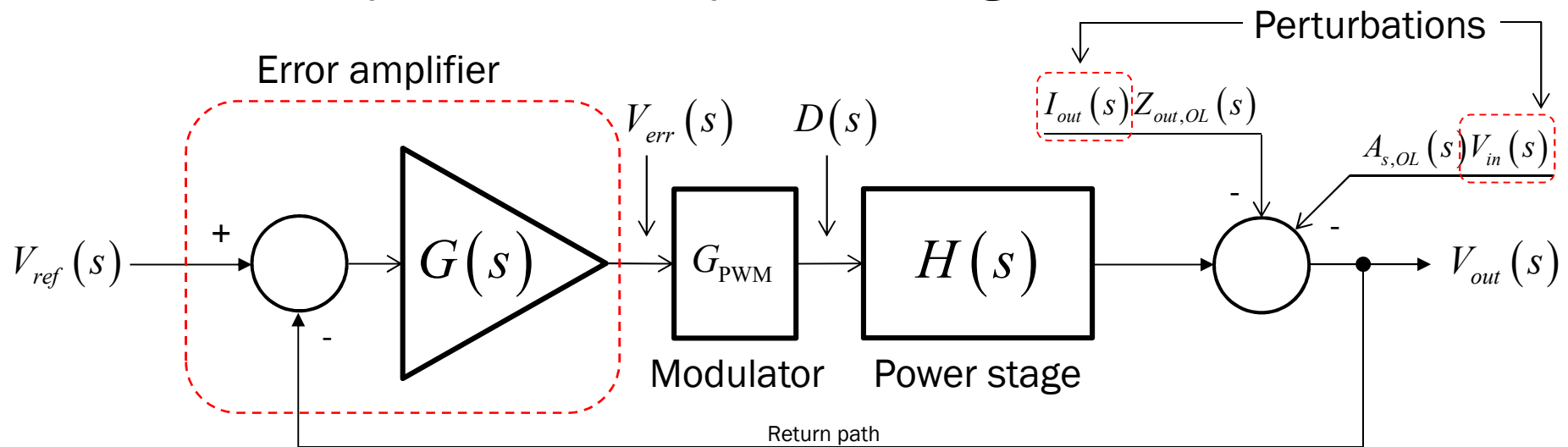- The whole system is built by associating blocks



Compensate for:


- ✓ Speed
- ✓ Precision
- ✓ Robustness

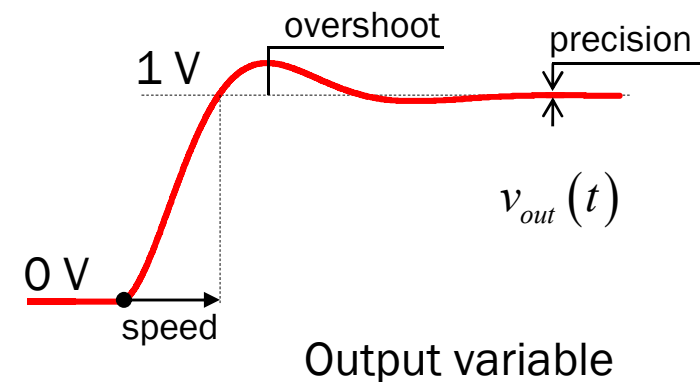

Identifying the Blocks in a Schematic

- It is important to recognize where the functions appear

Power stage

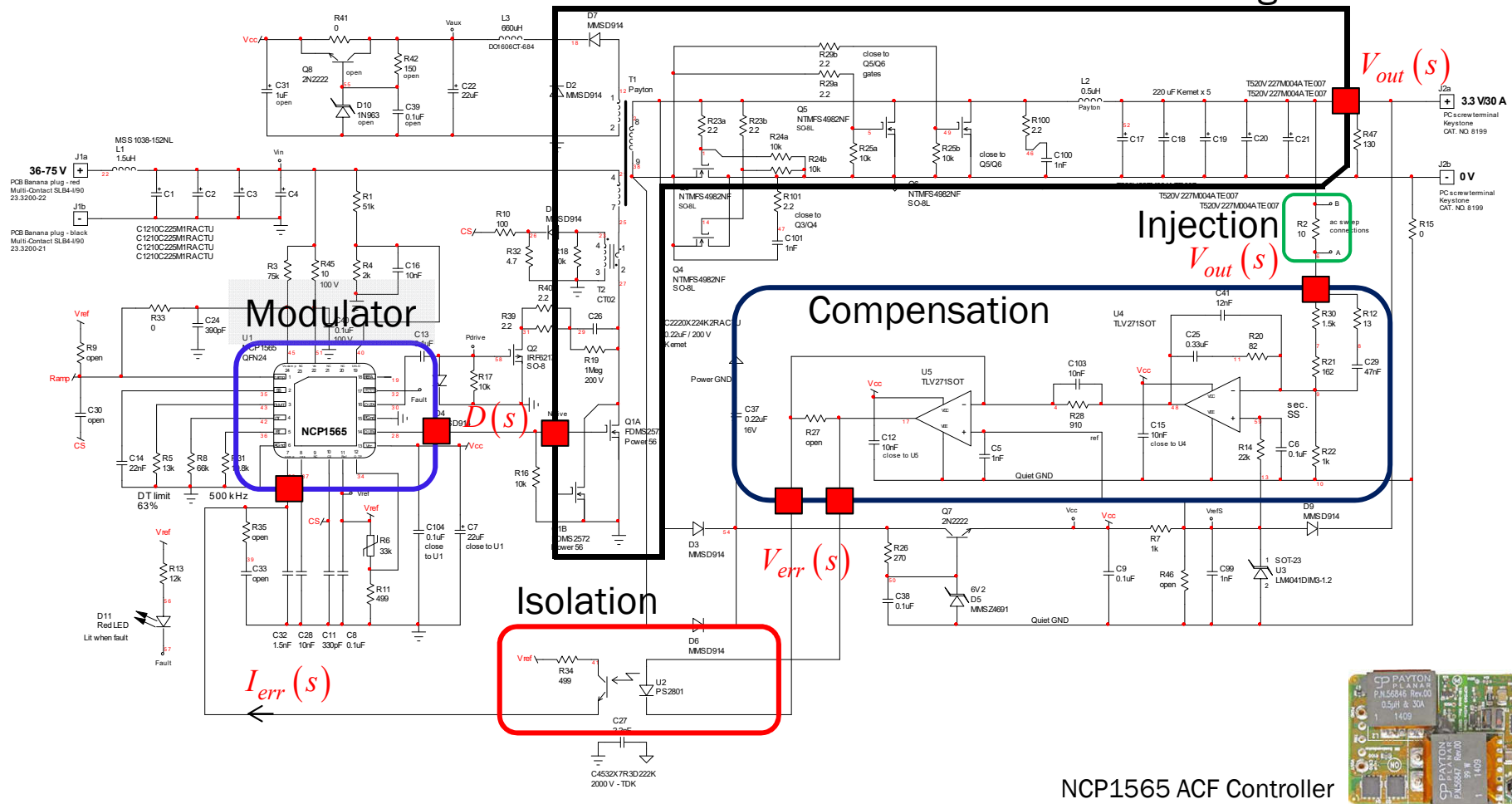


NCP1565 ACF Controller




Power Stage Response Analysis

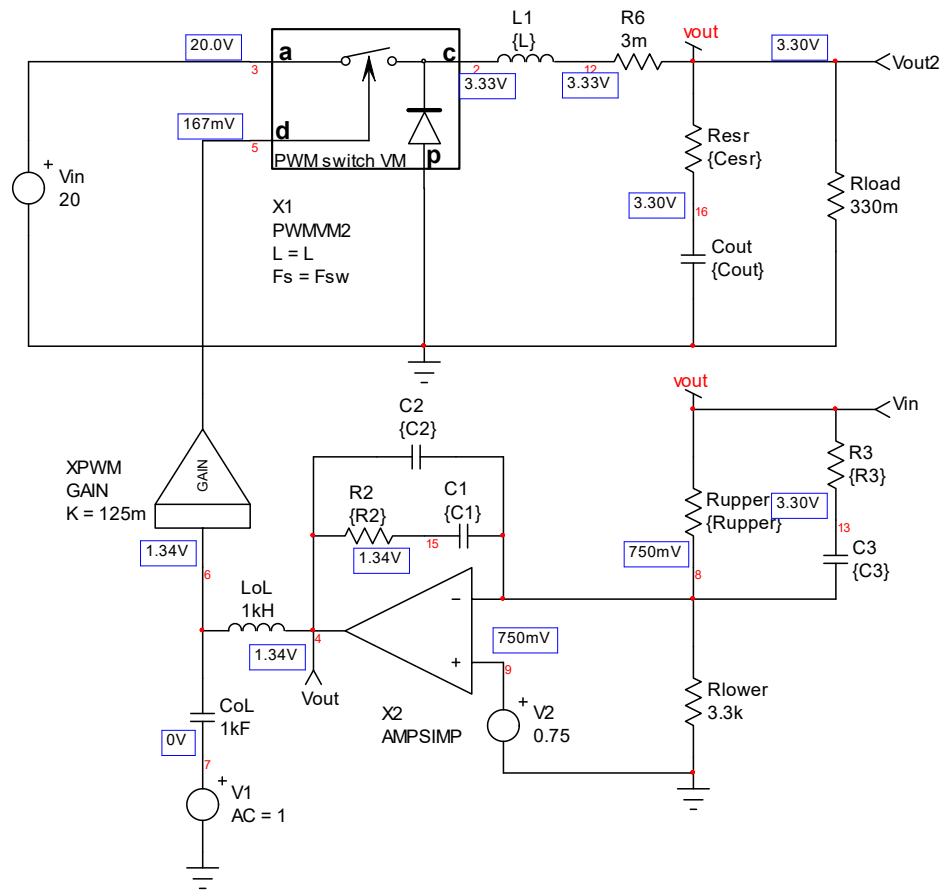- The power stage response is needed
- ❖ Simulation with averaged models: the PWM switch



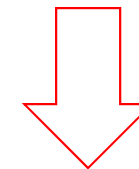
1. Fast (no switching)
2. Small-signal (linear)
3. Easy .PARAM sweep
4. Portable (SPICE2)




- Power stage model
- Nonlinearities
- Convergence issues

Dynamic Response with LTspice®

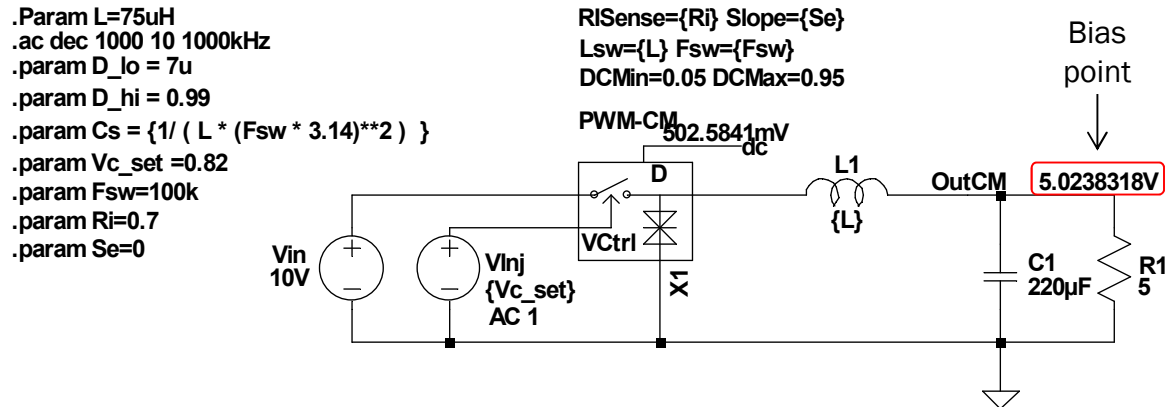- Average models are also available with this simulation platform



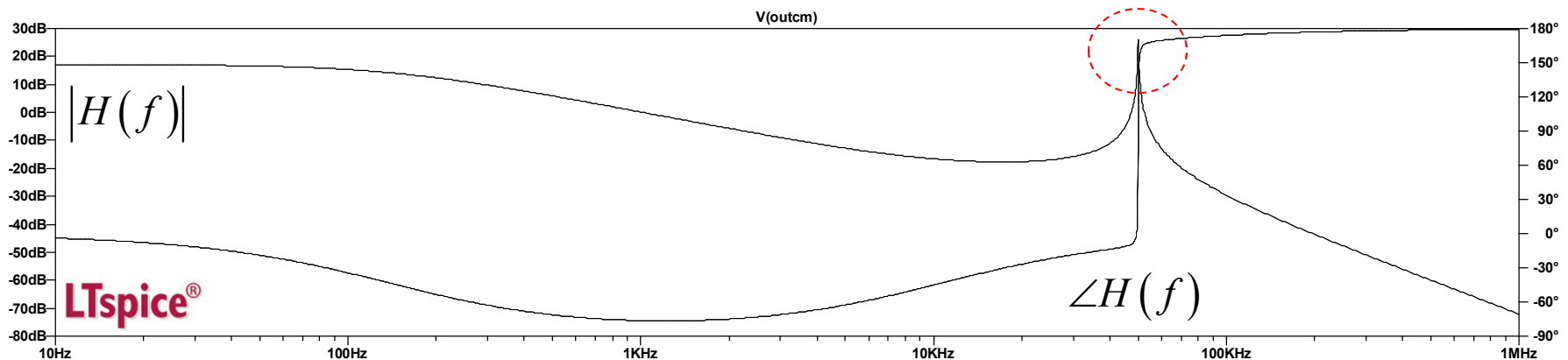
- Ac response is immediate, predicting sub-harmonic poles in CM



Models available at <http://cbasso.pagesperso-orange.fr/Spice.htm>

Piece-Wise Linear Simulations

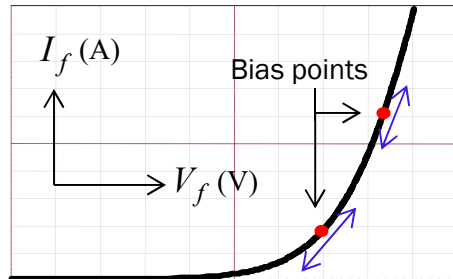- Simplis® is a PWL simulator: components are always linear




Model must be linearized

SPICE





SIMPLIS®

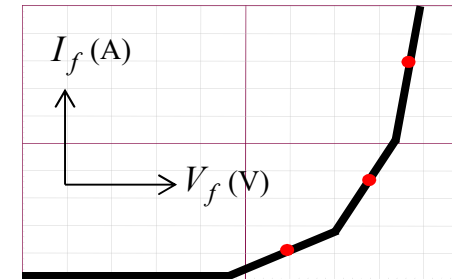

Model is already linear

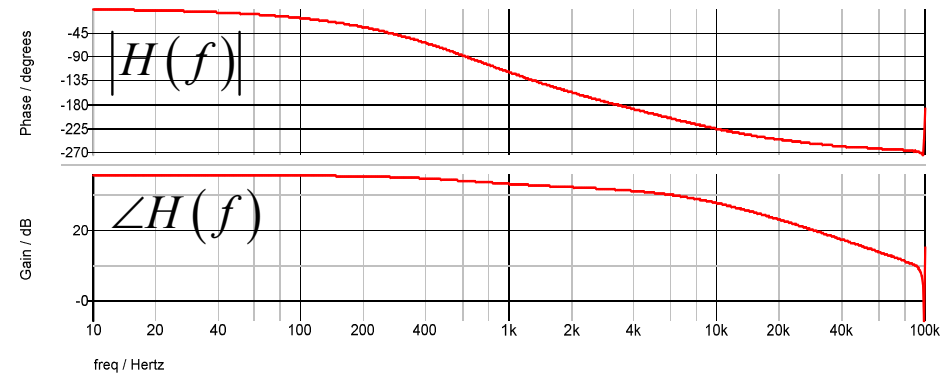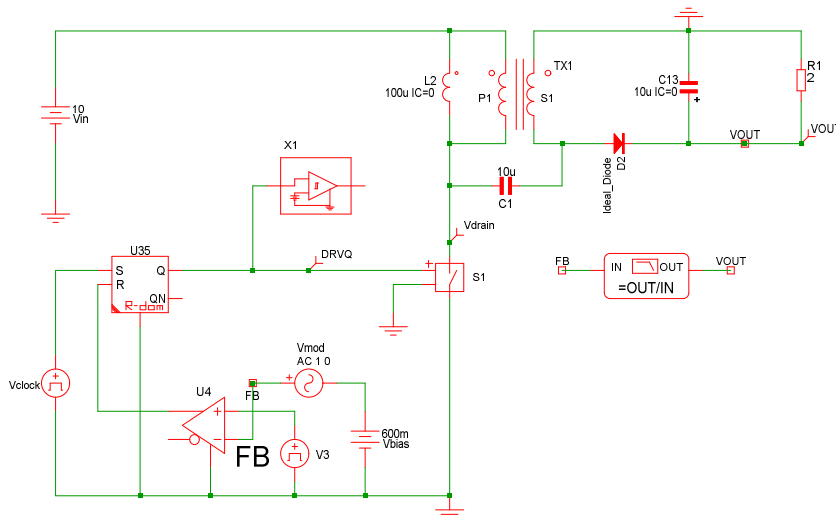- You can get an ac response from a switching circuit




Coupled-inductor SEPIC ac response (3 s)




Equation-Based Analytical Analysis

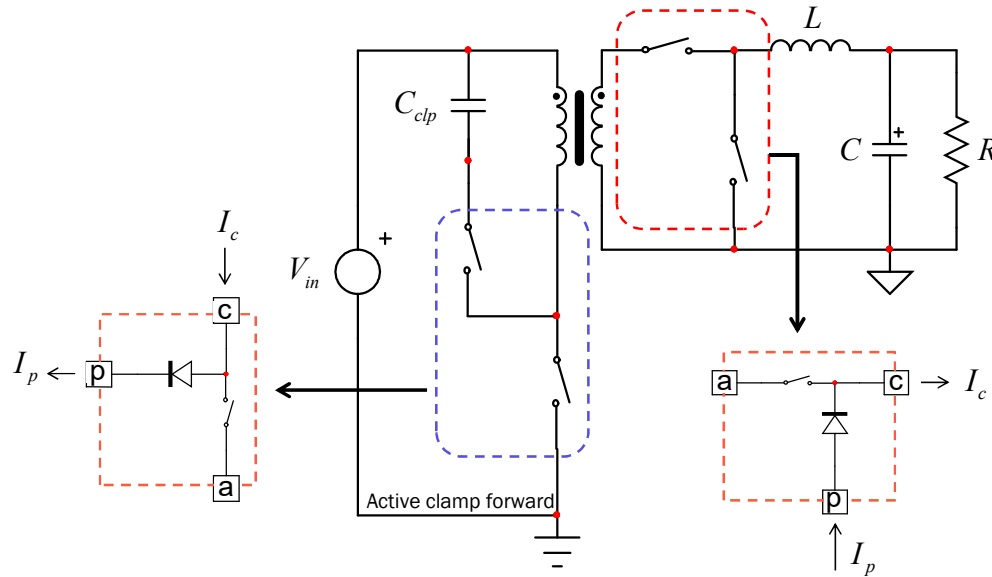- Identify a small-signal model and derive the transfer function



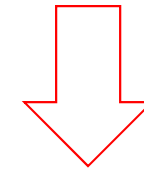1. Expressions are ready
2. See poles and zeros
3. Parasitic contributions
4. Parametric sweep



Extract



$$\frac{V_{out}(s)}{D(s)} = F_0 \frac{1 + \frac{s}{s_{zF}}}{1 + \frac{s}{\omega_{0F}Q_F} + \left(\frac{s}{\omega_{0F}}\right)^2} N \left(V_{in} - D_0 r_{on1} M_0 \frac{s C_{clp}}{1 + \frac{s}{\omega_{0M}Q_M} + \left(\frac{s}{\omega_{0M}}\right)^2} \right)$$

- Scared to try?
- Have the tools?
- Valid model?



Bench Experiments

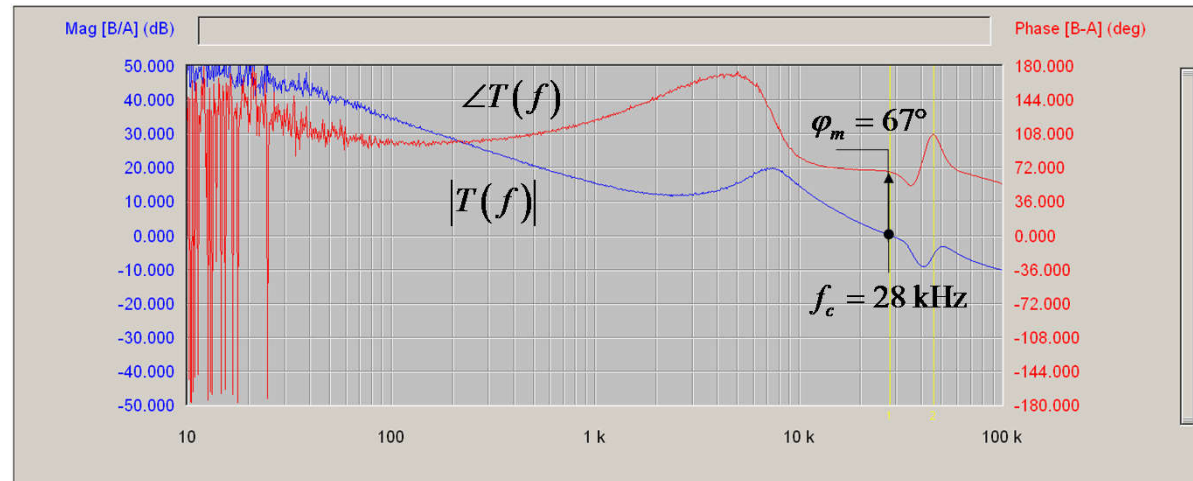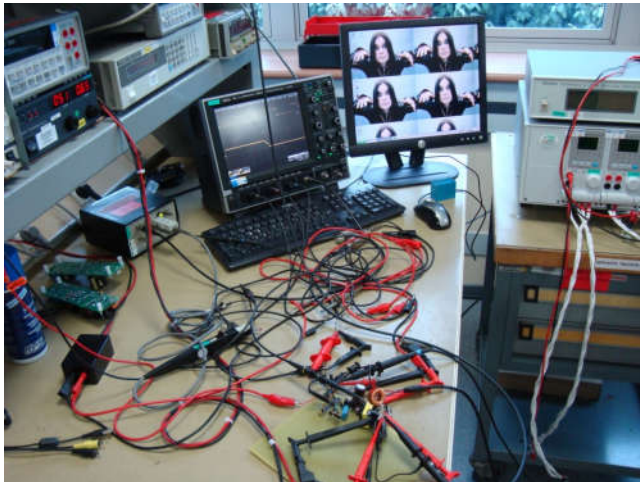- Build a prototype and extract the power stage response



- ❖ You need to have all components on hand (special parts, XFMR)
- ❖ Board can be difficult to measure (isolation path, complex loop)
- ❖ Check if results match the model – refine model and analyses

This is the ultimate stage – do NOT skip it!



Course Agenda




- Blocks in a Switching Converter
- Introduction to Small-Signal Modeling**
- Analytical Analysis of an Output Stage
- Simulation Models - Averaged or Switched?
- Crossover Frequency and Phase Margin
- Compensation Strategy
- Experiments on Prototypes
- Conclusion




Why do we Need a Transfer Function?

- ❑ The stabilization process starts with the plant response
- ❑ Without an equation, how to identify offenders and neutralize them?
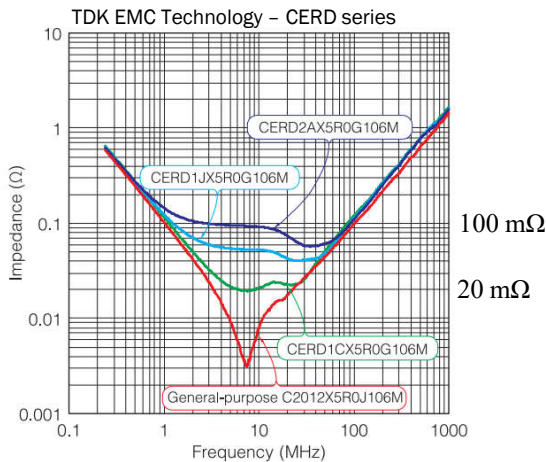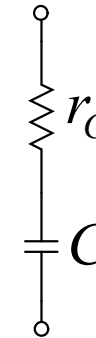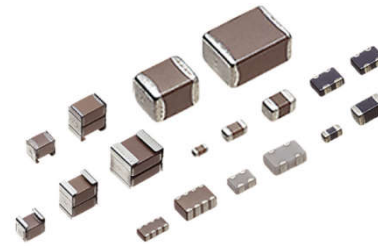
$$H(s) \approx H_0 \frac{1 + \frac{s}{\omega_{z1}}}{1 + \frac{s}{\omega_{p1}} \left(1 + \frac{s}{\omega_n Q} + \left(\frac{s}{\omega_n} \right)^2 \right)}$$



$$\omega_z = \frac{1}{r_C C}$$

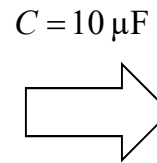

$C = 10 \mu\text{F}$

$$f_z \approx 159 \text{ kHz}$$

$$f_z \approx 796 \text{ kHz}$$

Is stability ensured in all cases?


- ❑ The ESR lumps all losses which vary with temperature and frequency!

http://www.ieca-inc.com/images/Equivalent_Series_Resistnace_ESR.pdf




How to Model a Switching Converter?

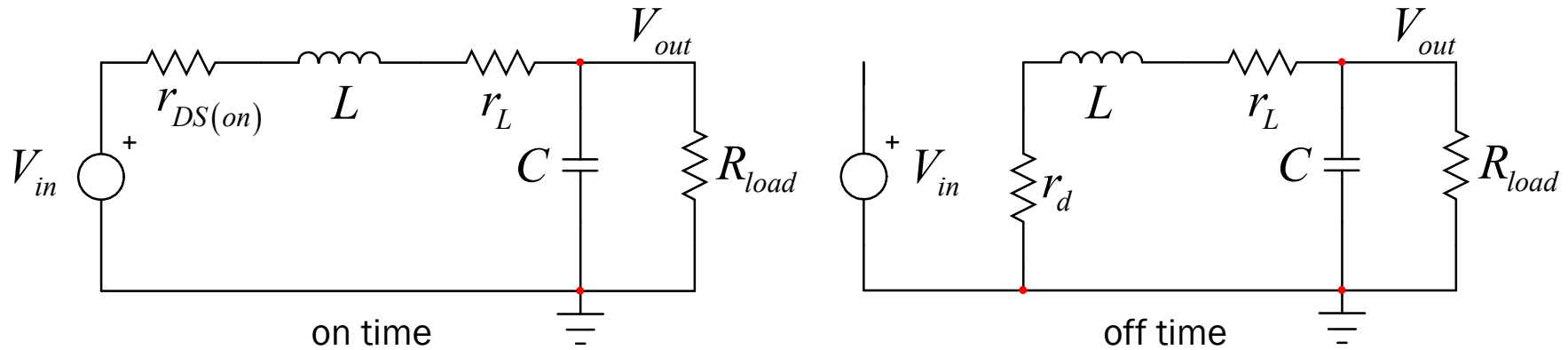- A switching converter is made of linear elements



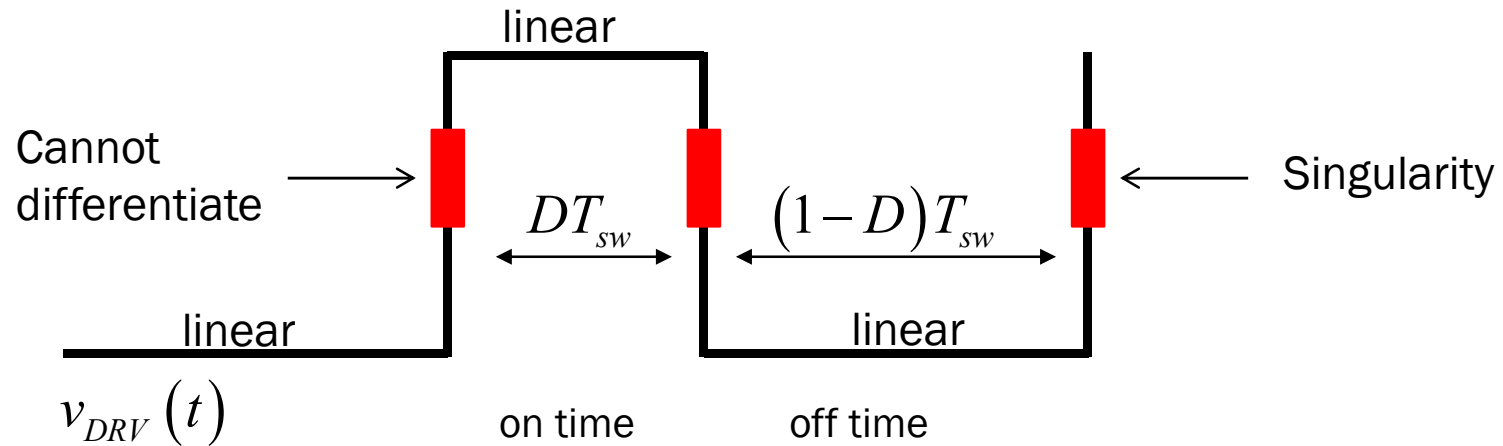- The non-linearity or discontinuity is coming from transitions



State Space Averaging (SSA)

- ❑ Despite linear networks, equation is discontinuous in time
- ❑ Introduced in 76, SSA weights on and off expressions

$$\dot{x} = \left[\mathbf{A}_1 D + \mathbf{A}_2 (1-D) \right] x(t) + \left[\mathbf{B}_1 D + \mathbf{B}_2 (1-D) \right] u(t)$$

valid during DT_{sw}

valid during $(1-D)T_{sw}$


A is the state coefficient matrix
B is the source coefficient matrix

- ❑ This equation is now continuous in time: singularity is gone
- ❑ However, it became a nonlinear equation
- You need to linearize it by perturbation (or differentiation)
- If you add a new element, you have to restart from scratch!

S.Ćuk, *Modeling, Analysis and Design of Switching Converters*, Ph. D. Thesis, Caltech November 1976

The Triode Small-Signal Model

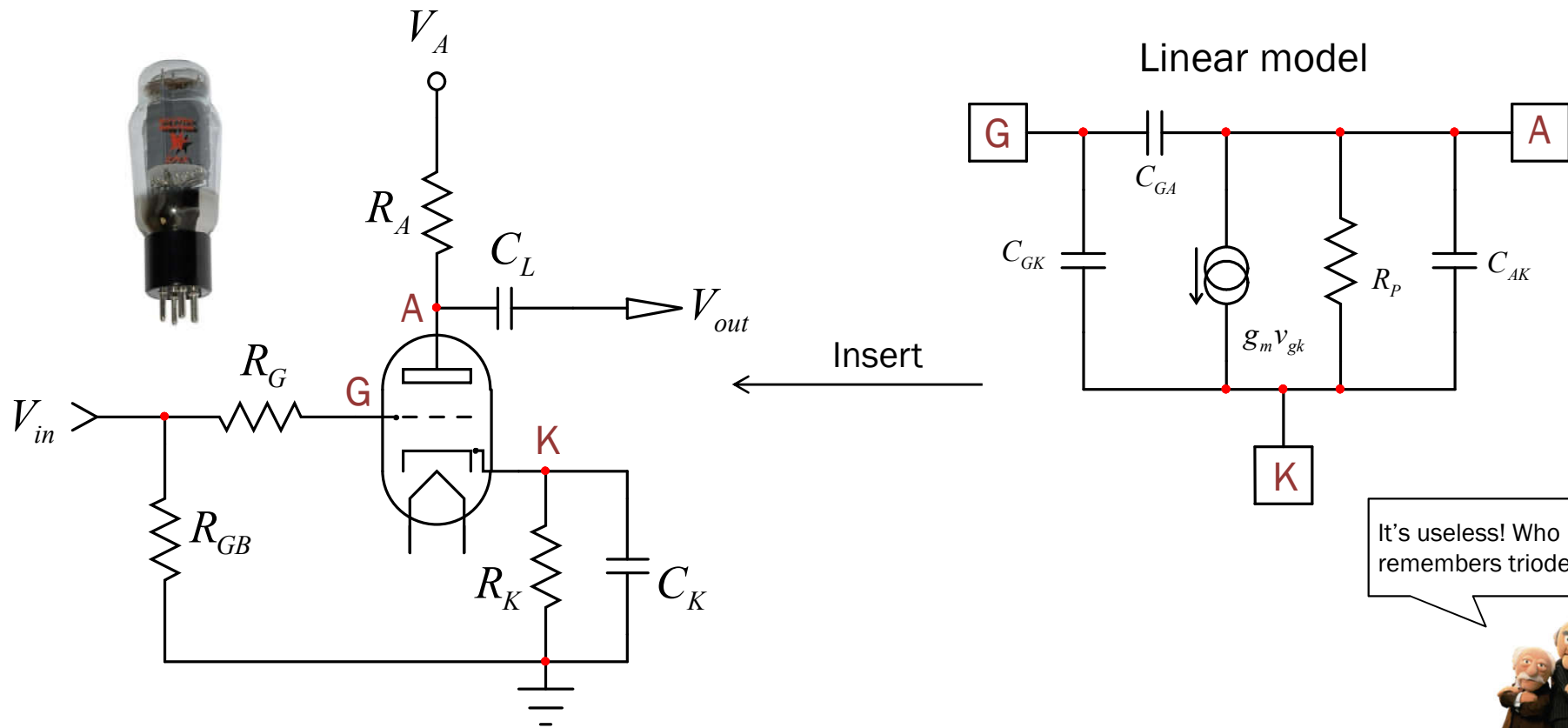- ❑ A triode is a highly non-linear component
- ❑ Replace it by its small-signal model to get the response



It's useless! Who remembers triodes?




<http://web.eecs.umich.edu/~mmccorq/diversions/simulation/index.html>




The PWM Switch Model in Voltage Mode

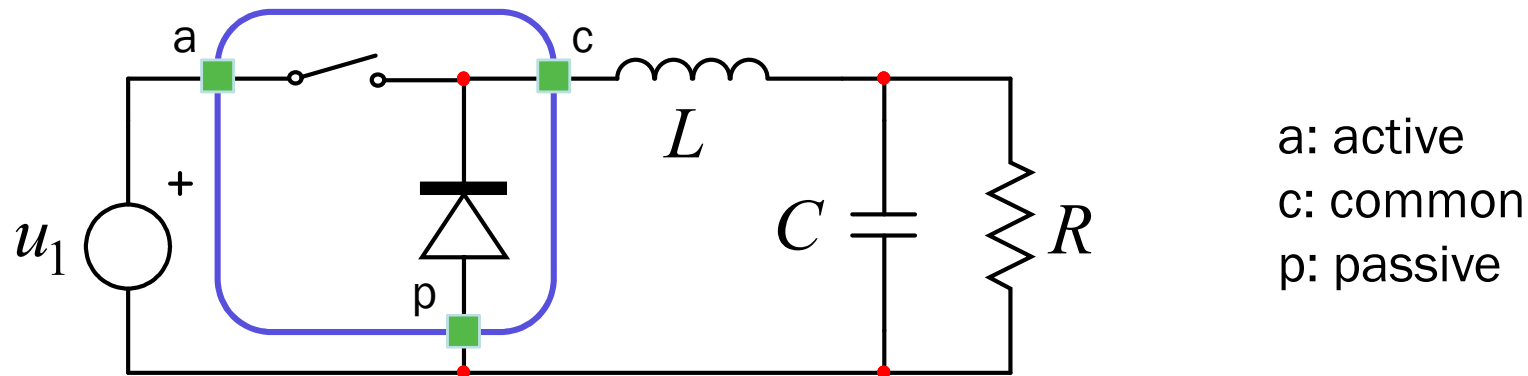- We know that non-linearity is brought by the switching cell




- Why don't we linearize the cell alone?

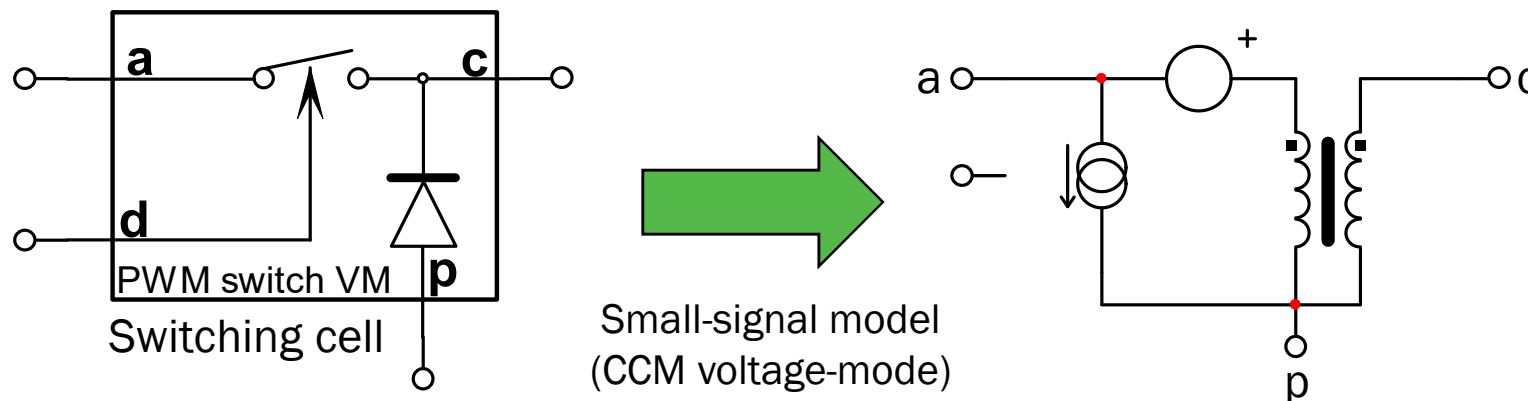

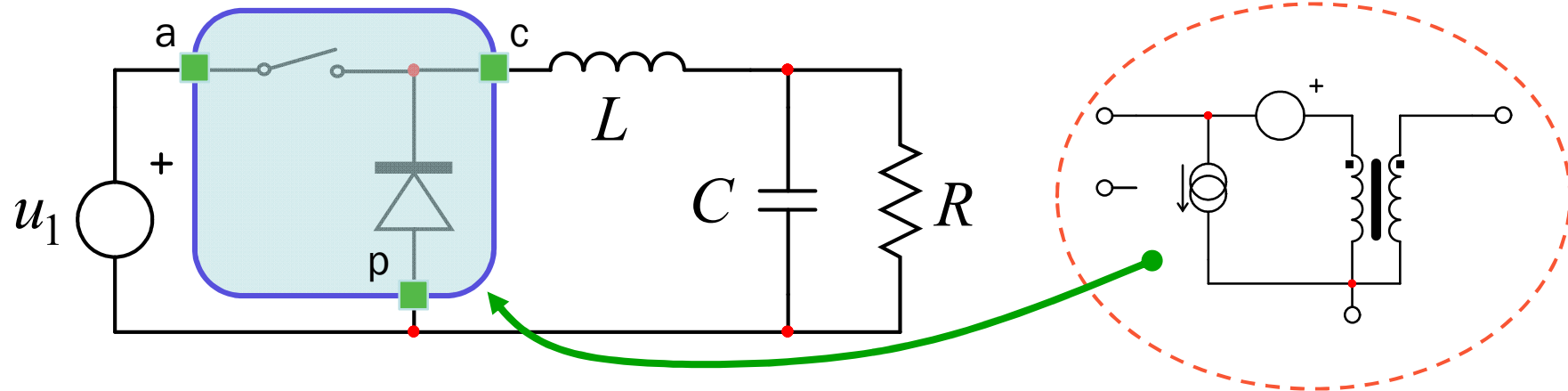V. Vorpérian, *Simplified Analysis of PWM Converters using Model of PWM Switch, parts I and II*, IEEE Transactions on Aerospace and Electronic Systems, Vol. 26, NO. 3, 1990


Replace the Switches by the Model

- Like in a bipolar circuit, replace the switching cell...




- ...and solve a set of linear equations!

Small-signal model

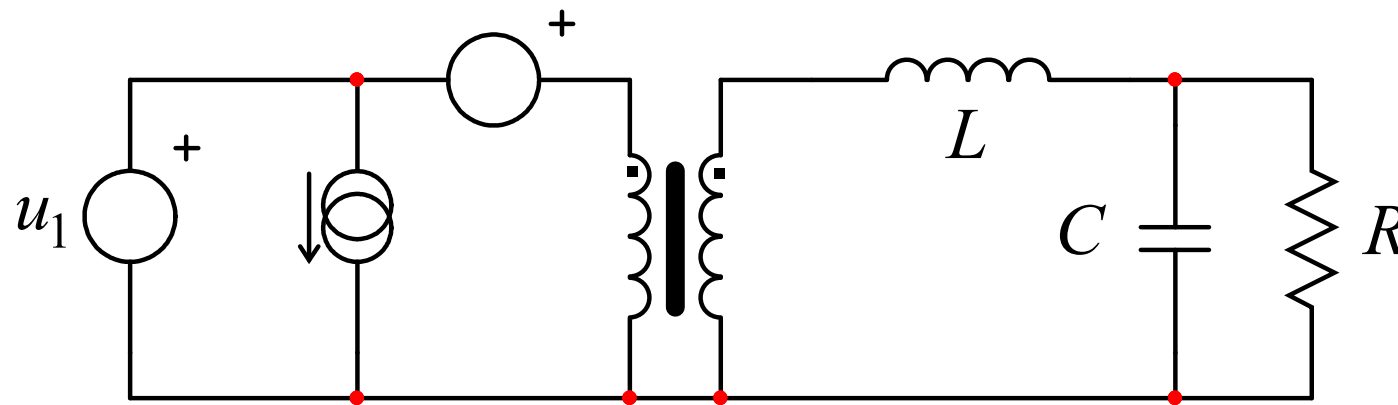


An Invariant Model fits all Structures!

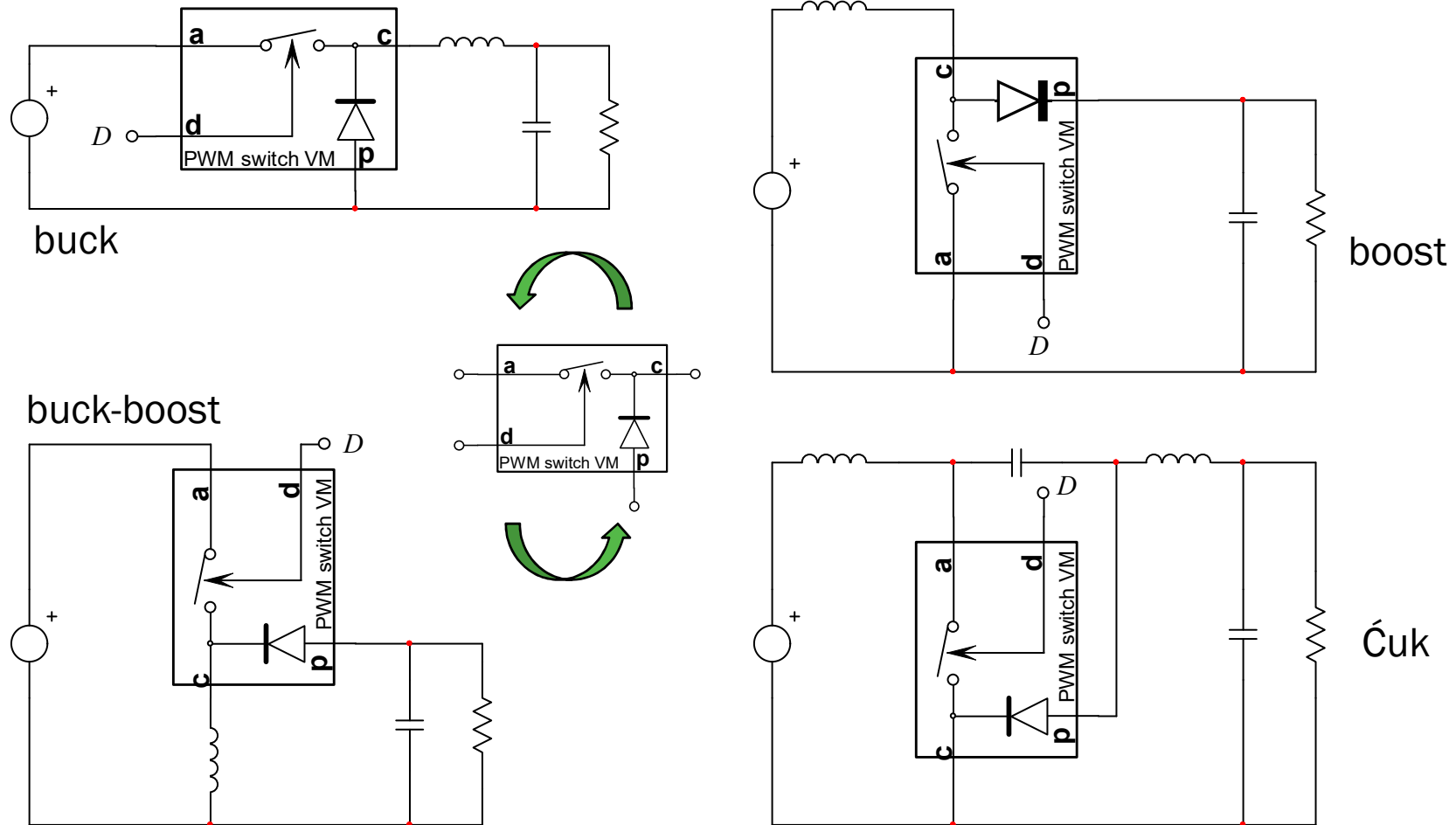- The switching cell made of two switches is everywhere!



Rearrange the Schematic

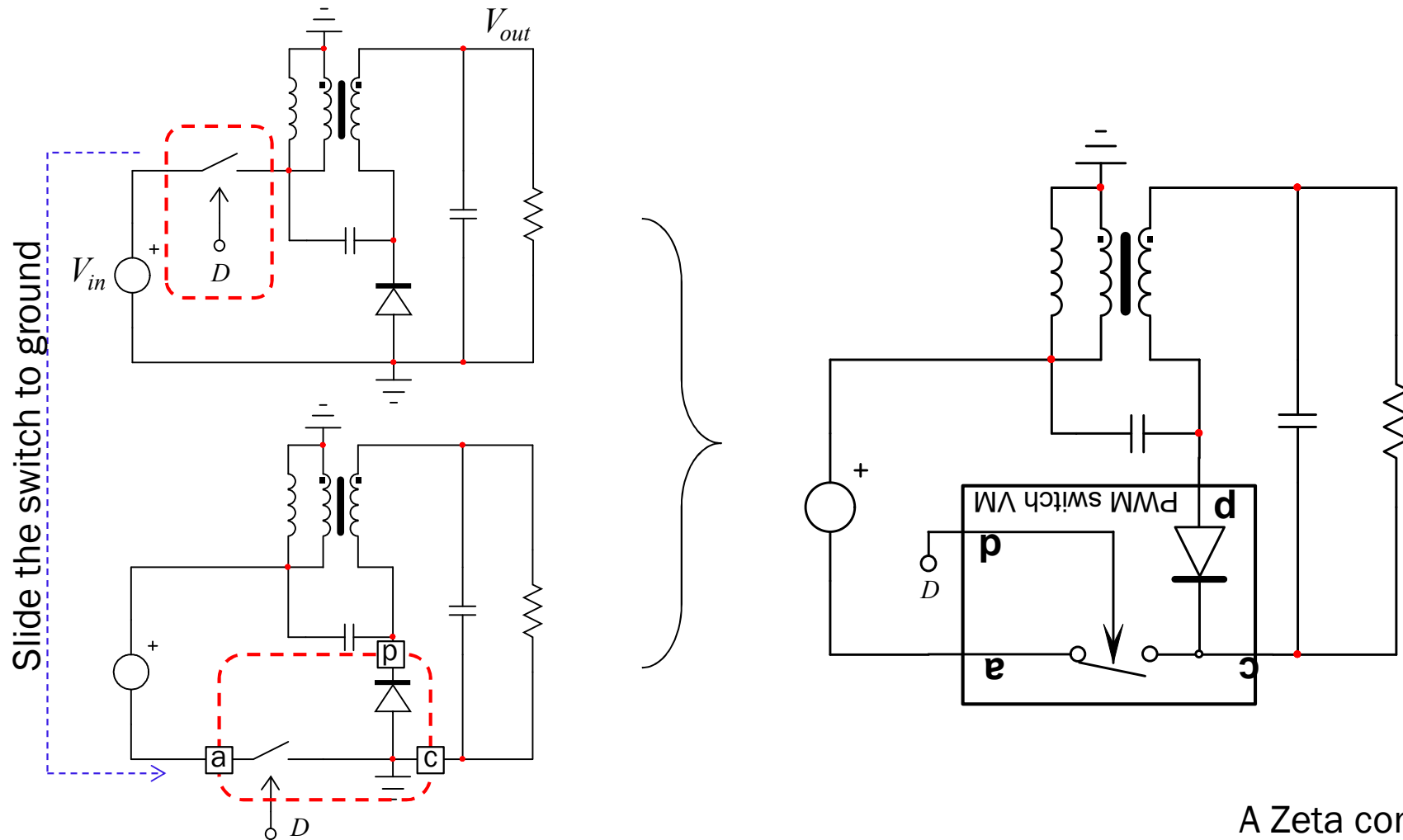
- ❑ You sometimes need to rework the sketch to reveal the model



A Zeta converter

Combine PWM Switches

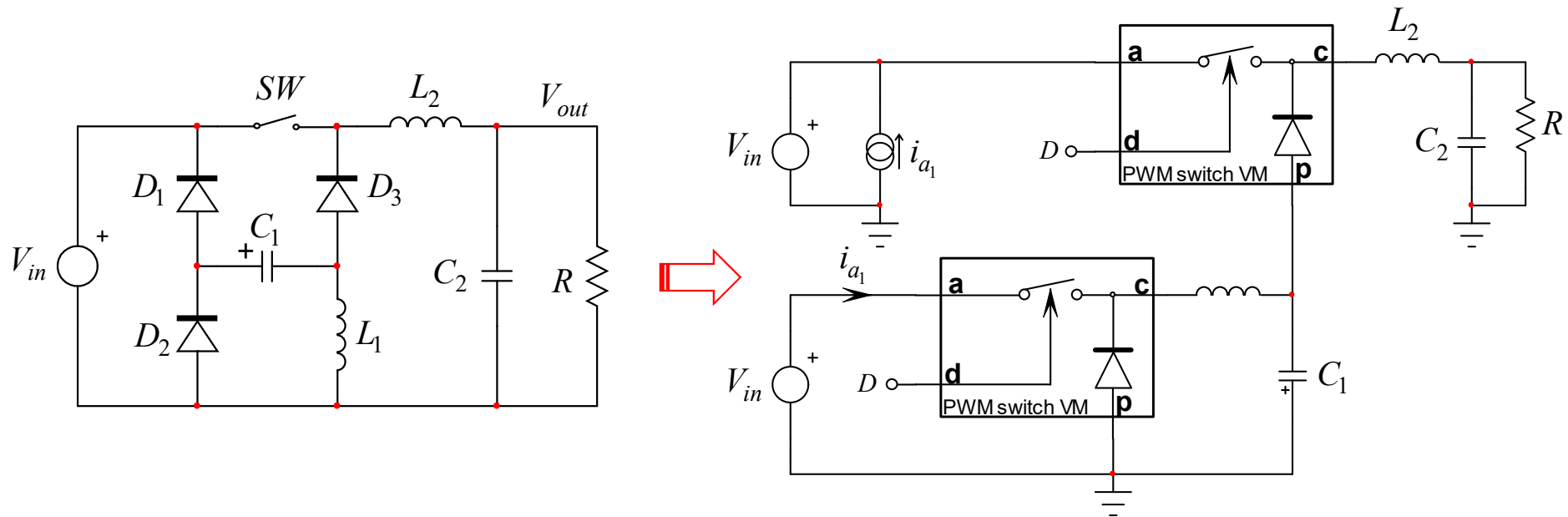- ❑ Some complicated structures need more work



- ❖ You need to reveal networks during DT_{SW} and $(1-D)T_{SW}$
- ❖ Combine two PWM switch models at the end
- ❖ Run .DC, .AC or .TRAN analyses with this circuit


Oh yeah, and who's gonna do it, uh?



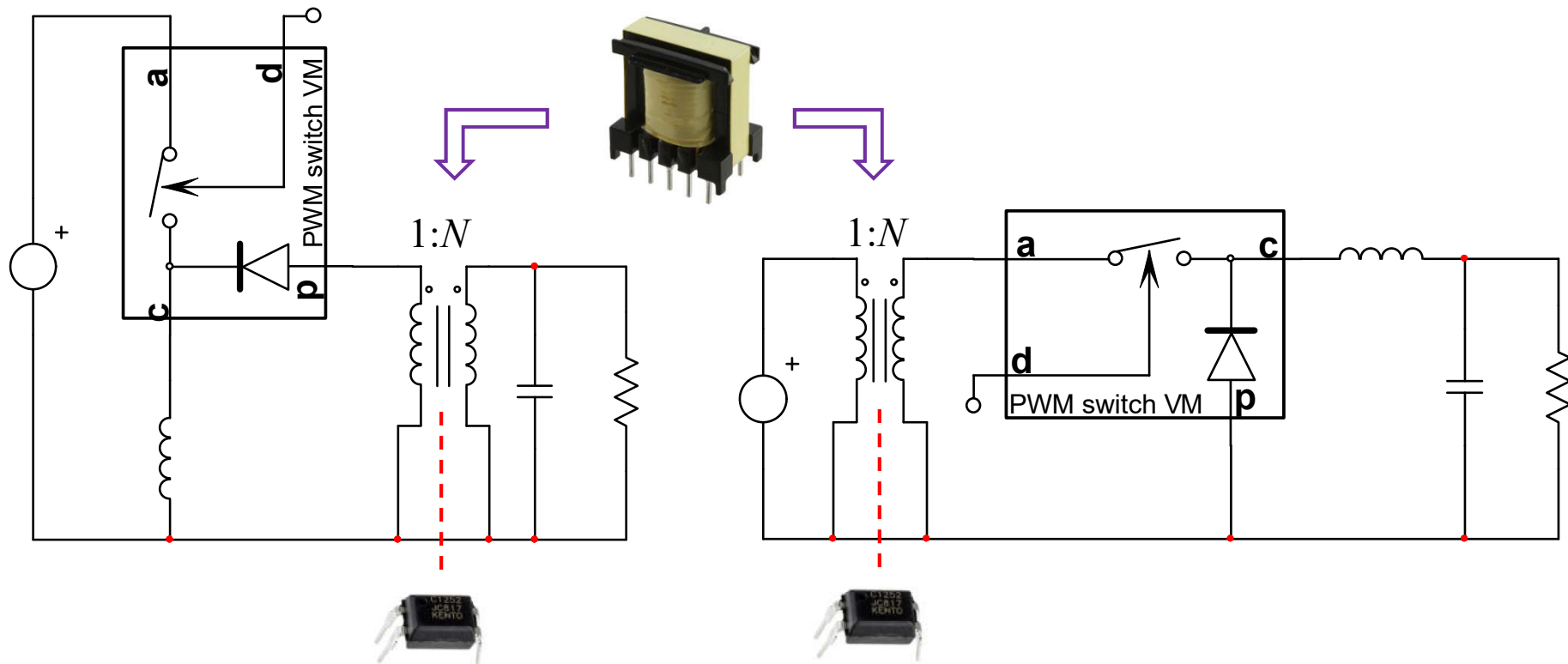V. Vorpérian, *Fast Analytical Techniques for Electrical and Electronic Circuits*, Cambridge University Press, 978-0-52162-442-8, 2002

It also Works for Isolated Structures


- Modeling a flyback or a forward converter is very convenient




- You can easily add an optocoupler when studying stability

CCM Common Passive Configuration

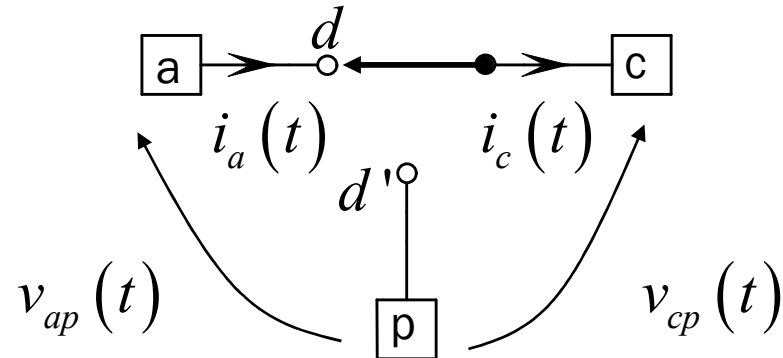- The PWM switch is a single-pole double-throw model




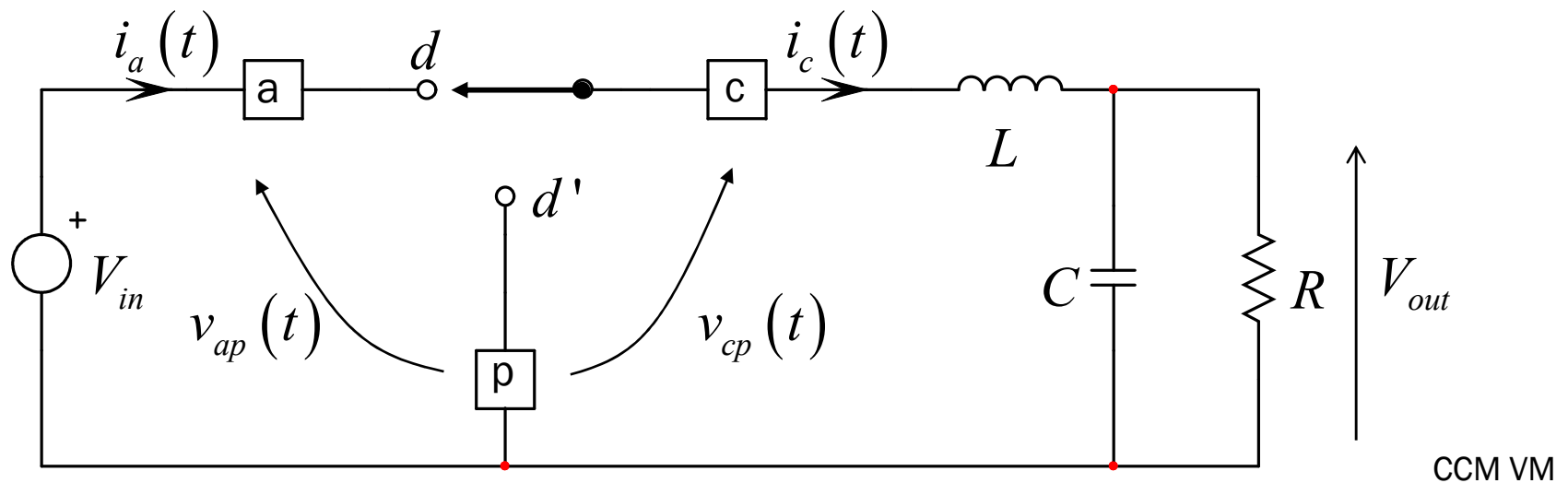- Install it in a buck and draw its terminal waveforms



The Common Passive Configuration

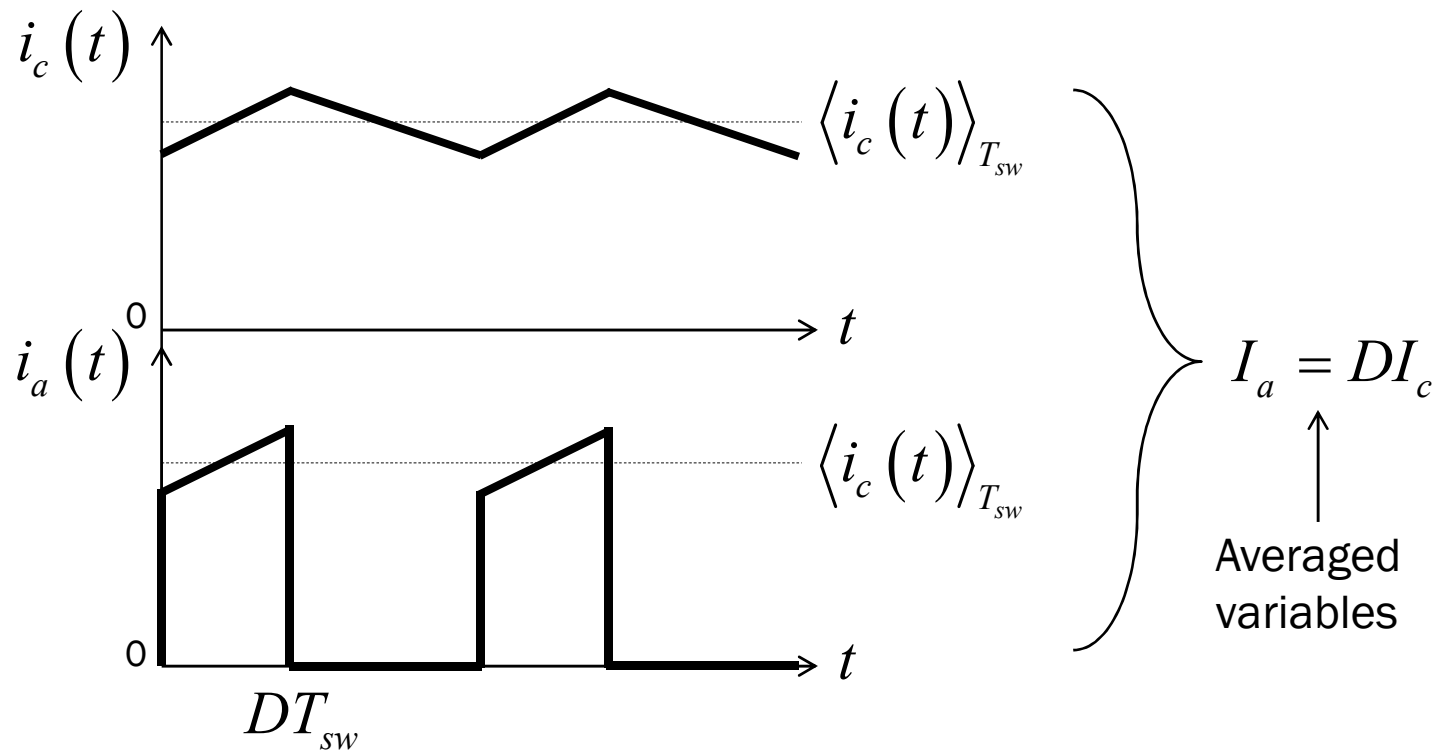- Average the current waveforms across the PWM switch




$$\langle i_a(t) \rangle_{T_{sw}} = I_a = \frac{1}{T_{sw}} \int_0^{DT_{sw}} i_a(t) dt = D \langle i_c(t) \rangle_{T_{sw}} = DI_c$$

CCM VM

The Common Passive Configuration

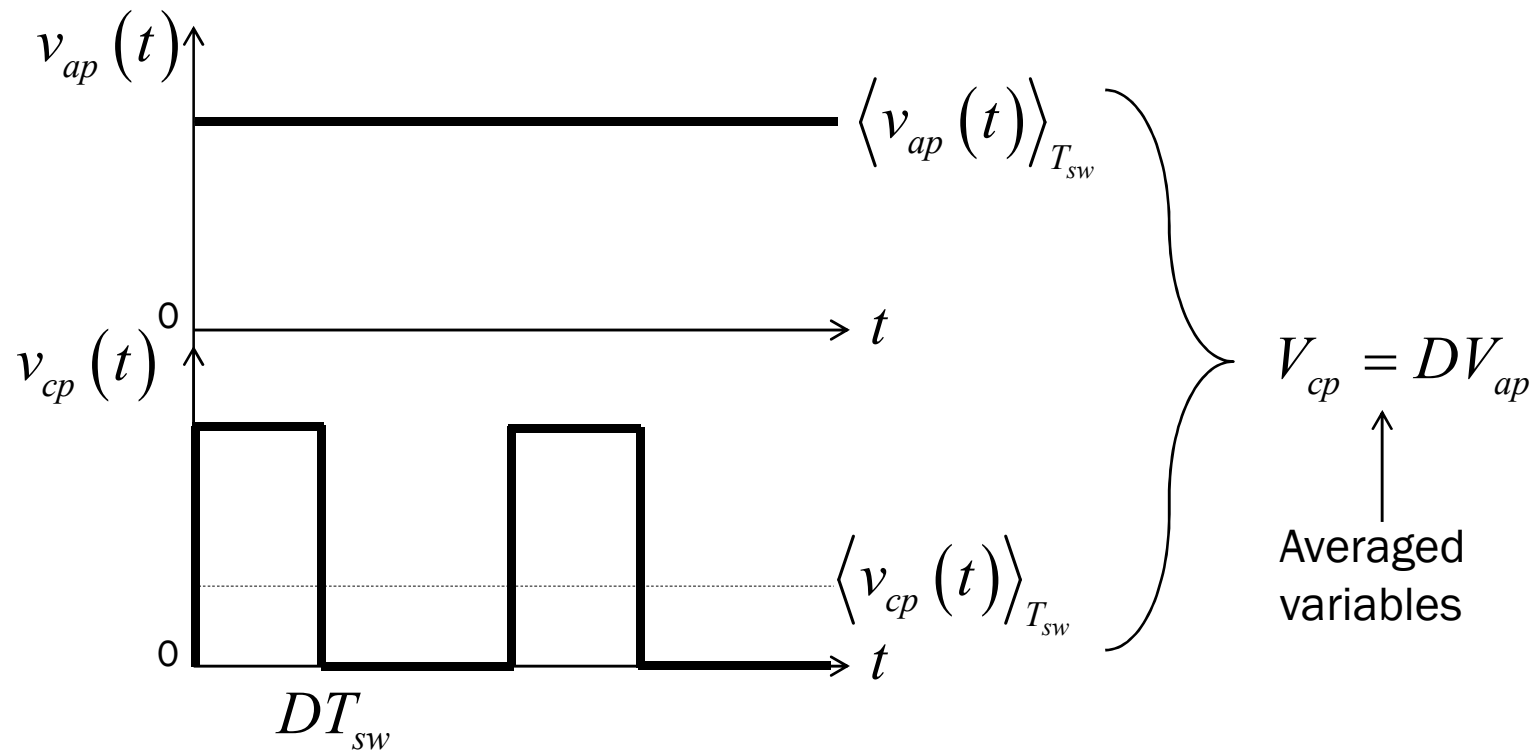- Average the voltage waveforms across the PWM switch




$$\langle v_{cp}(t) \rangle_{T_{sw}} = V_{cp} = \frac{1}{T_{sw}} \int_0^{DT_{sw}} v_{cp}(t) dt = D \langle v_{ap}(t) \rangle_{T_{sw}} = DV_{ap}$$


CCM VM

A Two-Port Representation

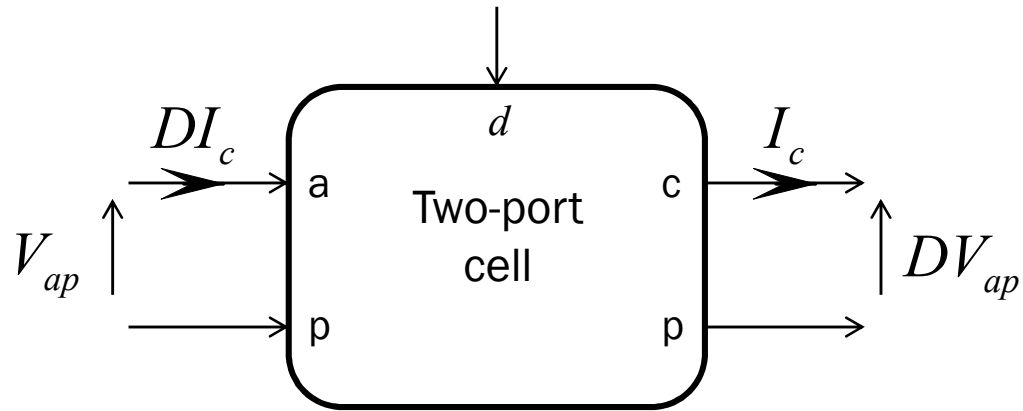- We have a link between input and output variables




- We can involve current and voltage sources

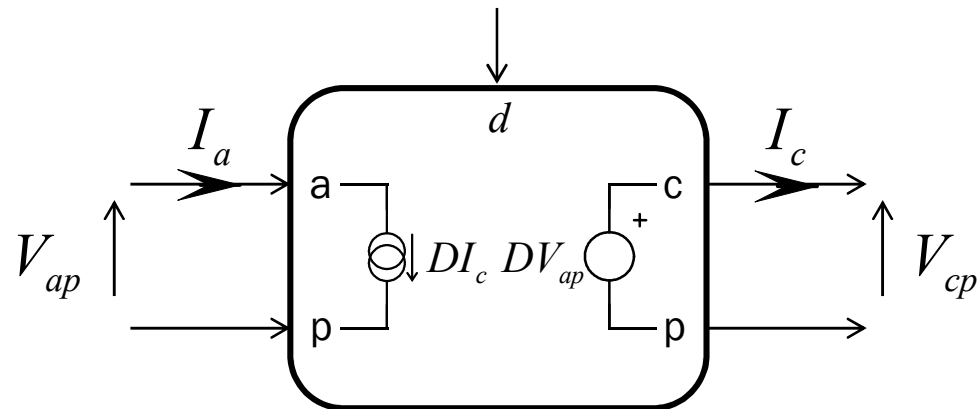


CCM VM

A Dc Transformer Model

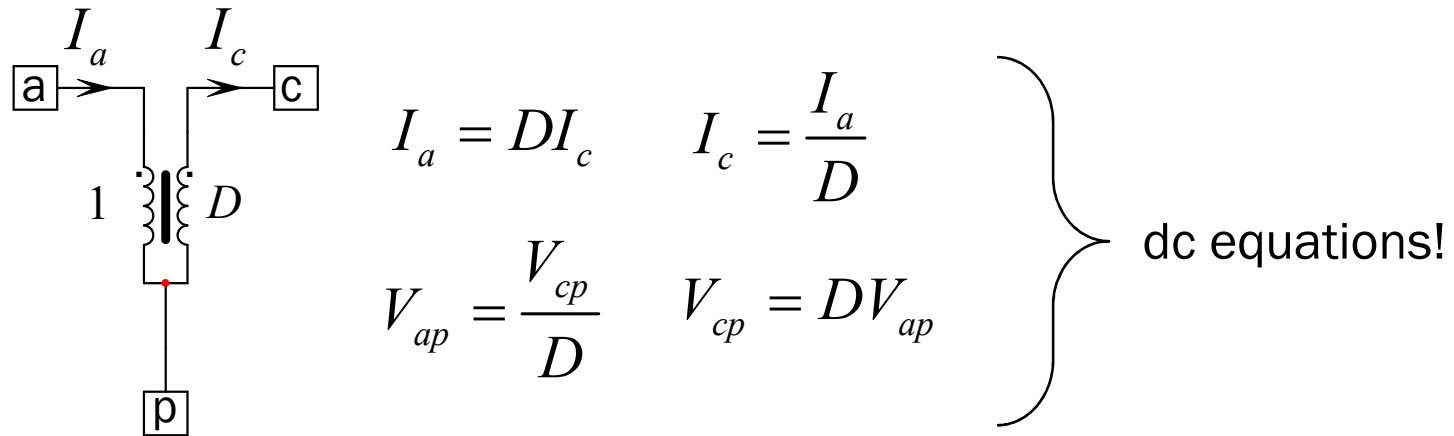- The large-signal model is a dc "transformer"!




- It can be plugged into any 2-switch CCM converter

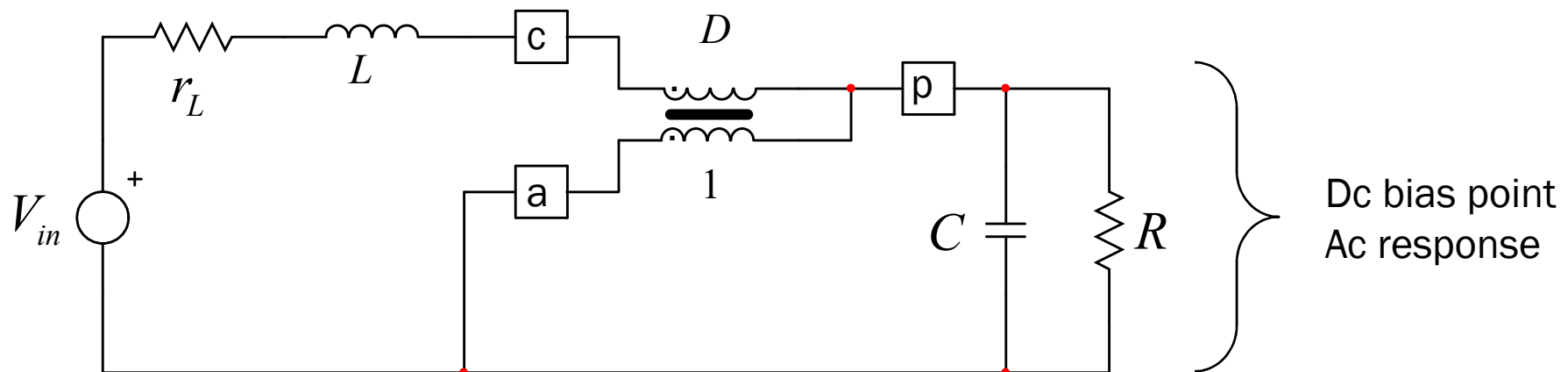


CCM VM

Simulate Immediately

- ❑ SPICE can get you the dc bias point

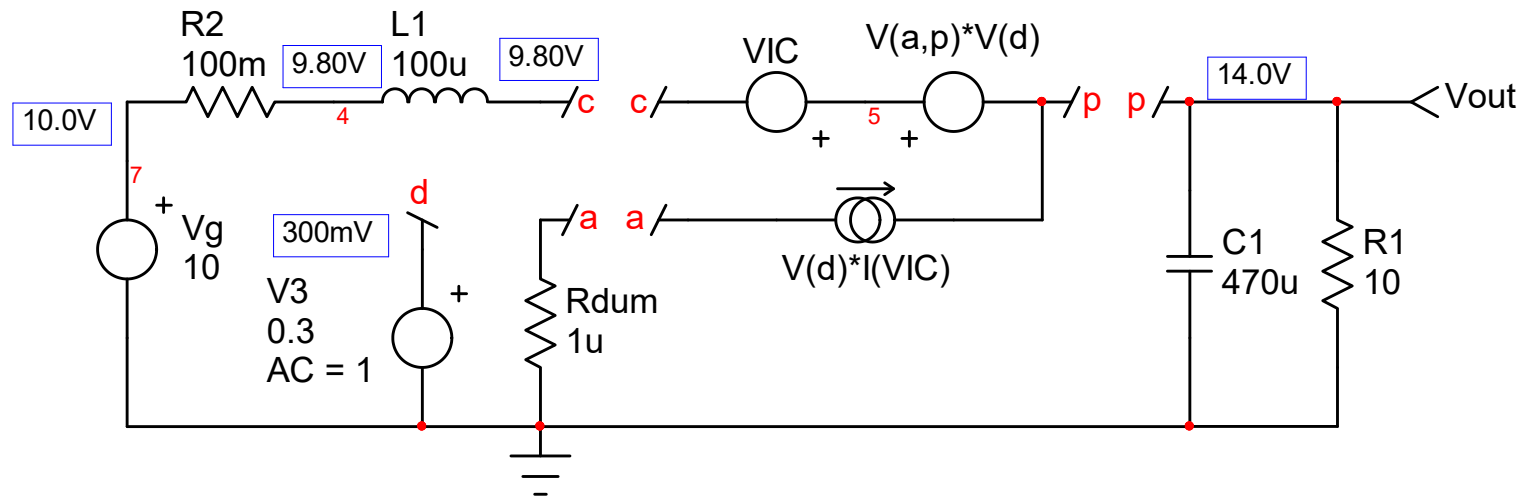


- ❑ ...but also the ac response as it linearizes the circuit

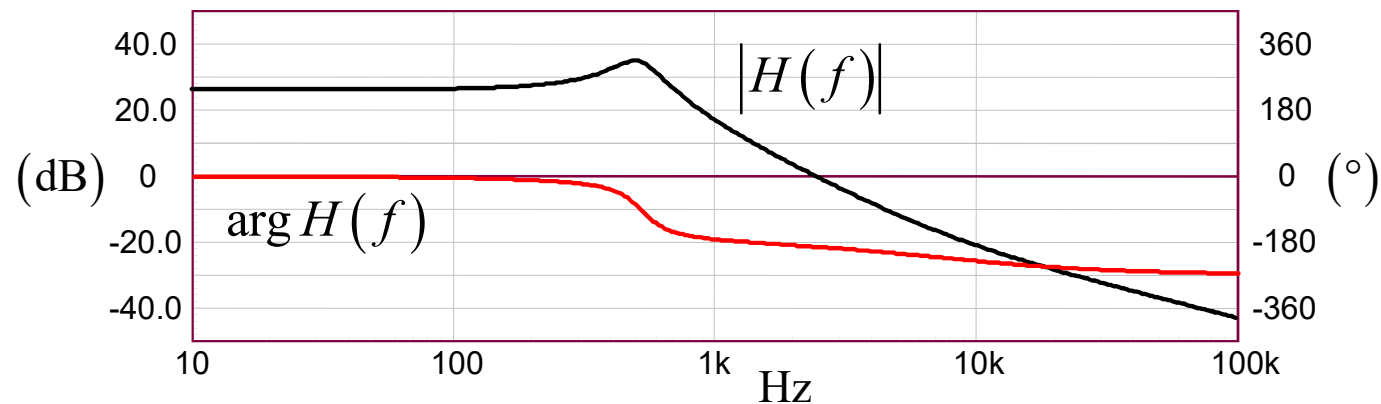

CCM VM


A Small-Signal Model

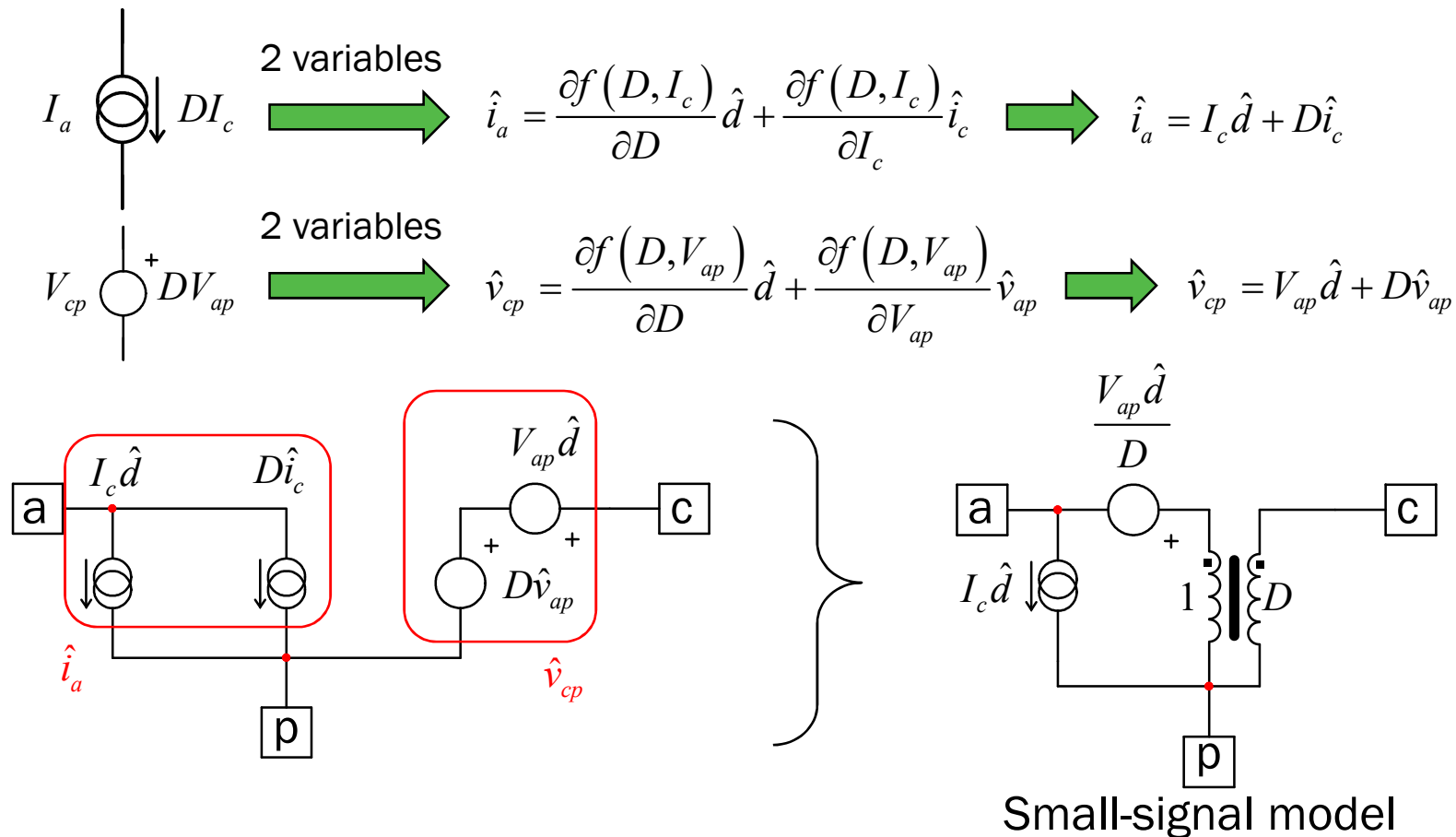- We need a small-signal version to get the ac response
- ❖ Perturb equations or run partial differentiation



Use it to Compute the Bias Point

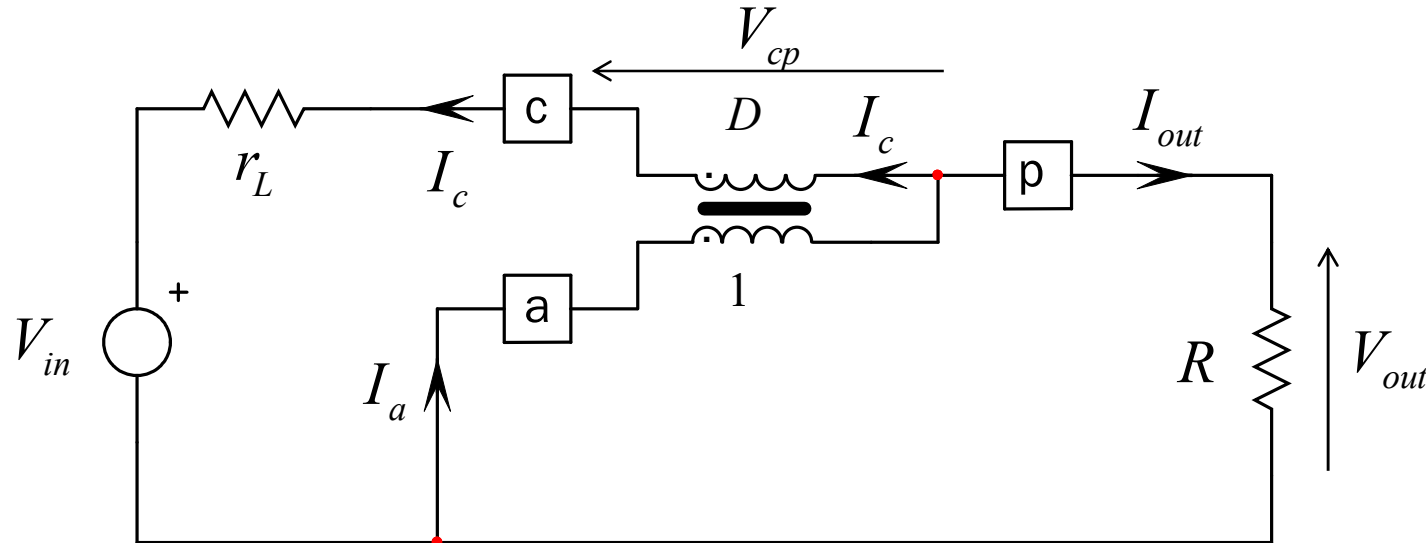- Derive the dc transfer function: open caps., short inductors



$$V_{out} = I_{out} R$$

$$V_{in} + r_L I_c - V_{cp} = V_{out}$$

$$V_{out} = (I_a - I_c) R$$

$$V_{in} + r_L I_c + D V_{out} = V_{out}$$

$$I_a = D I_c$$

$$I_c = \frac{V_{out} (1-D) - V_{in}}{r_L}$$

$$V_{out} = I_c (D-1) R$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{(1-D) - \frac{r_L}{(D-1)R}}$$




$$\frac{V_{out}}{V_{in}} = \frac{1}{D'} \frac{1}{1 + \frac{r_L}{RD'^2}}$$

CCM VM



Plotting Transfer Functions

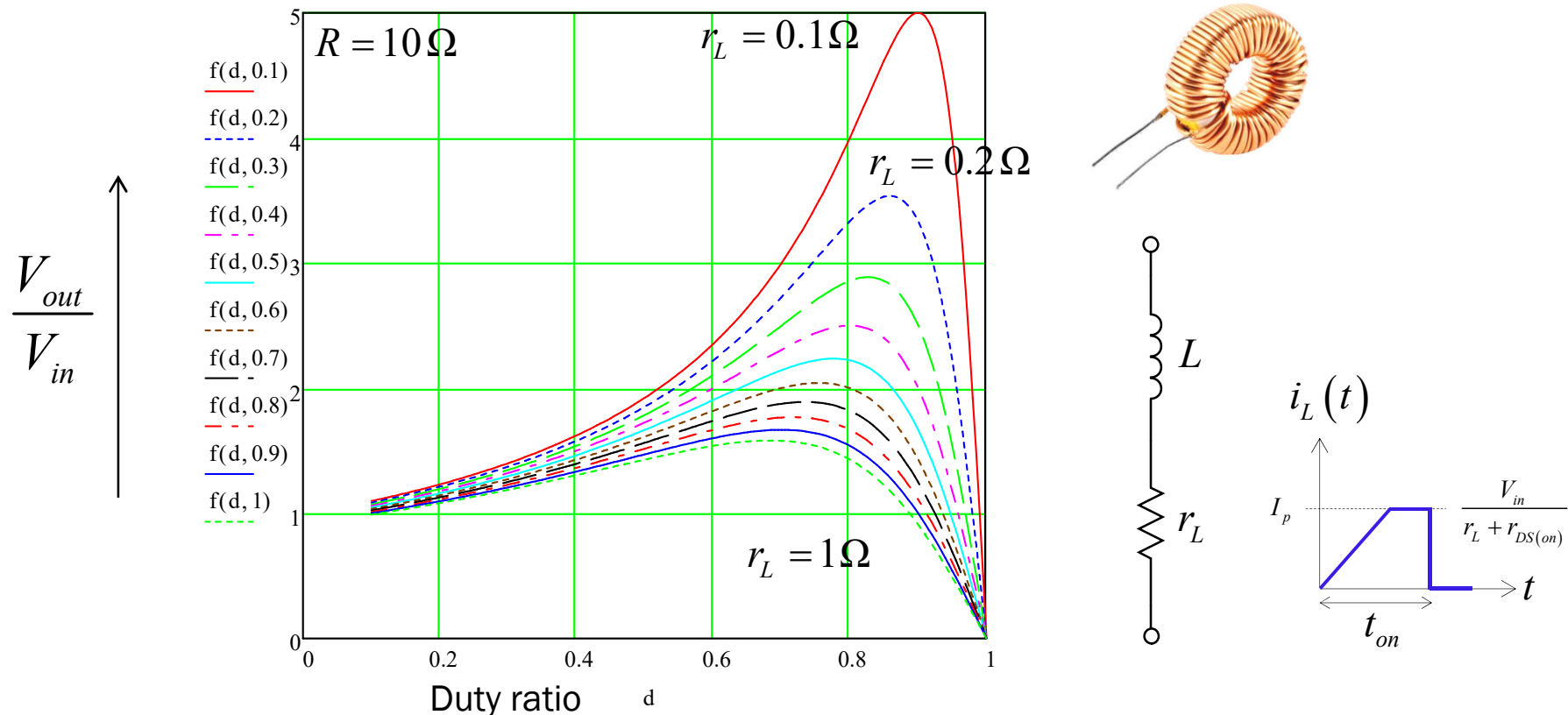- Plot the lossy boost transfer function in a snapshot




- Above a certain conversion ratio, latch-up can occur

CCM VM

Changing the Operating Mode

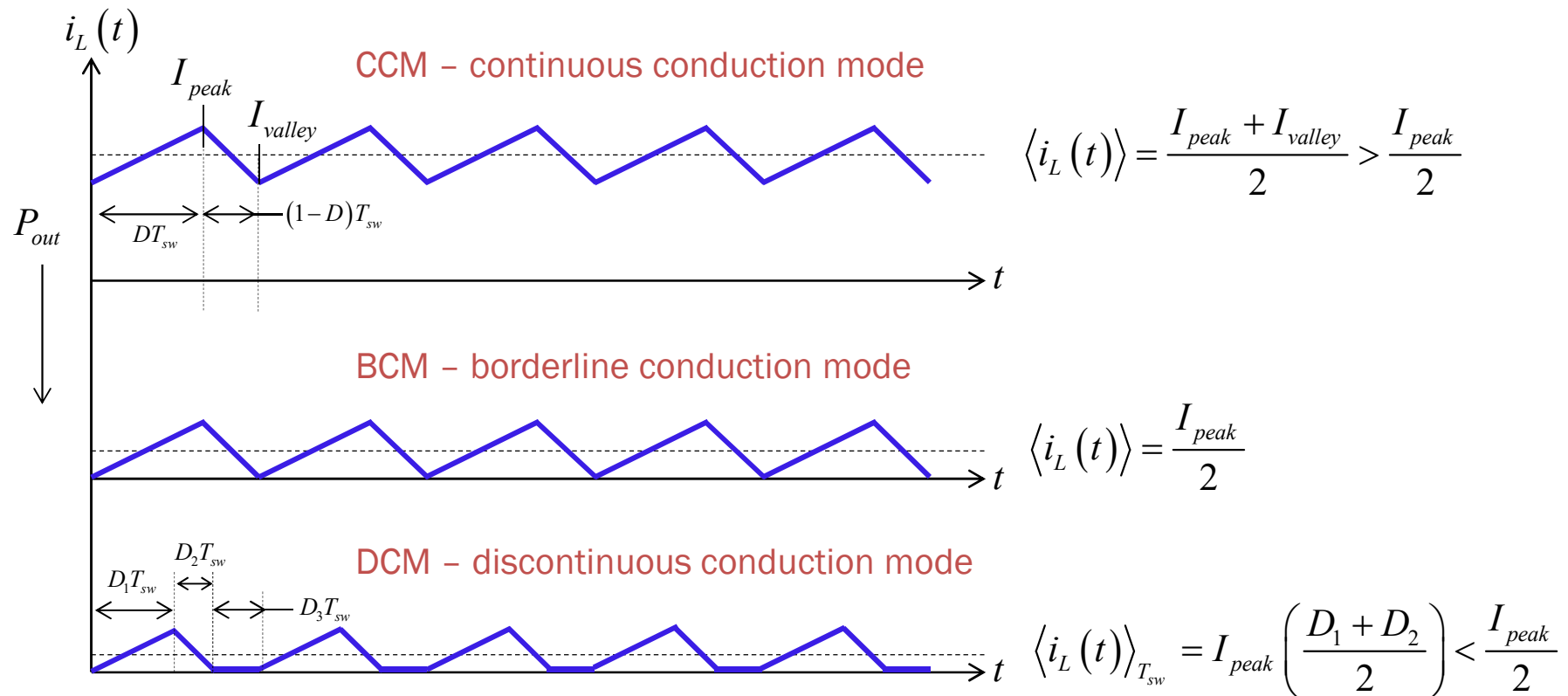- The average inductor current reduces as I_{out} gets smaller





- When the load becomes lighter, DCM is entered

CCM: continuous conduction mode – DCM: discontinuous conduction mode

A Similar Configuration in DCM

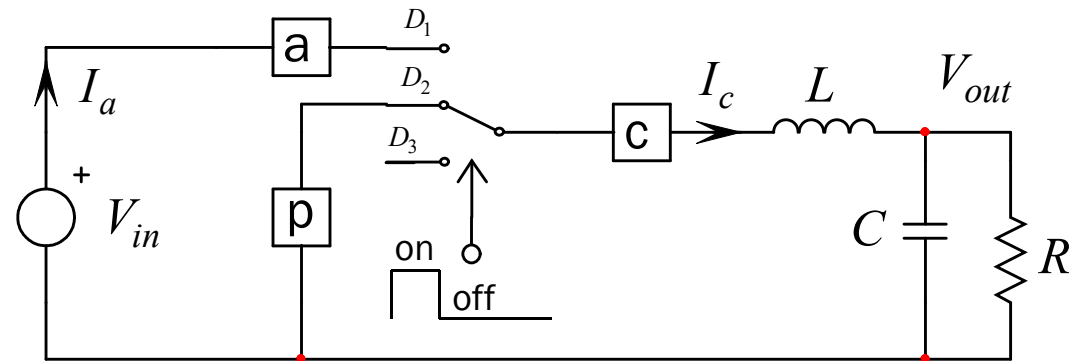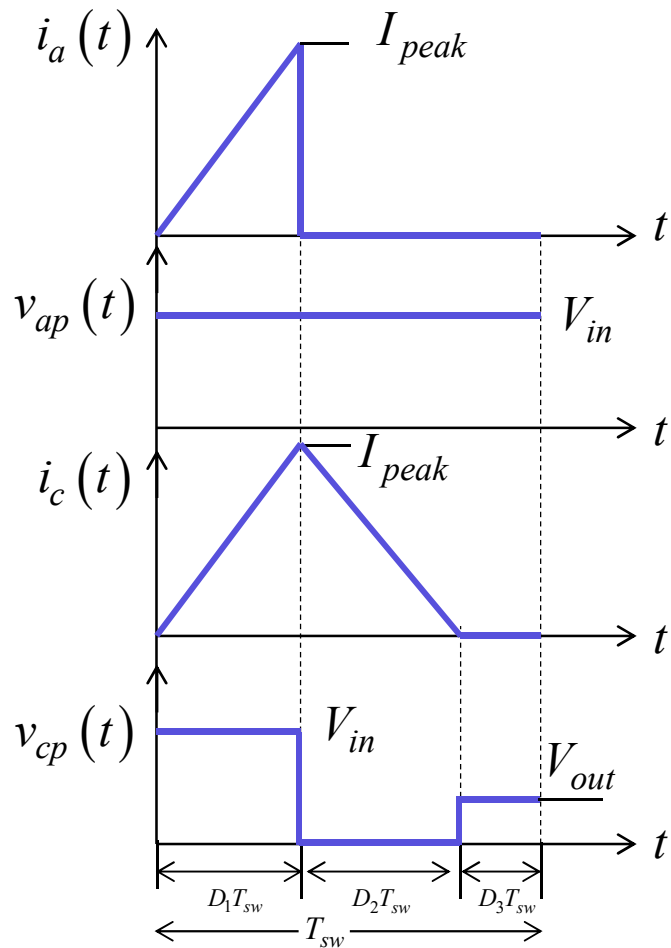□ Draw the waveforms in the "common passive" configuration



□ Average the waveforms:

$$I_a = \frac{I_{peak}}{2} D_1$$


$$I_c = \frac{I_{peak}}{2} D_1 + \frac{I_{peak}}{2} D_2 = \frac{I_{peak}}{2} (D_1 + D_2)$$

$$I_c = \frac{2I_a}{D_1} \frac{D_1 + D_2}{2} = I_a \frac{D_1 + D_2}{D_1}$$

DCM VM

Derive V_{cp} to Unveil the New Model

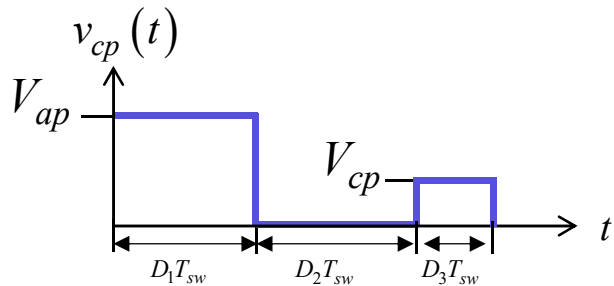
□ The addition of the third event complicates the equations



$$V_{cp} = V_{ap} D_1 + V_{cp} D_3 \quad D_1 + D_2 + D_3 = 1$$

$$V_{cp} = V_{ap} D_1 + V_{cp} (1 - D_1 - D_2)$$
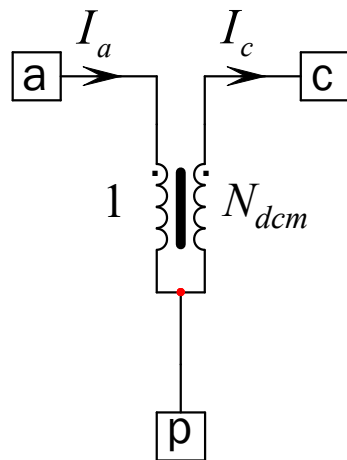
$$V_{cp} = V_{ap} \frac{D_1}{D_1 + D_2}$$



$$I_a = N_{dcm} I_c \quad I_c = \frac{I_a}{N_{dcm}}$$

$$V_{ap} = \frac{V_{cp}}{N_{dcm}} \quad V_{cp} = N_{dcm} V_{ap}$$

$$N_{dcm} = \frac{D_1}{D_1 + D_2} \rightarrow f(D_1)$$

Control input

DCM VM

Finally, Get the D_2 Value

- In DCM the inductor average voltage per cycle is always 0

$$\longrightarrow V_{cp} = V_{out}$$

- What is the averaged inductor peak current?

$$\left. \begin{aligned} I_{peak} &= \frac{\langle v_L(t) \rangle_{D_1 T_{sw}}}{L} D_1 T_{sw} \\ \langle v_L(t) \rangle_{D_1 T_{sw}} &= V_{ac} \end{aligned} \right\} V_{ac} = L \frac{I_{peak}}{D_1 T_{sw}}$$

- The peak current uses a previous expression

$$I_c = \frac{I_{peak}}{2} (D_1 + D_2) \longrightarrow I_{peak} = \frac{2I_c}{D_1 + D_2}$$



$$\longrightarrow D_2 = \frac{2LF_{sw}}{D_1} \frac{I_c}{V_{ac}} - D_1$$

DCM VM

Simulate with the DCM Model

☐ Check the converter is operating in DCM:
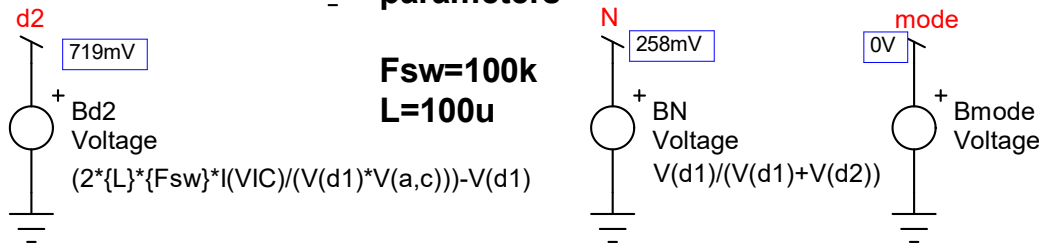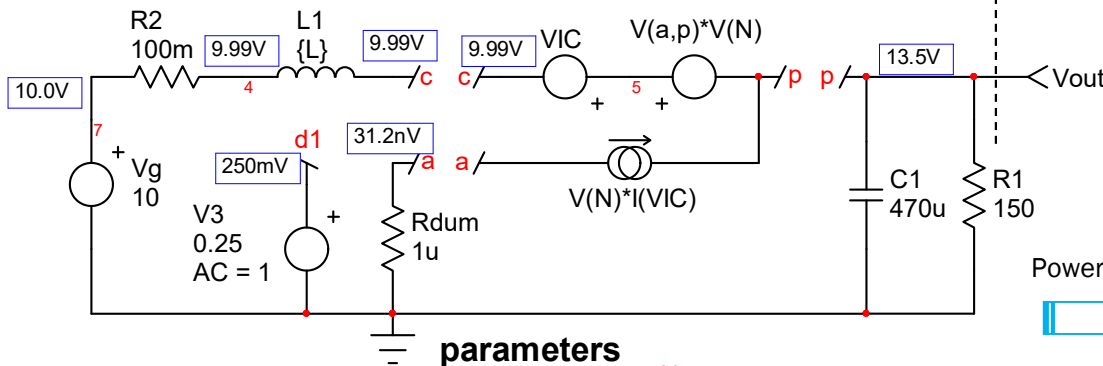
$$R_{crit} = \frac{2F_{sw}LV_{out}^2}{V_{in}^2 \left(1 - \frac{V_{in}}{V_{out}}\right)}$$




parameters

Fsw=100k
L=100u

$$\frac{(2 * \{L\} * \{Fsw\} * I(VIC) / (V(d1) * V(a,c))) - V(d1)}{1 : 0} > (1 - V(d1)) ?$$

Power stage

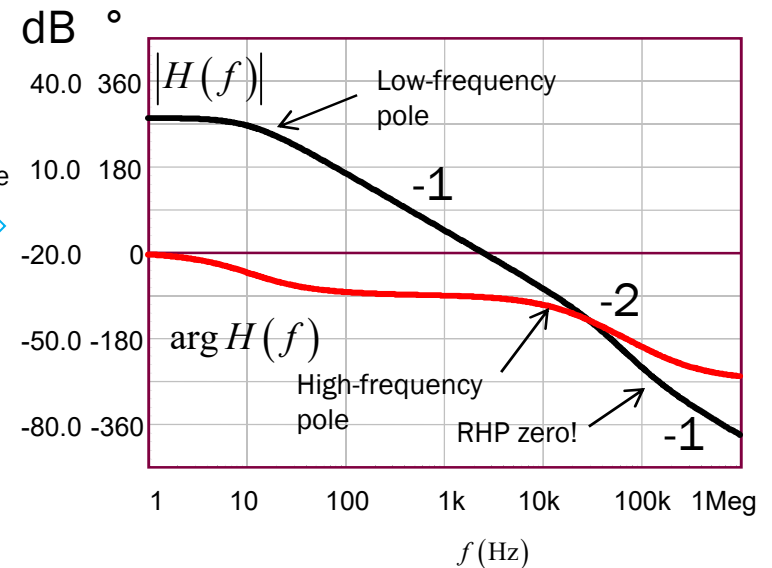

☐ In light load, the converter is still a second-order system

❖ There is a high-frequency right-half-plane zero

For a comprehensive analysis see APEC 2013 seminar: *Small-Signal Modeling and Analytical Analysis of Power Converter*





Course Agenda

- Blocks in a Switching Converter
- Introduction to Small-Signal Modeling
- Analytical Analysis of an Output Stage**
- Simulation Models - Averaged or Switched?
- Crossover Frequency and Phase Margin
- Compensation Strategy
- Experiments on Prototypes
- Conclusion



The Project: A VM Boost Converter

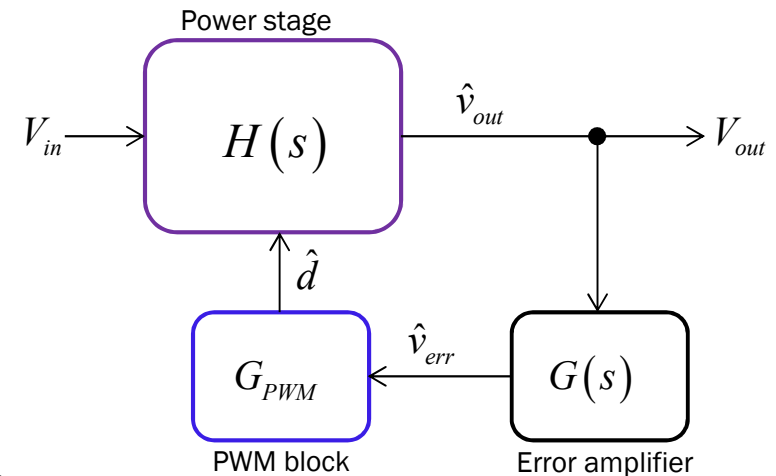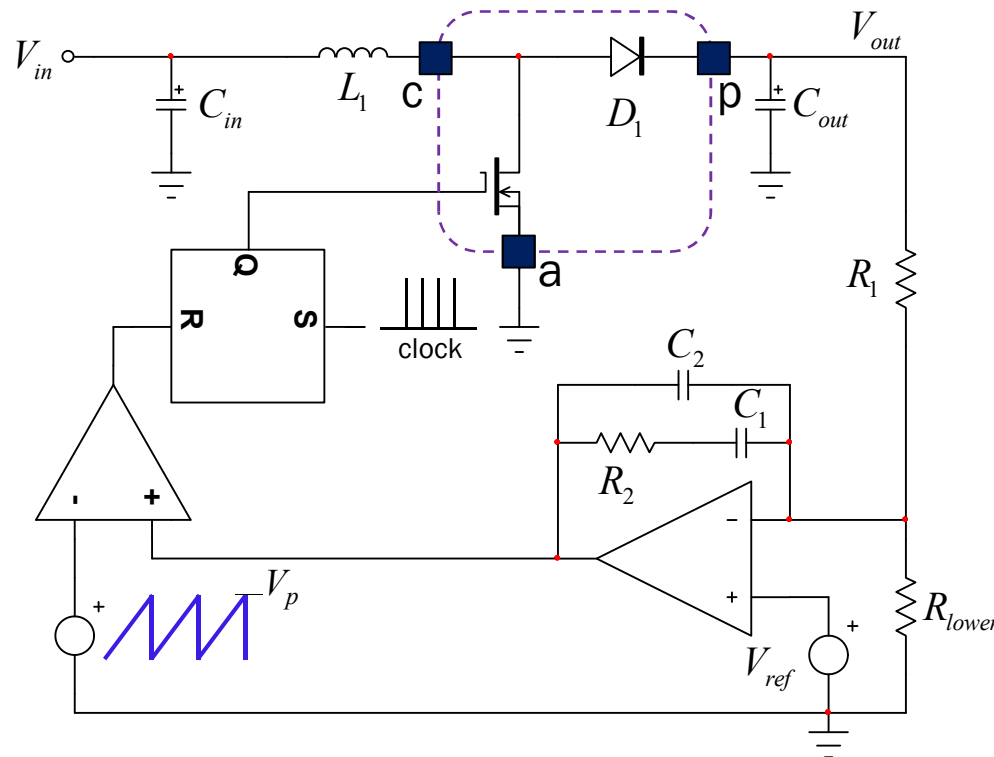- We want to build and stabilize a voltage-mode boost converter
- ❖ Input range is 8-12 V, output voltage is 15 V, 1 A




- Identify the blocks and model them separately

The Naturally-Sampled Modulator

- It's role is to convert a voltage V_{err} into a duty ratio D



$$d(t) = \frac{v_{err}(t)}{V_p} \xrightarrow[\text{over } T_{sw}]{\text{average}} D(V_{err}) = \frac{V_{err}}{V_p} \longrightarrow G_{PWM} = \frac{dD(V_{err})}{V_{err}} = \frac{1}{V_p}$$

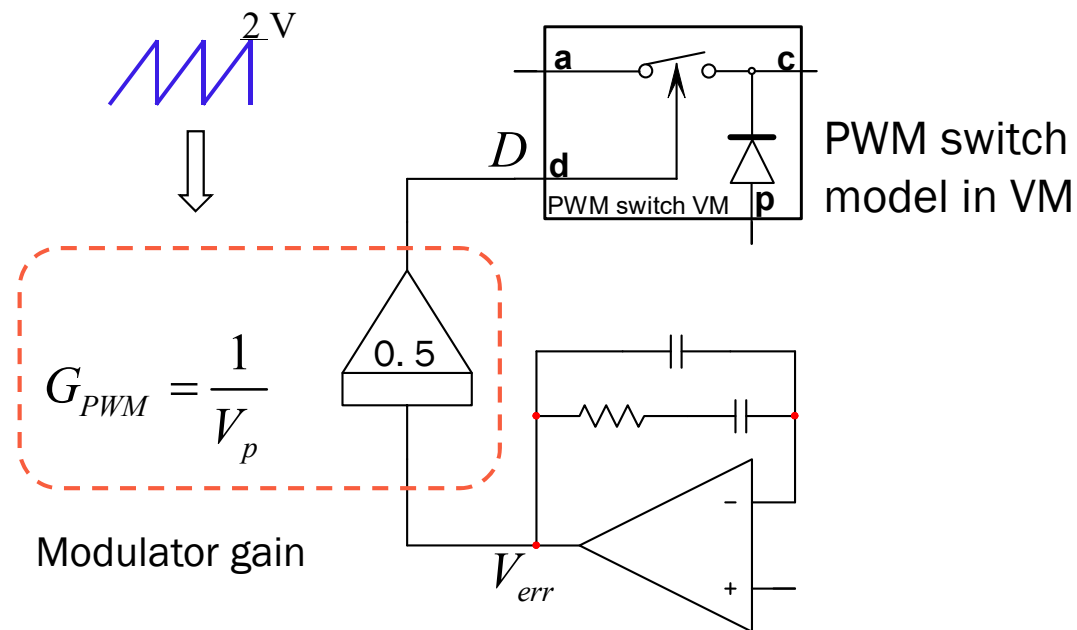- It is a simple block inserted before the D input of the model



A Flat Frequency Response

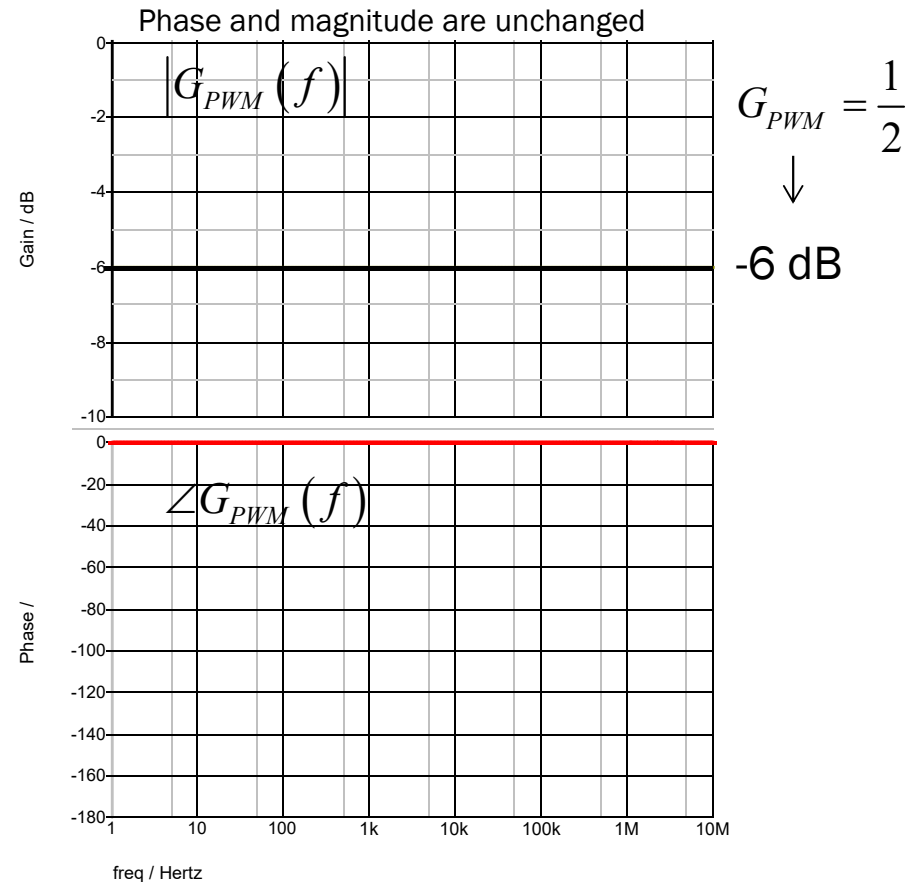
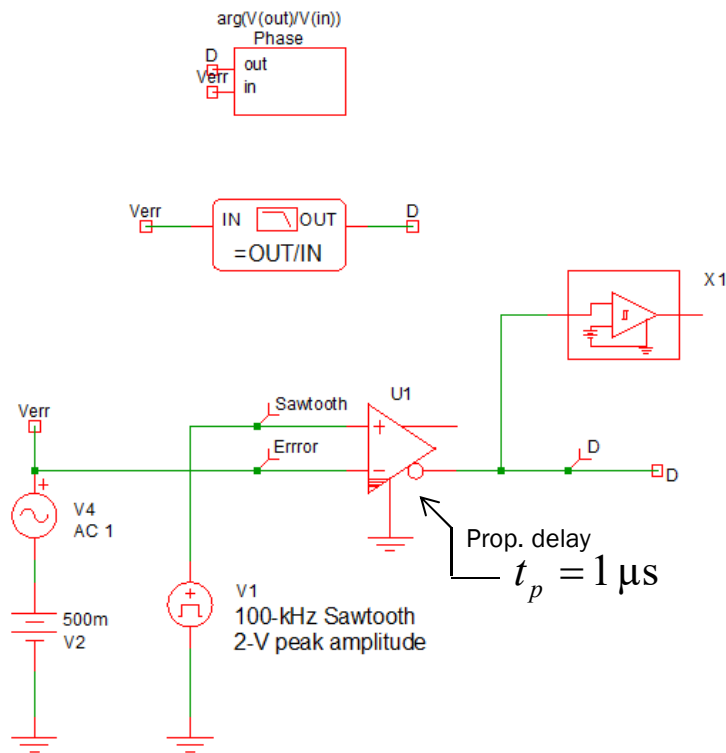
- This modulator can be simulated with Simplis®



- With a perfect comparator, no lag in the phase response

Watch for the Comparator Delay

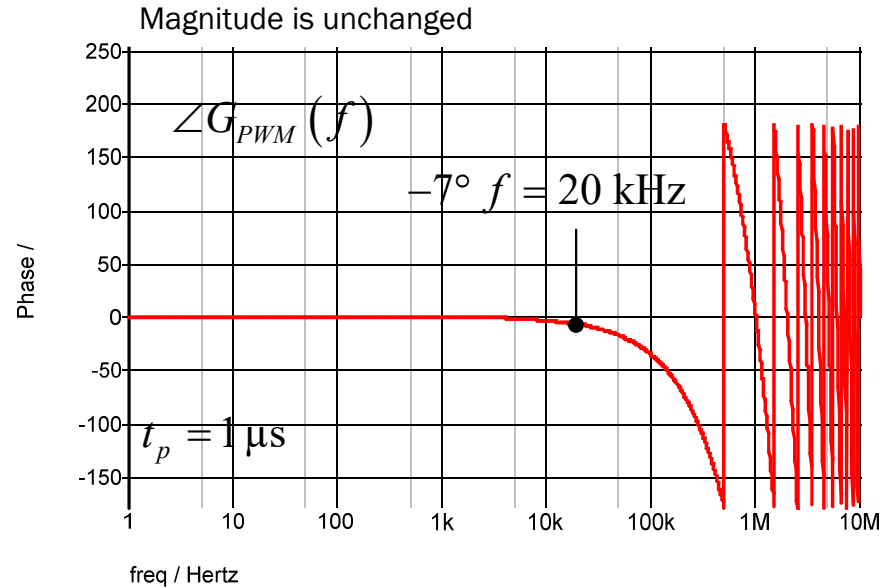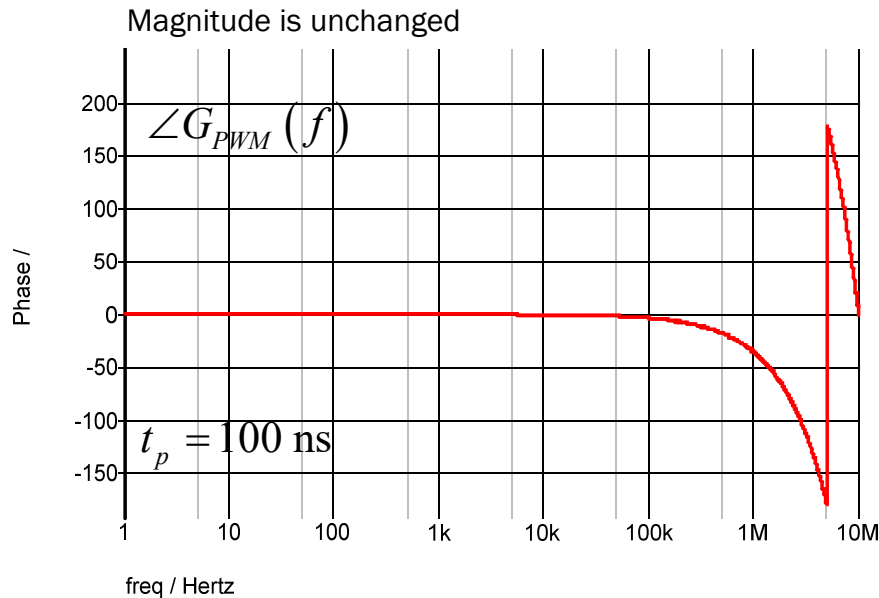
- The comparator is affected by a propagation delay t_p




- Assume you reduce bias currents for standby, prop. delay rises!
- ❖ Phase margin can be affected and stability at stake
- ❖ For your high-bandwidth designs, you must include this delay

Model the Delay for High-Speed Designs

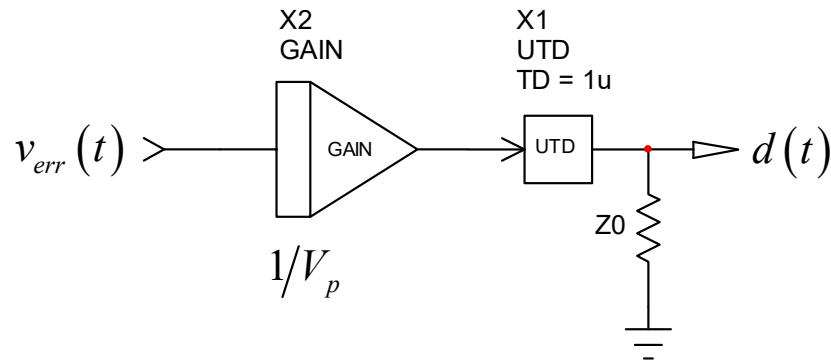- It can be a simple delay line in a SPICE simulation




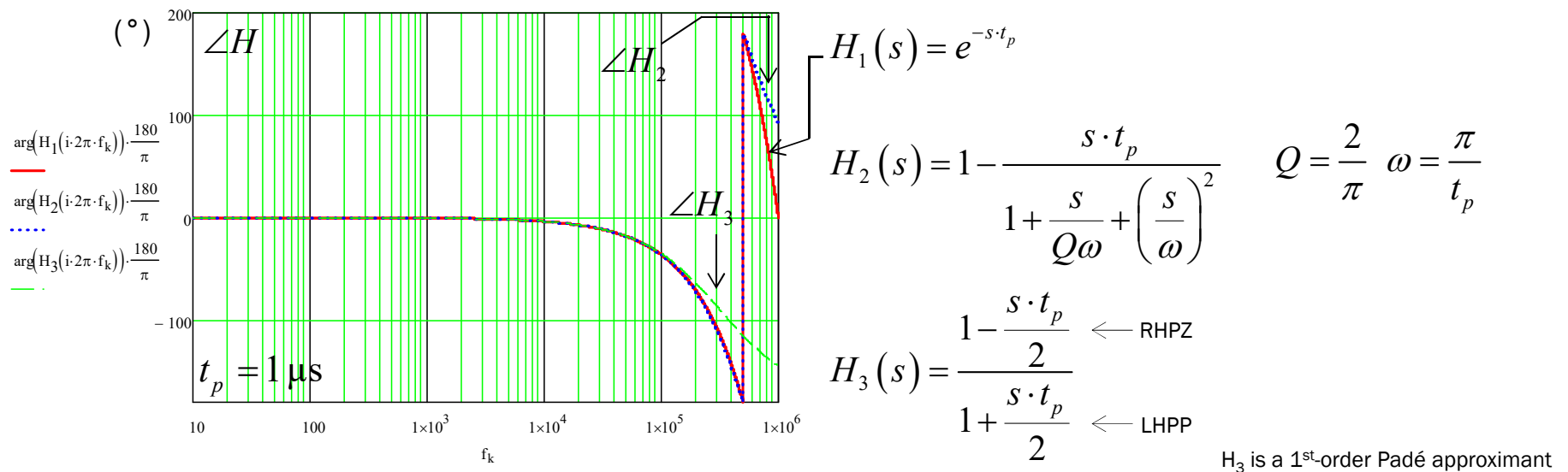- First- and second-order approximants can also be used



Analyzing the CCM Boost Converter

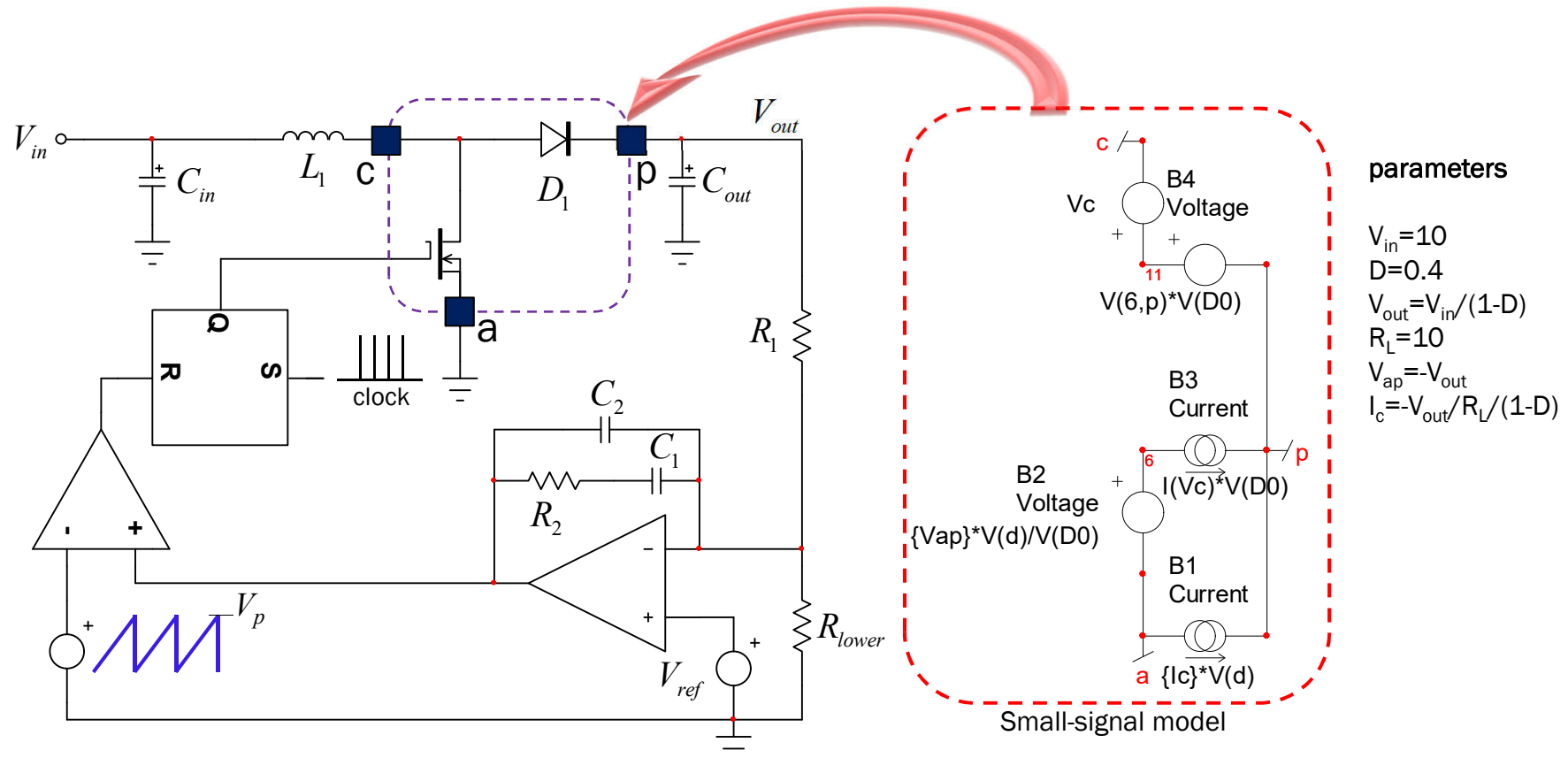- Plug the small-signal model of the PWM switch in the schematic





- Capture the new schematic featuring the linear sources

Compare Large- and Small-Signal

- Confirm both approaches deliver the exact same response

parameters

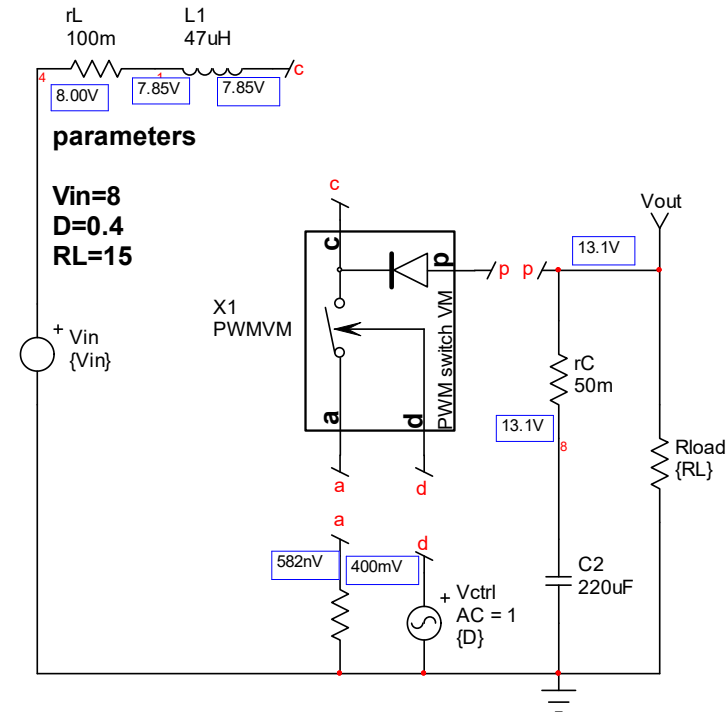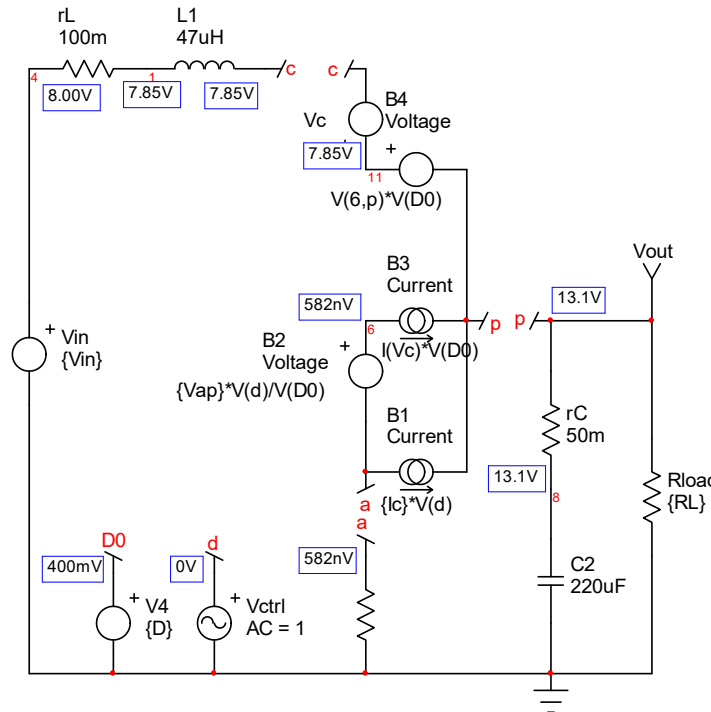
$V_{in}=8$
 $D=0.4$
 $V_{out}=V_{in}/(1-D)$
 $R_L=15$
 $V_{ap}=-V_{out}$
 $I_c=-V_{out}/R_L/(1-D)$



- Run this sanity check to confirm the linearized model is ok
- ❖ Operating points and dynamic responses must match


We are Good to Go!

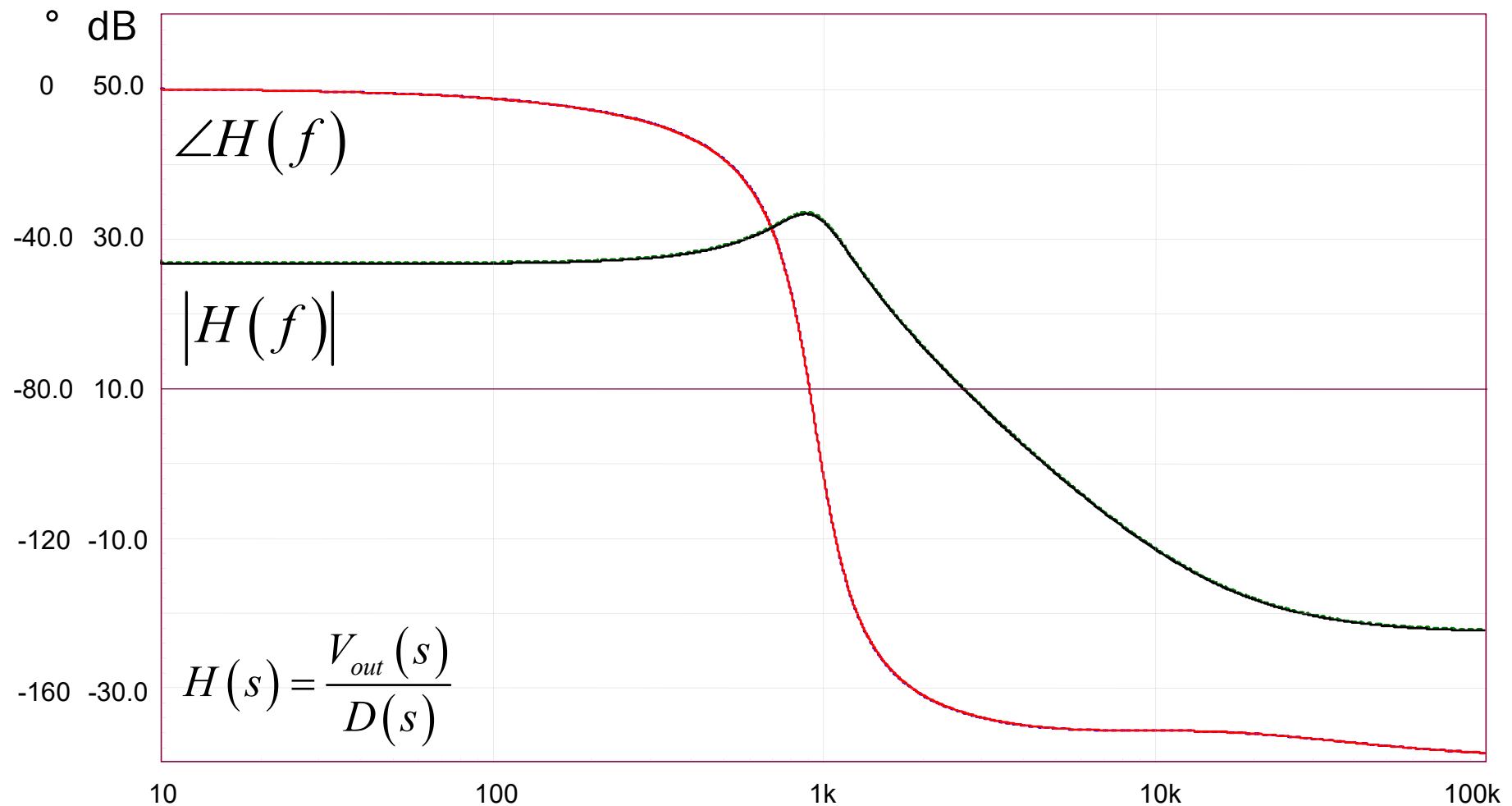☐ Refer to these curves after rearranging or simplifying the circuit



Rearrange and Simplify the Sketch

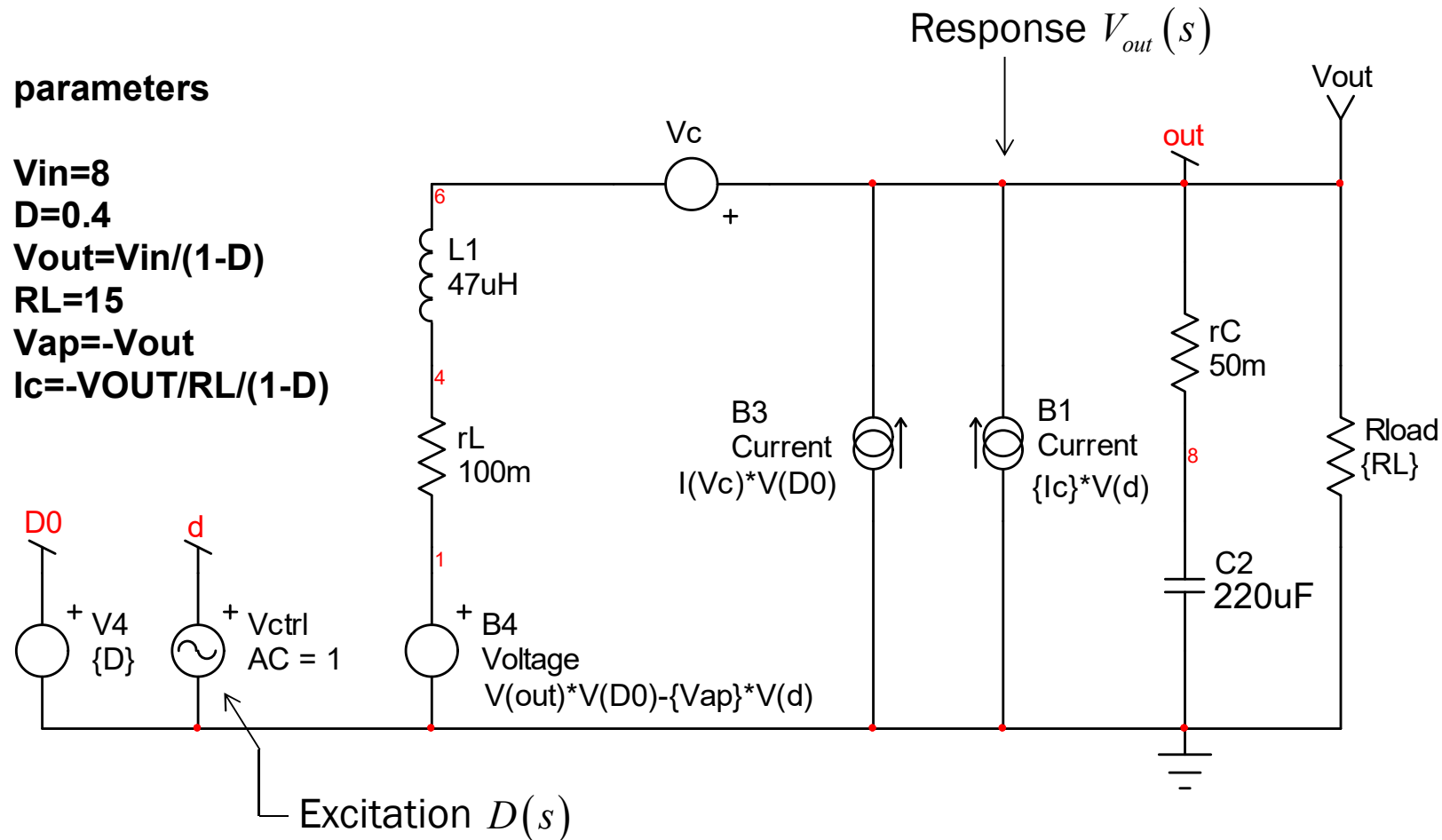□ We want the control to output transfer function $\frac{V_{out}(s)}{D(s)}$



How to Determine the Transfer Function?


- We can use the Fast Analytical Circuits Techniques

$$\frac{V_{out}(s)}{D(s)} = H_0 \frac{1 + a_1s + a_2s^2}{1 + b_1s + b_2s^2}$$

↑ Same dimension

$$\left. \begin{array}{l} a_1 \text{ and } b_1 \text{ [s]} \\ a_2 \text{ and } b_2 \text{ [s}^2\text{]} \end{array} \right\} \begin{array}{l} a_1 = \tau_1 + \tau_2 \\ \text{Nulled response} \\ a_2 = \tau_1\tau_2^1 \end{array} \quad \begin{array}{l} b_1 = \tau_1 + \tau_2 \\ \text{Zeroed excitation} \\ b_2 = \tau_1\tau_2^1 \end{array}$$

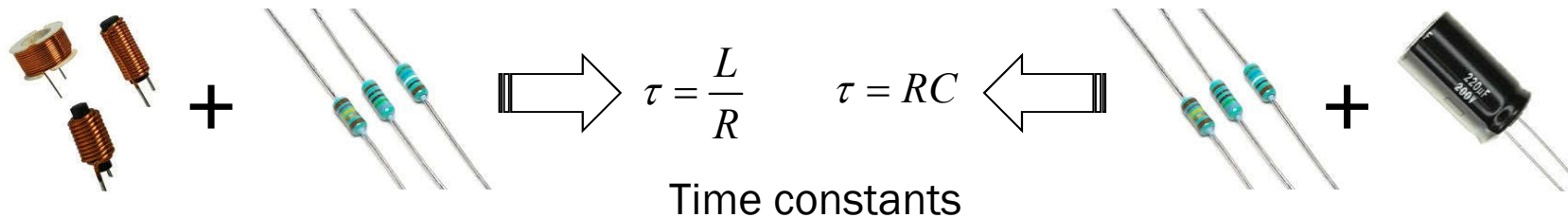- Energy-storing elements are combined with resistances




- Capacitors and inductors behave differently for $s = 0$ and $s \rightarrow \infty$



Fast Analytical Techniques at a Glance

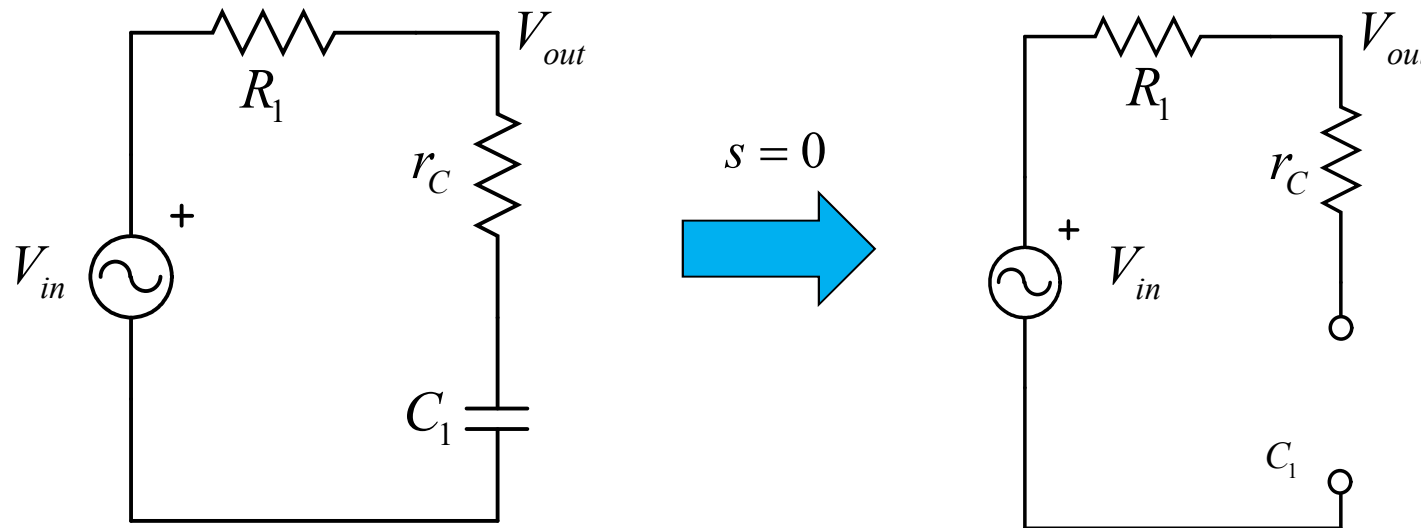- Look at the circuit for $s = 0$
 - Capacitors are open circuited
 - Inductors are short circuited
- } SPICE operating point calculation




- Determine the gain in this condition

$$H_0 = V_{out} / V_{in} = 1$$

Fast Analytical Techniques at a Glance

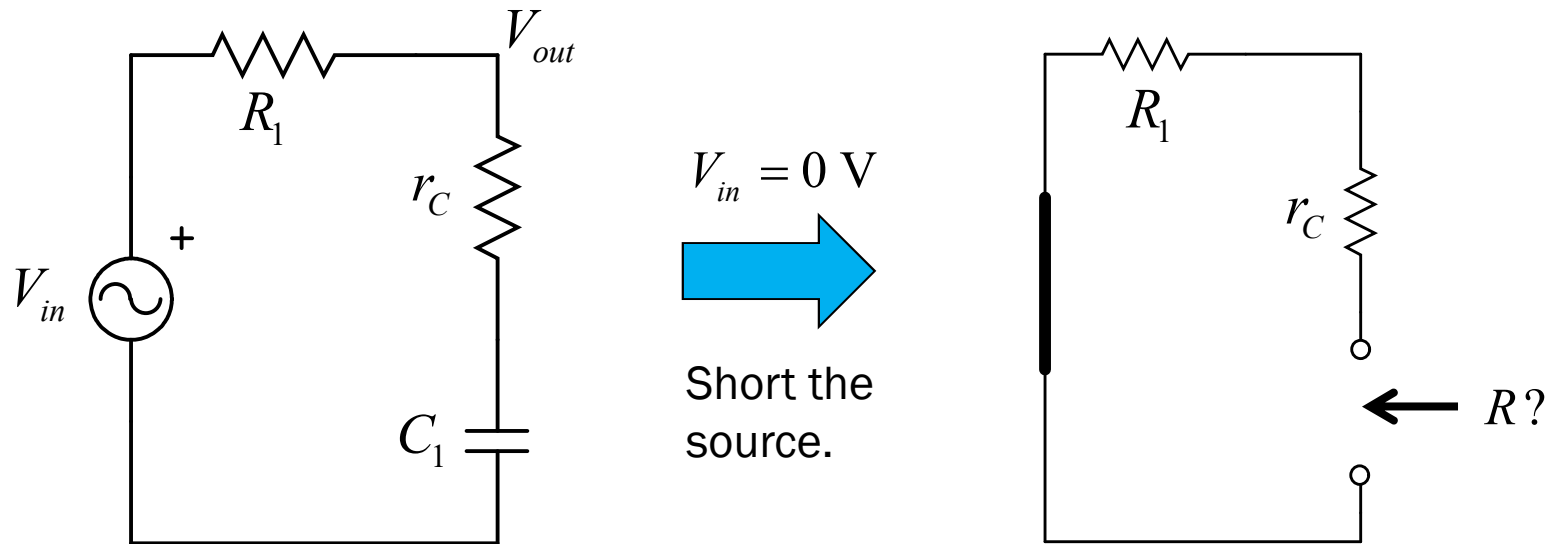
- Look at the resistance driving the storage element
 1. When the excitation is turned off, $V_{in} = 0$ V



- Remove the capacitor and look into its terminals
 - The first time constant is $\tau_1 = (r_C + R_1) C_1$

Fast Analytical Techniques at a Glance

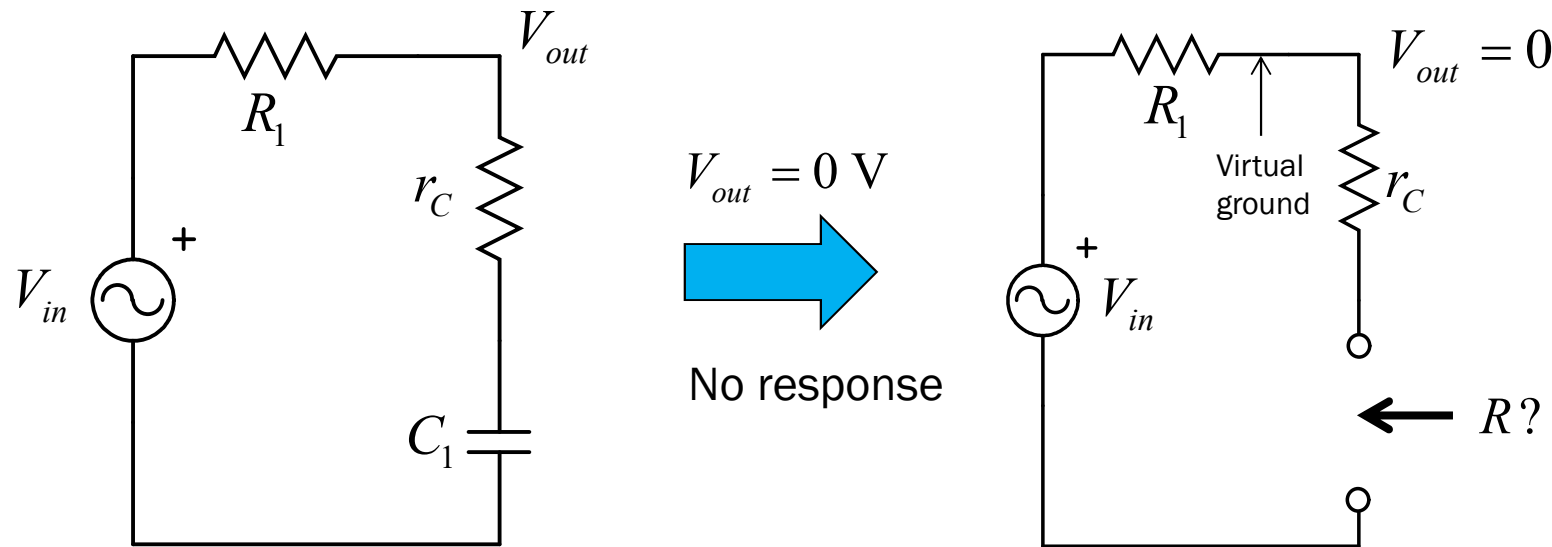- Look at the resistance driving the storage element
- 2. When the excitation is back but $V_{out} = 0$ V



- Remove the capacitor and look into its terminals
- The second time constant is $\tau_2 = r_C C_1$

Combining Time Constants

- By combining time constants, we have

$$H(s) = H_0 \frac{1 + s\tau_2}{1 + s\tau_1} = \frac{1 + sr_C C_1}{1 + s(r_C + R_1)C_1}$$


- Rearrange the equation to unveil a pole and a zero

$$H(s) = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \left. \vphantom{H(s)} \right\} \begin{aligned} \omega_z &= \frac{1}{r_C C_1} & H_0 &= 1 \\ \omega_p &= \frac{1}{(r_C + R_1)C_1} \end{aligned}$$

- This is a *low-entropy* expression

Higher-Order Systems

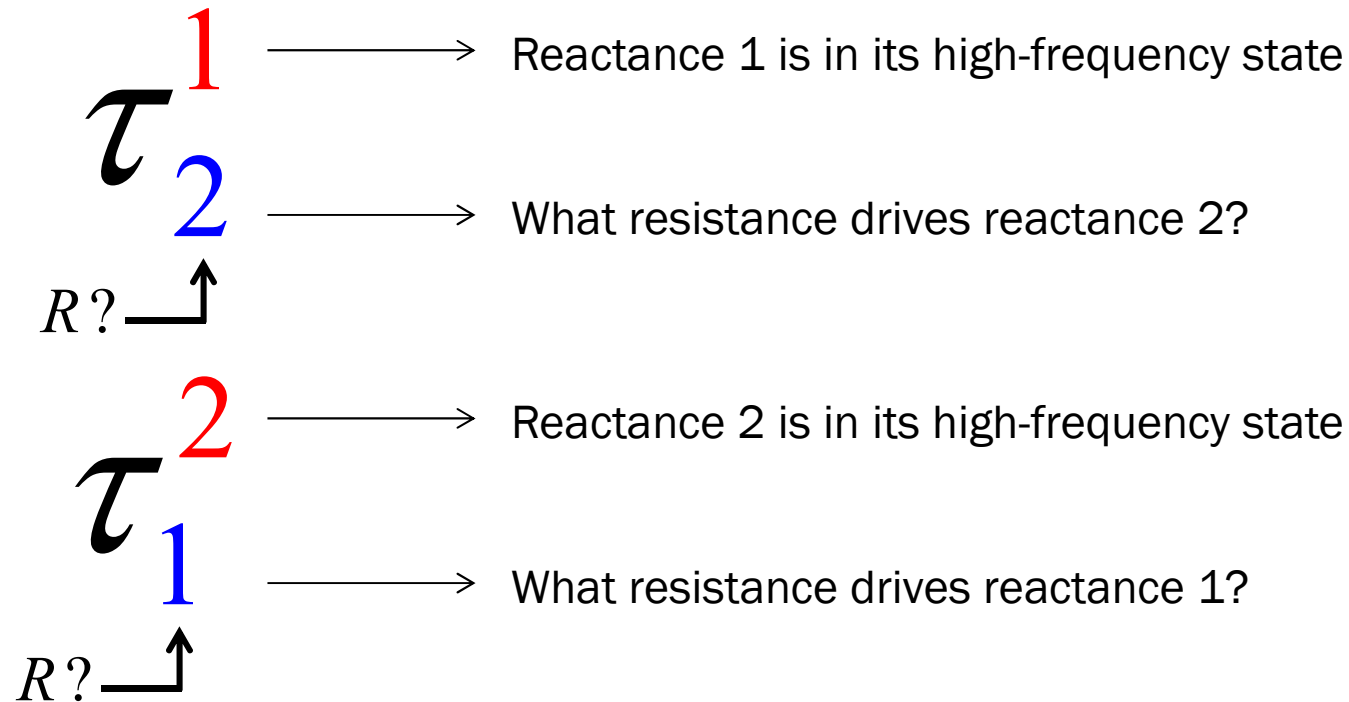- Set one reactance into its high-frequency state




- There is redundancy: pick the simplest result


$$b_2 = \tau_1 \tau_2^1 \iff b_2 = \tau_2 \tau_1^2$$

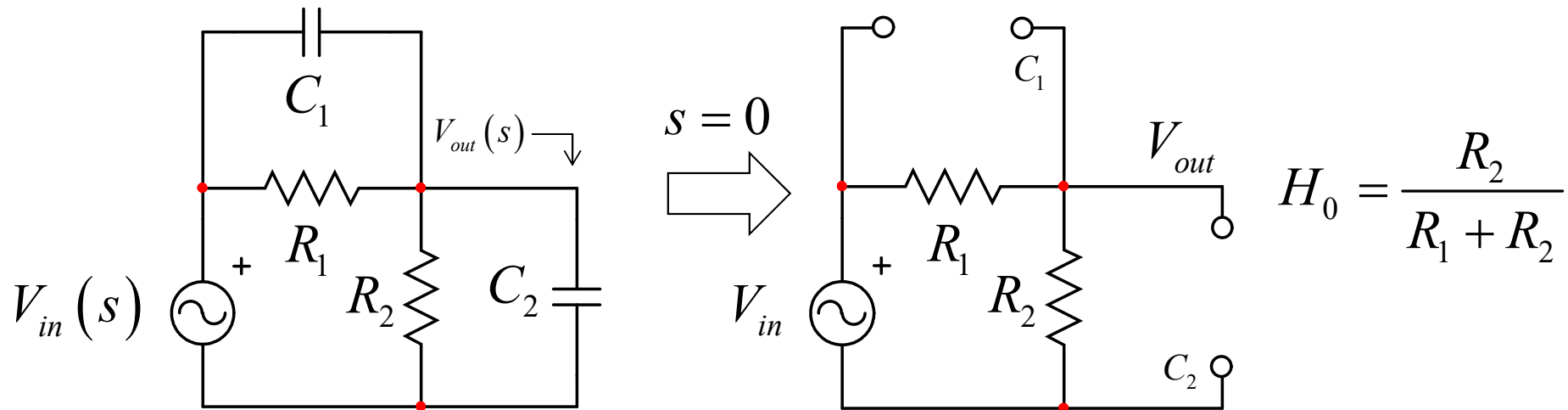Example with Capacitors

□ Assume the following 2-capacitor circuit




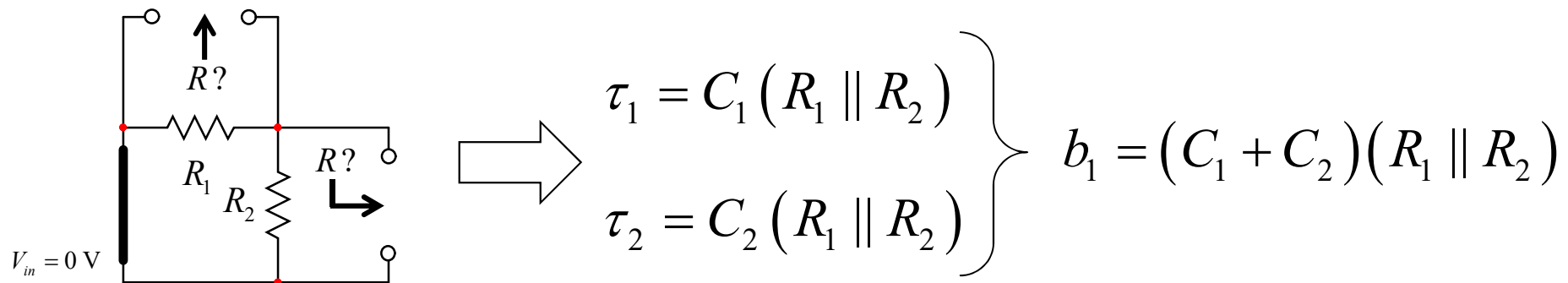□ Determine the two time constants while V_{in} is 0 V




Determining the Higher-Order Term

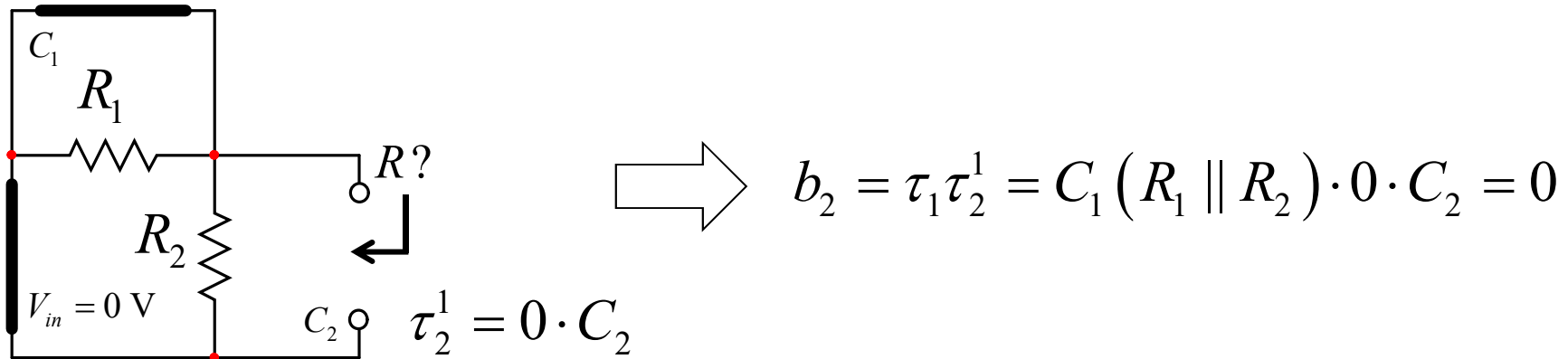- Place C_1 in its high-frequency and look into C_2



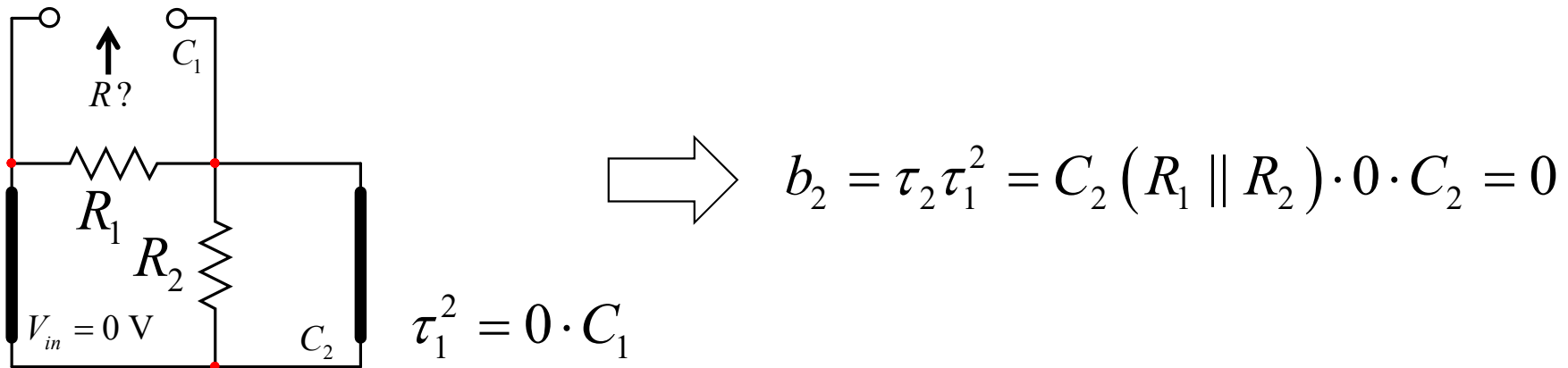- Place C_2 in its high-frequency and look into C_1




Denominator is Completed

- The denominator can be assembled


$$D(s) = 1 + b_1s + b_2s^2 = 1 + (C_1 + C_2)(R_1 \parallel R_2)s + 0 \cdot s^2$$

- Is there a zero in this network?

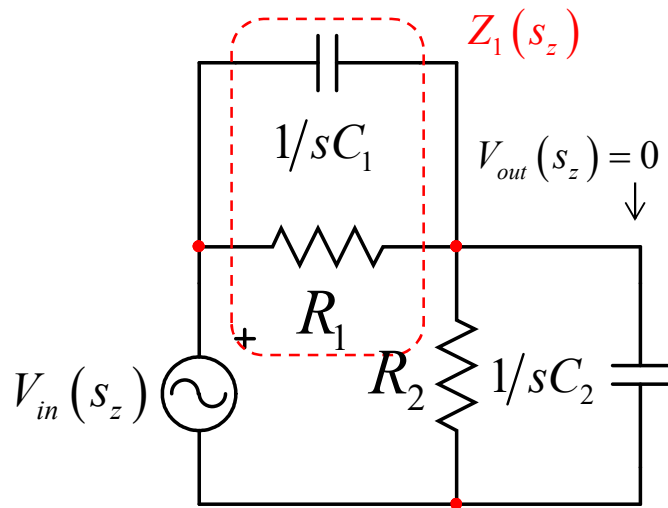

$$\left. \begin{array}{l} Z_1(s_z) \rightarrow \infty \\ N(s) \rightarrow \infty \\ 1 + sR_1C_1 \rightarrow 0 \end{array} \right\} \begin{array}{l} s_z = -\frac{1}{R_1C_1} \\ \omega_z = \frac{1}{R_1C_1} \end{array}$$
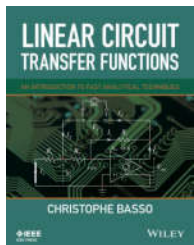
$$H(s) = \frac{R_2}{R_1 + R_2} \frac{1 + sr_C C_1}{1 + s(C_1 + C_2)(R_1 \parallel R_2)} = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$



C. Basso, *Linear Circuits Transfer Functions: An Introduction to Fast Analytical Techniques*, Wiley 2016

No algebra!



Check with Mathcad®

□ It is easy to check results versus a raw expression

$$R_1 := 50\text{k}\Omega \quad R_2 := 10\text{k}\Omega \quad C_1 := 100\text{nF} \quad C_2 := 10\text{nF} \quad \|(x,y) := \frac{x \cdot y}{x + y}$$

$$H_0 := \frac{R_2}{R_1 + R_2}$$

$$\tau_1 := C_1 \cdot (R_1 \parallel R_2) = 833.333\mu\text{s} \quad \tau_2 := C_2 \cdot (R_1 \parallel R_2) = 83.333\mu\text{s} \quad b_1 := \tau_1 + \tau_2 = 916.667\mu\text{s}$$

$$\tau_{12} := C_2 \cdot 0 = 0\mu\text{s} \quad \tau_{21} := C_1 \cdot 0 \quad b_2 := \tau_2 \cdot \tau_{21} = 0\mu\text{s}^2$$

$$N_1(s) := 1 + s \cdot R_1 \cdot C_1 \quad D_1(s) := 1 + b_1 \cdot s + b_2 \cdot s^2 \quad H_1(s) := H_0 \cdot \frac{N_1(s)}{D_1(s)}$$

$$\omega_z := \frac{1}{R_1 \cdot C_1} \quad \omega_p := \frac{1}{b_1}$$


Low-entropy formula

$$H_3(s) := H_0 \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$

$$f_z := \frac{\omega_z}{2\pi} = 31.831\text{Hz} \quad f_p := \frac{\omega_p}{2\pi} = 173.624\text{Hz} \quad \sqrt{f_z \cdot f_p} = 74.341\text{Hz}$$

$$Z_1(s) := (R_1) \parallel \left(\frac{1}{s \cdot C_1} \right) \quad Z_2(s) := (R_2) \parallel \left(\frac{1}{s \cdot C_2} \right) \quad H_2(s) := \frac{Z_2(s)}{Z_2(s) + Z_1(s)}$$


Raw formula

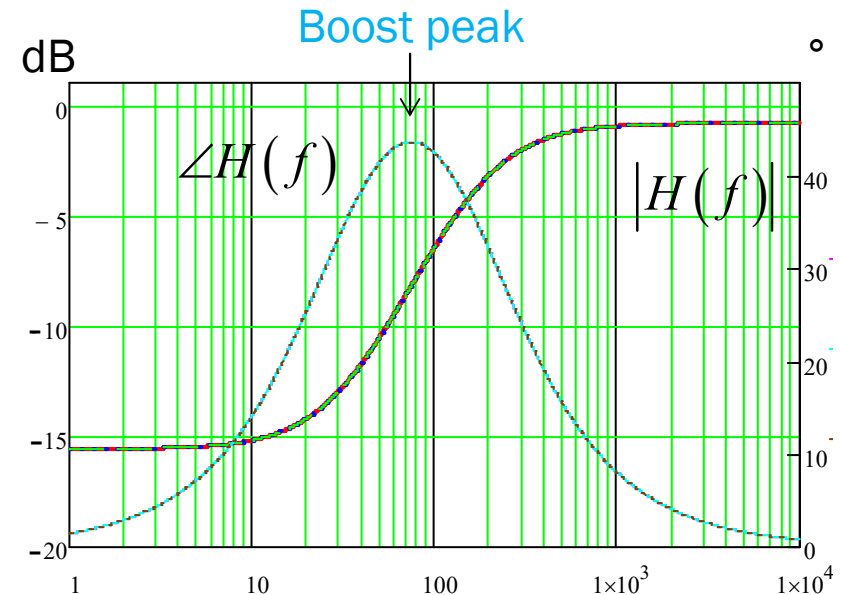

Comparison between raw and low-entropy formula: perfect match

Dc Analysis – Short L_1 and Open C_2

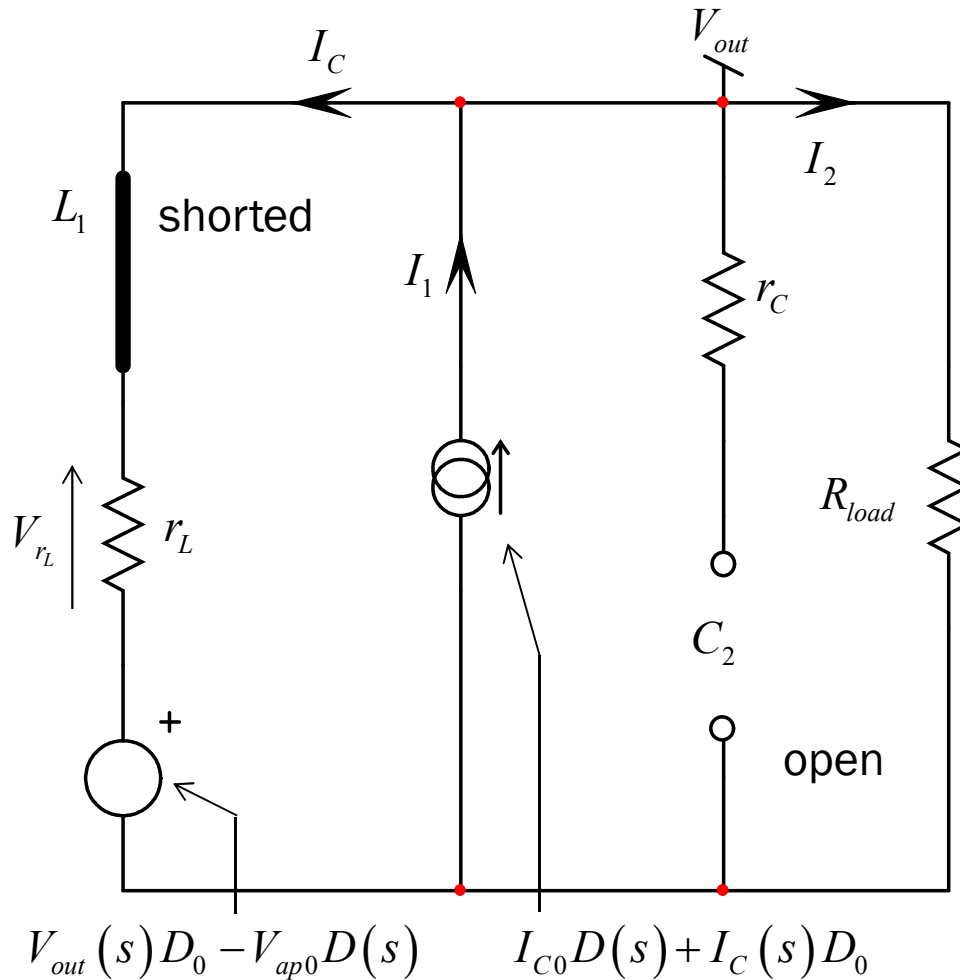□ Apply KCL on a simple circuit without reactances, $s = 0$



$$I_C(s) = \frac{V_{out}(s) - V_{out}(s)D_0 + V_{ap0}D(s)}{r_L}$$

$$I_2(s) = I_{C0}D(s) - I_C(s)(1 - D_0)$$

$$V_{out}(s) = I_2(s)R_{load} \quad V_{ap0} = -V_{out}$$

Substitute
rearrange


$$H_0 = V_{in}R_L \frac{[(1 - D_0)^2 R_L - r_L]}{[(1 - D_0)^2 R_L + r_L]^2}$$

$r_L \rightarrow 0, V_{out} = V_{in} \frac{1}{1 - D_0}$

$$H_0 \approx \frac{V_{in}}{(1 - D_0)^2}$$

Excitation is Turned off - τ_1

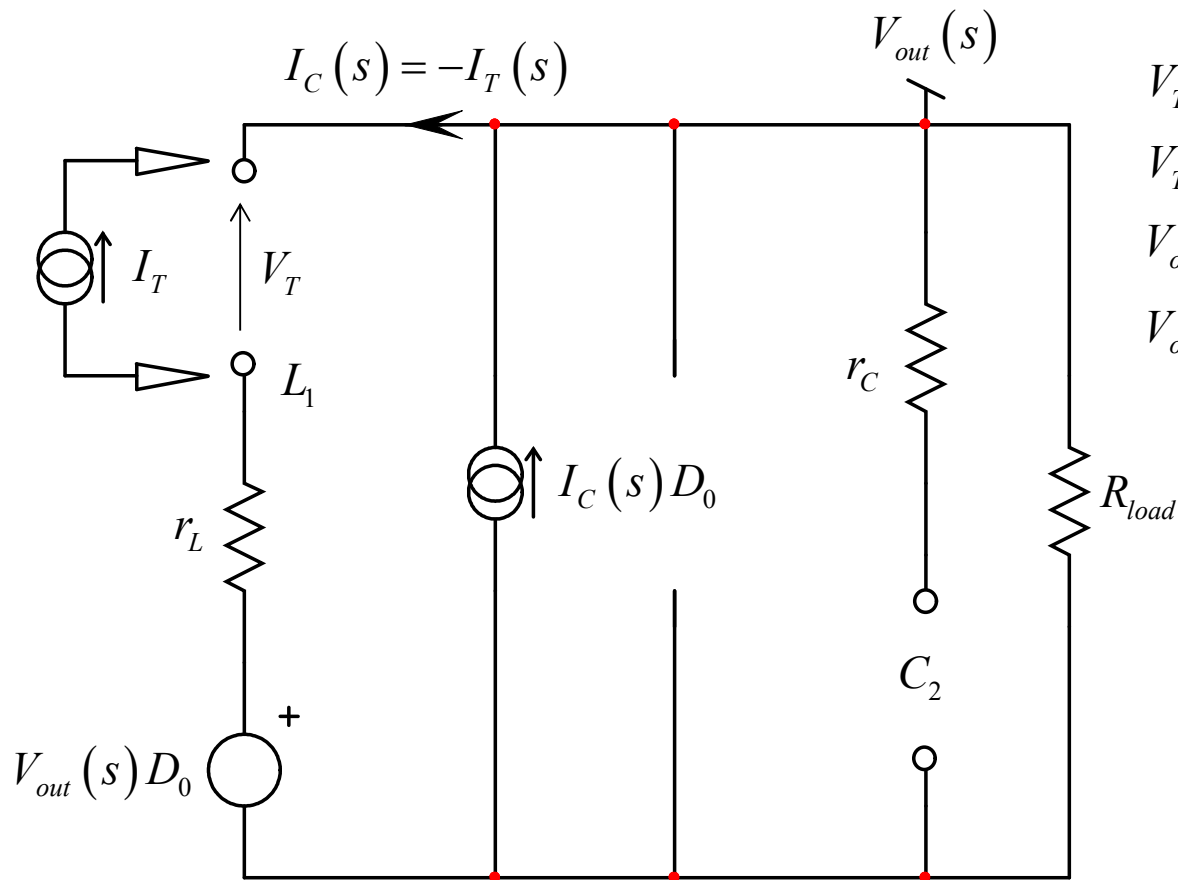- All expressions featuring $D(s)$ are set to 0




$$V_T(s) = V_{out}(s) + I_T(s)r_L - V_{out}(s)D_0$$

$$V_T(s) = I_T(s)r_L + V_{out}(s)(1 - D_0)$$

$$V_{out}(s) = [I_C(s)D_0 - I_C(s)]R_{load}$$

$$V_{out}(s) = I_C(s)(D_0 - 1)R_{load}$$

$$= I_T(s)(1 - D_0)R_{load}$$

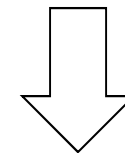


Substitute
rearrange

$$\tau_1 = \frac{L_1}{r_L + R_{load}(1 - D_0)^2}$$

Excitation is Turned off - τ_2

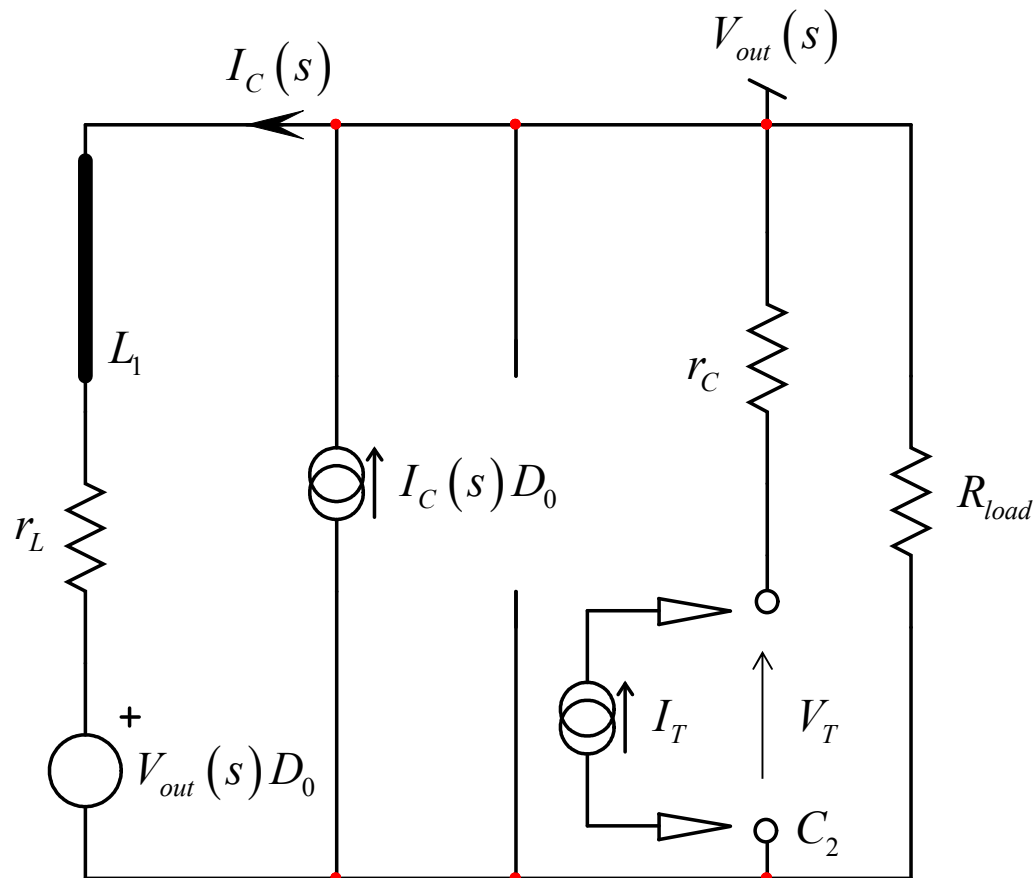- Inductor L_1 is replaced by a short circuit




$$I_C(s) = \frac{V_{out}(s) - V_{out}(s)D_0}{r_L}$$

$$I_C(s) = \frac{V_{out}(s)(1 - D_0)}{r_L}$$

$$V_{out}(s) = R_{load} [I_C(s)(D_0 - 1) + I_T(s)]$$

$$V_{out}(s) = V_T(s) - I_T(s)r_C$$

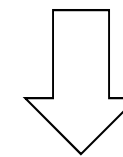


Substitute
rearrange

$$\tau_2 = \left[r_C + \frac{r_L}{(1 - D_0)^2 + \frac{r_L}{R_{load}}} \right] C_2$$

Excitation is Turned off - τ_2^1

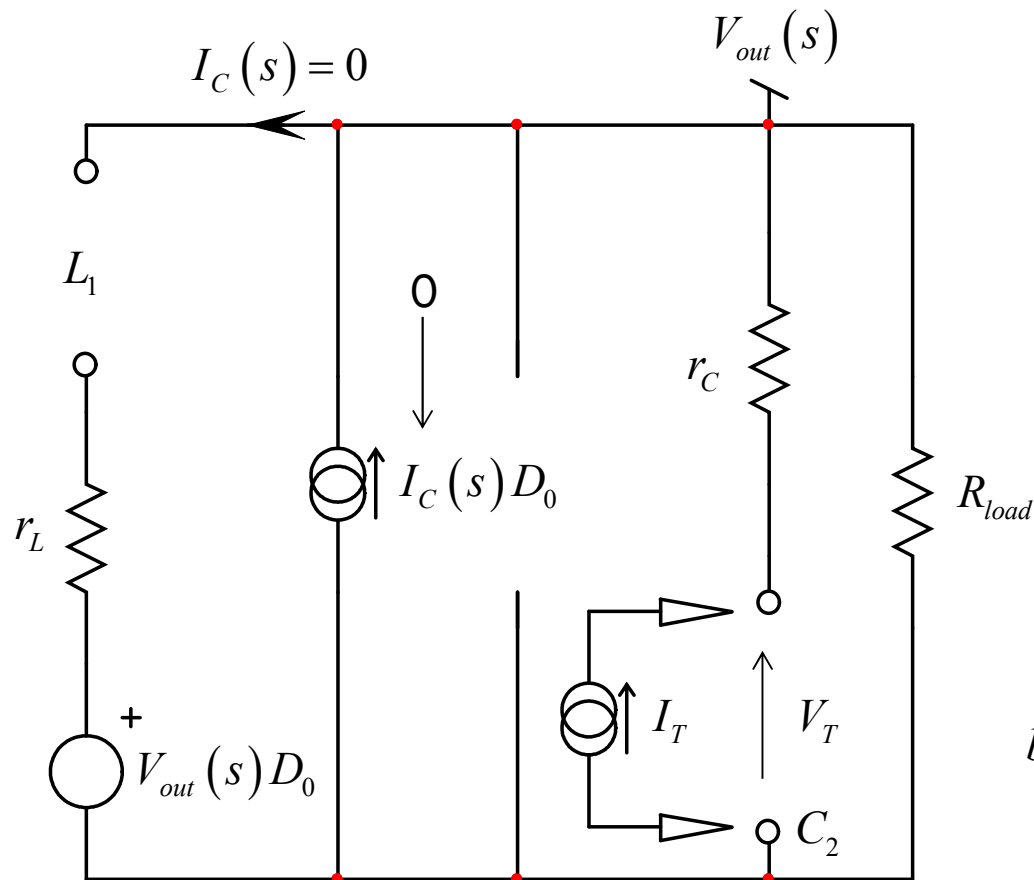- Inductor L_1 is replaced by an open circuit



$$I_C(s) = 0$$

↓

$$\tau_2^1 = (r_C + R_{load})C_2$$

↓

$$b_2 = \tau_1 \tau_2^1 = \frac{L_1}{r_L + R_{load} (1 - D_0)^2} (r_C + R_{load}) C_2$$

Denominator Expression

□ The 2nd-order denominator can be formed

$$b_1 = \tau_1 + \tau_2 = \frac{L_1}{r_L + R_{load} (1 - D_0)^2} + \left[r_C + \frac{r_L}{(1 - D_0)^2 + \frac{r_L}{R_{load}}} \right] C_2$$


$$b_2 = \tau_1 \tau_2 = \frac{L_1}{r_L + R_{load} (1 - D_0)^2} (r_C + R_{load}) C_2$$

$$D(s) = 1 + \left[\frac{L_1}{r_L + (1 - D_0)^2 R_{load}} + C_2 \left(r_C + \frac{R_{load} r_L}{R_{load} (1 - D_0)^2 + r_L} \right) \right] s + \left[L_1 C_2 \frac{r_C + R_{load}}{r_L + (1 - D_0)^2 R_{load}} \right] s^2$$


$$\omega_0 = \frac{1}{\sqrt{L_1 C_2}} \sqrt{\frac{r_L + R_{load} D_0'^2}{r_C + R_{load}}} \quad Q \approx \frac{\omega_0}{\frac{r_L}{L_1} + \frac{1}{C(r_C + R_{load})}}$$

Determining the Numerator

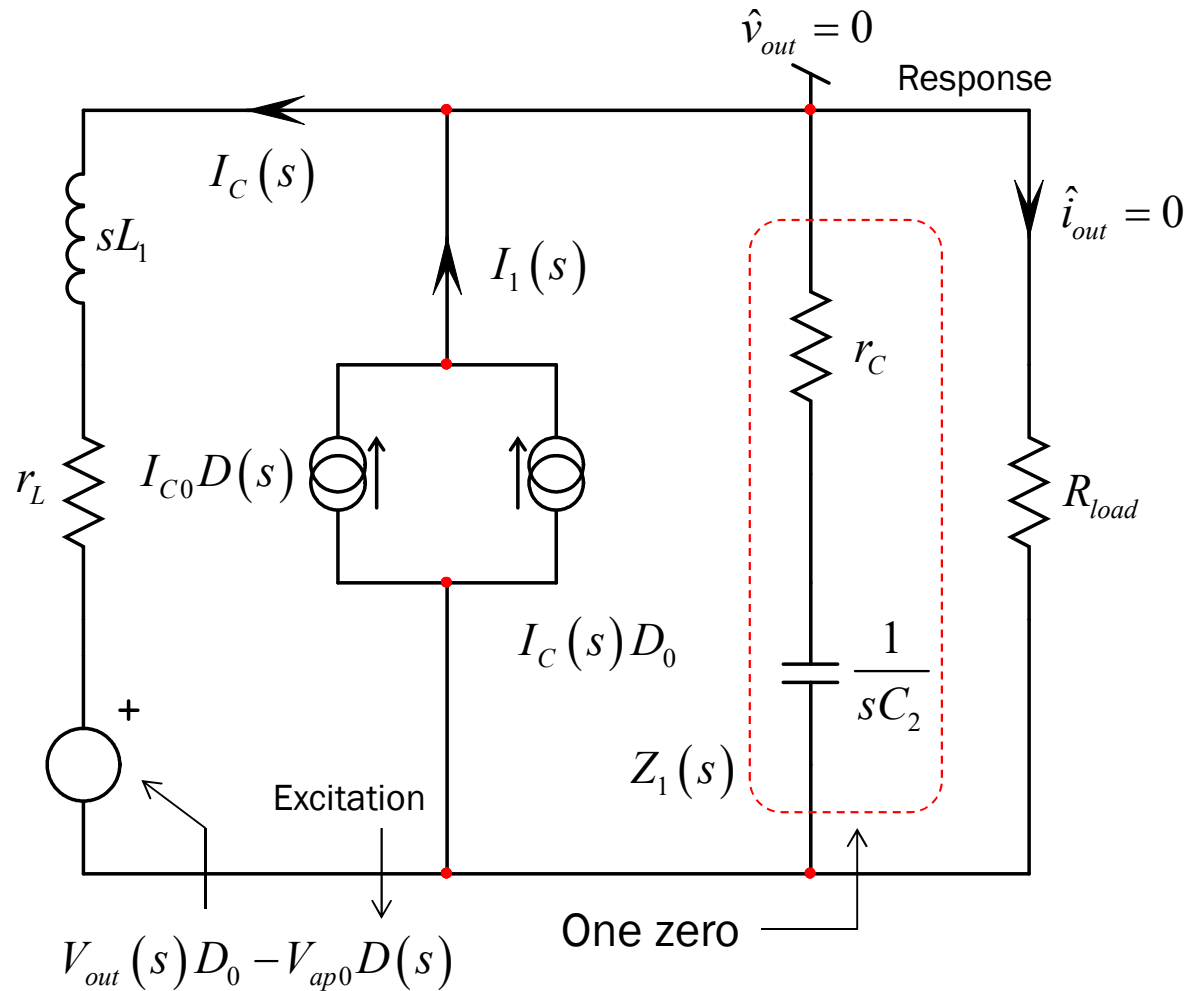- To determine zeros, bring the excitation back



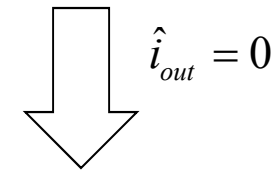“What conditions in the transformed circuit null the response?”



$$Z_1(s) = r_C + \frac{1}{sC_2} = 0$$

$$I_1 = I_C$$

What if L_1 and C_2 are in HF state?

First Zero is Easy

- The equivalent series resistance brings the first zero

$$Z_1(s_z) = r_C + \frac{1}{sC_2} = 0 \quad \longrightarrow \quad Z_1(s_z) = \frac{1 + sr_C C_2}{sC_2} = 0$$

- The negative (LHP) root is simply


$$s_{z_1} = -\frac{1}{r_C C_2} \quad \longrightarrow \quad \omega_{z_1} = \frac{1}{r_C C_2}$$

- Almost there...

$$H(s) = H_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) (\dots)}{1 + b_1 s + b_2 s^2}$$

Equate Current Expressions

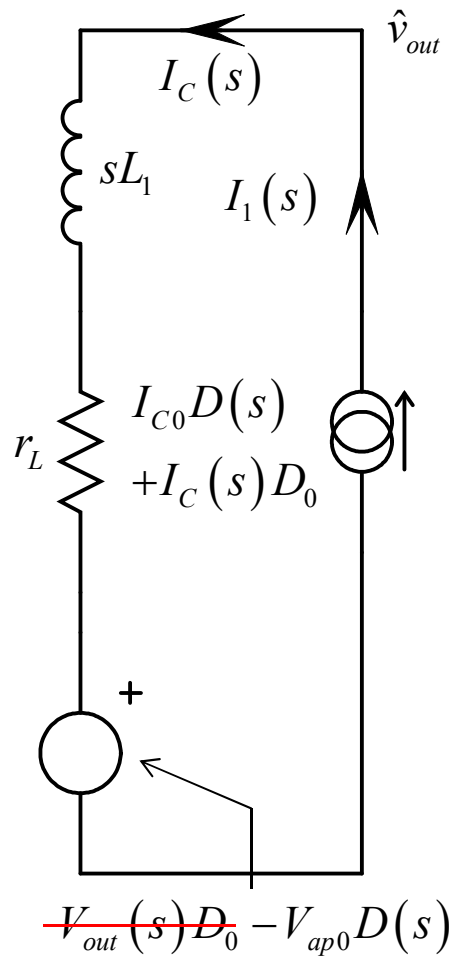□ The output null implies that $\hat{v}_{out} = 0$



$$I_1 - I_C = 0 \quad I_C(s) = \frac{V_{ap0}D(s)}{sL_1 + r_L}$$

↑ ↑

$$I_1(s) = I_{C0}D(s) + I_C(s)D_0 \quad \text{Substitute } I_C \text{ in } I_1$$

$$I_{C0}D(s) + \frac{V_{ap0}D(s)}{r_L + sL_1} D_0 - \frac{V_{ap0}D(s)}{r_L + sL_1} = 0$$

Solve for the root

$$s_{z_2} = \frac{(1 - D_0)^2 R_{load} - r_L}{L_1} \xrightarrow{r_L \ll R_{load}} \omega_{z_2} \approx \frac{(1 - D_0)^2 R_{load}}{L_1}$$

Positive root, RHPZ!

The CCM Boost Transfer Function

- Assemble pieces to express the transfer function

$$\frac{V_{out}(s)}{D(s)} = H_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 - \frac{s}{\omega_{z_2}}\right)}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2} \quad \omega_{z_1} = \frac{1}{r_C C_2} \quad \omega_{z_2} \approx \frac{(1 - D_0)^2 R_{load}}{L_1}$$

$$\omega_0 = \frac{1}{\sqrt{L_1 C_2}} \sqrt{\frac{r_L + R_{load} D^2}{r_C + R_{load}}} \quad Q \approx \frac{\omega_0}{\frac{r_L}{L_1} + \frac{1}{C_2 (r_C + R)}} \quad H_0 \approx \frac{V_{in}}{(1 - D_0)^2}$$


$$\omega_0 \approx \frac{1 - D_0}{\sqrt{L_1 C_2}} \quad Q \approx (1 - D_0) R_{load} \sqrt{\frac{C_2}{L_1}}$$

- Time to check the dynamic response



Checking Ac Responses

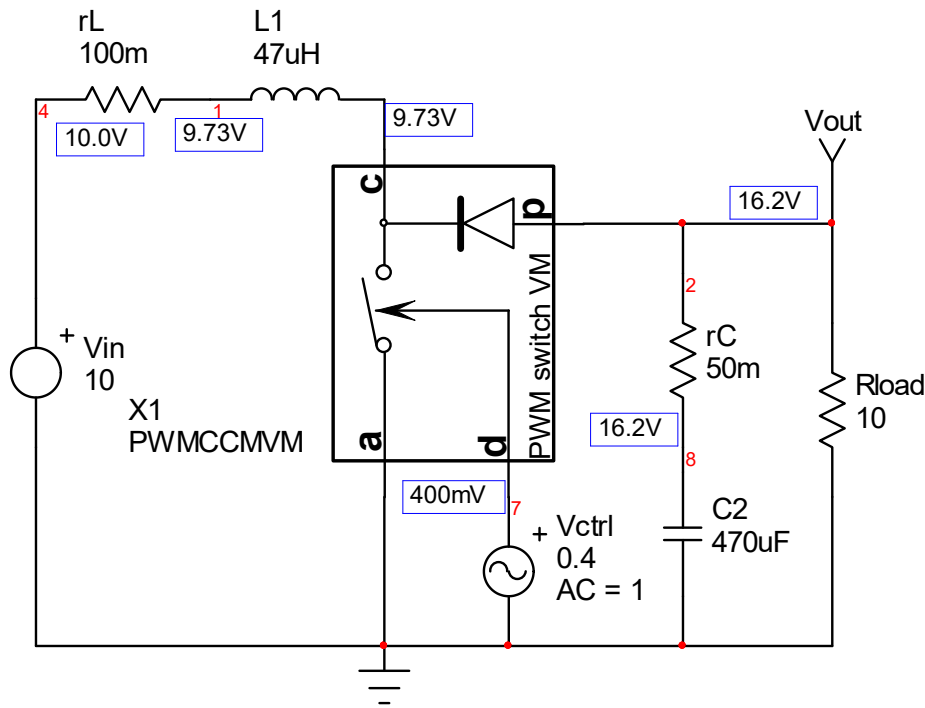- Capture a simple boost converter schematic




$$\begin{aligned}
 r_L &:= 0.1\Omega & r_C &:= 0.05\Omega & C_2 &:= 470\mu\text{F} & L_1 &:= 47\mu\text{H} \\
 D_0 &:= 40\% & V_{in} &:= 10\text{V} & R_L &:= 10\Omega & |(x,y) &:= \frac{x \cdot y}{x + y} \\
 V_{out} &:= \frac{R_L \cdot V_{in} \cdot (1 - D_0)}{r_L \left[\frac{R_L (1 - D_0)^2}{r_L} + 1 \right]} = 16.216\text{V} & V_{ap} &:= -V_{out} \\
 I_{C0} &:= \frac{V_{out} - (V_{in} + D_0 \cdot V_{out})}{r_L} = -2.703\text{A} \\
 H_0 &:= \frac{D_0 \cdot R_L \cdot V_{ap} - R_L \cdot V_{ap} + I_{C0} \cdot R_L \cdot r_L}{R_L \cdot D_0^2 - 2 \cdot R_L \cdot D_0 + R_L + r_L} = 25.566\text{V} & 20 \log \left(\frac{|H_0|}{1\text{V}} \right) &= 28.153 \\
 R_{\tau_{au1}} &:= r_L + (1 - D_0)^2 \cdot R_L = 3.7\Omega & \tau_1 &:= \frac{L_1}{R_{\tau_{au1}}} = 12.703\mu\text{s} \\
 R_{\tau_{au2}} &:= r_C + \frac{r_L}{(1 - D_0)^2 + \frac{r_L}{R_L}} = 0.32\Omega & \tau_2 &:= C_2 \cdot R_{\tau_{au2}} = 150.527\mu\text{s} \\
 b_1 &:= \tau_1 + \tau_2 = 163.23\mu\text{s} & \tau_{12} &:= C_2 \cdot (r_C + R_L) = 4.724 \times 10^3 \mu\text{s} & b_2 &:= \tau_1 \cdot \tau_{12} = 6 \times 10^4 \mu\text{s}^2 \\
 \omega_{z1} &:= \frac{1}{r_C \cdot C_2} & f_{z1} &:= \frac{\omega_{z1}}{2\pi} = 6.773\text{kHz} & D(s) &:= 1 + b_1 \cdot s + b_2 \cdot s^2 \\
 \omega_{z2} &:= -\frac{D_0 \cdot V_{ap} - V_{ap} + I_{C0} \cdot r_L}{I_{C0} \cdot L_1} & f_{z2} &:= \frac{\omega_{z2}}{2\pi} = 11.852\text{kHz} \\
 \omega_0 &:= \frac{1}{\sqrt{b_2}} = 4.082 \times 10^3 \frac{1}{\text{s}} & f_0 &:= \frac{\omega_0}{2\pi} = 649.74\text{Hz} \\
 Q &:= \frac{\sqrt{b_2}}{b_1} = 1.501 & H_1(s) &:= H_0 \cdot \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \cdot \left(1 - \frac{s}{\omega_{z2}}\right)}{D(s)}
 \end{aligned}$$

- Check versus the Mathcad[®] plots



SPICE and Mathcad® Plots

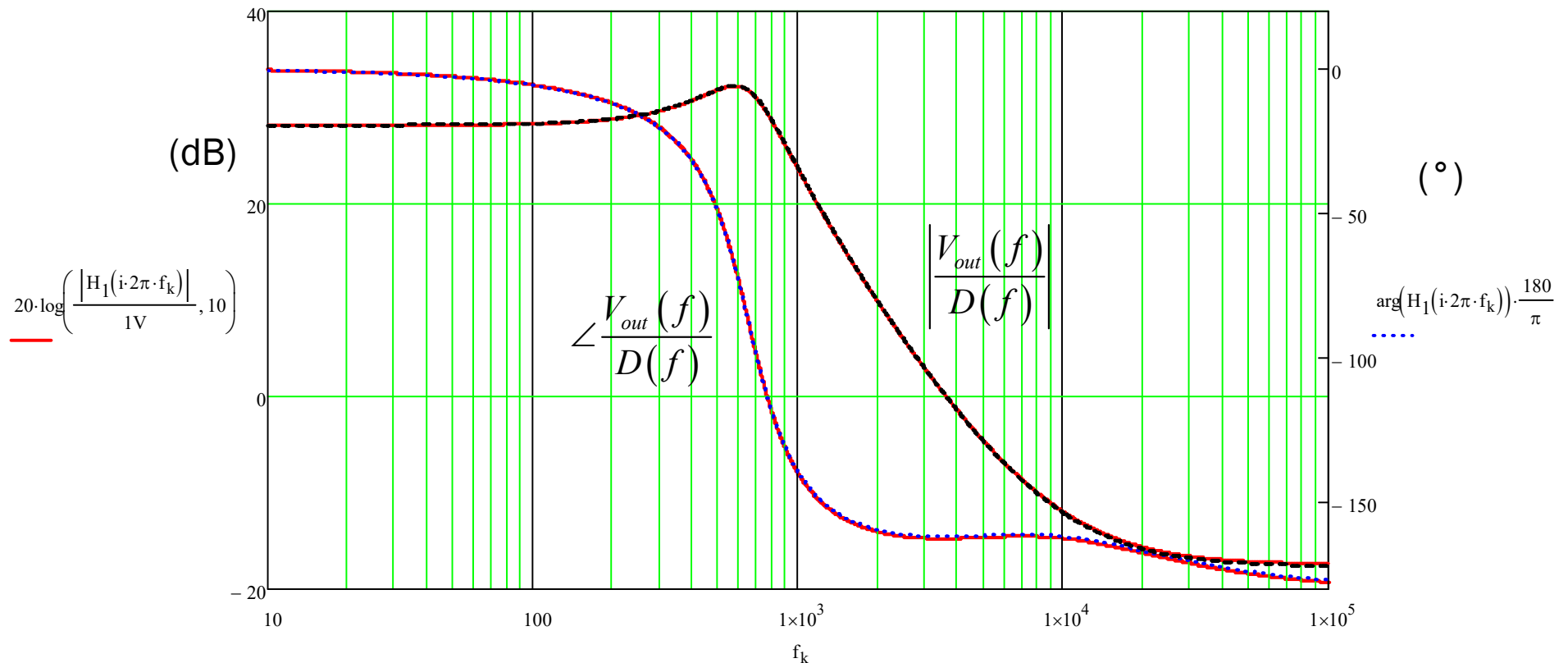- Curves superimpose: transfer function is correct!



- A deviation would indicate a flaw in the analysis



Course Agenda

- Blocks in a Switching Converter
- Introduction to Small-Signal Modeling
- Analytical Analysis of an Output Stage
- Simulation Models - Averaged or Switched?**
- Crossover Frequency and Phase Margin
- Compensation Strategy
- Experiments on Prototypes
- Conclusion




Switching and Dynamic Response

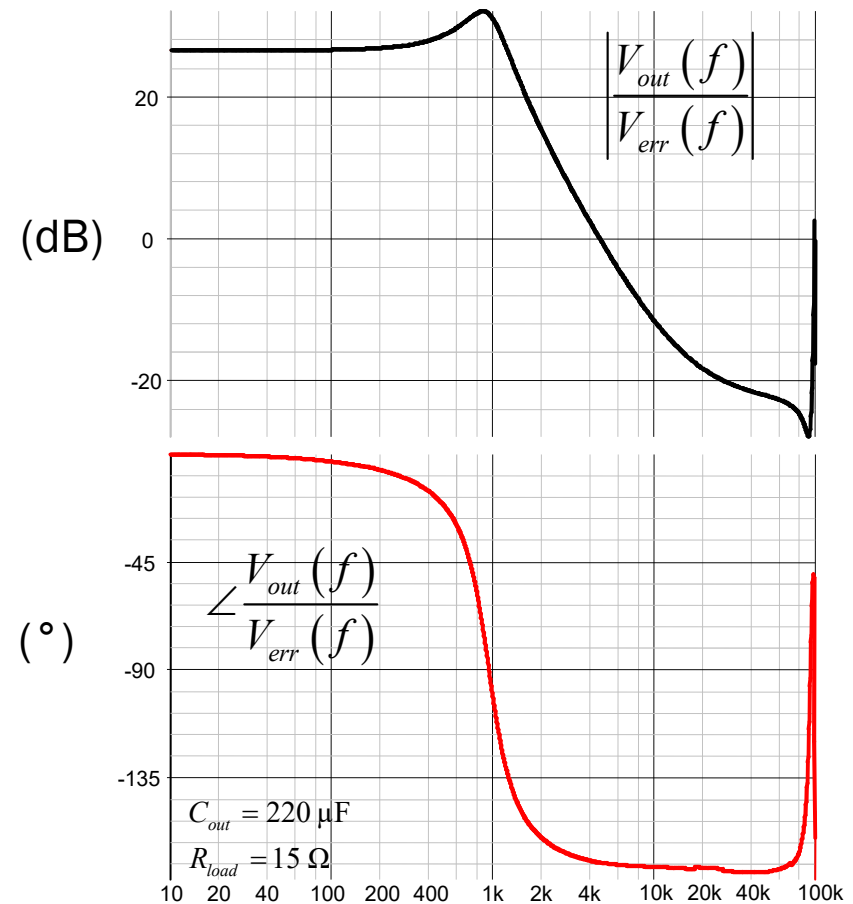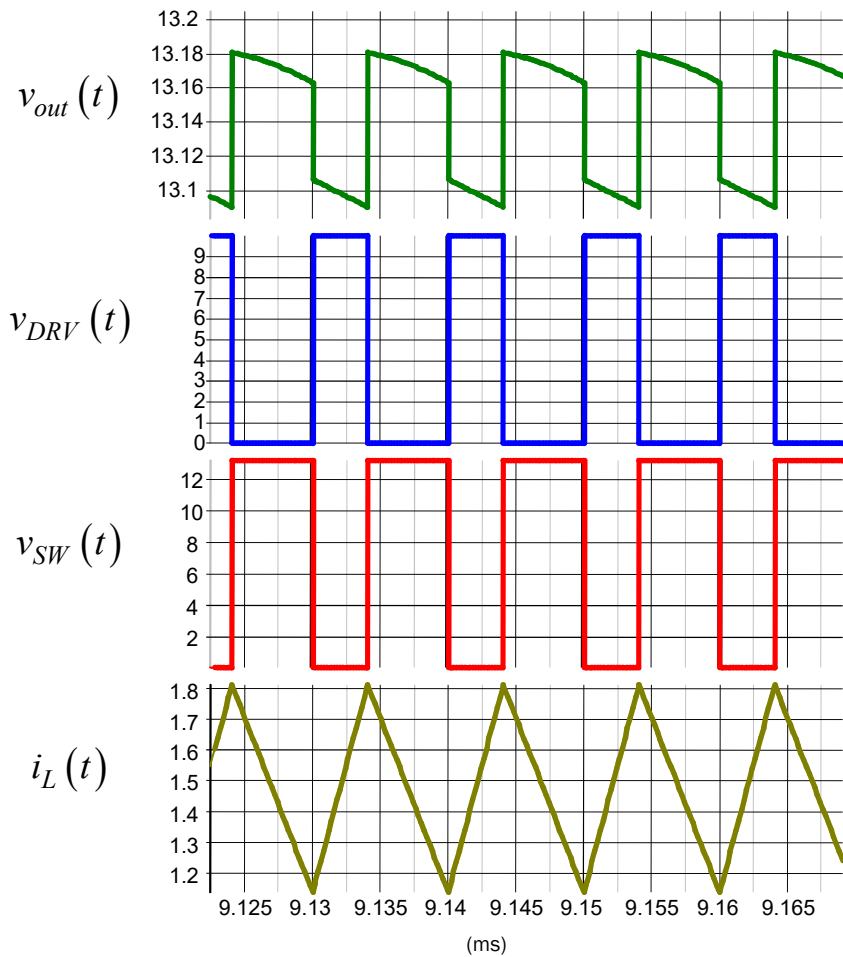□ You have cycle-by-cycle and dynamic analyses in one shot



Current Mode and Subharmonic Poles


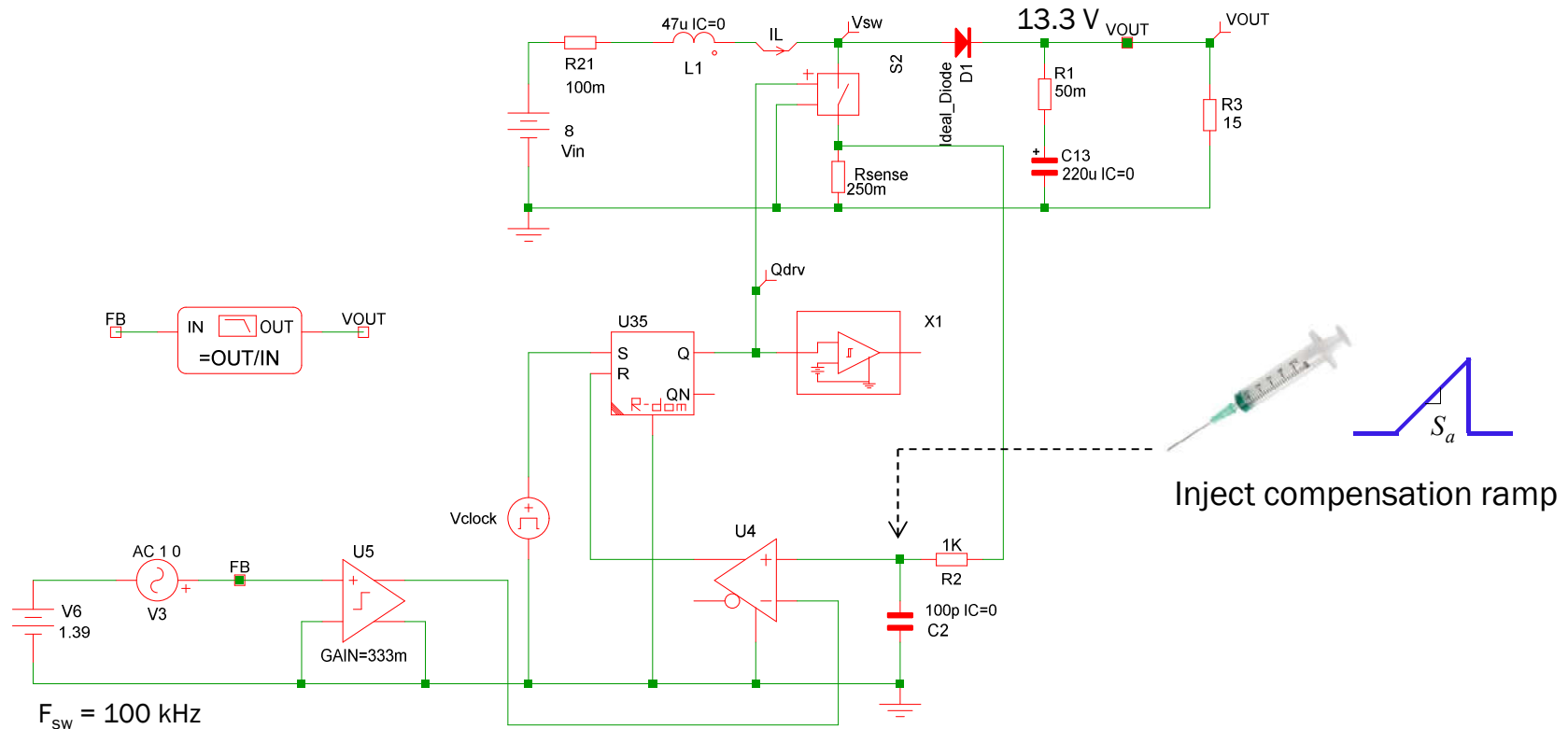
□ It is easy to implement current mode control



□ Inject external ramp to damp the subharmonic poles at $F_{sw}/2$

Dynamic Responses Reveal Peaking

- Subharmonic poles need to be damped

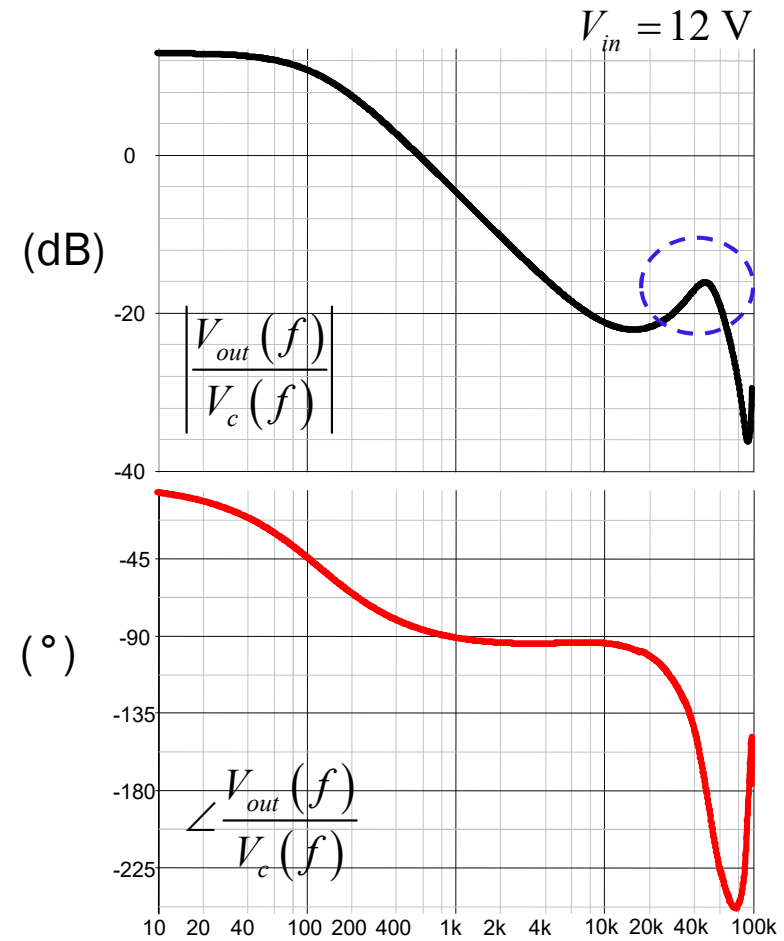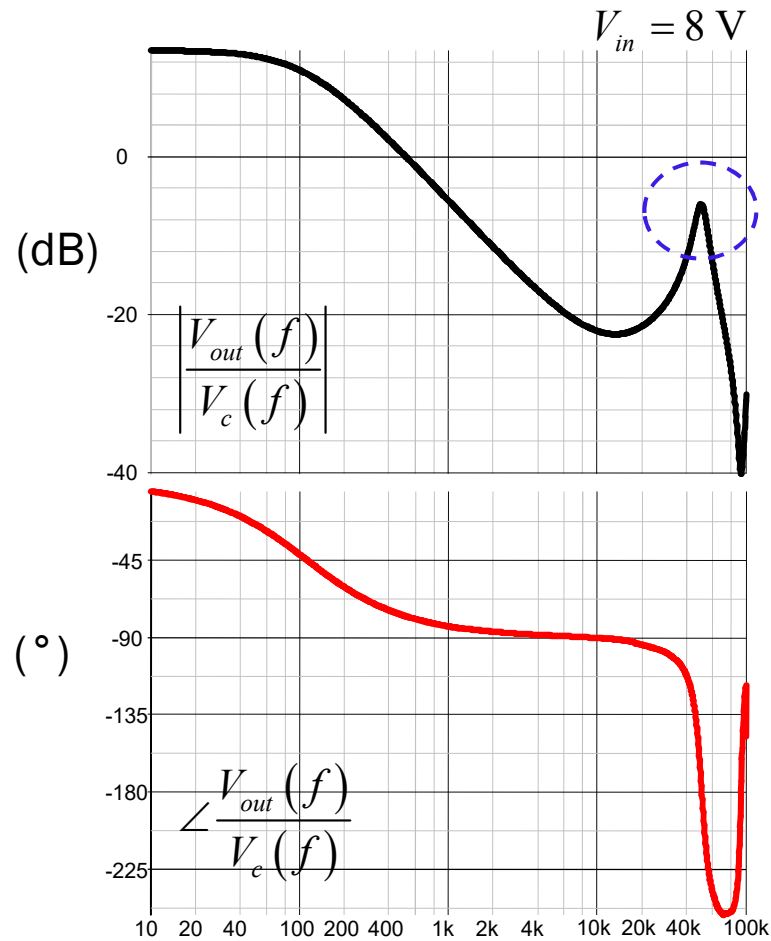

How Much Ramp Should you Inject?

- Damp the double poles located at $F_{sw}/2$

$$Q = \frac{1}{\pi(m_c D' - 0.5)} \quad m_c = 1 + \frac{S_a}{S'_n}$$

External ramp slope [V]/[s] → To be determined
 On-time slope [V]/[s] → $\frac{V_{in}}{L} R_{sense}$


- Adjust m_c to reduce Q to 1

$$m_c = \frac{\frac{1}{\pi} + 0.5}{1 - D} = \frac{0.818}{1 - 0.42} \approx 1.41 \longrightarrow S_a = S'_n (m_c - 1) = \frac{8}{47\mu} \times 0.25 \times 0.41 \approx 28 \text{ kV/s}$$

Amount of external ramp to damp Q

From simulation \nearrow

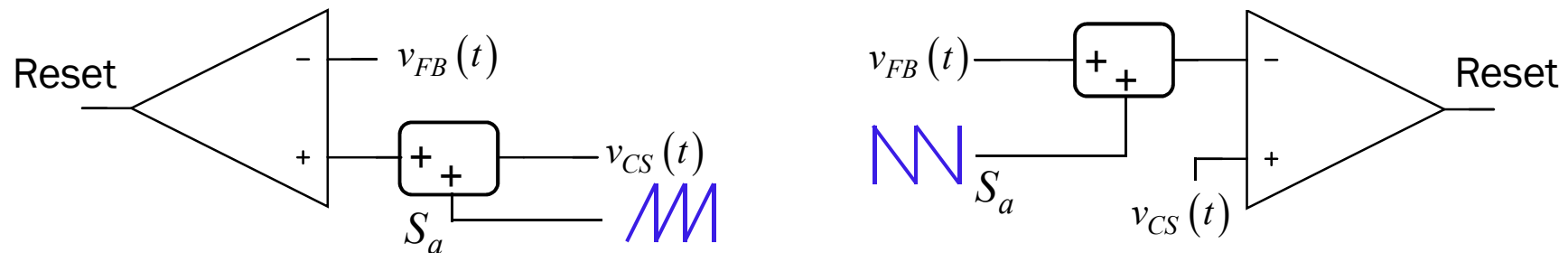- Add a positive ramp to $v_{CS}(t)$ or a negative ramp to $v_{FB}(t)$




R. Ridley, A New Small-Signal Model for Current Mode Control, Ph. D. dissertation, Virginia Polytechnic Institute and State University, 1990


How to Generate a Compensation Ramp?

- Buffer the oscillation ramp and inject on the CS pin

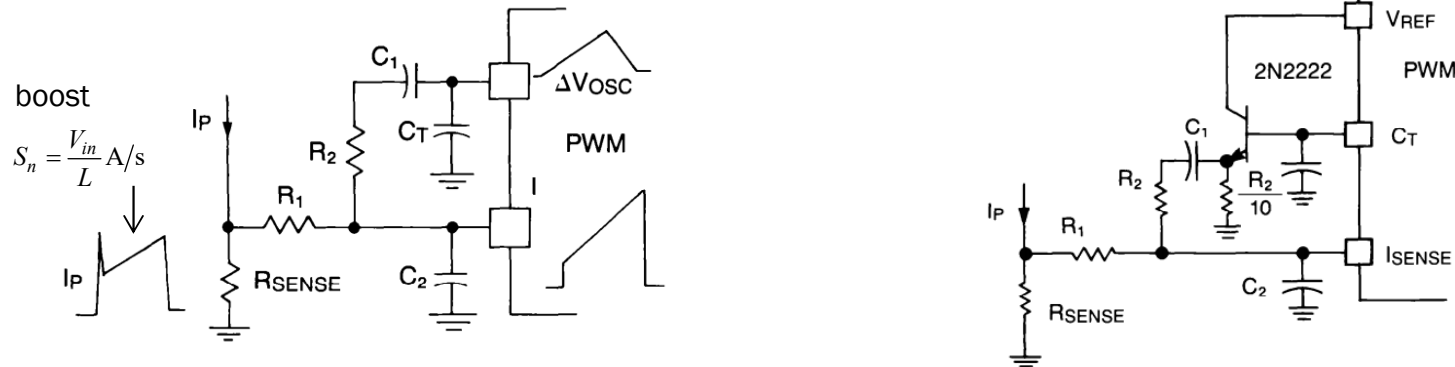Unitrode U-111, *Practical Considerations in current mode power supplies*




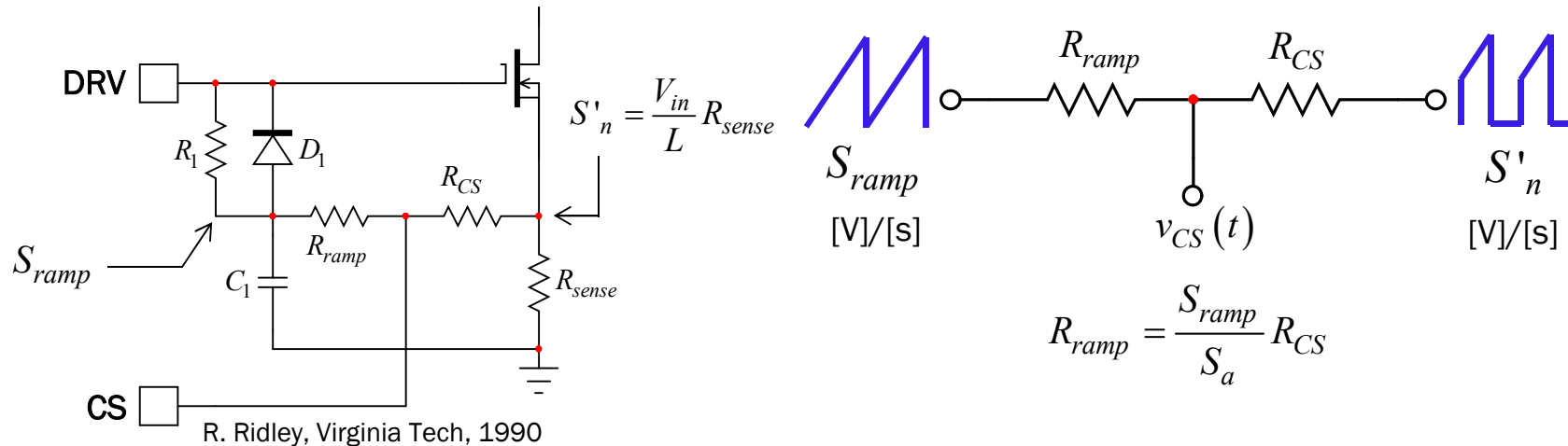- Risks exist to disturb oscillator – use a low-impedance pin



Size Ramp to Meet Compensation Needs

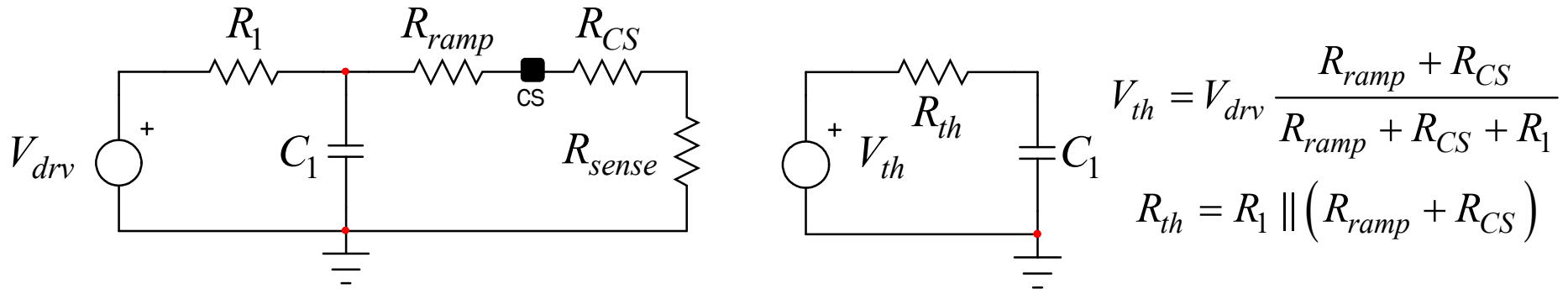- Simplify the charging scheme by neglecting R_{sense}



- The slope of this ramp is obtained by differentiation

$$v_{C_1}(t) = V_{th} \left(1 - e^{-\frac{t}{\tau}} \right) \quad \frac{dv_{C_1}(t)}{dt} = V_{th} \frac{e^{-\frac{t}{\tau}}}{\tau} \quad \rightarrow \quad S_{ramp} \approx \frac{V_{th} \left(1 - \frac{t_{on}}{\tau} \right)}{\tau} \quad \text{At } t = t_{on}$$

Considering $R_{CS} \ll R_{ramp}$:
$$S_{ramp} \approx \frac{V_{drv} \frac{R_{ramp}}{R_{ramp} + R_1} \left(1 - \frac{t_{on}}{C_1 (R_1 \parallel R_{ramp})} \right)}{C_1 (R_1 \parallel R_{ramp})}$$

Build a Low-Impedance Ramp

- Adopt a low charging current (1 mA) to spare the driver:

$$R_1 = \frac{V_{drv}}{I_{chg}} = \frac{12}{1m} = 12 \text{ k}\Omega$$




Choose: $S_{ramp} = 300 \text{ mV}/\mu\text{s}$
 $R_{ramp} = 19 \text{ k}\Omega$
 $t_{on} = 5 \mu\text{s}$

$$C_1 = V_{drv} \frac{1 + \sqrt{1 - \frac{4S_a t_{on} (R_1 + R_{ramp})}{R_{ramp} V_{drv}}}}{2R_1 S_a} = 2.6 \text{ nF}$$

↓
2.2 nF
↓
0.34 V/ μs



$$R_{CS} = R_{ramp} \frac{S_a}{S_{ramp}} \approx 1.5 \text{ k}\Omega$$

- Check simulation results are ok

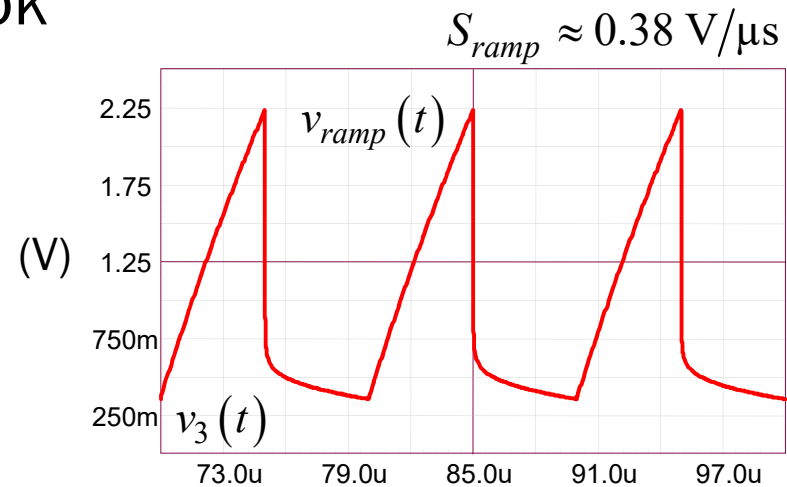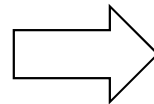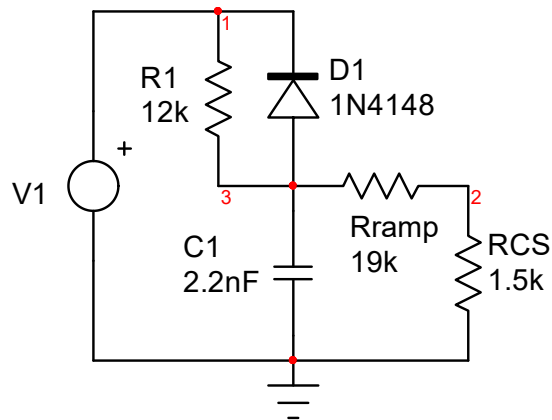


Implement the Circuit in the Converter

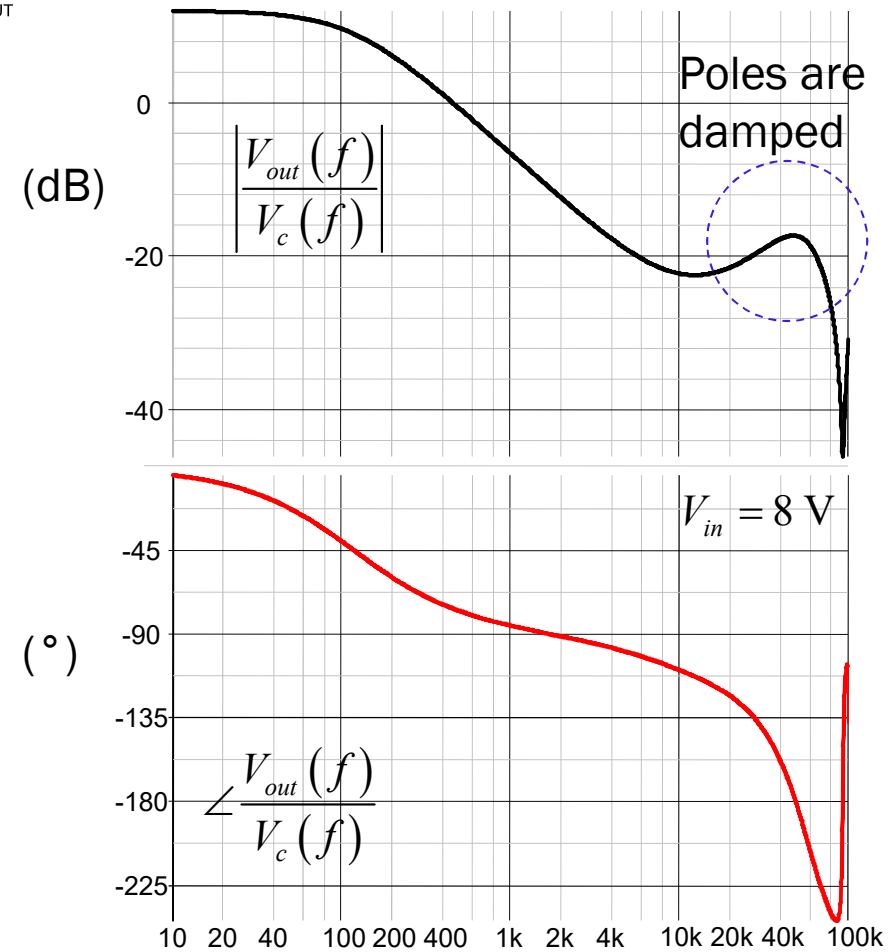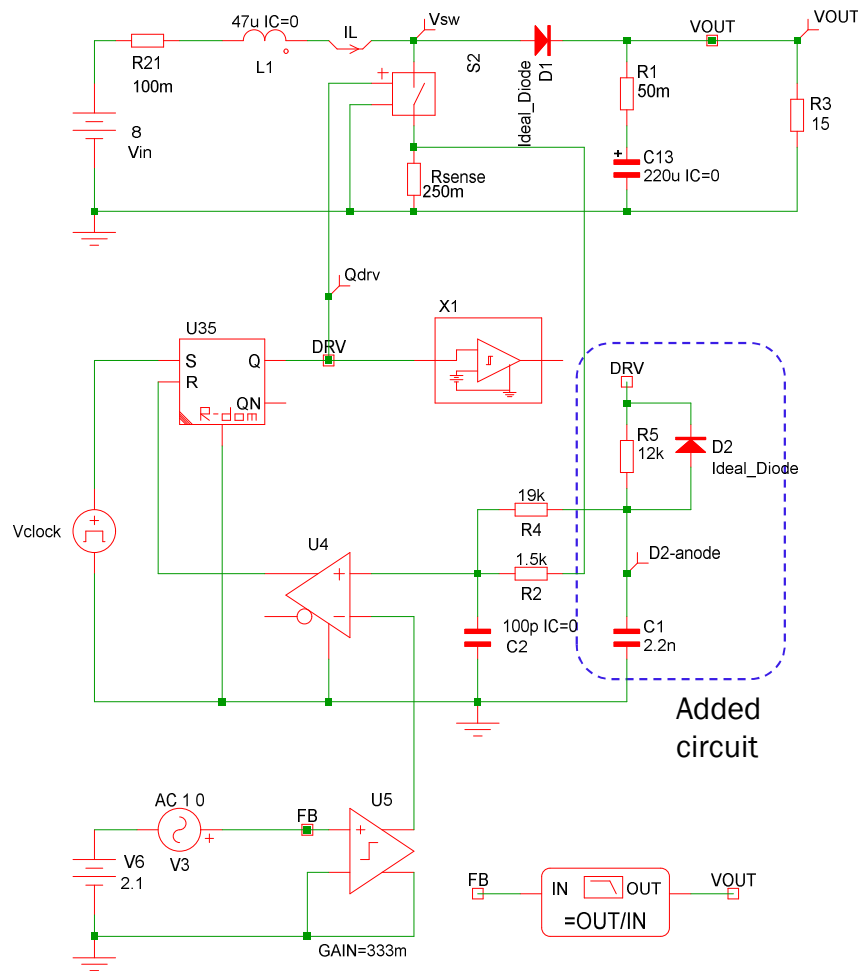□ You can immediately check the impact on the response



The PWM Switch Model in Current Mode

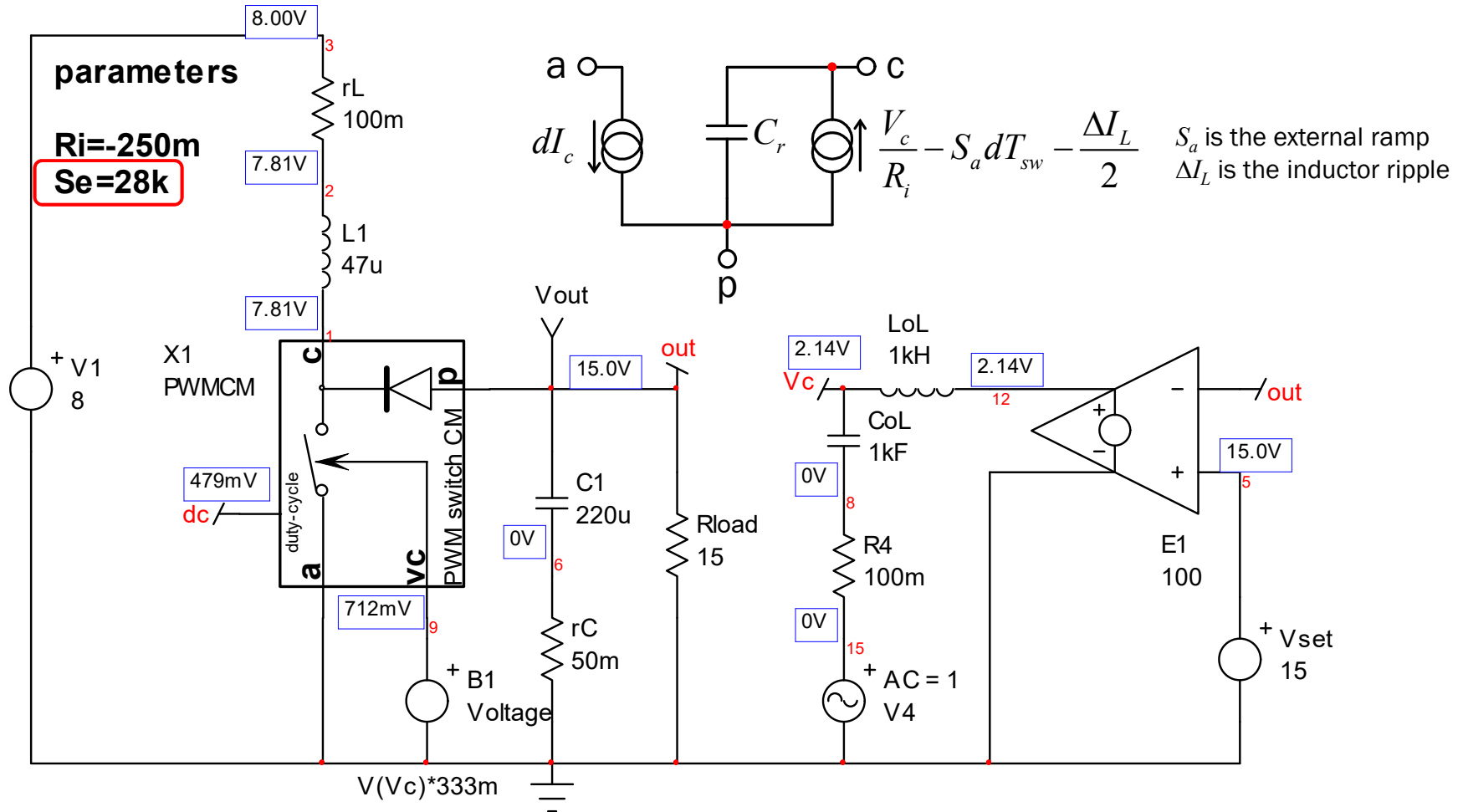
- A current mode version predicts the subharmonic poles



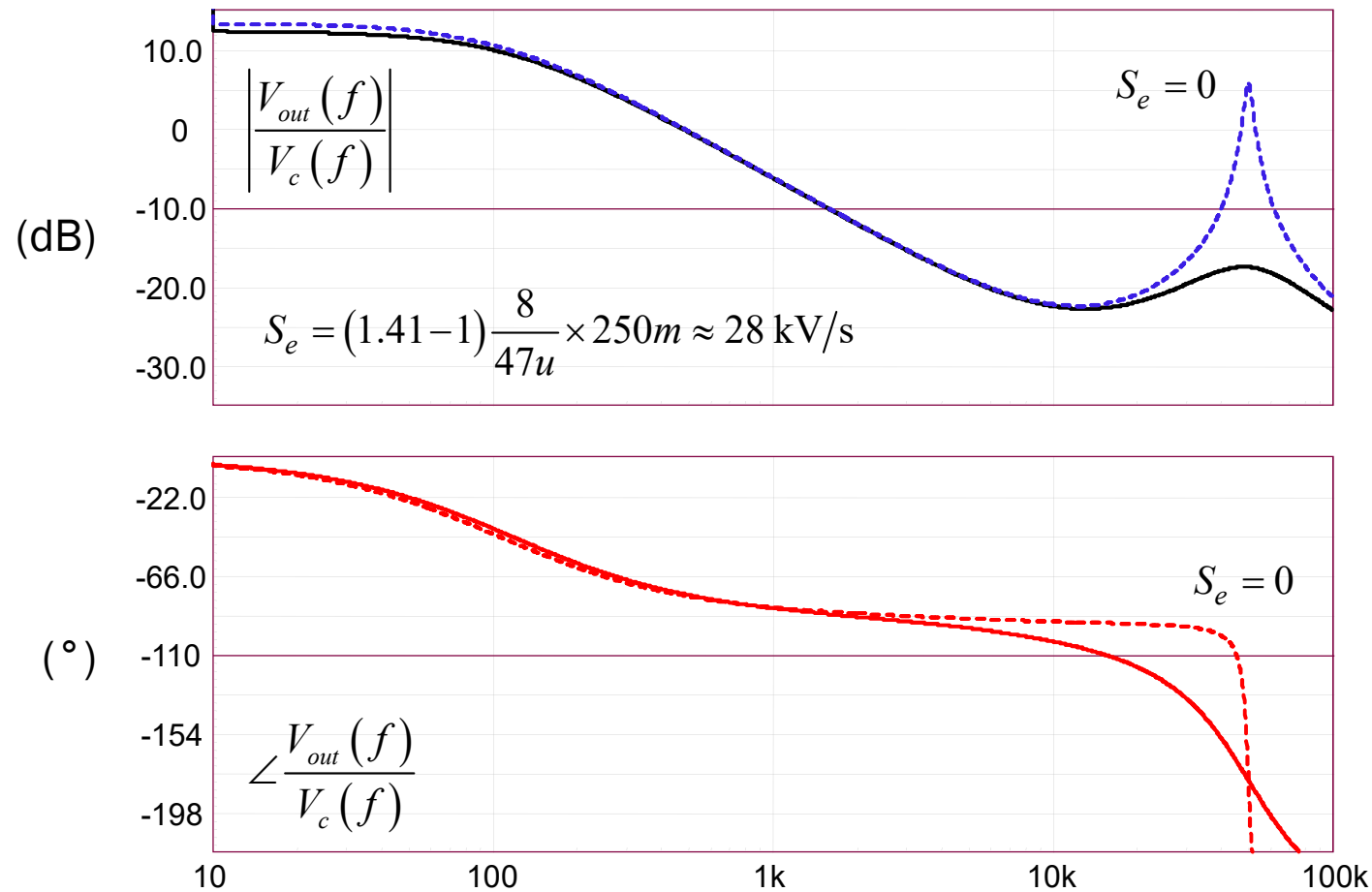V. Vorpérian, "Analysis of current-controlled PWM converters using the model of the current-controlled PWM switch", PCIM conference proceedings, 1990, pp 183-195


Check Slope Compensation is Effective

- The compensation ramp S_e or S_a is passed as a parameter



Voltage-Mode Control is Easy

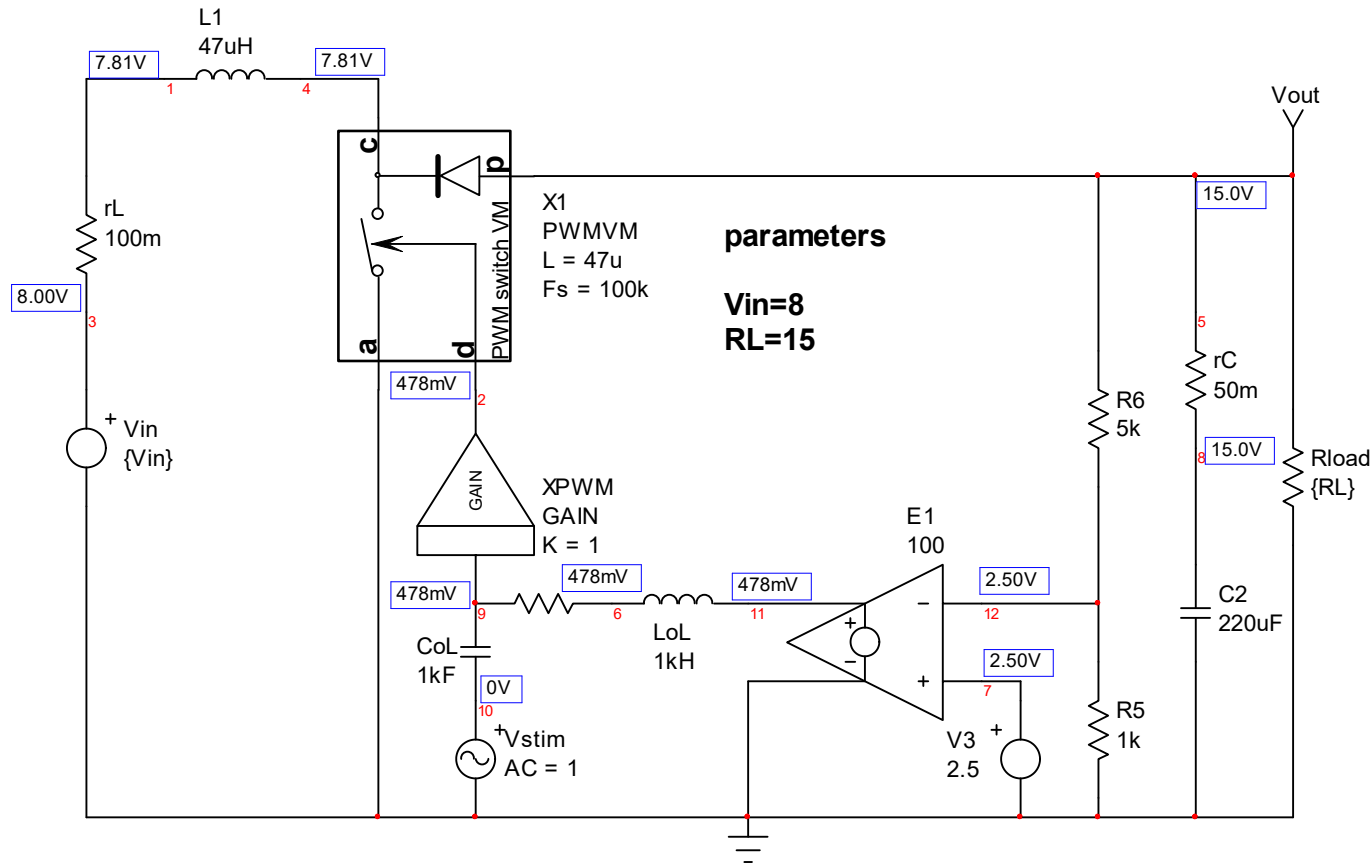- Choose the auto-toggling DCM-CCM PWM switch



$$R_{crit} = 2F_{sw}L \frac{M^3}{M-1}$$


$$M = \frac{V_{out}}{V_{in}}$$

$$R_{crit} \approx 71 \Omega$$


- Reduce the output current to automatically enter DCM

Dynamic Response is Immediate

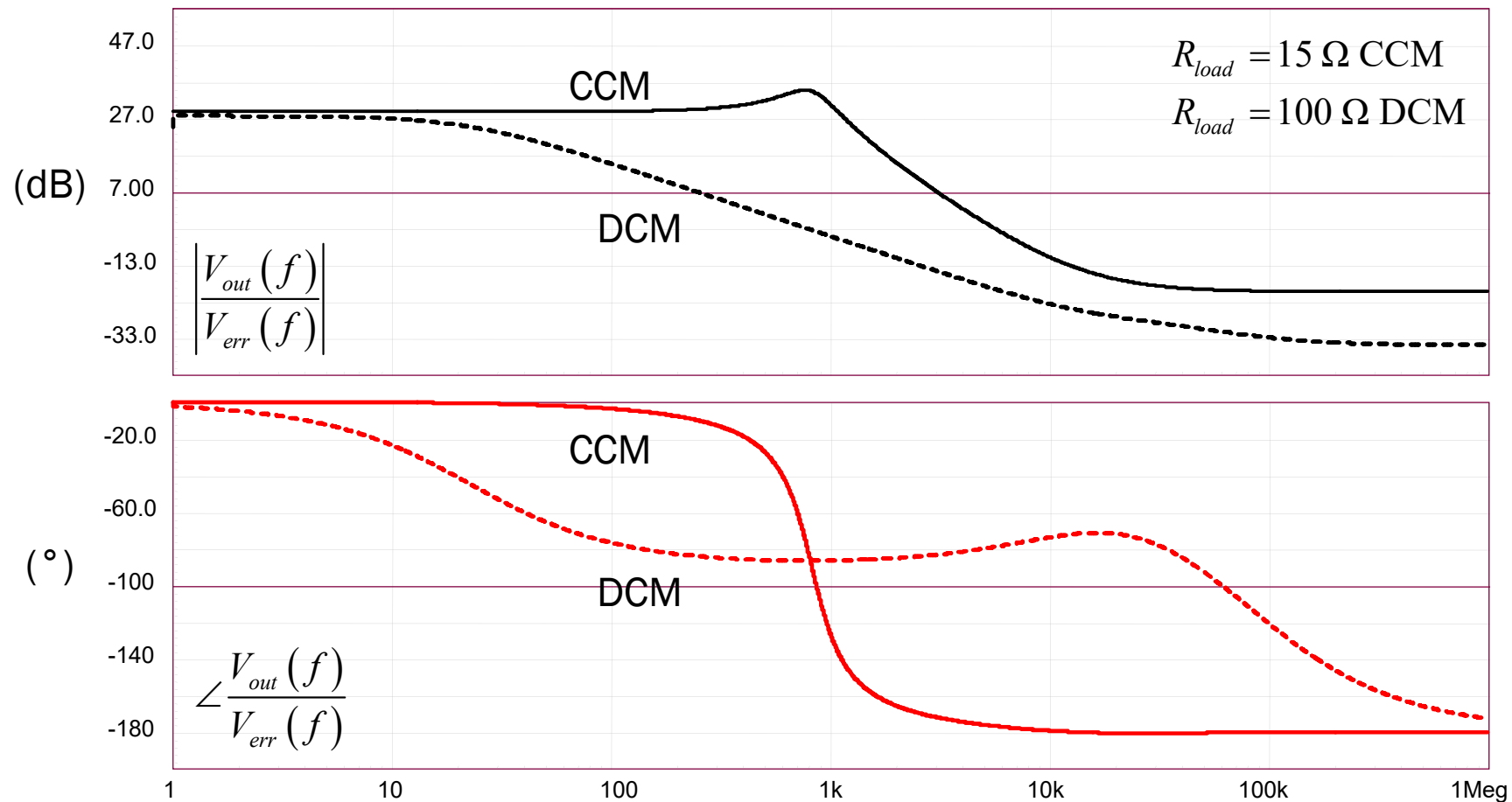- The DCM response is still of second order with a RHPZ




Port the Models to Other Platforms

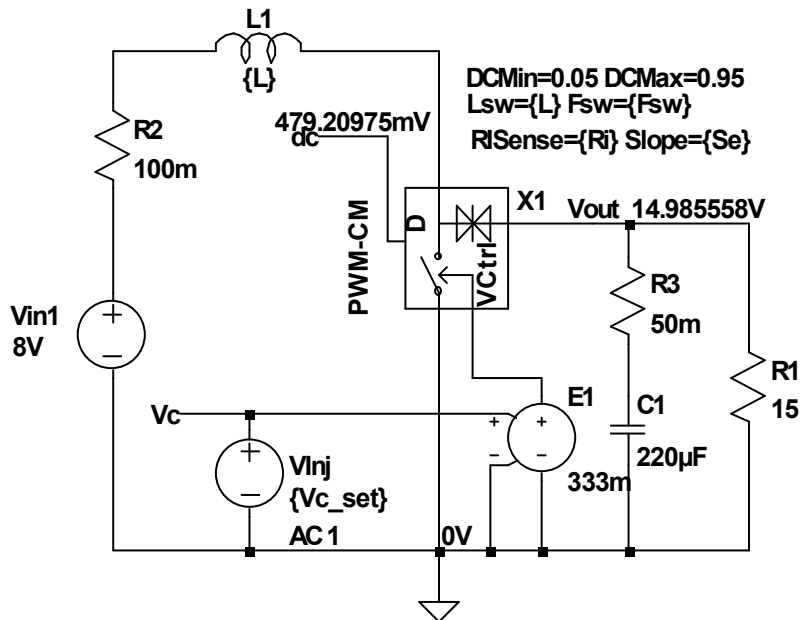



LTspice lends itself well to this type of simulations.
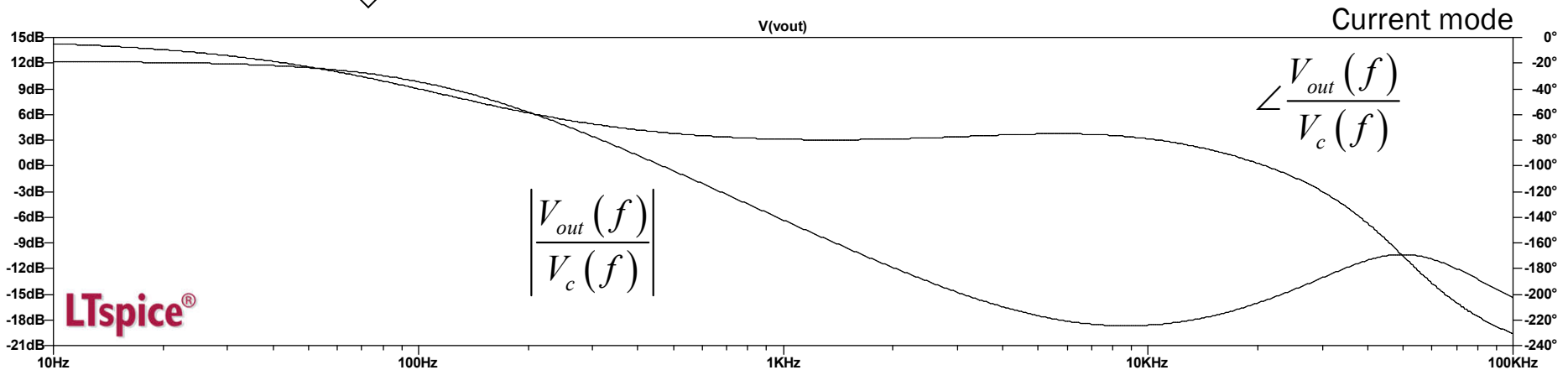
```
.param L=47uH
.ac dec 1000 10 100kHz
.param Vc_set=2.09
.param Fsw=100k
.param Ri=-250m
.param Se=24.4k
```





No Simple Average Model for LLC

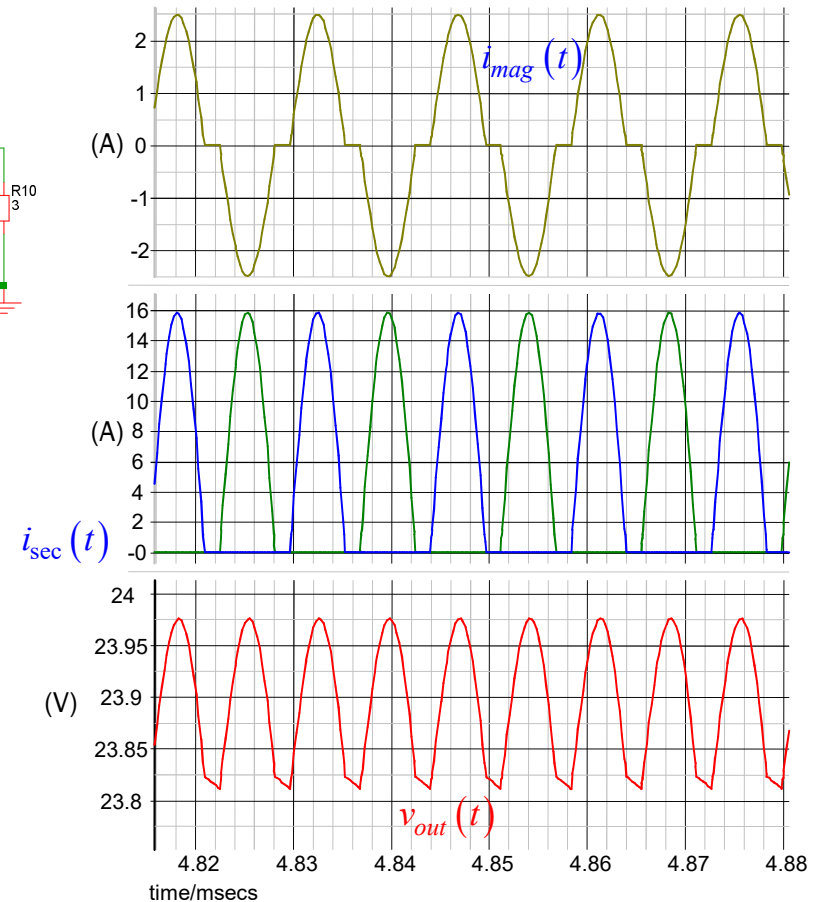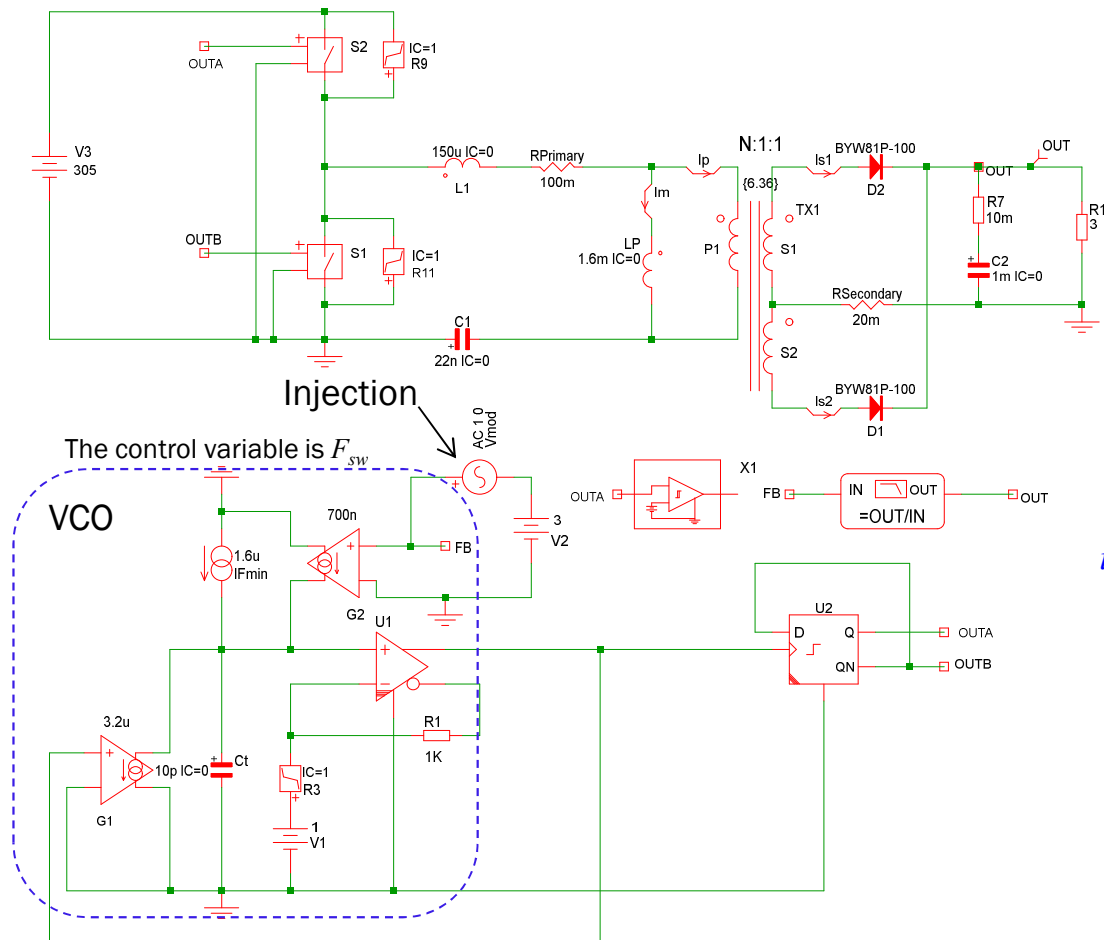□ PWL simulation is perfectly suited for a LLC converter



Dynamic Response of a LLC

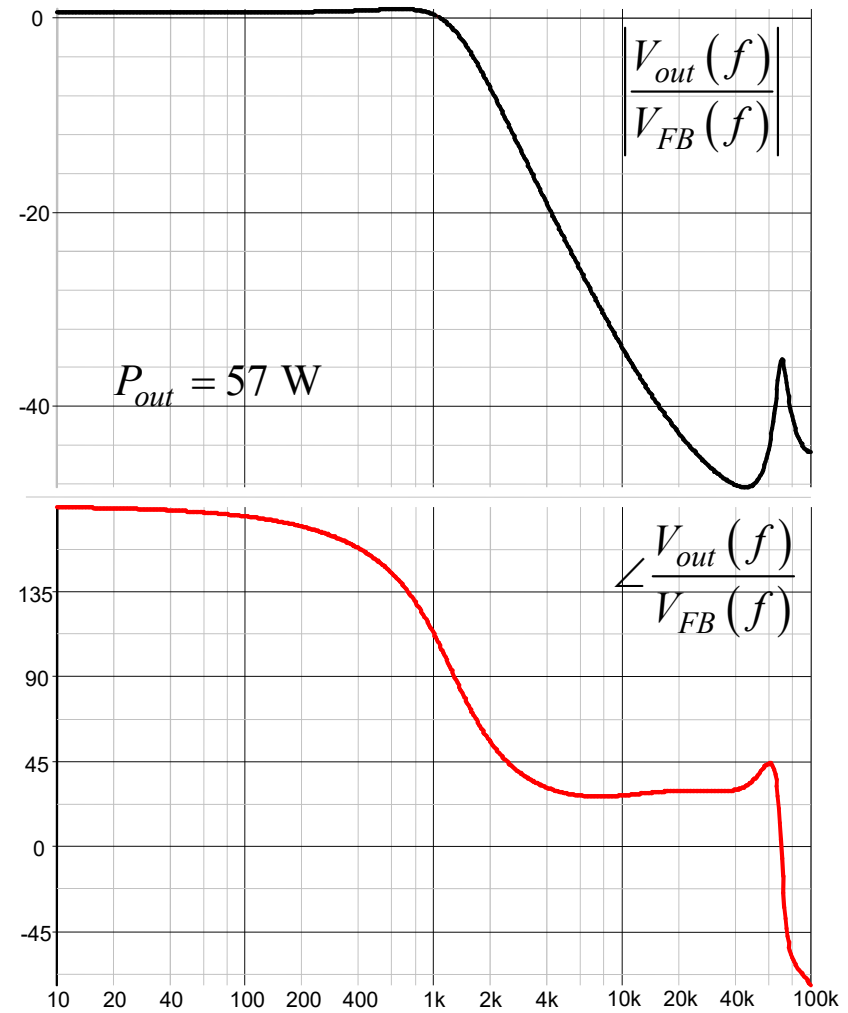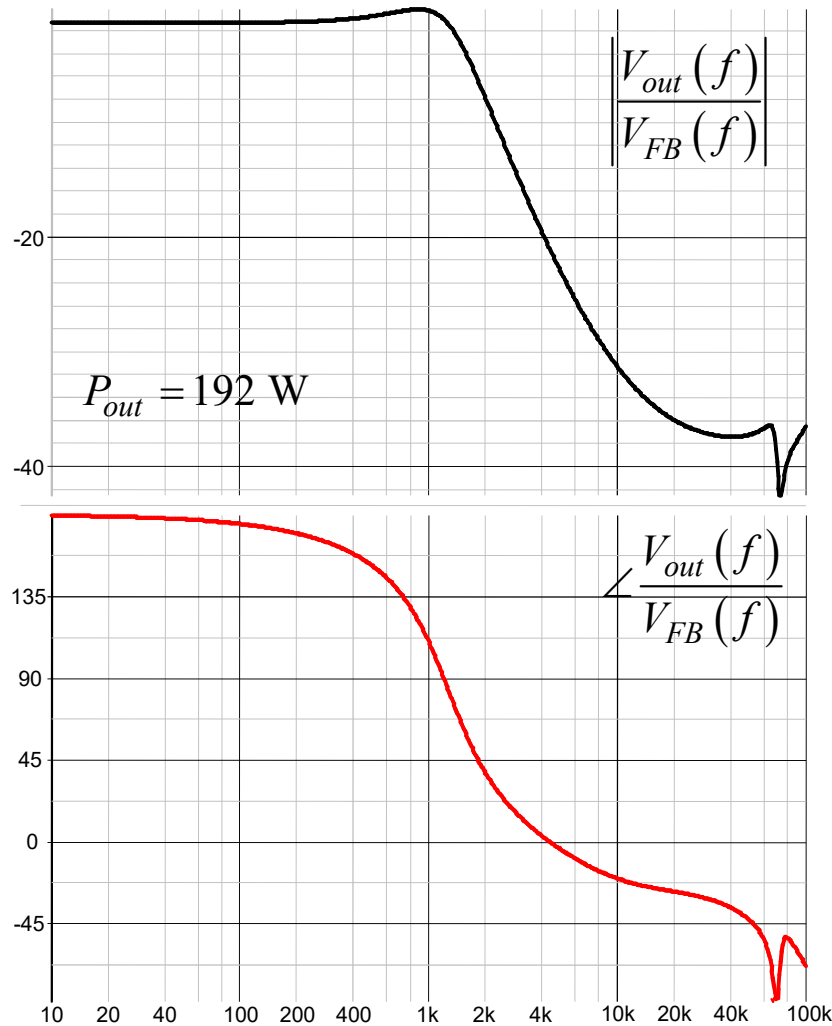- The Bode plot for two different loads is obtained in 10 s




Course Agenda

- Blocks in a Switching Converter
- Introduction to Small-Signal Modeling
- Analytical Analysis of an Output Stage
- Simulation Models - Averaged or Switched?
- Crossover Frequency and Phase Margin**
- Compensation Strategy
- Experiments on Prototypes
- Conclusion




What Type of Transient Response?

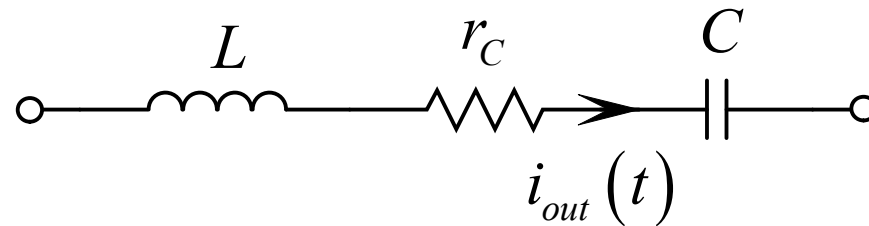- ❑ Parasitics affect the response to a load step




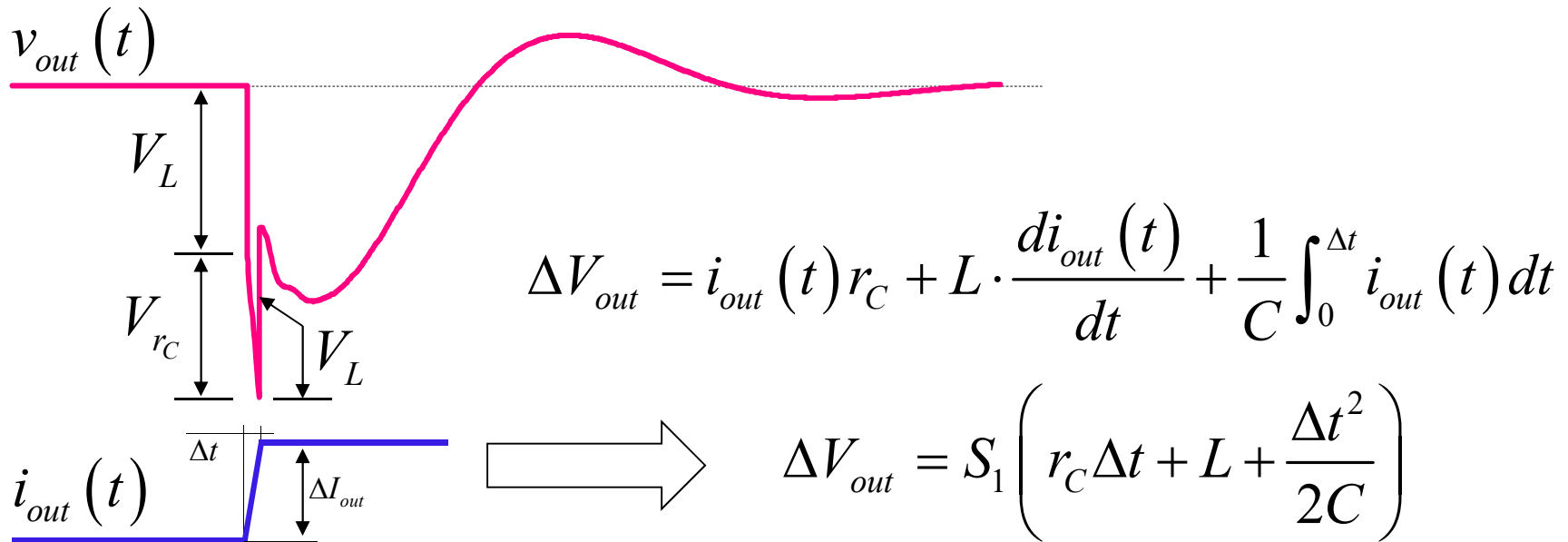- ❑ The drop is a combination of three voltages



How to Study the Compensation Effects?

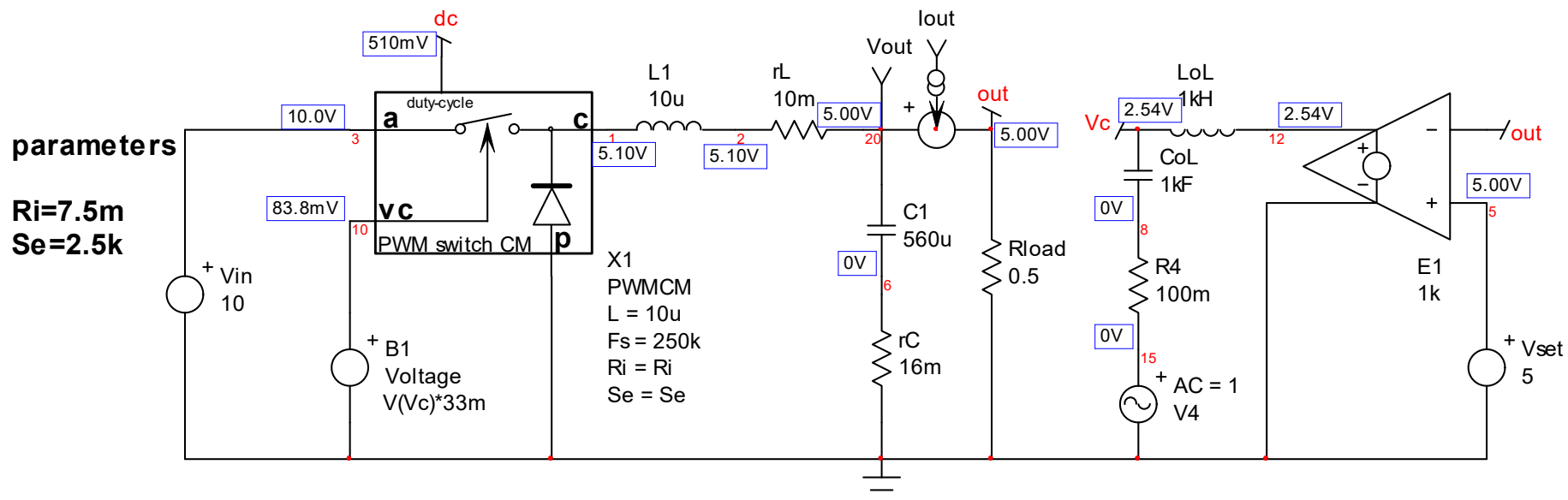
- A nonlinear average model is the ideal tool
- ❖ Auto-bias the output to its operating point, $I_{out} = 10\text{ A}$



- Check all operating points are correct ($V_{out} = 5\text{ V}$)
- Extract magnitude and phase information from the Bode plot

You Need the Power Stage Response

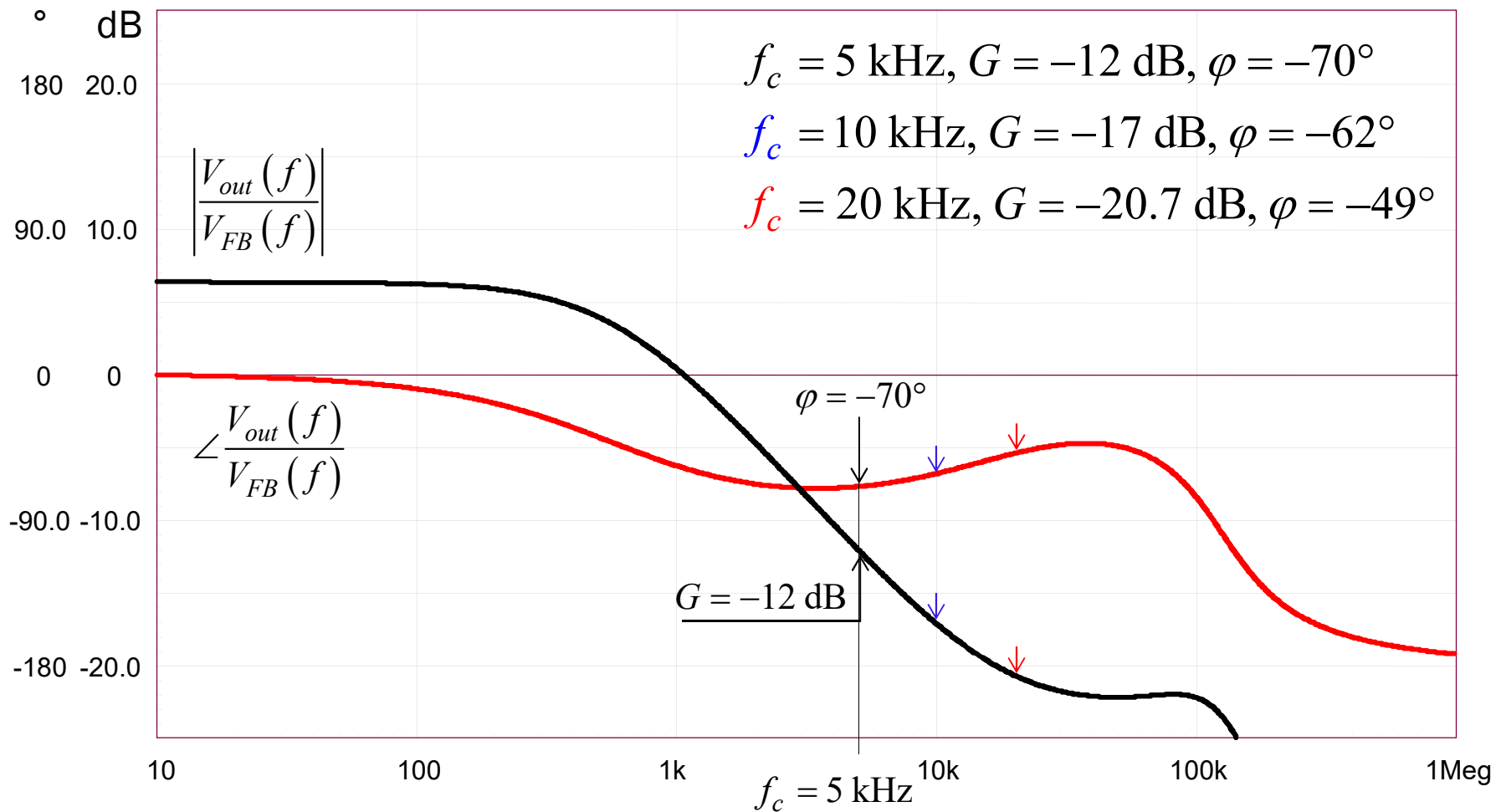- Select a crossover frequency f_c : read magnitude and phase



Capture these Values in the Sheet

□ You can automate the compensation elements computation

Power stage
data

k-factor
automation

parameters

Rupper=10k
Rlower=Rupper
fc=20k
pm=60


Gfc=-20.7
pfc=-49

$G=10^{(-Gfc/20)}$
boost=pm-(pfc)-90
pi=3.14159
 $K=\tan((\text{boost}/2+45)*\pi/180)$
 $C2=1/(2*\pi*fc*G*k*Rupper)$
 $C1=C2*(K^2-1)$
 $R2=k/(2*\pi*fc*C1)$

fp1=1/(2*pi*R2*C2)
fz1=1/(2*pi*R2*C1)


PWR stage response

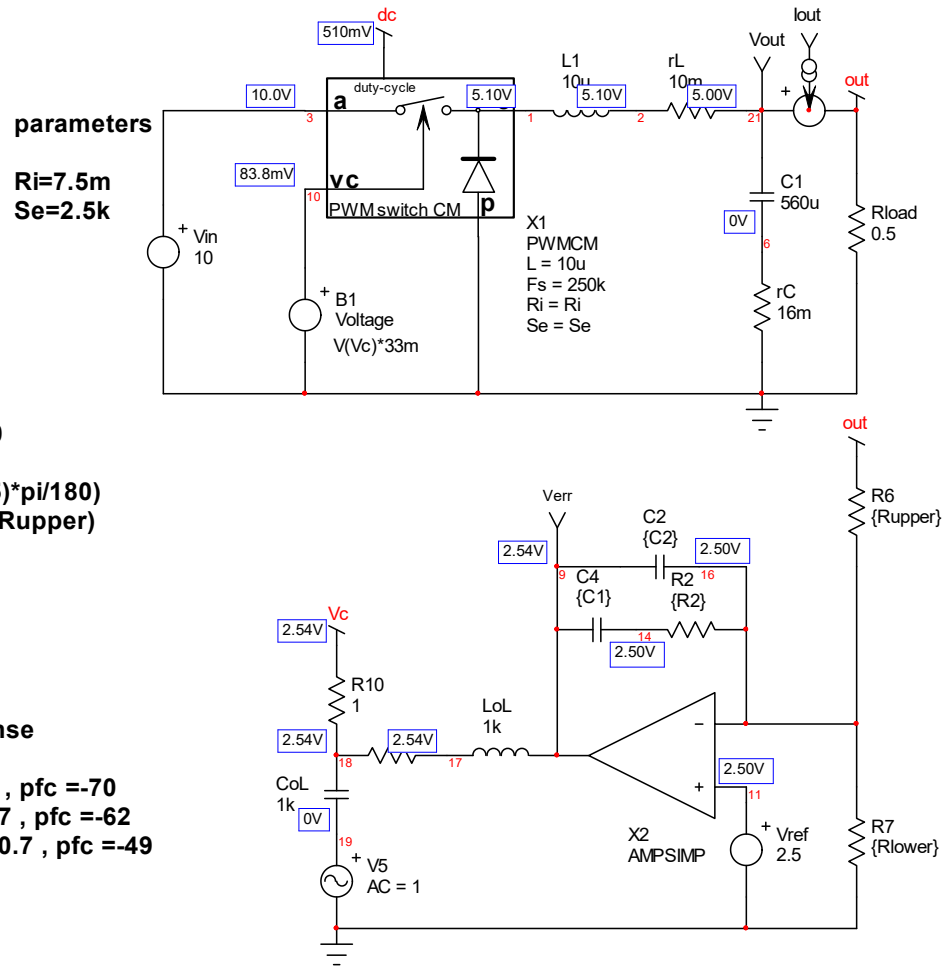fc=5 kHz, Gfc =-12 , pfc =-70
fc=10 kHz, Gfc =-17 , pfc =-62
fc=20 kHz, Gfc =-20.7 , pfc =-49




Check the Open-Loop Gain Data

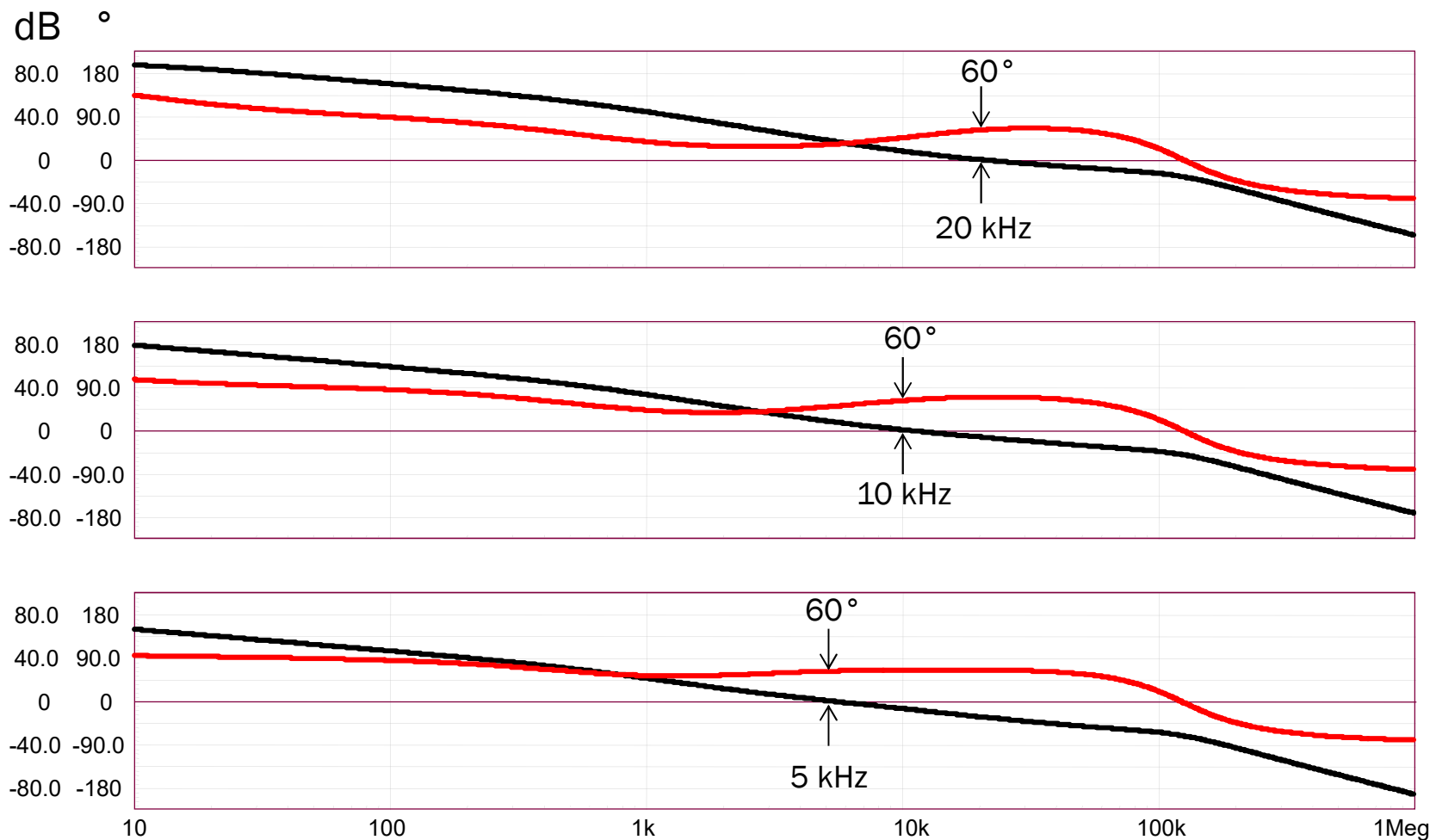- Verify compensation is correct at the three selected points




Step-Load the Output of the Converter

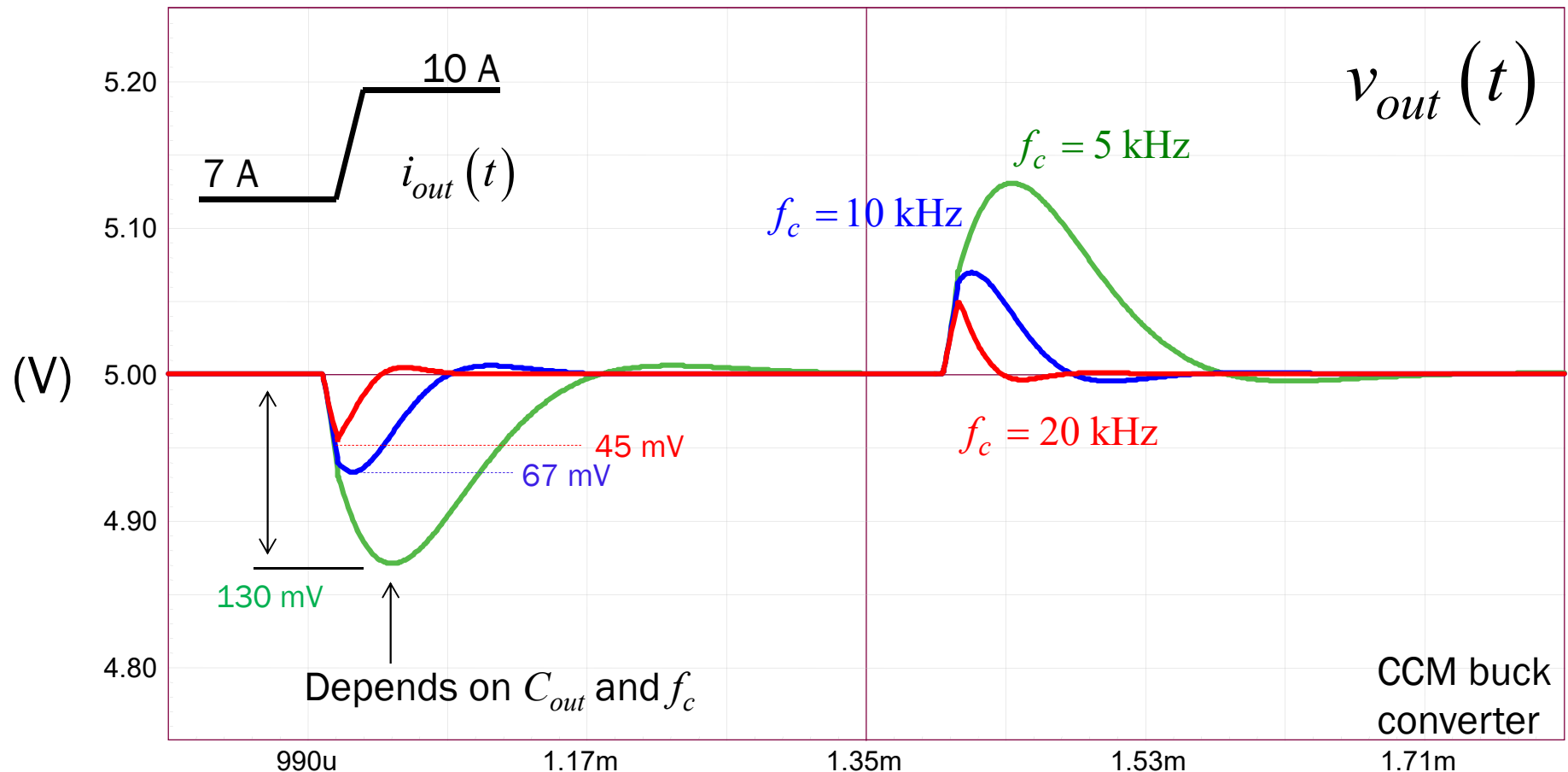- With constant 60° phase margin the crossover affects the drop




Sweep Phase Margin at Constant f_c

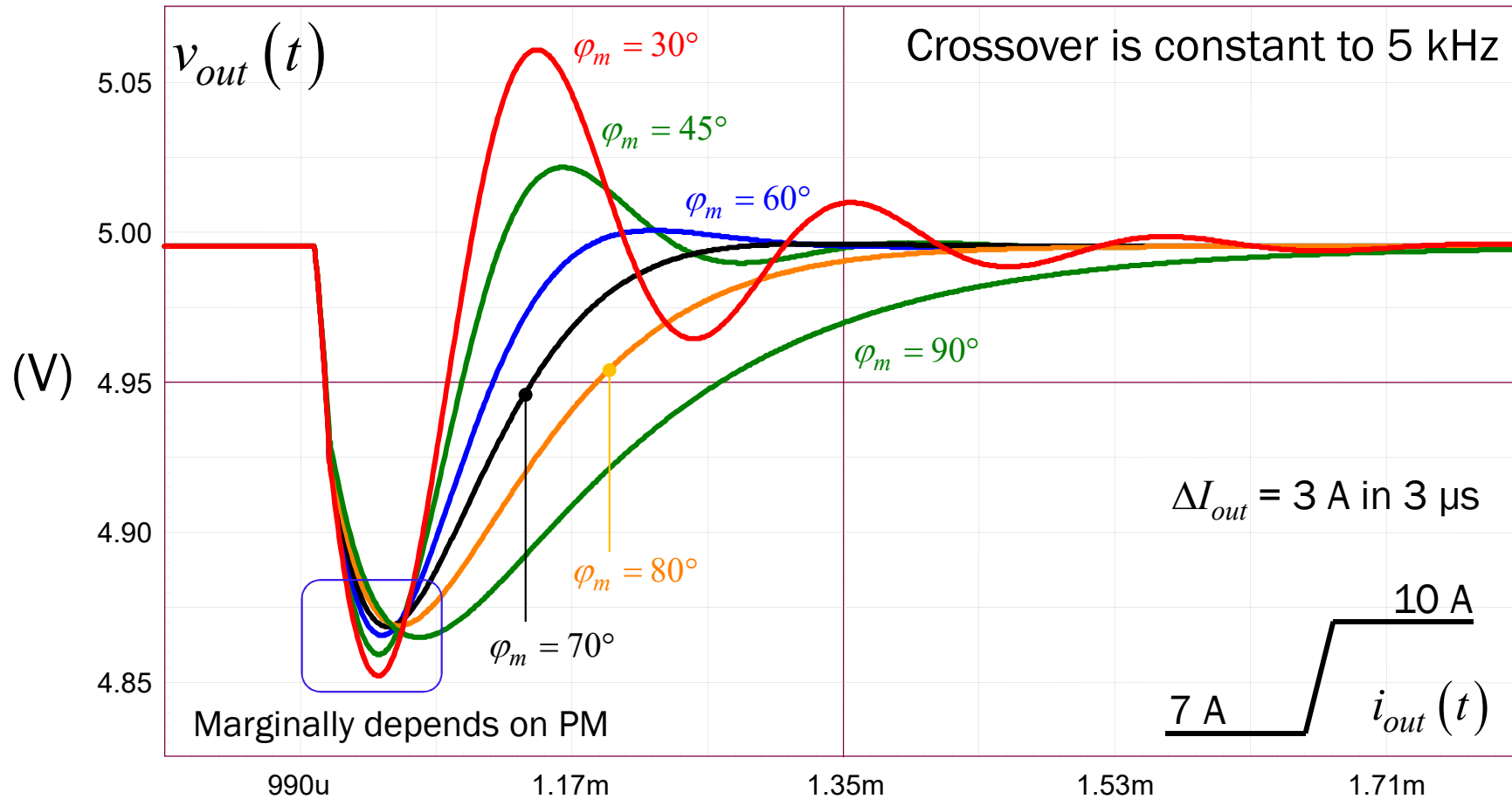- The phase margin affects the overshoot and recovery




Link Phase Margin with Quality Factor

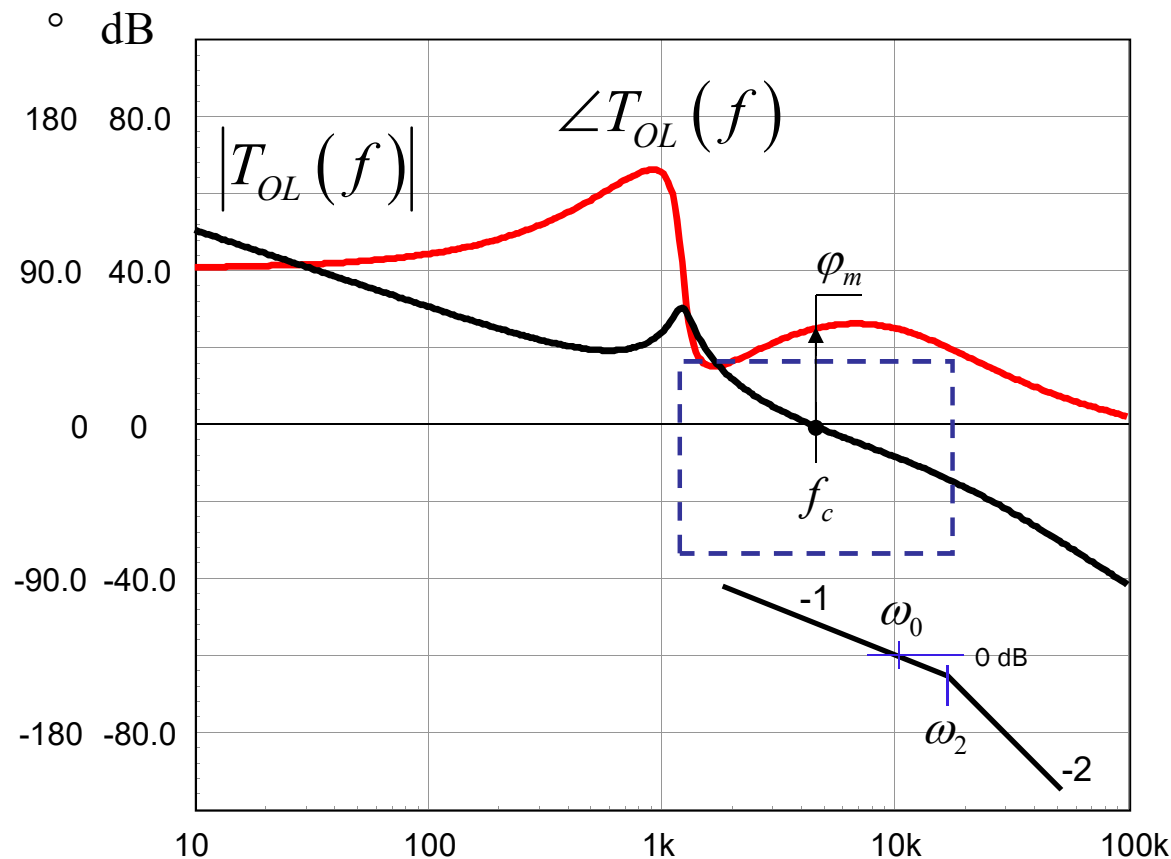- We can observe the loop gain in the vicinity of crossover



Open-loop ac analysis

Approximation of $T(s)$
around f_c

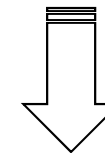


$$T_{OL}(s) = \frac{1}{\left(\frac{s}{\omega_0}\right)\left(1 + \frac{s}{\omega_2}\right)}$$



Deriving the Closed-Loop Gain

- Consider a unity return control system

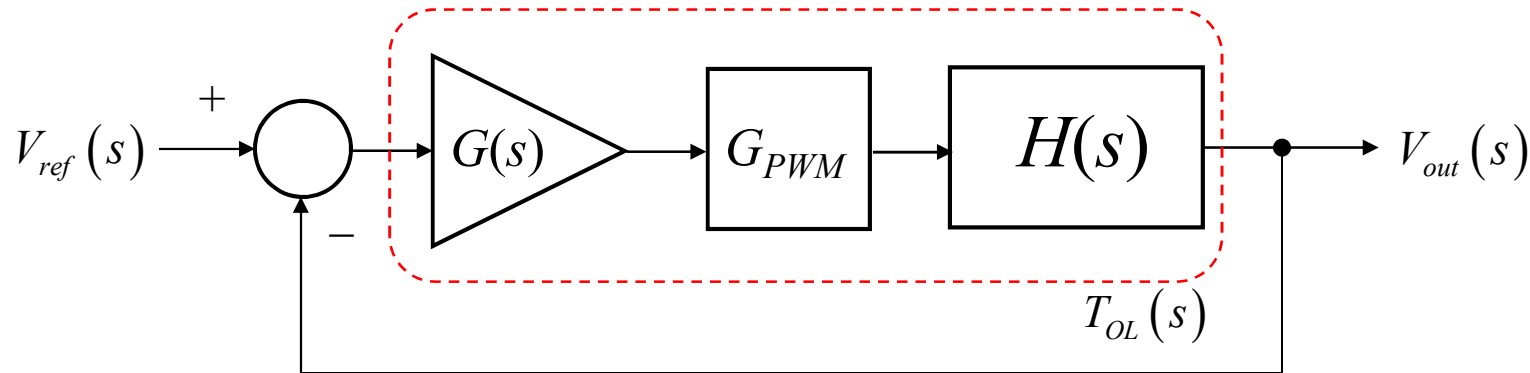

- We can derive the closed-loop transfer function



$$\frac{V_{out}(s)}{V_{ref}(s)} = \frac{T_{OL}(s)}{1 + T_{OL}(s)} = \frac{1}{\frac{s^2}{\omega_0\omega_2} + \frac{s}{\omega_0} + 1} = \frac{1}{1 + \frac{s}{\omega_c Q} + \left(\frac{s}{\omega_c}\right)^2}$$

$\omega_c = \sqrt{\omega_0\omega_2}$ ← Open-loop data
 $Q = \frac{\omega_0}{\omega_2}$
 ↑ Closed-loop data

Phase Margin and Transient Response

- Choose phase margin based on the response you want

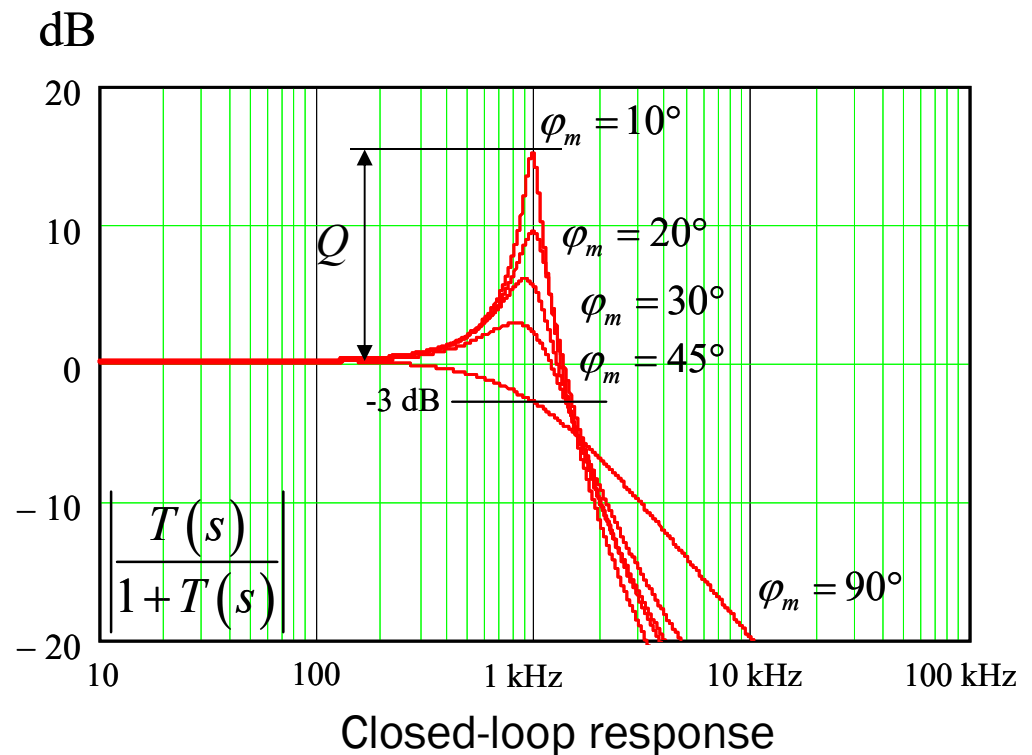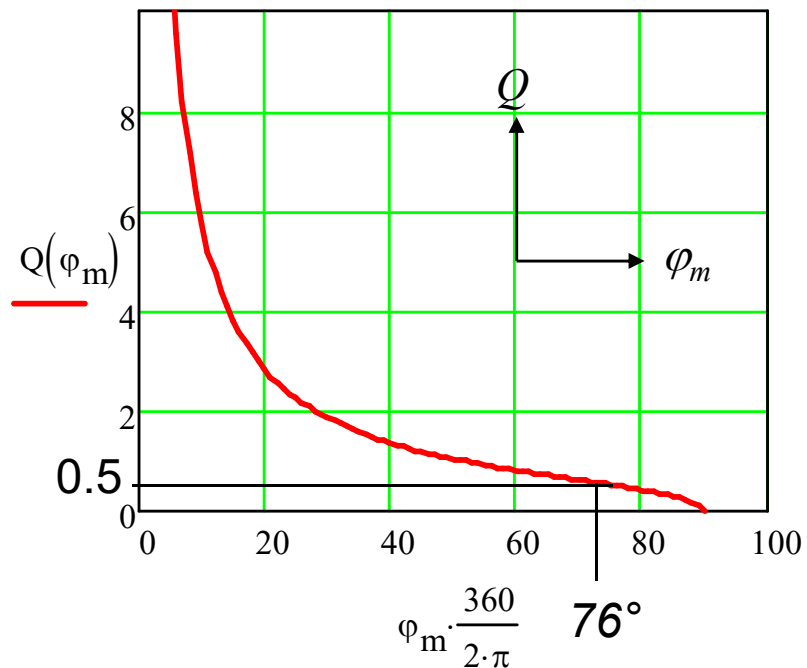
$$Q = \frac{\sqrt{\cos(\varphi_m)}}{\sin(\varphi_m)}$$



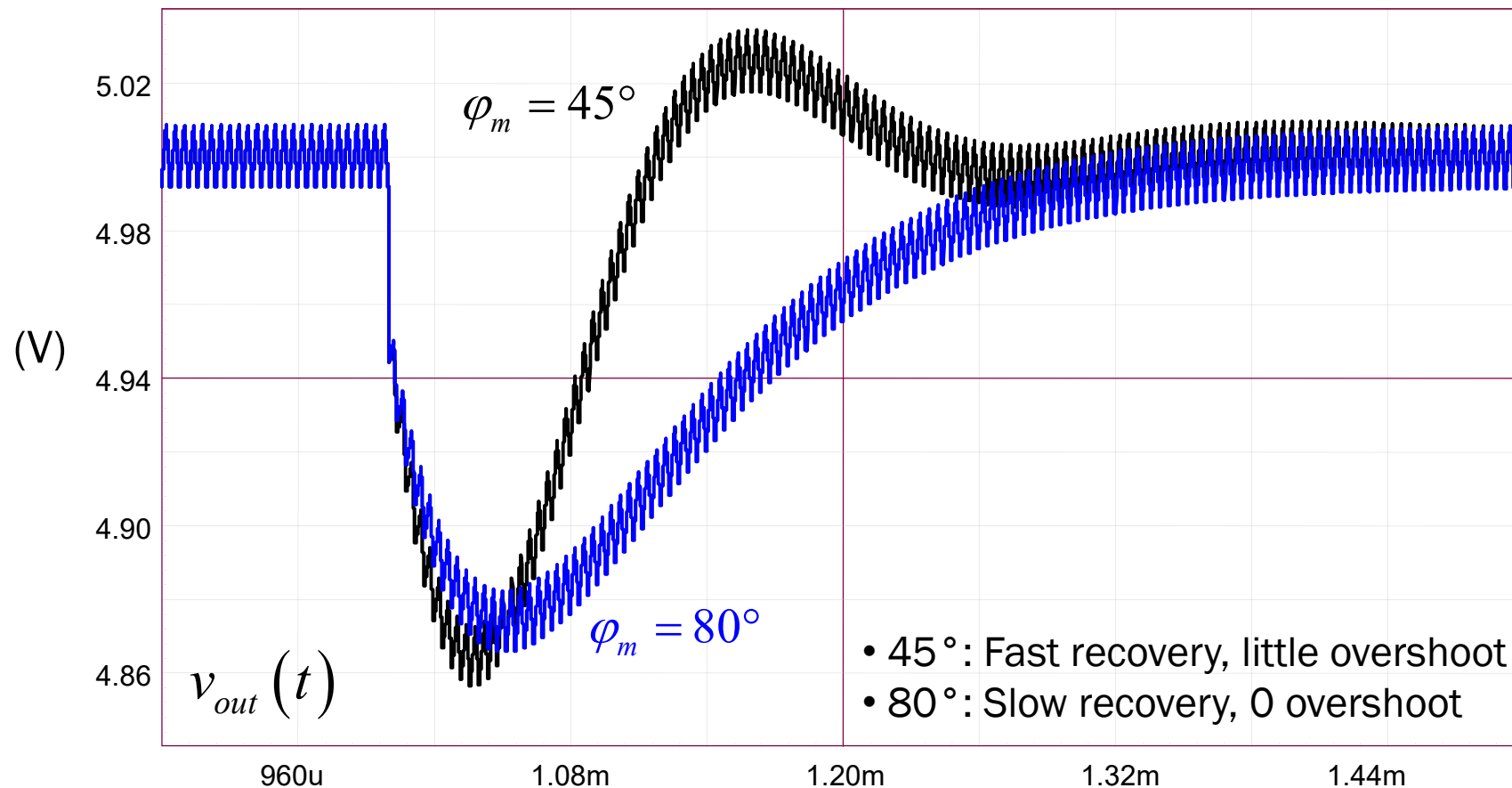C. Basso, "The Dark Side of Loop Control Theory", APEC 2012 Professional Seminar


What Transient Response is Wanted?

- Choose phase margin based on the response you want



How to Select Crossover Frequency?

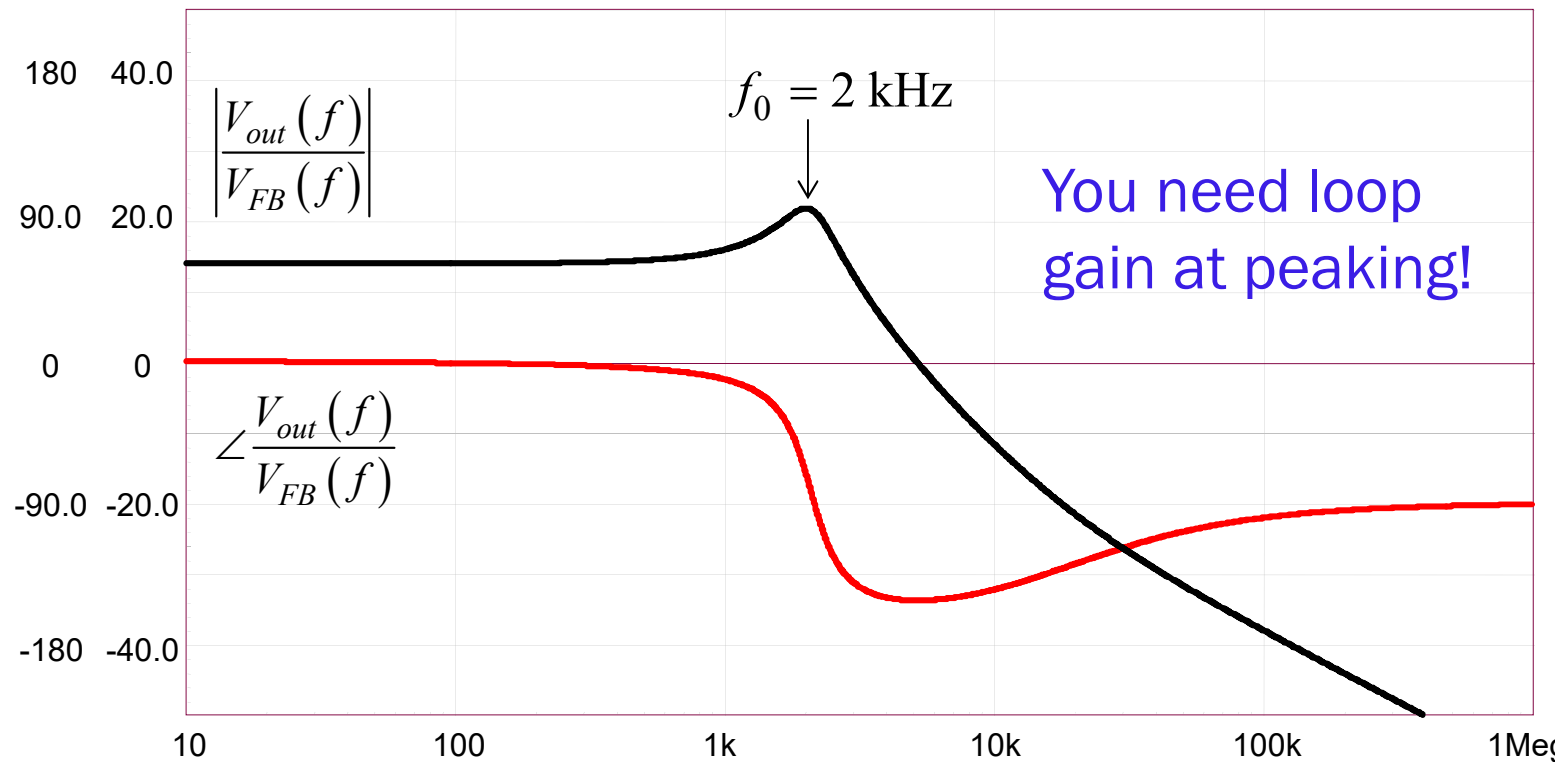
- Before selecting a value, there are limits to respect




- Crossover for a CCM VM buck must be: $3 \cdot f_0 < f_c < \frac{F_{SW}}{2}$
- ❖ In this example: $f_c > 6$ kHz

A Peaky Closed-Loop Output Impedance

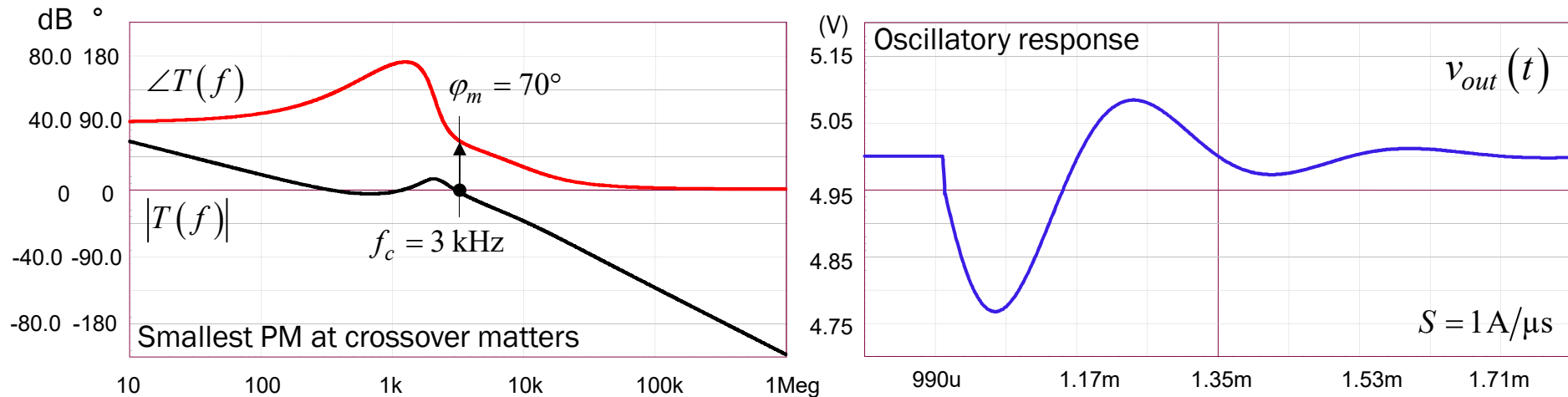- ❑ Too low a crossover and perturbation can't be fought




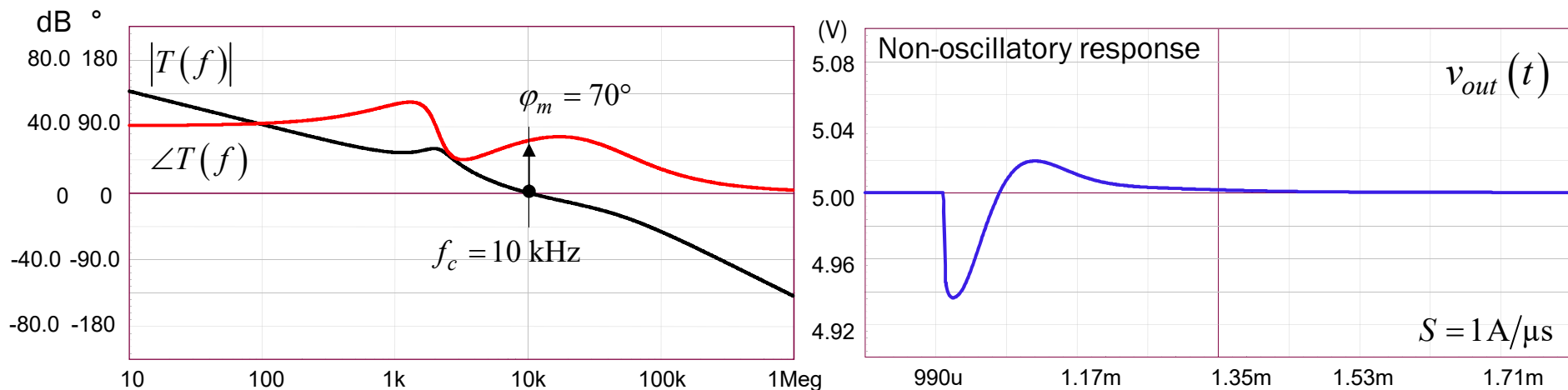- ❑ With enough gain, response is non-oscillatory



Beware of the Deceitful RHP Zero

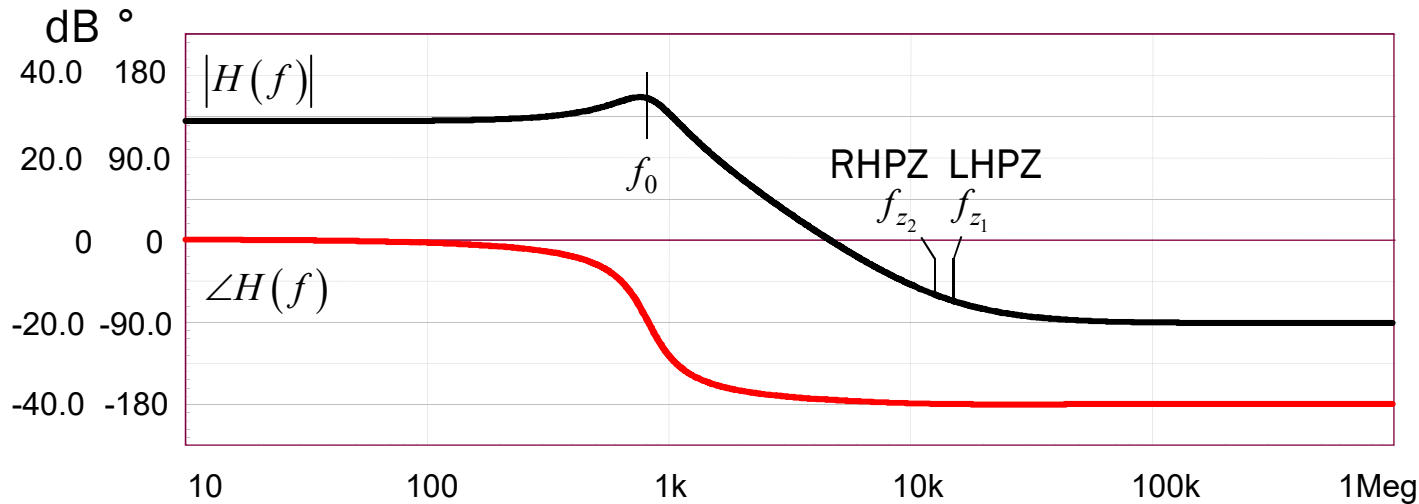□ Peaking also exists in the CCM VM boost and there is a RHPZ



$$f_0 = \frac{1-D}{2\pi\sqrt{LC}} = 817 \text{ Hz}$$

$$f_{z_1} = \frac{1}{2\pi r_C C} = 14.5 \text{ kHz}$$

$$f_{z_2} = \frac{R(1-D)^2}{2\pi L} = 13.8 \text{ kHz}$$

□ Crossover must be selected beyond resonance and below RHPZ

❖ Stay below 30% of the lowest RHPZ position (low V_{in} , high I_{out})

$$3 \cdot f_0 < f_c < 0.3 \cdot f_{z_2}$$


$$V_{in} = 8 \text{ V}$$

$$L = 47 \mu\text{H}$$

$$D = 47.8\%$$

$$R = 15 \Omega$$

$$C = 220 \mu\text{F}$$

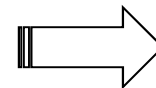


$$2.4 \text{ kHz} < f_c < 4.1 \text{ kHz}$$

Similar remarks for a buck-boost but different RHPZ

Less Constraints in Current Mode

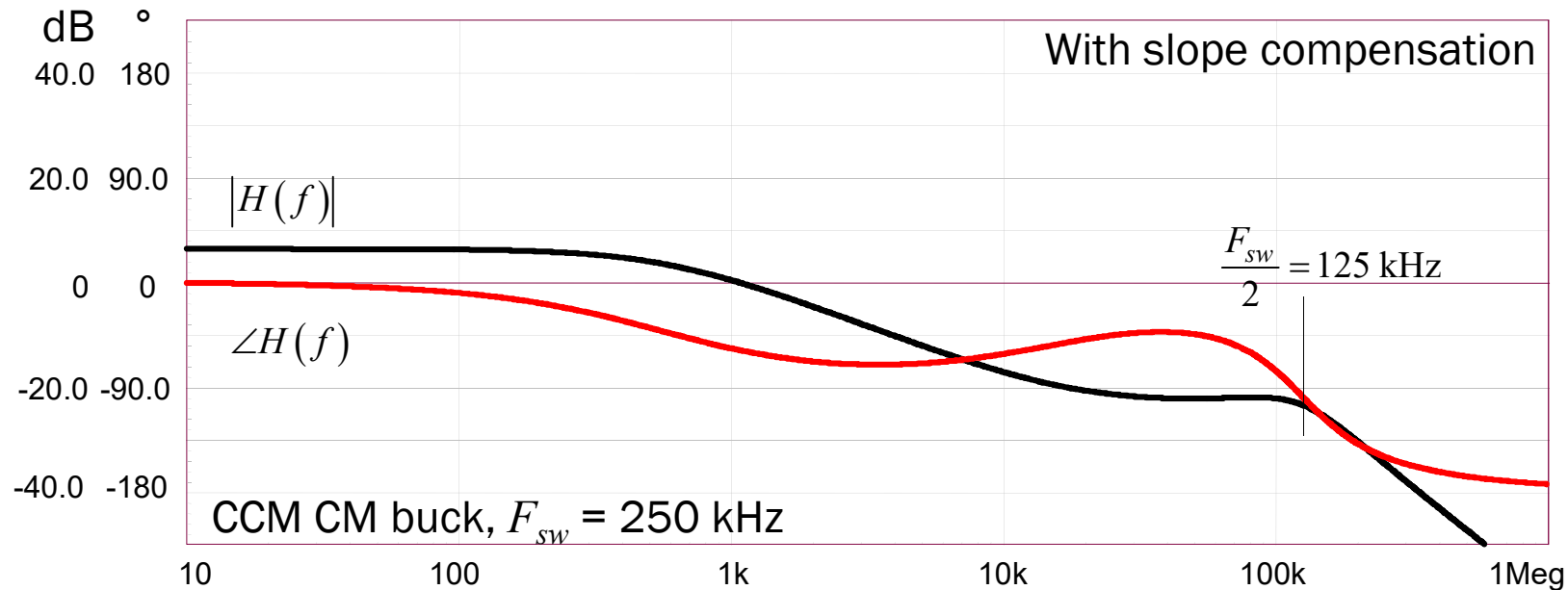- Once the poles are damped, the *theoretical* crossover limit is $F_{sw}/2$




- ❖ Don't push f_c too far as it increases susceptibility to noise 🍷
- ❖ As f_c goes up, beware of various delays (conversion time, prop. del.)

➡ Choose crossover to meet transient response, not more!

RHP Zero is Still There in Current Mode

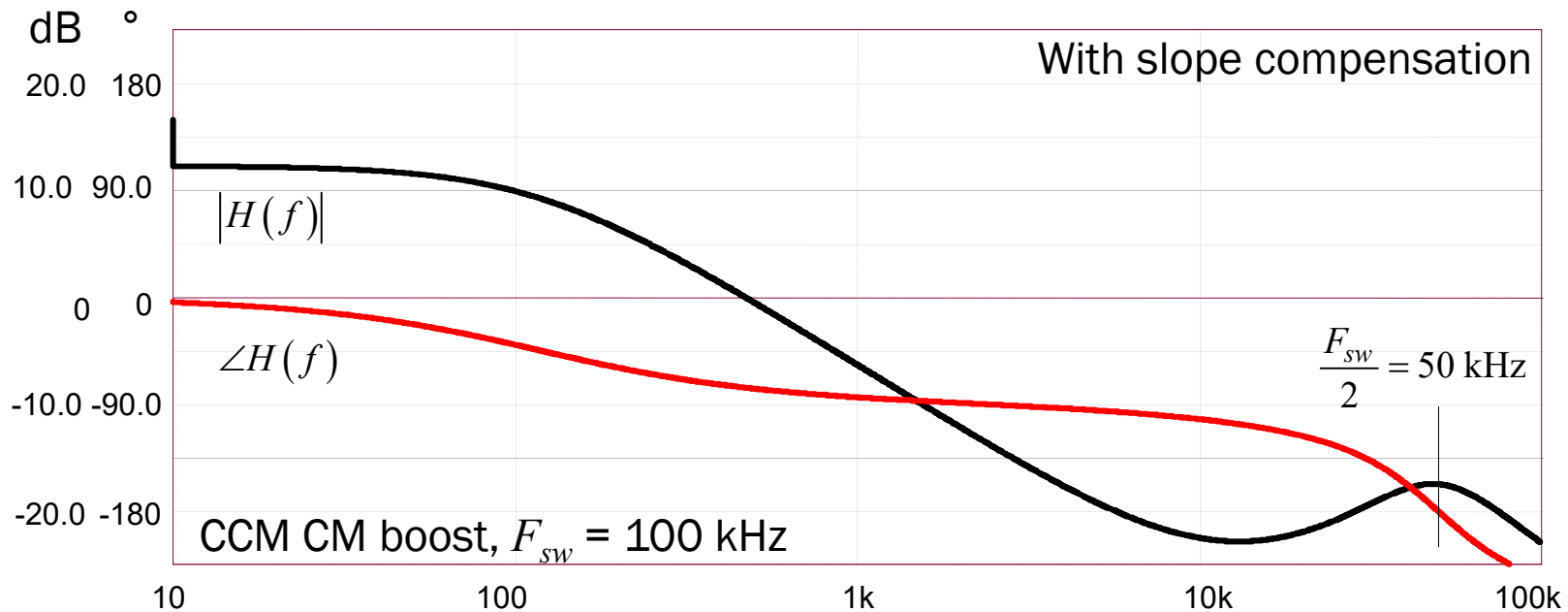- In boost and buck-boost CM, the RHPZ still fixes the upper limit




- ❖ Stay below 30% of the lowest RHPZ position (low V_{in} , high I_{out})

$$f_c < 0.3 \cdot f_{z_2} \quad \Rightarrow \quad f_c < 4.1 \text{ kHz}$$

Similar remarks for a buck-boost but different RHPZ


Output Impedance and Transient Response

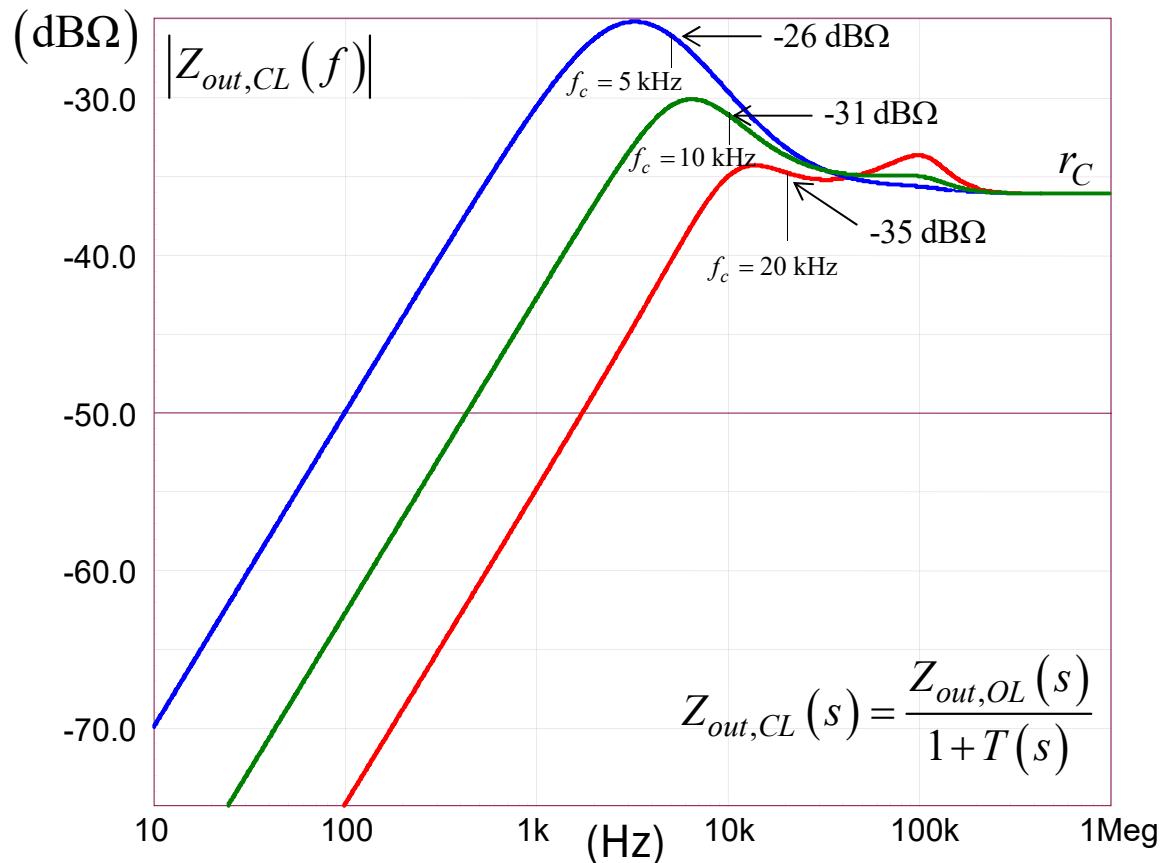□ The closed-loop output impedance changes with crossover



If C_{out} 's impedance dominates at f_c then

$$r_C \ll \frac{1}{2\pi f_c C_{out}}$$

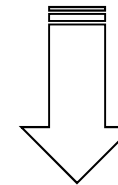


$$\Delta V_{out} \approx \frac{\Delta I_{out}}{2\pi f_c C_{out}}$$

□ As crossover improves, Z_{out} approaches the minimum set by r_C

A Simple Guide to Crossover Selection

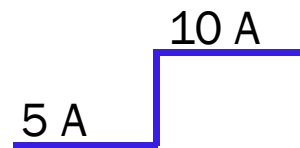- ❑ Select the output capacitor based on ripple current, ESR etc.
- ✓ Choose the crossover frequency to meet undershoot specs




$$\Delta V_{out} < 100 \text{ mV}$$




$$C_{out} = 560 \mu\text{F}$$

$$r_C = 5 \text{ m}\Omega$$

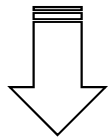
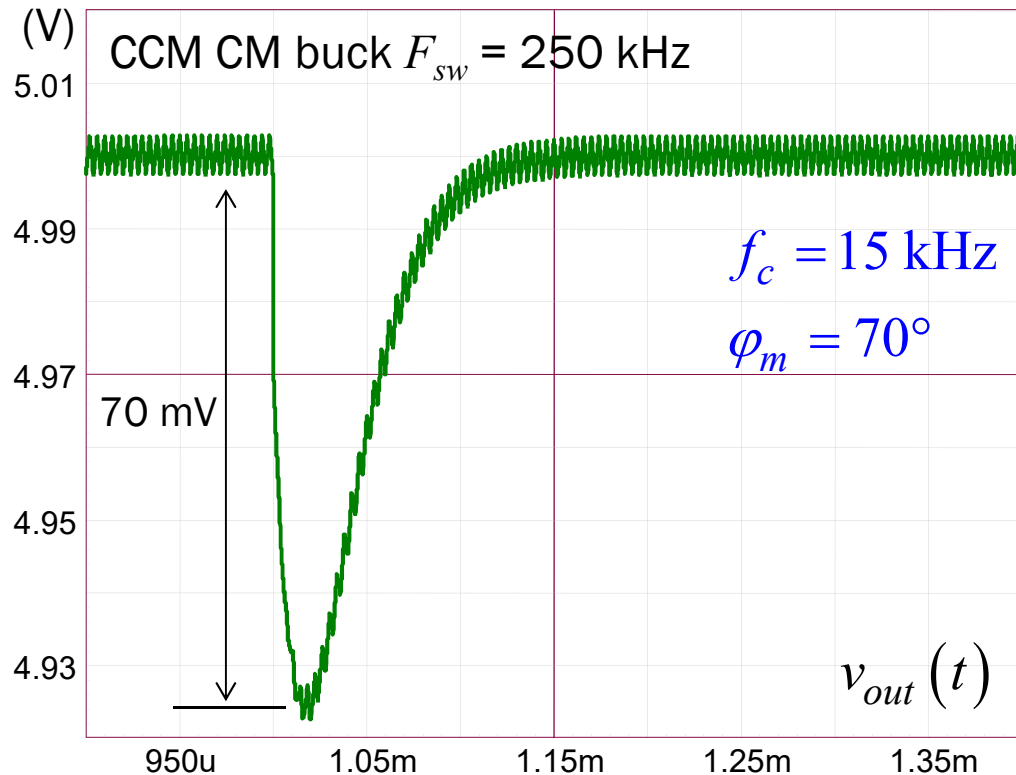
$$f_c \approx \frac{\Delta V_{out}}{2\pi C_{out} \Delta I_{out}} = 15 \text{ kHz}$$



- ❑ It surely is an approximation as the system is nonlinear but it's a guide




Course Agenda

- Blocks in a Switching Converter
- Introduction to Small-Signal Modeling
- Analytical Analysis of an Output Stage
- Simulation Models - Averaged or Switched?
- Crossover Frequency and Phase Margin
- Compensation Strategy**
- Experiments on Prototypes
- Conclusion



Stabilizing a Voltage-Mode Boost Converter

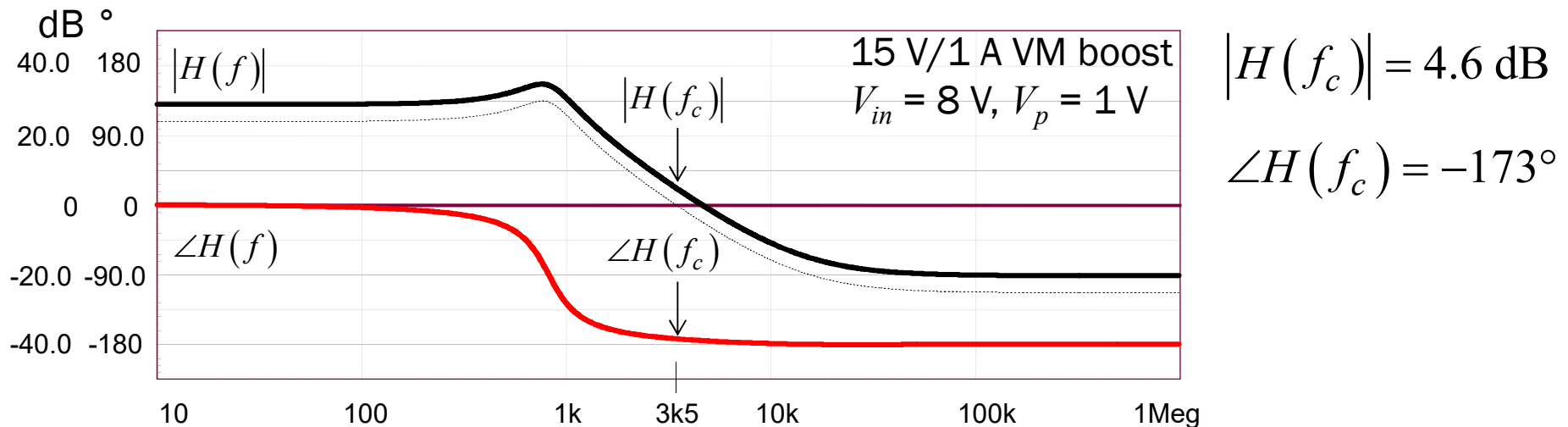- Whether you use SPICE, Simplis[®], Mathcad[®] or the bench...
- You start the process with the power stage ac response



- We select a crossover frequency f_c of 3.5 kHz
- ❖ Read the power stage Bode plot at f_c :
- ❖ Shift the curve down by 4.6 dB to crossover the 0-dB axis at f_c
- We choose a 50° phase margin

Place Poles and Zeros

- ❑ k factor is a way to go but conditional stability can happen in CCM
- ❑ We will adopt the following strategy:
 - ✓ A double zero located slightly below the resonant frequency f_0
 - ✓ A 1st pole adjusted to cancel the RHPZ or ESR contribution
 - ✓ A 2nd pole is adjusted to meet the phase margin goal

$$\begin{aligned}V_{in} &= 8 \text{ V} \\L &= 47 \text{ } \mu\text{H} \\D &= 47.8\% \\R &= 15 \text{ } \Omega \\C &= 220 \text{ } \mu\text{F} \\r_C &= 50 \text{ m}\Omega\end{aligned}$$

$$f_0 = \frac{1-D}{2\pi\sqrt{LC}} = 817 \text{ Hz}$$


$$f_{z_1} = \frac{1}{2\pi r_C C} = 14.5 \text{ kHz}$$

$$f_{z_2} \approx \frac{R(1-D)^2}{2\pi \cdot L} = 13.5 \text{ kHz}$$

Compensation strategy:

$$f_{z_1} = f_{z_2} = 700 \text{ Hz}$$

$$f_{p_2} = 20 \text{ kHz}$$

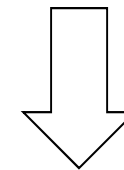

$$f_{p_1} = ?$$

D. Venable, *The k factor: A New Mathematical Tool for Stability Analysis and Synthesis*, Proceedings of Powercon 10, 1983, pp. 1-12

Create Phase Boost at Crossover

- ❑ The cumulated phase lags must be less than 360°
- ✓ The compensator op amp lags by 180°
- ✓ The pole at the origin lags by 90°

⇒ $boost = \varphi_m - \angle H(f_c) - 90^\circ \approx 133^\circ$

- ❑ Place the second pole to boost the phase by 133° at f_c

$$G(s) = -G_0 \frac{\left(1 + \frac{s}{s_{z_1}}\right) \left(1 + \frac{s}{s_{z_2}}\right)}{\left(1 + \frac{s}{s_{p_1}}\right) \left(1 + \frac{s}{s_{p_2}}\right)}$$

$$boost = \tan^{-1}\left(\frac{f_c}{f_{z_1}}\right) + \tan^{-1}\left(\frac{f_c}{f_{z_2}}\right) - \tan^{-1}\left(\frac{f_c}{f_{p_1}}\right) - \tan^{-1}\left(\frac{f_c}{f_{p_2}}\right)$$


$$f_{p_1} = \frac{f_c}{\tan\left[\tan^{-1}\left(\frac{f_c}{f_{z_1}}\right) + \tan^{-1}\left(\frac{f_c}{f_{z_2}}\right) - boost - \tan^{-1}\left(\frac{f_c}{f_{p_2}}\right)\right]}$$

⇒ $f_{p_1} \approx 14 \text{ kHz}$

From compensation strategy:

Adjust the Gain to Meet 0 dB at f_c

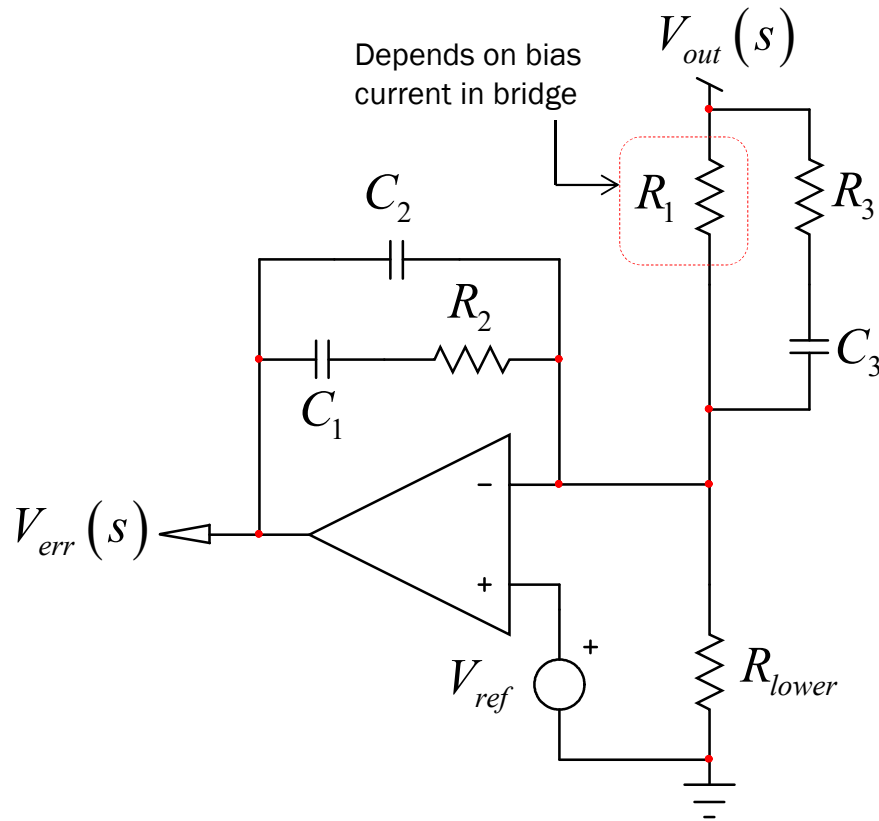- The crossover gain is adjusted by resistance R_2



$$\frac{1}{|H(f_c)|} \downarrow G_{f_c} R_1 f_{p_1} \sqrt{1 + \left(\frac{f_c}{f_{p_1}}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_{p_2}}\right)^2}$$

$$R_2 = \frac{G_{f_c} R_1 f_{p_1}}{f_{p_1} - f_{z_1}} \frac{\sqrt{1 + \left(\frac{f_c}{f_{p_1}}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_{p_2}}\right)^2}}{\sqrt{1 + \left(\frac{f_{z_1}}{f_c}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_{z_2}}\right)^2}}$$

$$C_1 = \frac{1}{2\pi f_{z_1} R_2} \quad C_2 = \frac{C_1}{2\pi f_{p_1} C_1 R_2 - 1}$$

$$C_3 = \frac{f_{p_2} - f_{z_2}}{2\pi R_{upper} f_{p_2} f_{z_2}} \quad R_3 = \frac{R_1 f_{z_2}}{f_{p_2} - f_{z_2}}$$

- Check all values are positive or revise phase margin goals!

C. Basso, *Designing Control Loops for Linear and Switching Power Supplies*, Artech House, 2012

Automate the Calculation in SPICE

□ A dedicated macro computes the component values

parameters

Rupper=5k
 fc=3.5k
 Gfc=4.58
 pfc=-173.476
 pm=50
 boost=pm-(pfc)-90

$G=10^{-(Gfc/20)}$
 $pi=3.14159$

fz1=700
 fz2=700
 fp2=20k

$C1=1/(2*pi*fz1*R2)$
 $C2=C1/(C1*R2*2*pi*fp1-1)$
 $C3=(fp2-fz2)/(2*pi*Rupper*fp2*fz2)$
 $R3=Rupper*fz2/(fp2-fz2)$


$a=sqrt((fc^2/fp1^2)+1)$
 $b=sqrt((fc^2/fp2^2)+1)$
 $c=sqrt((fz1^2/fc^2)+1)$
 $d=sqrt((fc^2/fz2^2)+1)$

$C_1 = 288 \text{ nF}$
 $C_2 = 7.5 \text{ nF}$
 $C_3 = 38 \text{ nF}$
 $R_2 = 676 \Omega$
 $R_3 = 83 \Omega$

$R2=((a*b)/(c*d))/(fp1-fz1)*Rupper*G*fp1$
 $fp1=fc/\tan((2*\atan(fc/fz1)-\tan(fc/fp2))-boost*pi/180)$


parameters

Vin=12
 RL=15

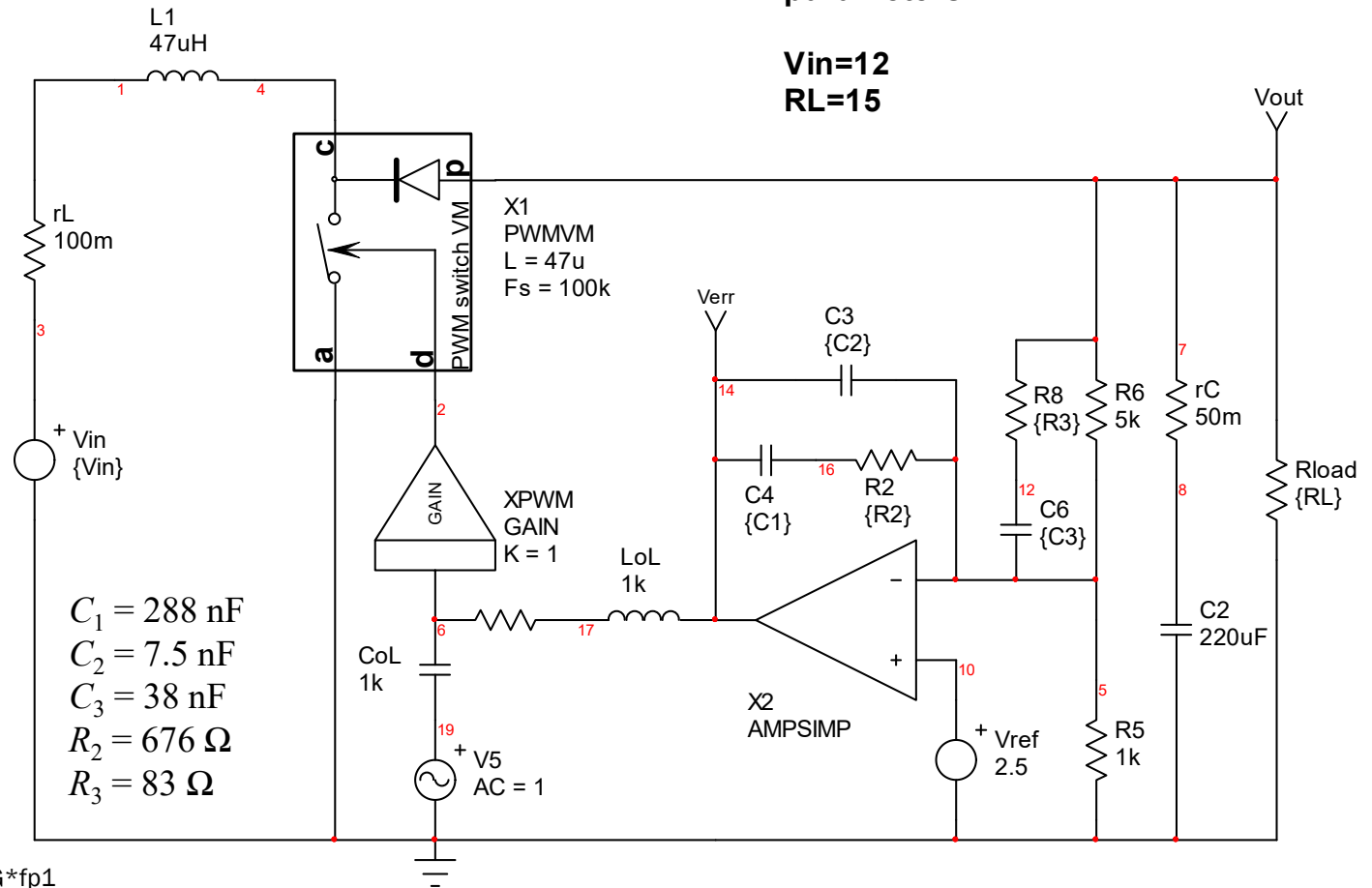

Check the Compensated Converter

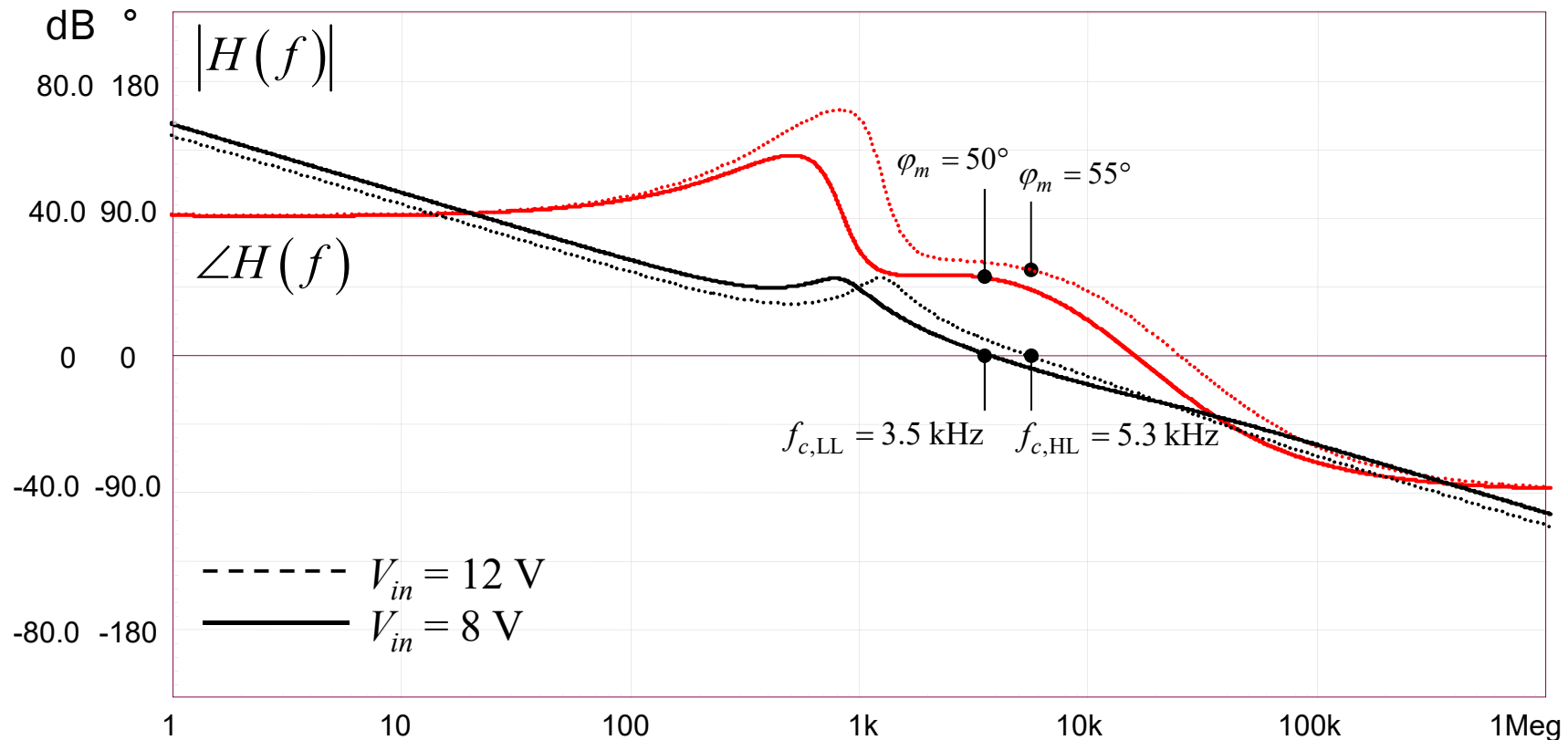
- Verify phase and gain margins at low- and high-line conditions



- ❖ If resonance is too high at high line, increase output capacitor

Check Transient Response

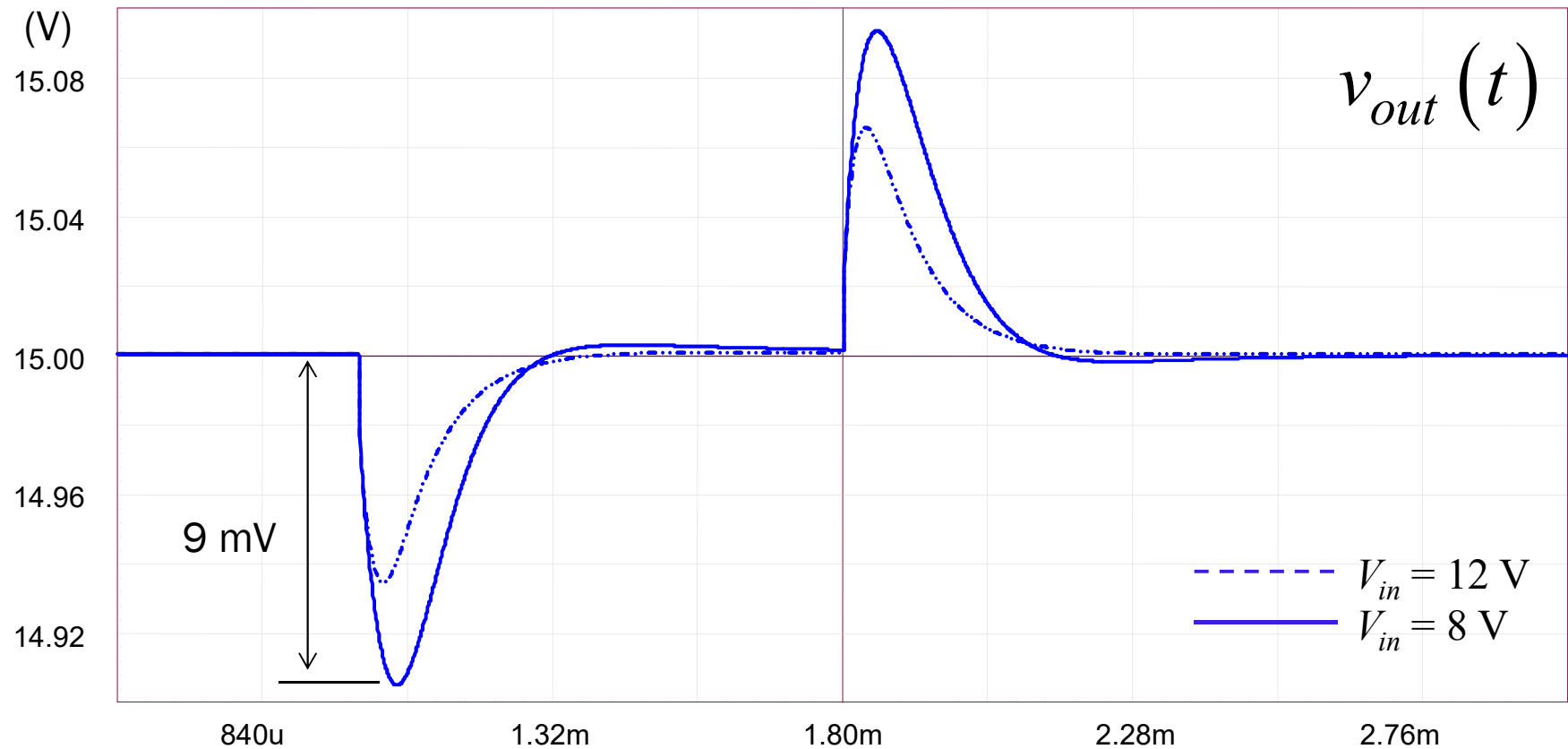
- The output current is varied from 0.5 to 1 A with a 1-A/ μ s slope



- Better response at high line with a slightly higher crossover

Stabilizing a Current-Mode Boost Converter

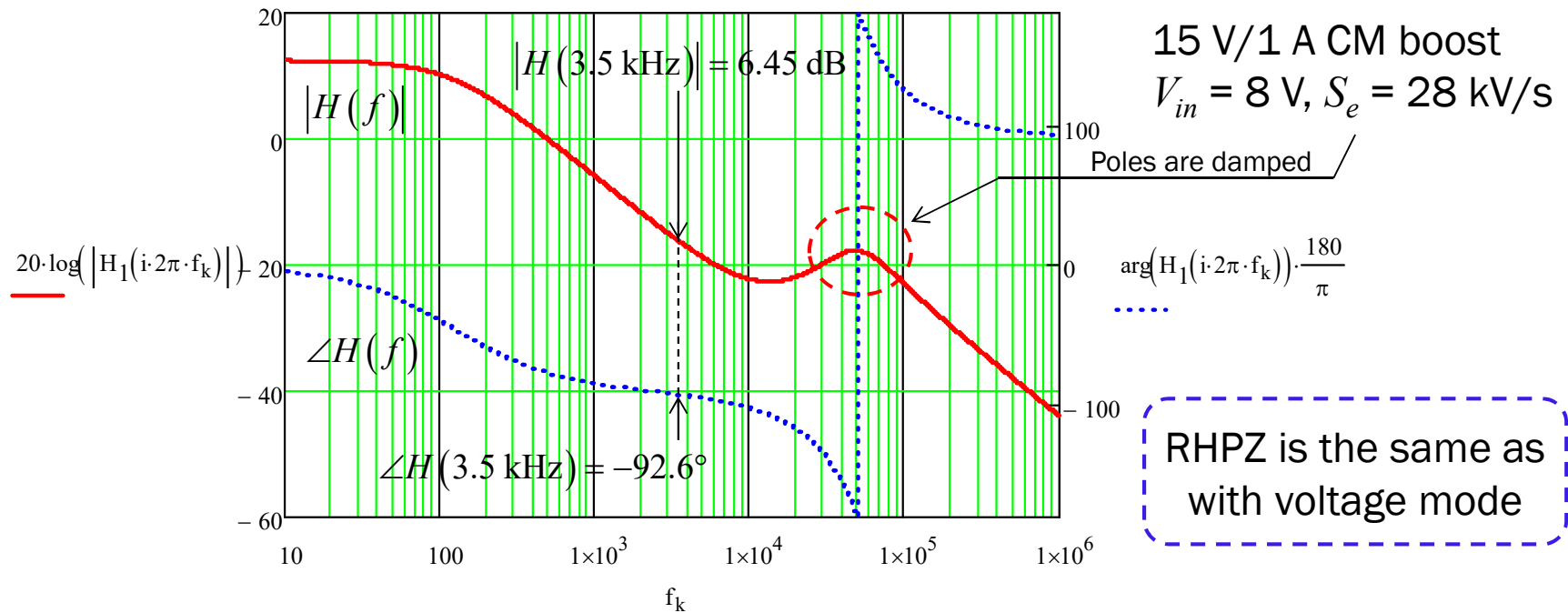- You start with the control-to-output transfer function



- For a phase boost below 90° we will use a type-2 compensator


⇒ $boost = \varphi_m - \angle H(f_c) - 90^\circ \approx 62.6^\circ$

Place Poles and Zeros

□ k factor lends itself well to stabilizing 1st-order circuits

$$k = \tan\left(\frac{\text{boost}}{2} + \frac{\pi}{4}\right) = 4.1$$
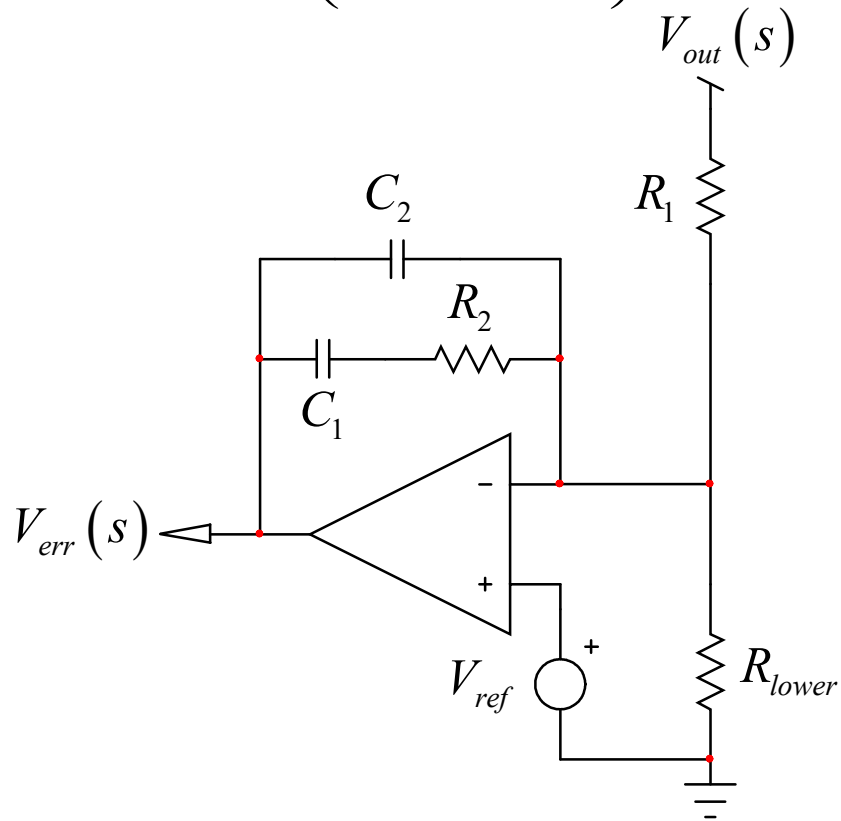
$$f_z = \frac{f_c}{k} \quad f_p = k \cdot f_c$$




$$R_2 = \frac{\frac{1}{|H(f_c)|} \downarrow G_{f_c} R_1 f_p \sqrt{\left(\frac{f_c}{f_p}\right)^2 + 1}}{f_p - f_z \sqrt{\left(\frac{f_z}{f_c}\right)^2 + 1}} = 34.3 \text{ k}\Omega$$

$$C_1 = \frac{1}{2\pi f_z R_2} = 5.4 \text{ nF}$$

$$C_2 = \frac{C_1}{2\pi f_p C_1 R_2 - 1} = 343.7 \text{ pF}$$

Verify Crossover and Phase Margin

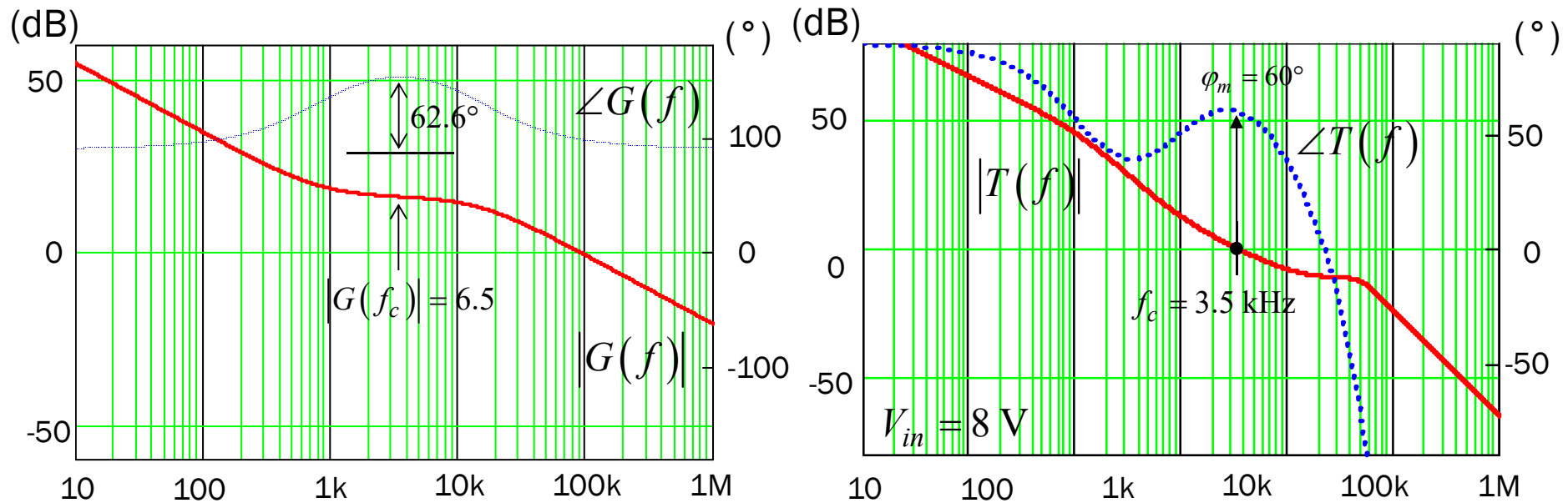- Plot the loop gain once compensator is designed



- Mathcad[®] can read the loop gain plot and extract data

$$f_{cc} := \text{root}\left(\left|T_{OL}(i \cdot 2\pi \cdot f_c)\right| - 1, f_c\right) \quad PM_{f_c} := \arg(T_{OL}(i \cdot 2\pi \cdot f_c)) = 60^\circ \quad f_g := \text{root}\left(\arg(T_{OL}(i \cdot 2\pi \cdot f_g)), f_g\right)$$


$$f_{cc} = 3.5 \cdot \text{kHz} \quad -20 \cdot \log\left(\left|T_{OL}(i \cdot 2\pi \cdot f_g)\right|, 10\right) = 10.53891 \quad f_g = 22.30226 \text{kHz} \quad f(\pi)$$

Crossover

Gain margin

Check Transient Response

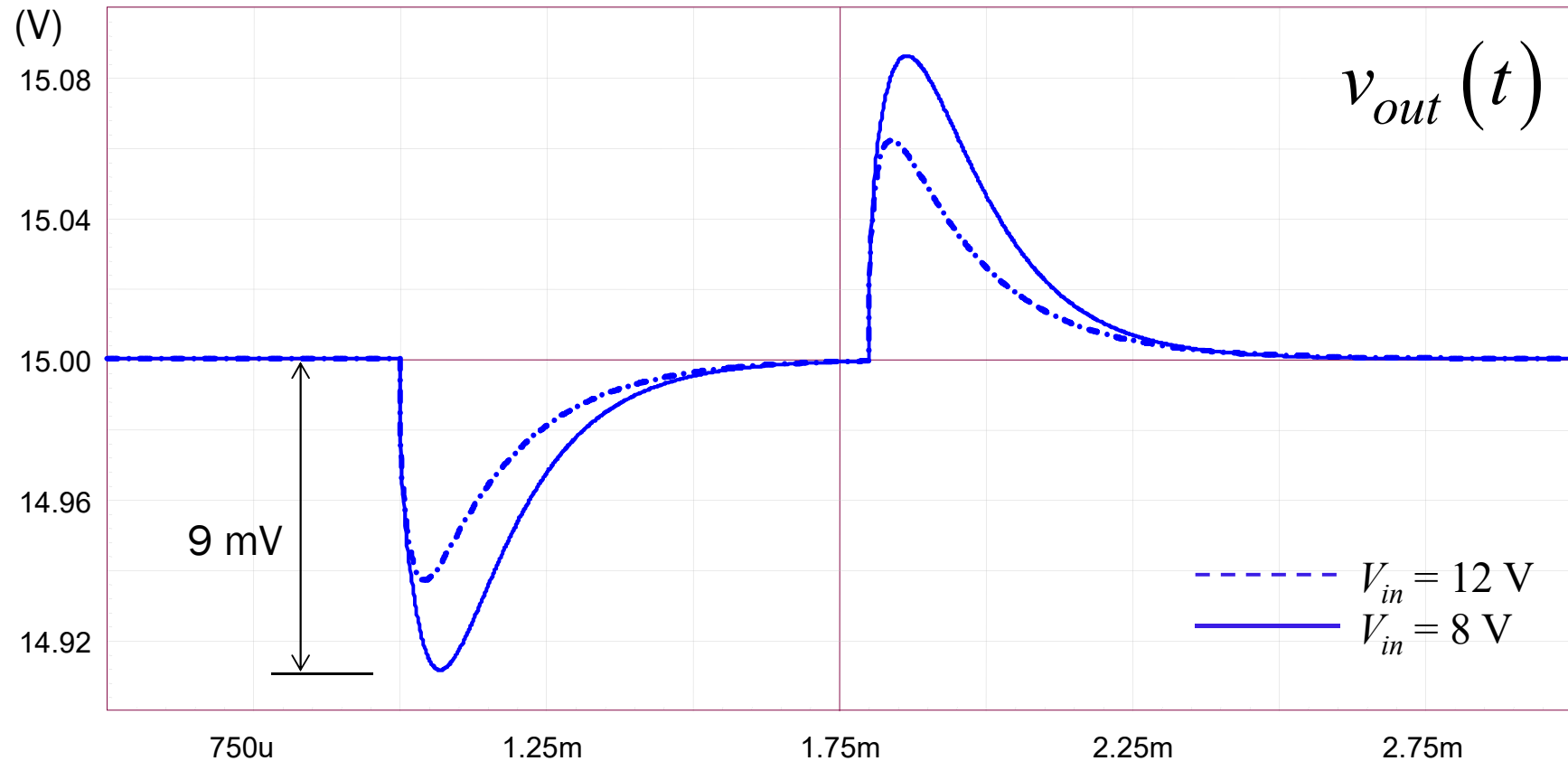
- The output current is varied from 0.5 to 1 A with a 1-A/ μ s slope



- Better response at high line with a slightly higher crossover

Stabilizing a Current-Mode Flyback Converter

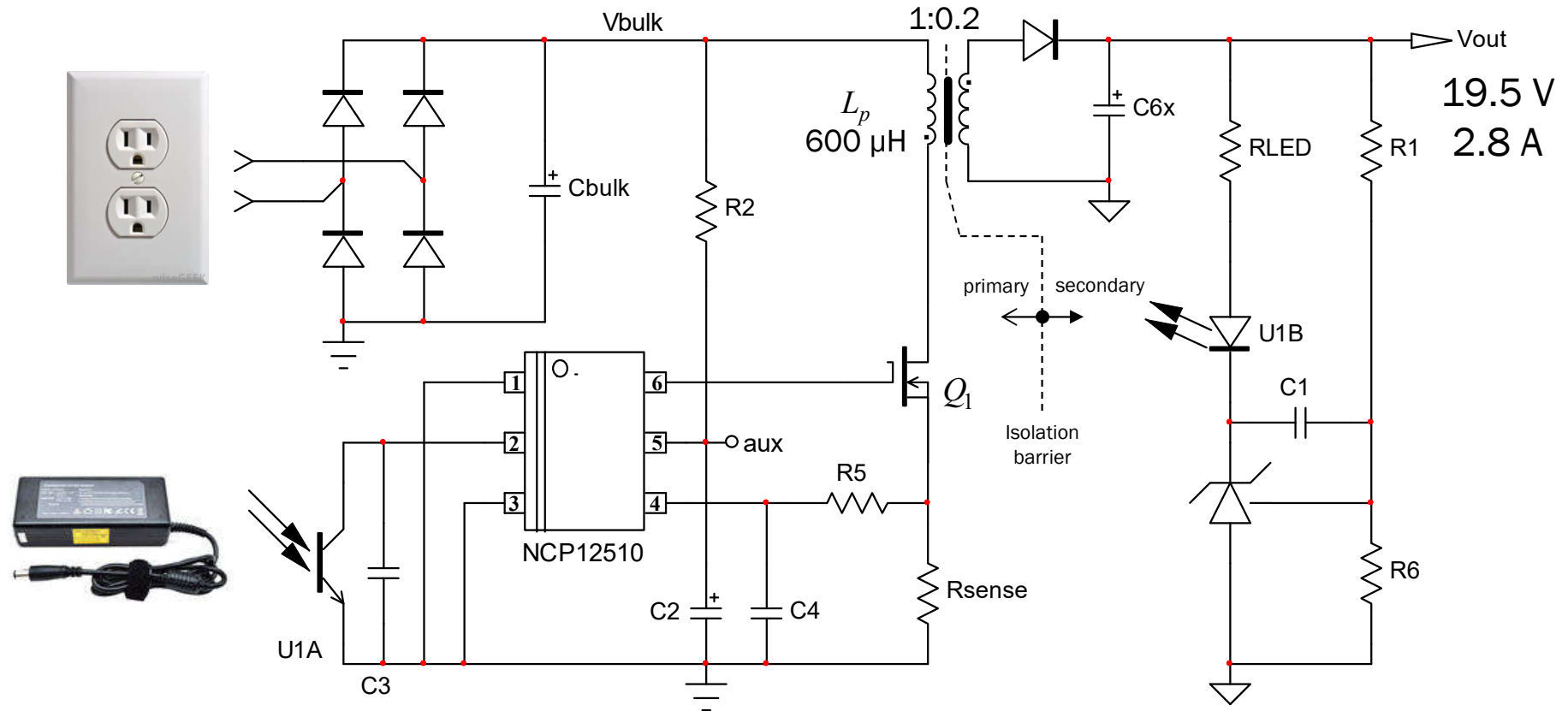
- This is an isolated power converter requiring an optocoupler



- The input voltage is the rectified mains and exhibits ripple

Check the True Minimum Input Voltage

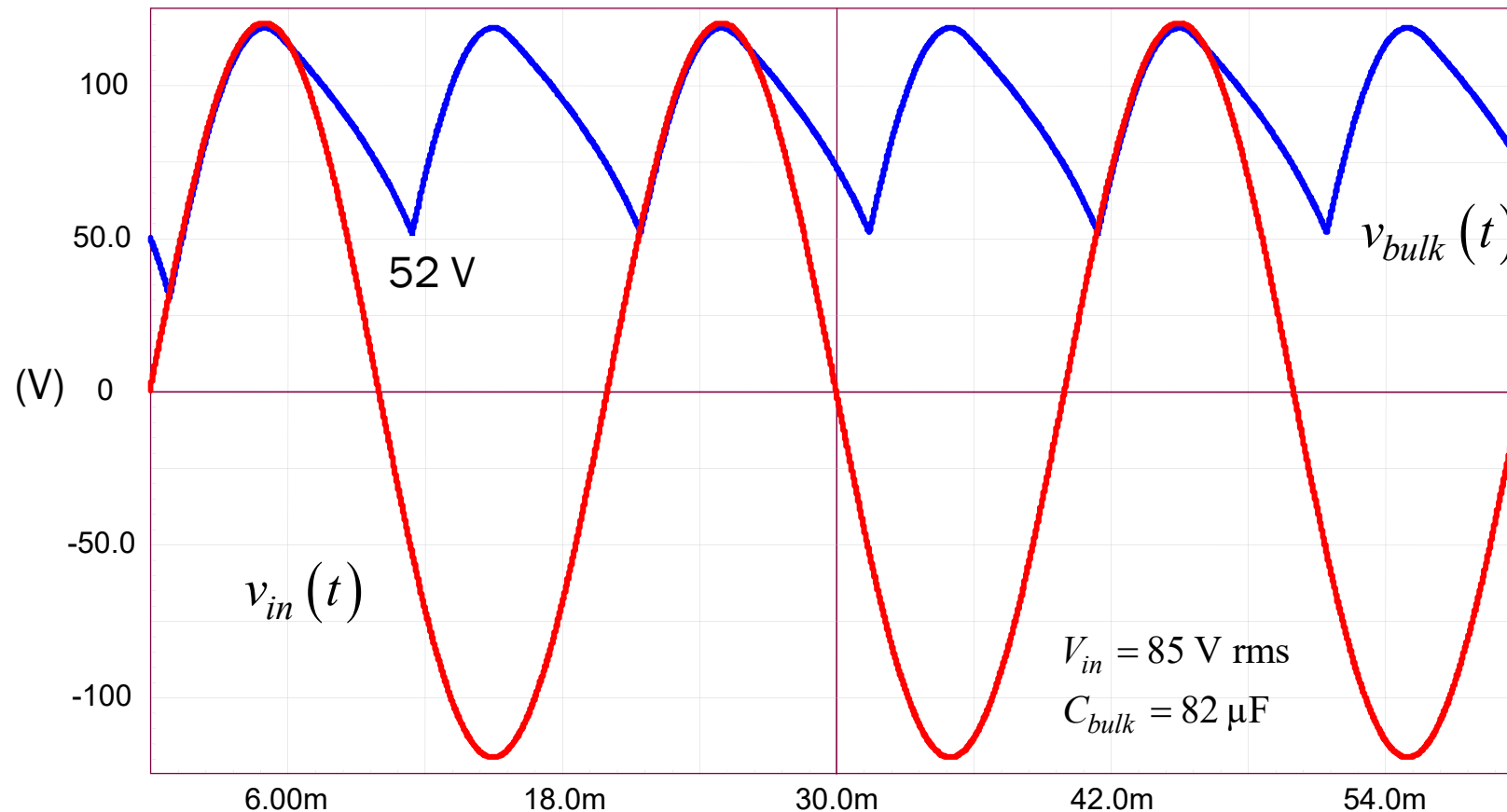- The rectified mains dips to a valley voltage at maximum P_{out}



- The power delivery and stability must be ensured down to 52 V

Evaluate the Compensation Ramp

□ This is a CCM-operated current-mode circuit: check the poles

$$Q = \frac{1}{\pi(m_c D' - 0.5)} \quad \frac{V_{out}}{V_{in}} = \frac{ND}{1-D} \longrightarrow D = \frac{V_{out}}{V_{out} + NV_{in}} = \frac{19}{19 + 0.2 \times 52} = 83\%$$


□ Damping is necessary!

$$Q = \frac{1}{\pi(m_c D' - 0.5)} = -0.96 \longrightarrow m_c = \frac{\frac{1}{-0.96} + 0.5}{1 - D} = \frac{0.818}{1 - 0.83} \approx 4.9$$

Check IC

D_{max} 

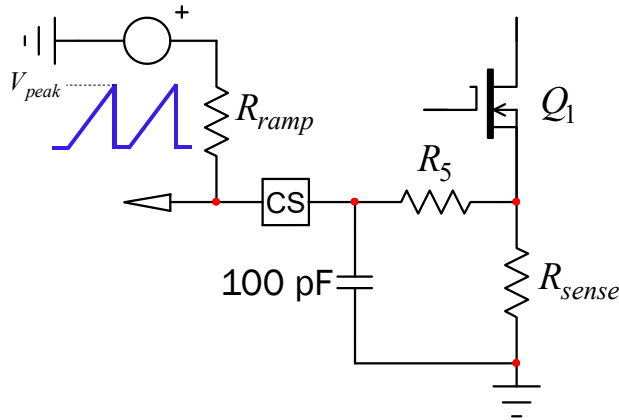□ Adjust series resistance to tune slope compensation level



$$S_{ramp} = \frac{V_{peak}}{D_{max} T_{sw}} = \frac{2.5}{0.8 \times 15\mu} = 208 \text{ mV}/\mu\text{s}$$

$$m_c = 4.9 \longrightarrow S_a = S'_n (m_c - 1) = \frac{V_{in}}{L_p} R_{sense} (m_c - 1)$$


$$S_a = \frac{52}{600\mu} \times 3.9 \times 0.25 = 84.5 \text{ mV}/\mu\text{s}$$

$$R_5 = \frac{S_a}{S_{ramp}} R_{ramp} = \frac{84m}{208m} \times 20k \approx 8 \text{ k}\Omega$$

Will affect maximum peak current!

Power Stage Dynamic Response


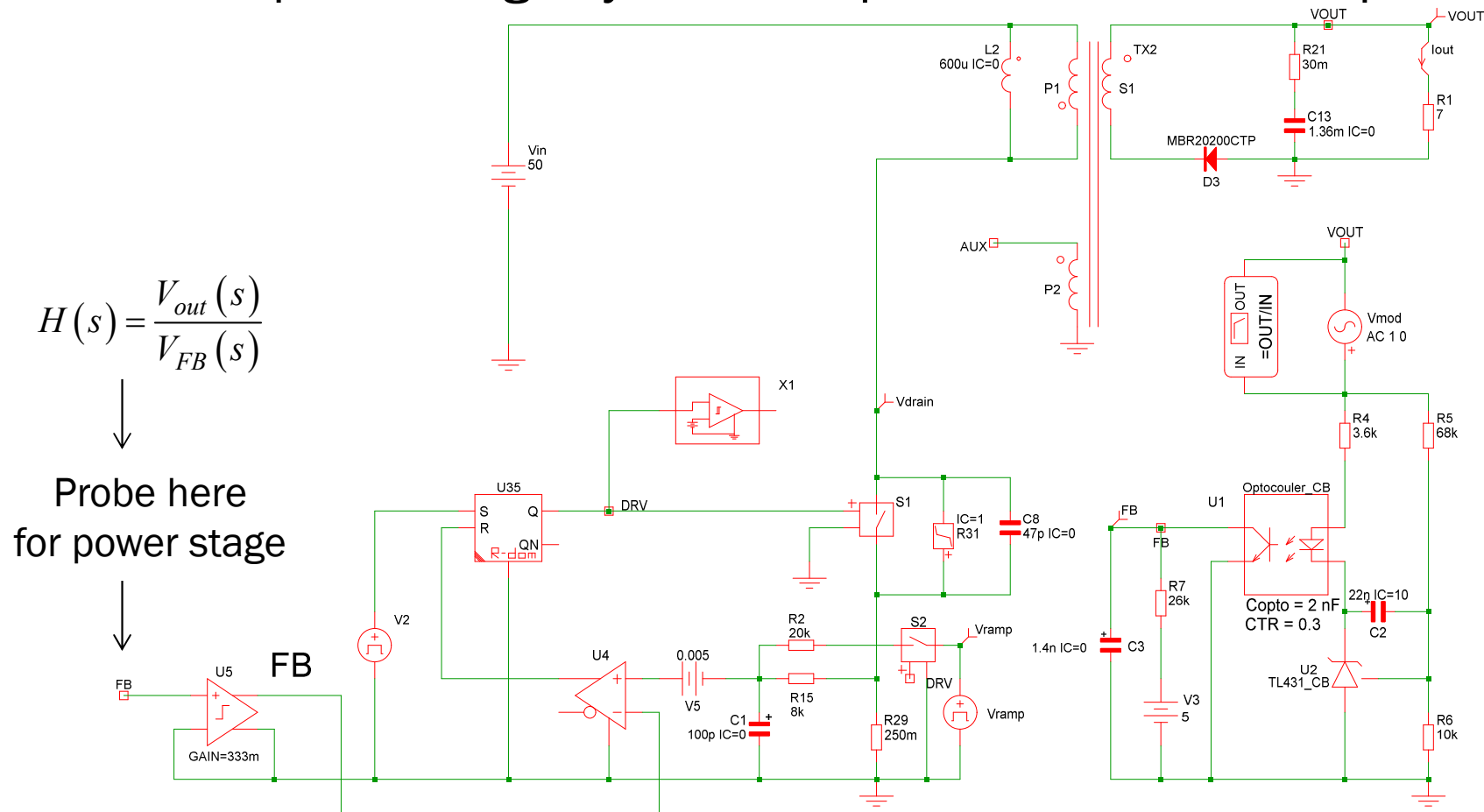
- ❑ Check power stage dynamic response at minimum input



- ❖ Make sure parasitics are well modeled and match reality

Simulation Confirms Complex Poles

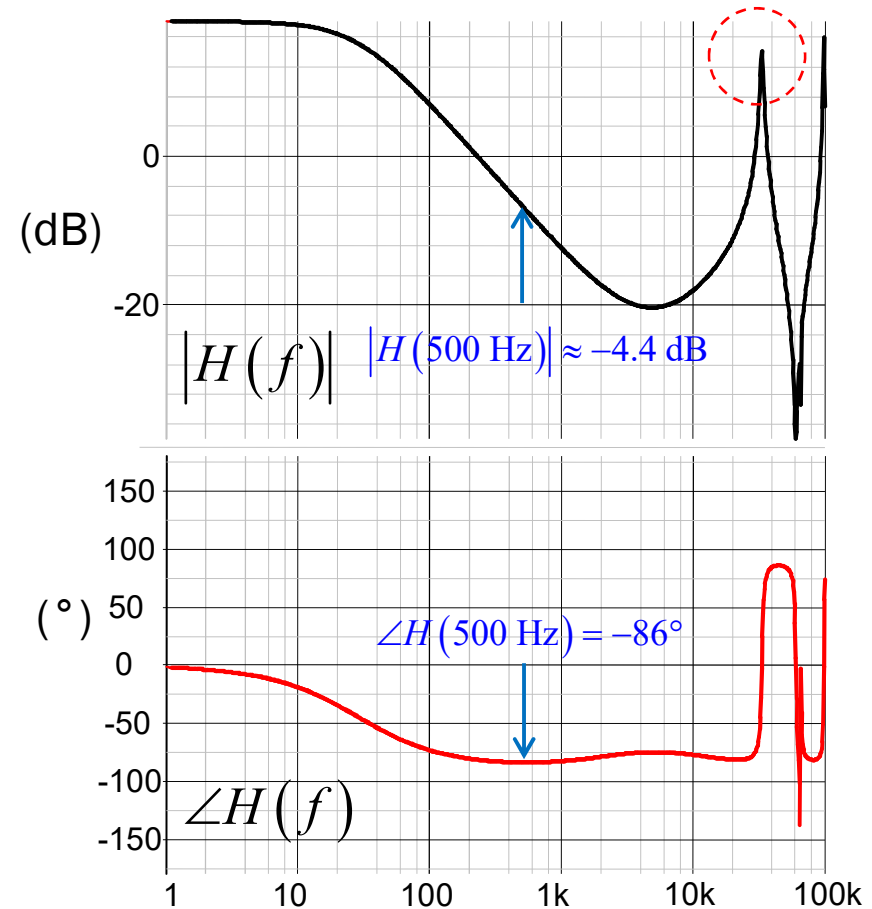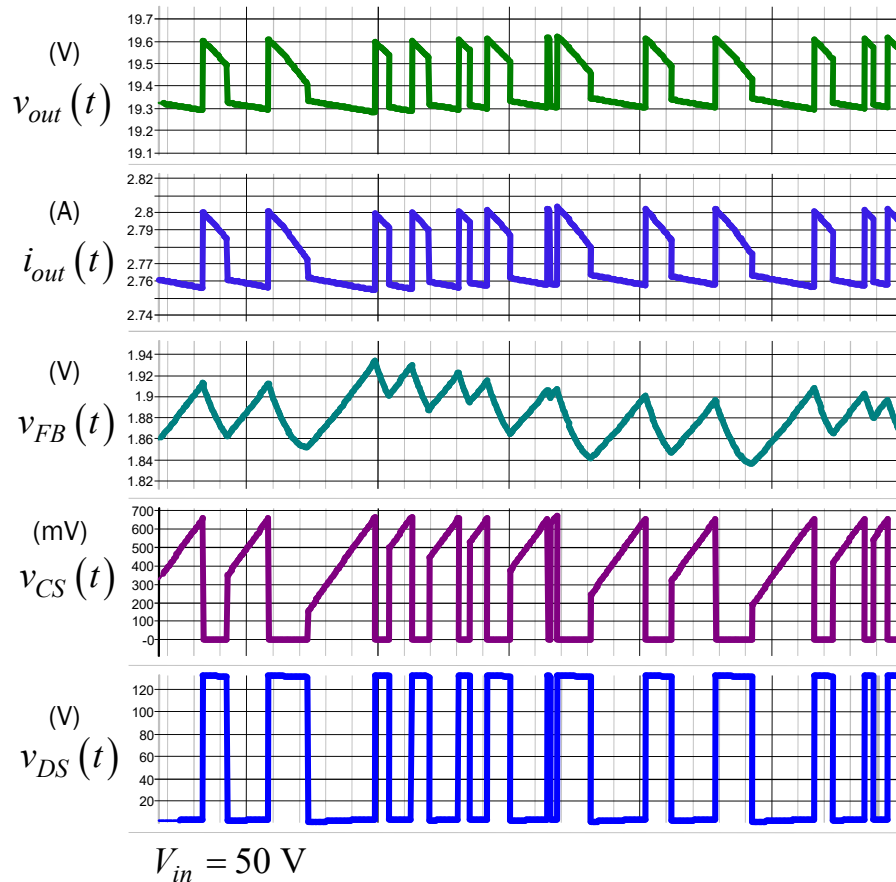
□ Damping is an absolute necessity at the lowest input



□ Simplis[®] cannot find a stable point, a little bit of ramp is needed

Know what Affects the Return Path

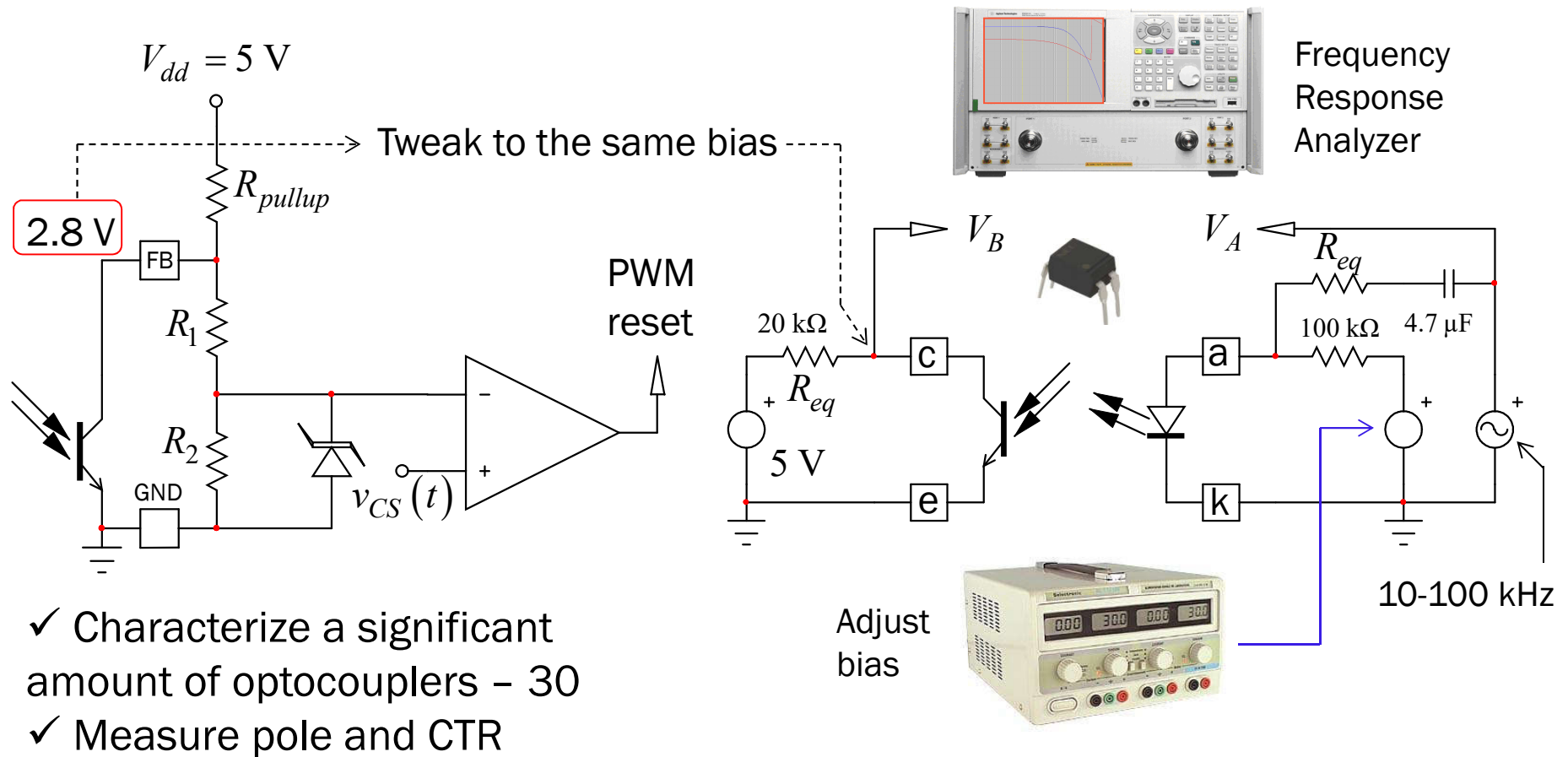
- The optocoupler hosts a low-frequency pole: characterize it
- ❖ Reproduce the controller internals where the opto connects



- ✓ Characterize a significant amount of optocouplers – 30
- ✓ Measure pole and CTR

A Simple Oscilloscope is Enough

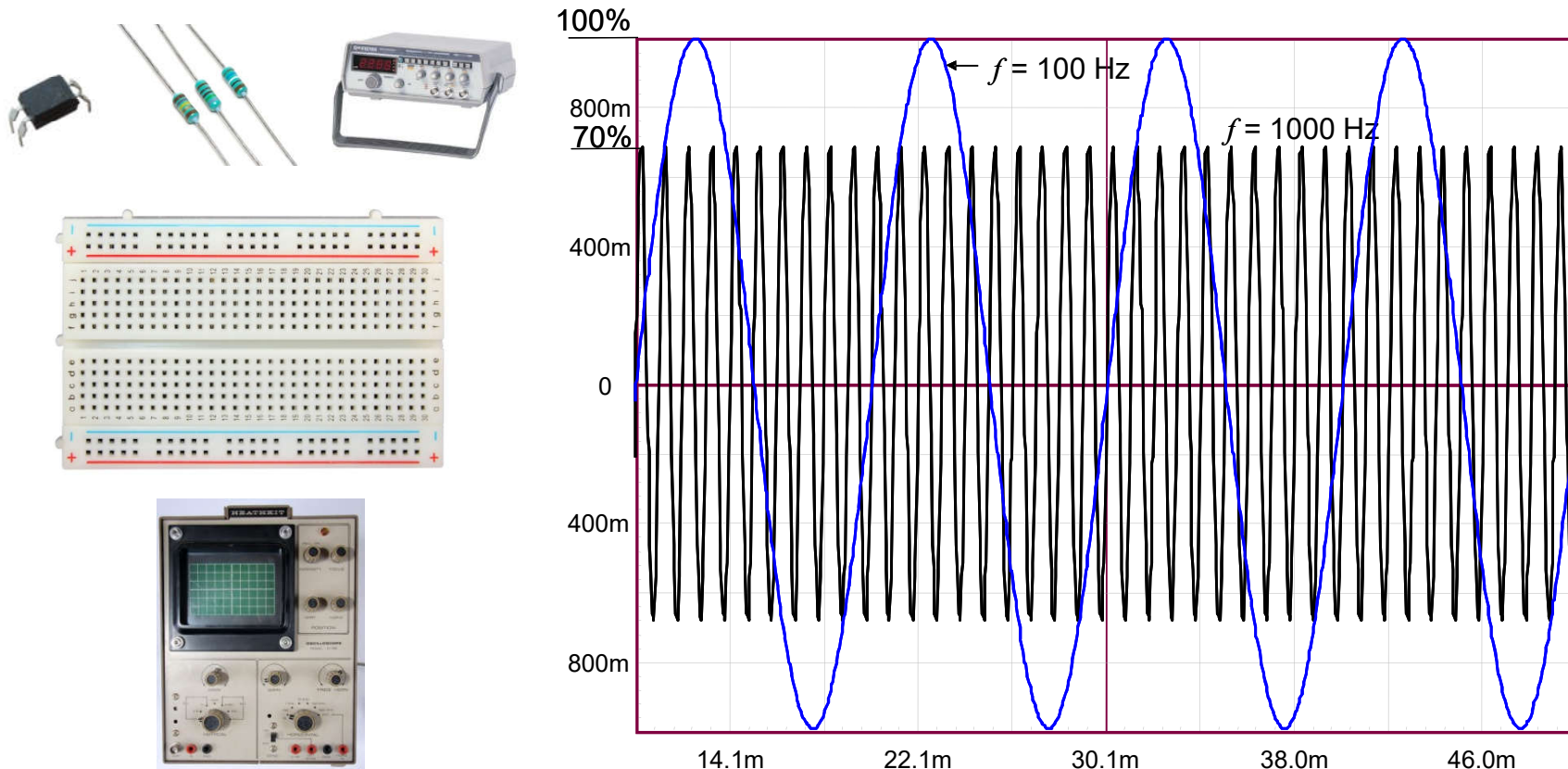
- Pole extraction can also be done with an oscilloscope



- 10 divisions is the low-frequency reference, 7 divisions is f_p

The Collector Resistance Affect the Pole

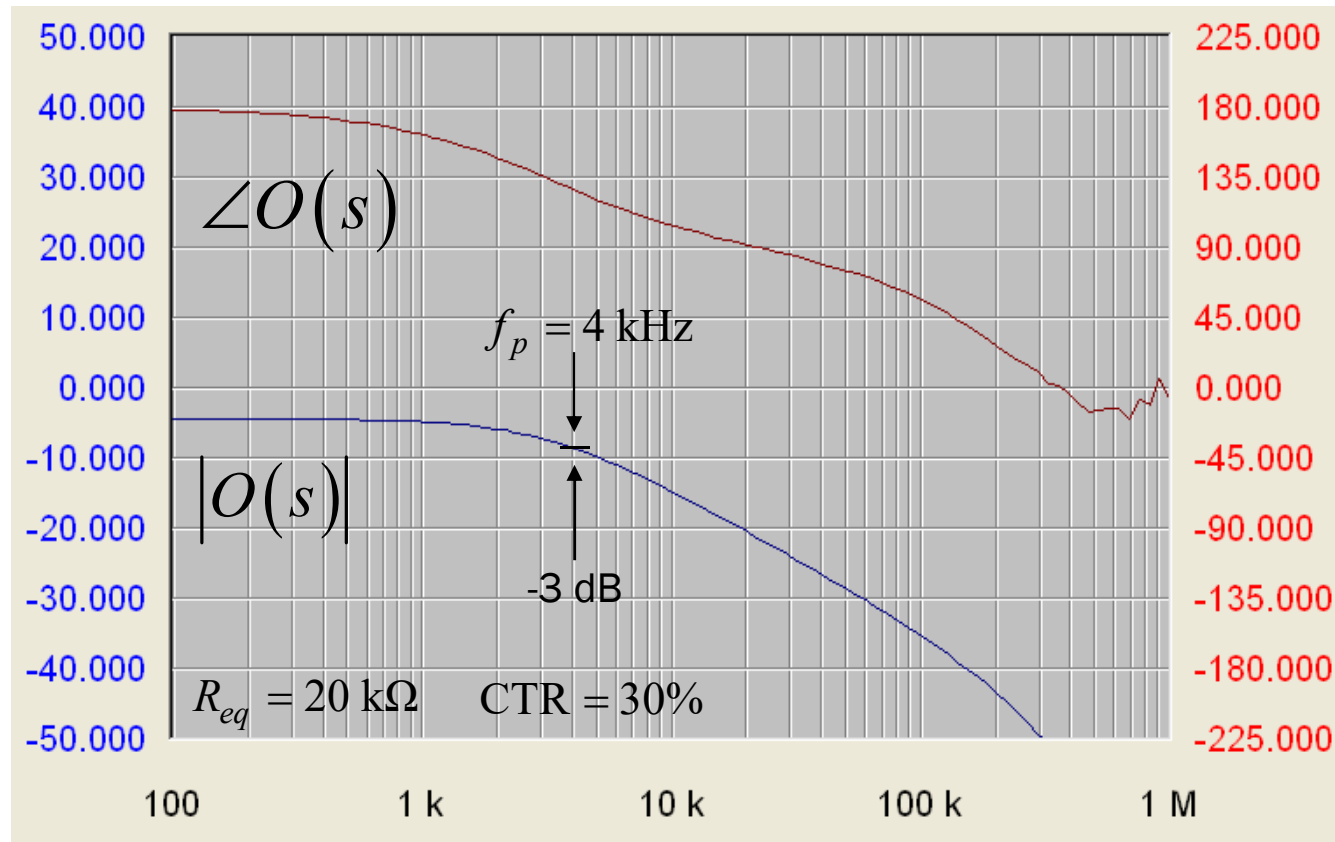- A low value pull-up resistor would offer a better bandwidth...



$$f_p = 4 \text{ kHz}$$

↓ R_{eq}
20 k Ω


$$C_{opto} \approx 2 \text{ nF}$$

...but would affect the standby power at $P_{out} = 0$

SFH615A-2

Build a Compensator with TL431

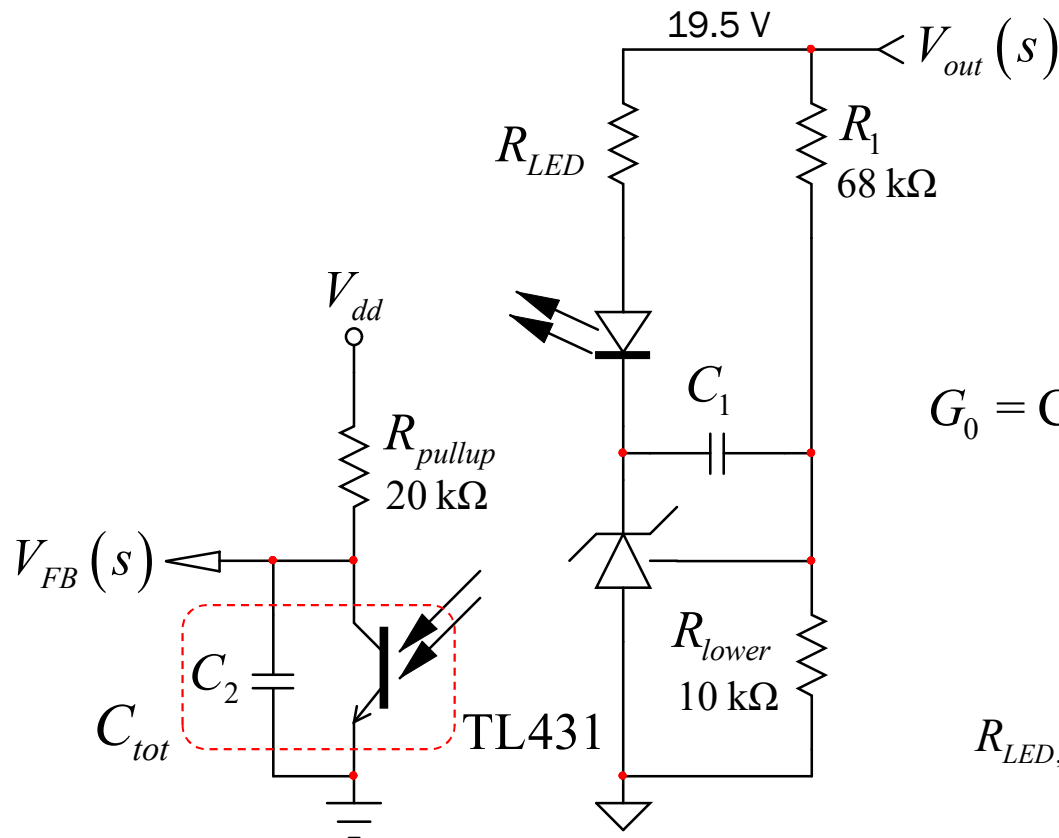- ❑ The TL431 requires a single capacitor for a type-2 response



$$G(s) = -G_0 \frac{1 + \frac{\omega_z}{s}}{1 + \frac{s}{\omega_p}}$$

$$G_0 = \text{CTR} \frac{R_{\text{pullup}}}{R_{\text{LED}}} \quad \omega_z = \frac{1}{R_1 C_1} \quad \omega_p = \frac{1}{R_{\text{pullup}} C_{\text{tot}}}$$

⚠ check bias!

$$R_{\text{LED,max}} \leq \frac{V_{\text{out}} - V_f - V_{\text{TL431,min}}}{V_{\text{dd}} - V_{\text{CE,sat}}} R_{\text{pullup}} \text{CTR}_{\text{min}}$$

- ❑ The fast lane clamps down on the minimum gain

<http://cbasso.pagesperso-orange.fr/Downloads/PPTs/Chris%20Basso%20APEC%20seminar%202011.pdf>

Place Poles and Zeros to Boost the Phase

- Determine the necessary boost for a phase margin of 70°

$$\text{boost} = \varphi_m - \angle H(f_c) - 90^\circ = 66^\circ$$

- k factor is a good tool for stabilizing current mode converters

$$k = \tan\left(\frac{\text{boost}}{2} + \frac{\pi}{4}\right) = 4.7 \quad f_z = \frac{f_c}{k} \quad f_p = k \cdot f_c$$

- ❖ Maximum crossover depends on worst-case RHPZ at 50 V:

$$f_{z_2} = \frac{(1-D)^2 R_{load}}{2\pi D L_p N^2} \approx 1.6 \text{ kHz} \rightarrow f_c < 0.3 \cdot f_{z_2} \rightarrow f_c = 500 \text{ Hz}$$


- Place the zero and the pole at:

$$f_z = f_c^2 / k = 500^2 / 4.7 \approx 106 \text{ Hz} \quad f_p = k \cdot f_c = 4.7 \times 500 \approx 2.3 \text{ kHz}$$

Adjust Mid-Band Gain to Crossover at f_c

- The mid-band gain depends on the LED series resistance

$$G_0 = \text{CTR} \frac{R_{\text{pullup}}}{R_{\text{LED}}} = 10^{20} \overset{\text{from the mag. graph}}{-G_{f_c}} = 10^{\frac{4.4}{20}} = 1.66$$

$$\Rightarrow R_{\text{LED}} = 3.6 \text{ k}\Omega \xrightarrow{\text{ok}} R_{\text{LED,max}} \leq 20.4 \text{ k}\Omega$$


- Determine the capacitor values



$$C_1 = \frac{1}{2\pi R_1 f_z} = 22 \text{ nF} \quad C_{\text{tot}} = \frac{1}{2\pi R_{\text{pullup}} f_p} = 3.4 \text{ nF} \quad \longrightarrow \quad C_2 = C_{\text{tot}} - C_{\text{opto}} = 1.4 \text{ nF}$$

- C_2 must be located close to the control circuit




Check Individual Response

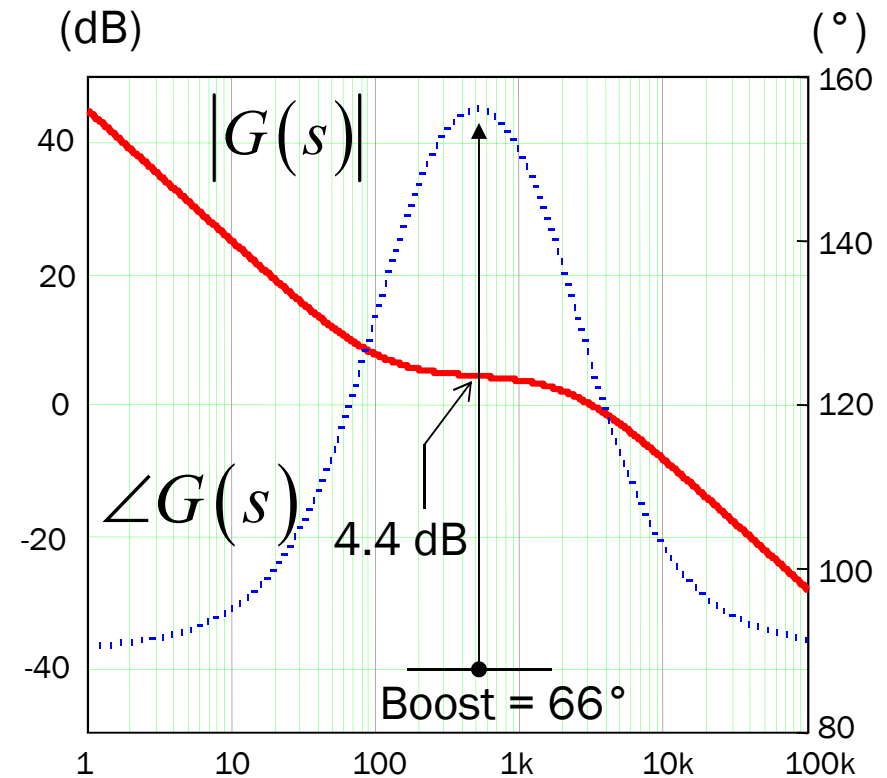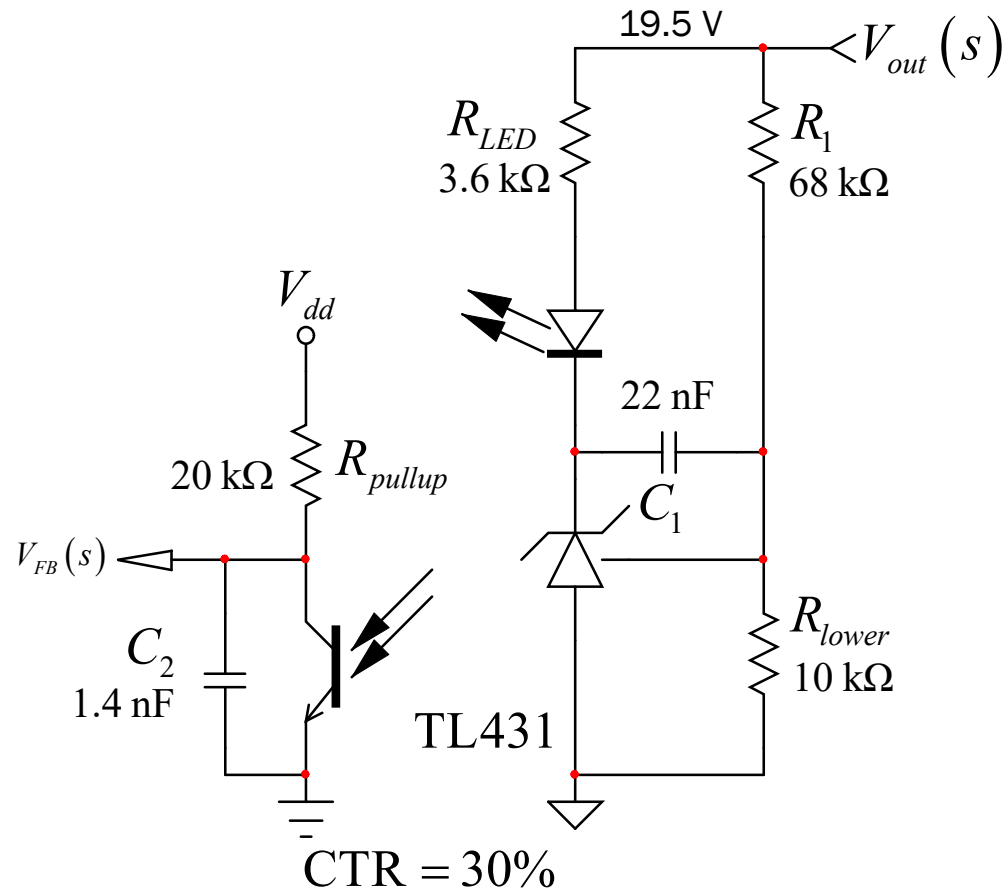- ❑ Use Mathcad® or SPICE to confirm the compensator response



Check Loop Gain T across Line/Load


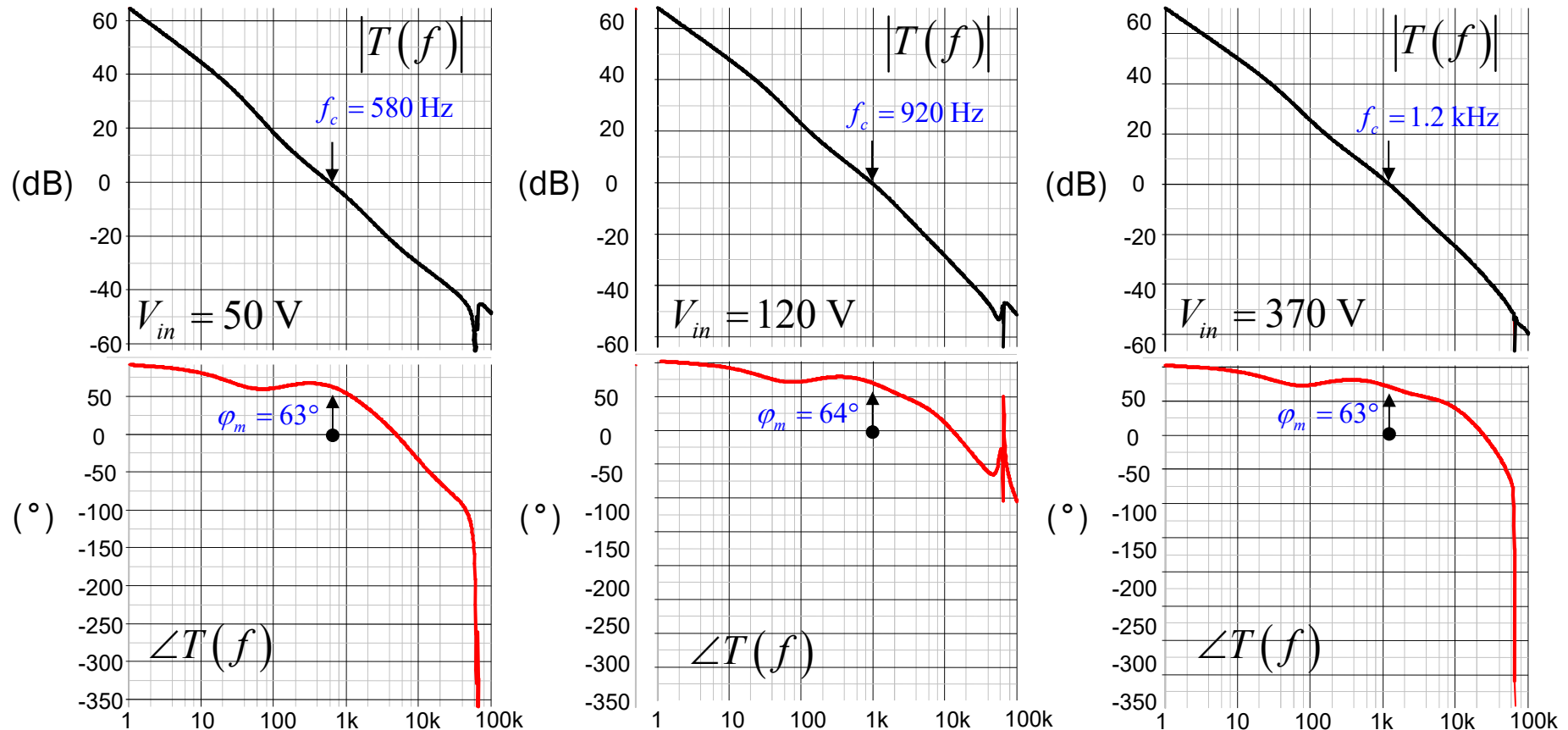
□ The loop is compensated as per specifications



❖ CTR variations will affect crossover, check margins

Load Step on the Output

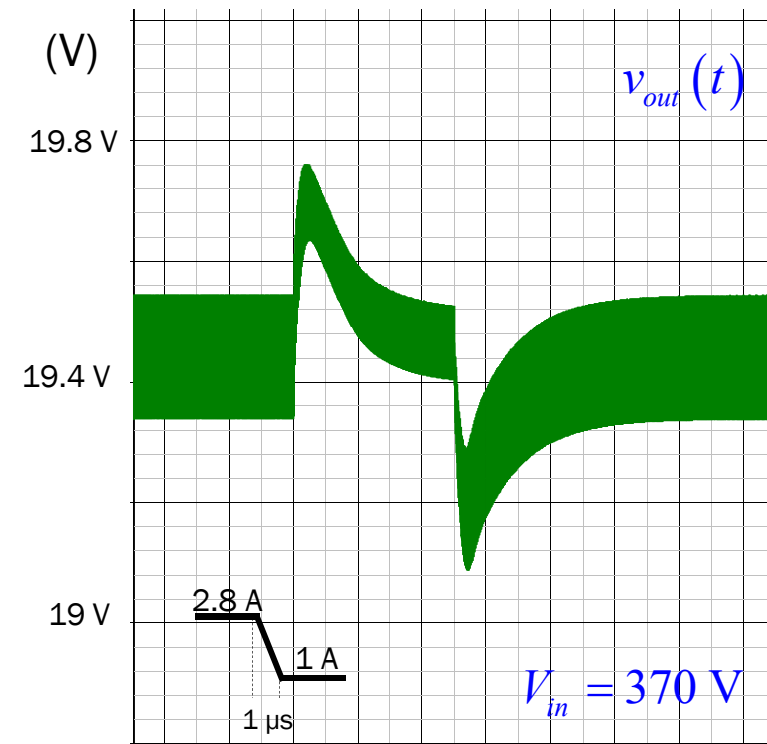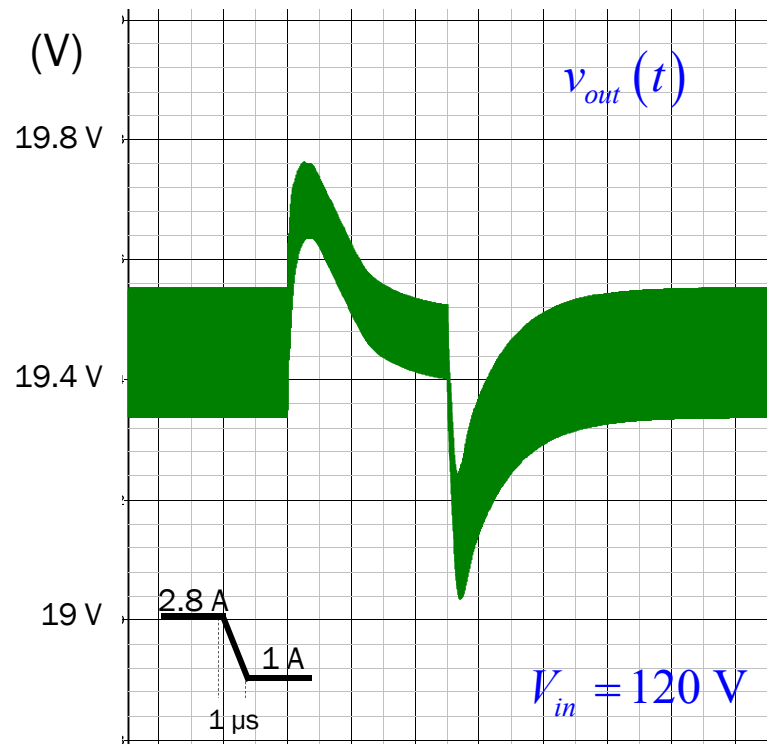- Check transient response at both line extremes



- As converter heats up, L_p goes down. Check at high temp also



Course Agenda

- Blocks in a Switching Converter
- Introduction to Small-Signal Modeling
- Analytical Analysis of an Output Stage
- Simulation Models - Averaged or Switched?
- Crossover Frequency and Phase Margin
- Compensation Strategy
- Experiments on Prototypes**
- Conclusion




Building Prototypes

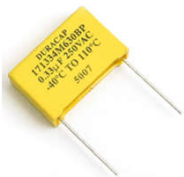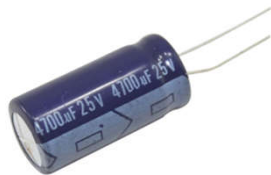- ❑ Bench experiment is a mandatory step
 - ✓ Are the assumptions adopted for the analytical model confirmed?
 - Feed the model back with real measurements, refine simulations
 - ✓ Check the behavior in temperature, particularly stability
- ❑ Characterize the selected components
 - ✓ Are parasitics within the data-sheet specs (r_C and r_L)?
 - ✓ What is the inductor saturation current?



ESR?
 f_0 ?
C at bias?

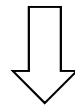Know the components you will later use in a high-volume project.




Characterization



ESR?
 f_0 ?
Capacitance
 I_{sat} ?

Checking the Saturation Current

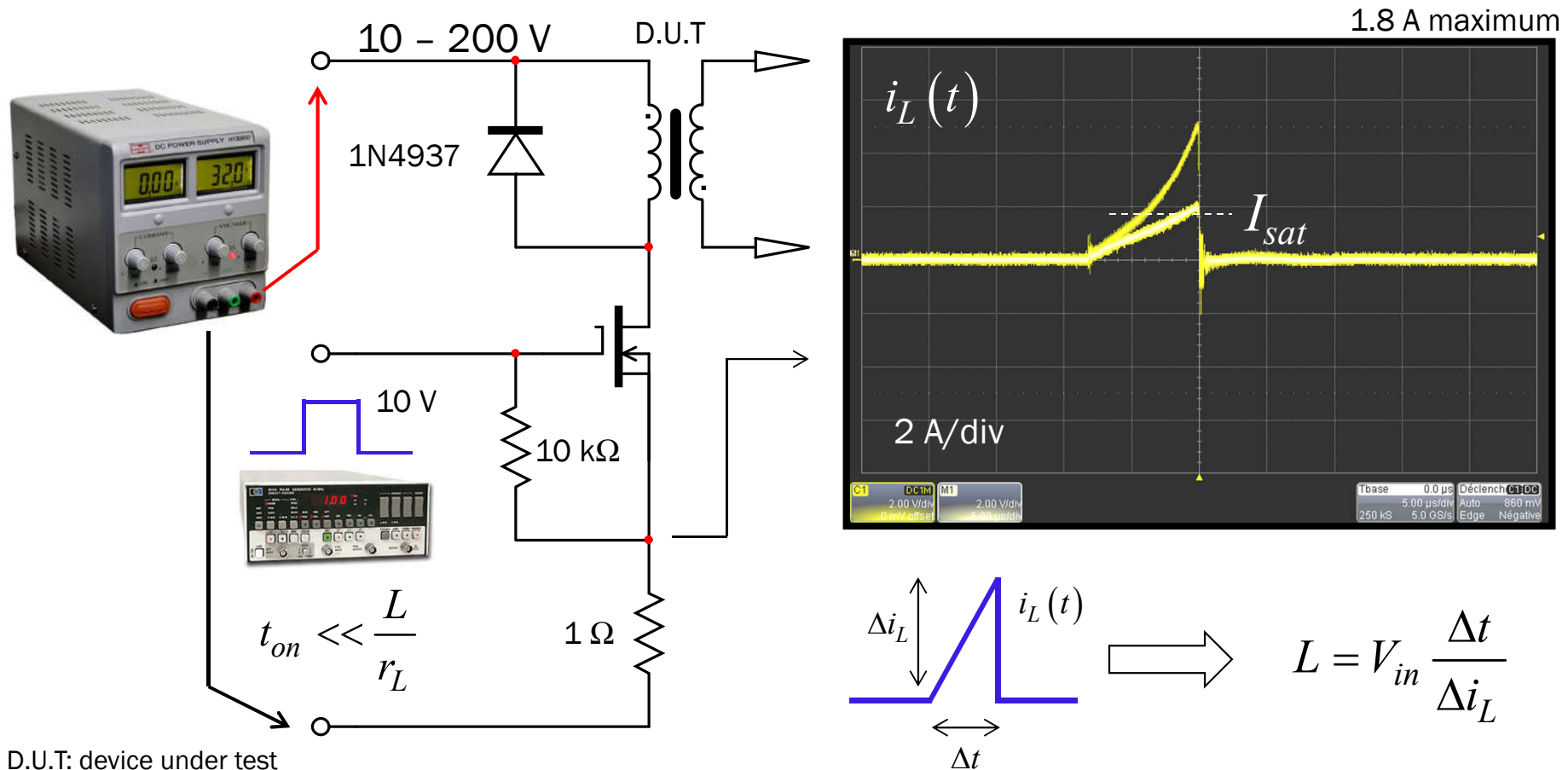
- ❑ Measure the inductance in the linear zone
- ❑ Check the saturation current at the maximum operating temp.



D.U.T: device under test

A Boost Converter in Voltage Mode

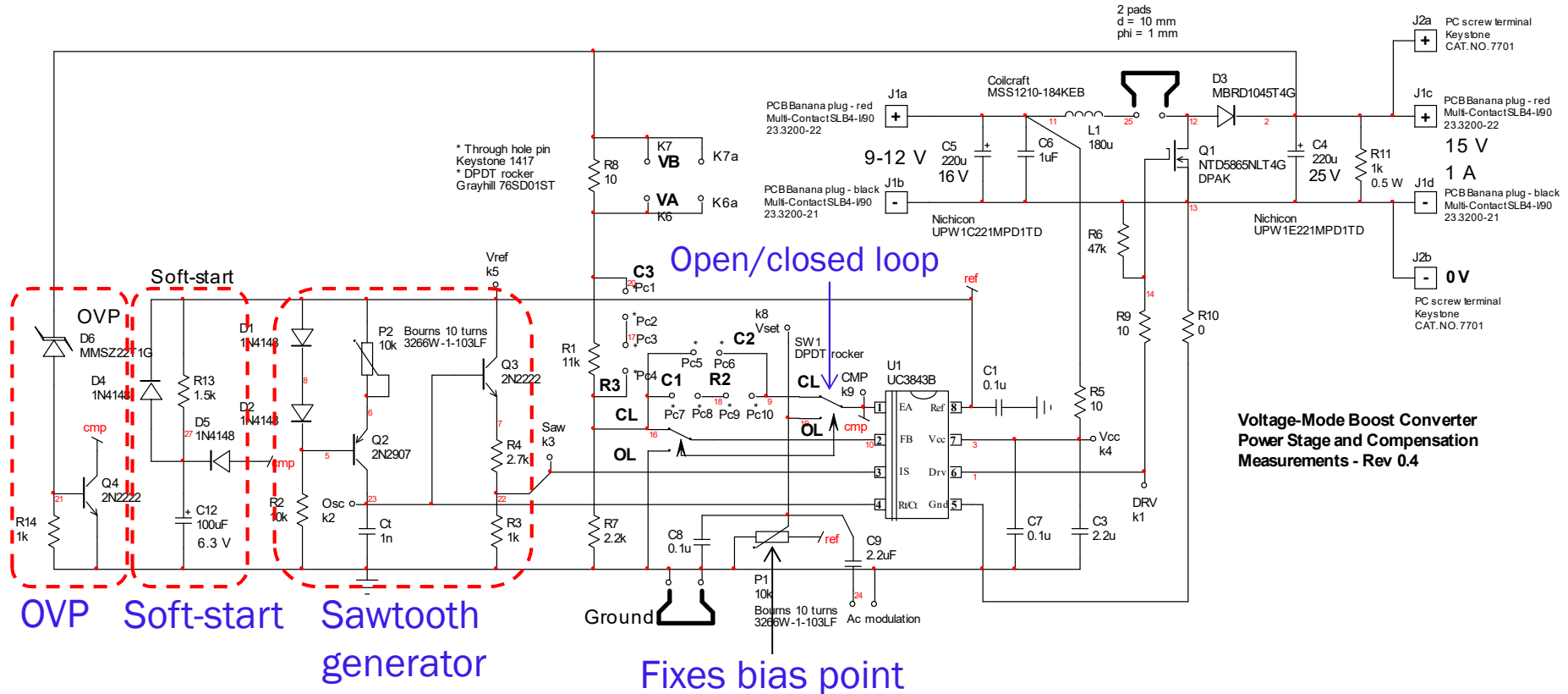
□ A converter using a UC3843 has been assembled



- ❖ The soft-start avoids inductor saturation at power on
- ❖ The OVP circuit protects in no-load operations

A Convenient VM Board to Test

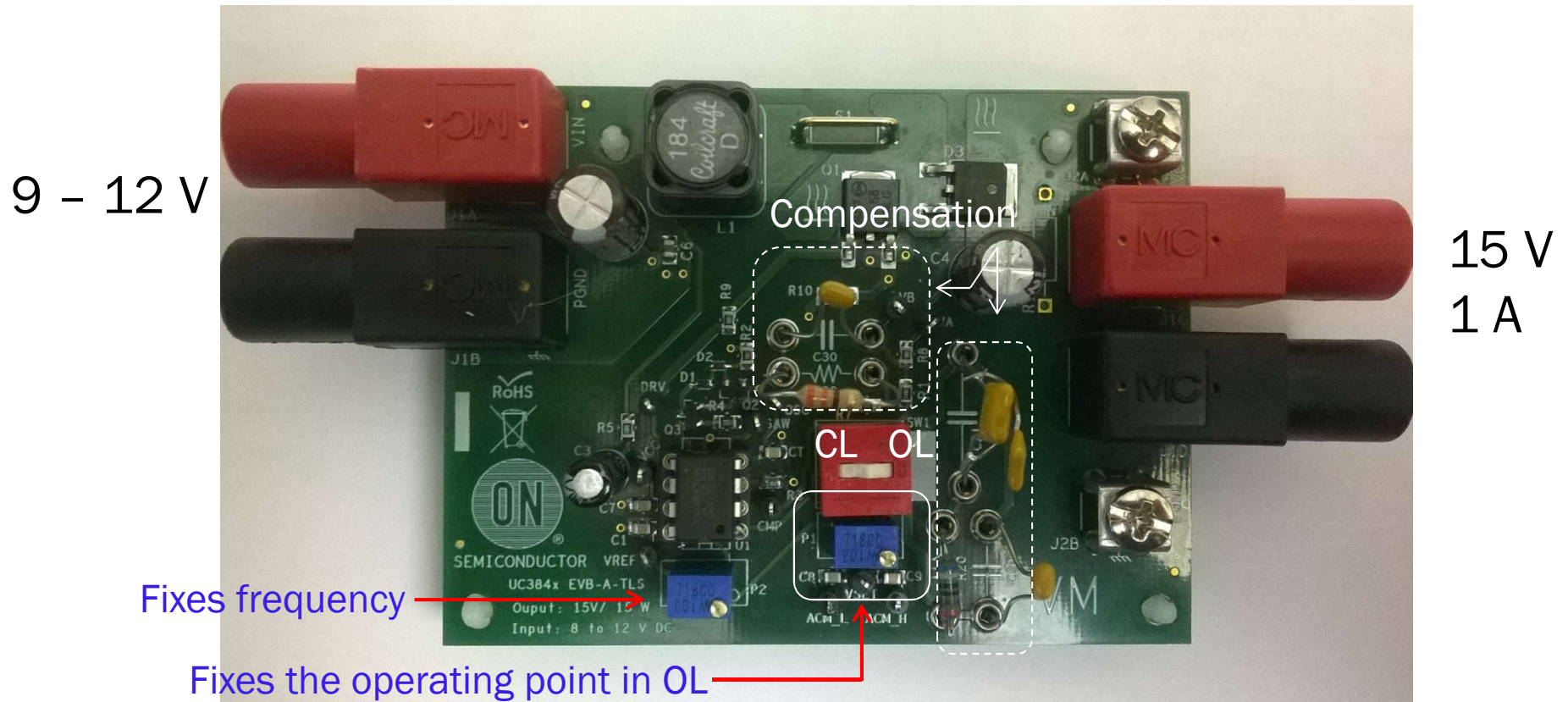
- ❑ The board includes switches to measure open and closed loops



- ❑ It works from 9 to 12 V and delivers 15 V at a 1-A output current

Get the Power Stage Response

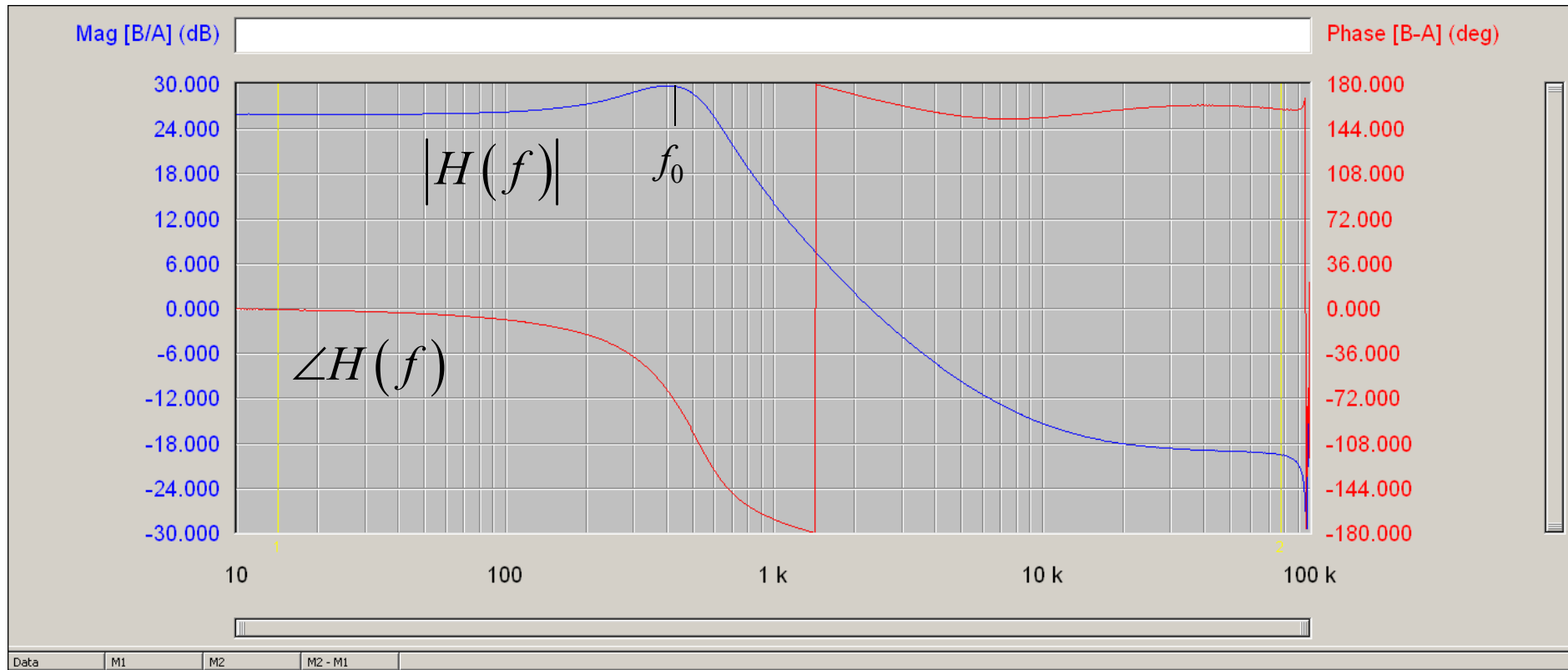
- The first thing is to measure the power stage dynamic response




- Measured for $V_{in} = 9\text{ V}$ and $I_{out} = 1\text{ A}$

The Open-Loop Response is Ringing

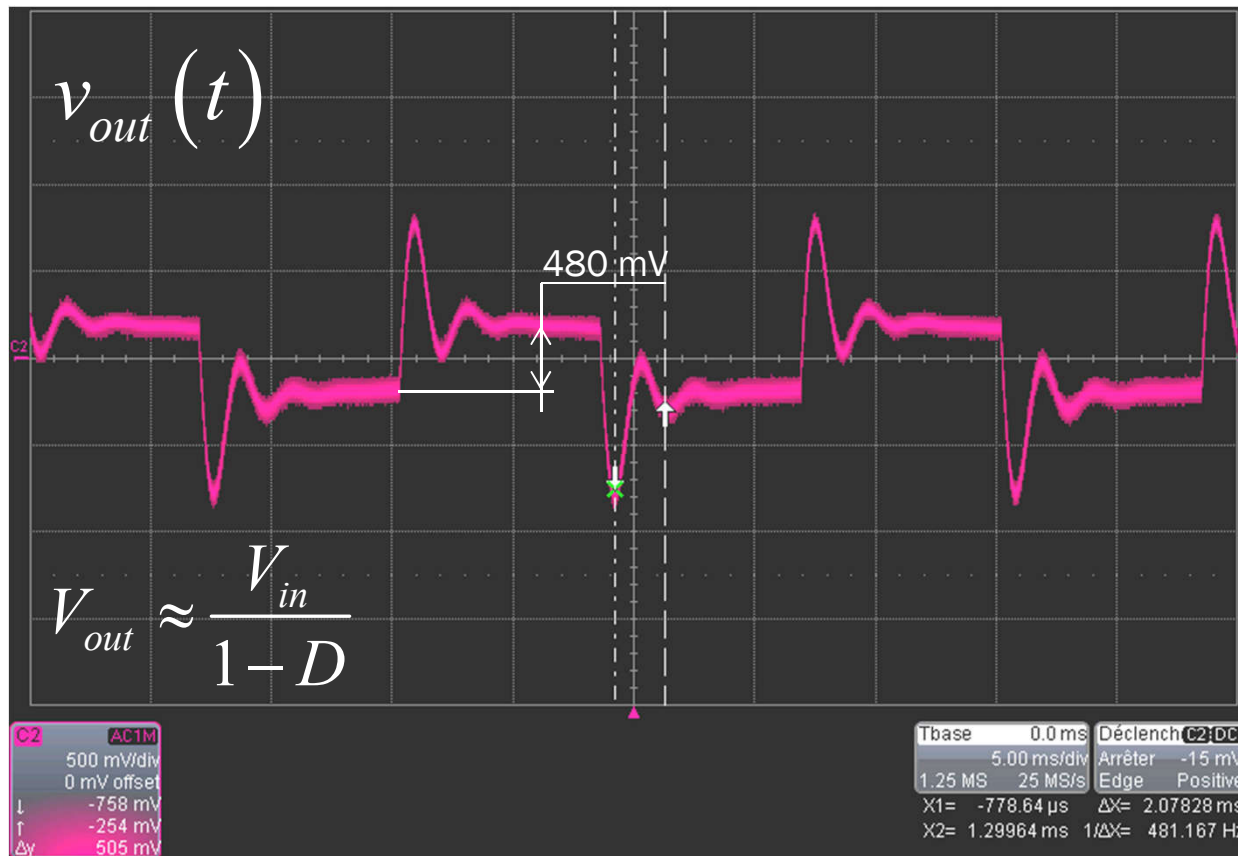- The LC filter rings at the resonant frequency



0.5 A to 1 A
in 1 μ s/A

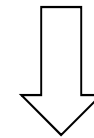


$$R_{out} \approx \frac{0.48}{0.5} = 0.96 \Omega$$


- ❖ This is why you need enough gain at f_0 to damp oscillations

Measure Parasitics on the Board

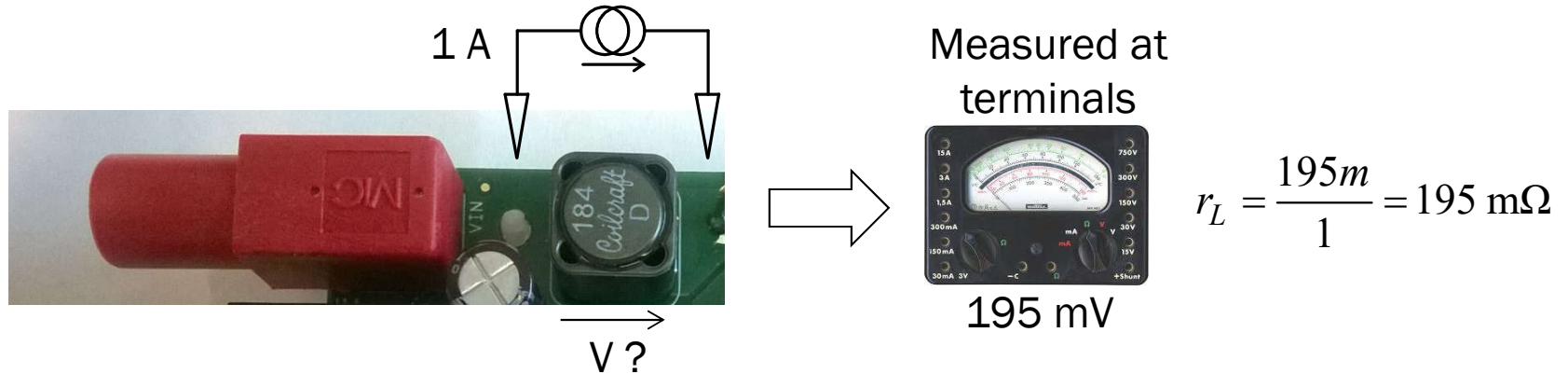- Inject a 1-A current in the inductor, measure the drop




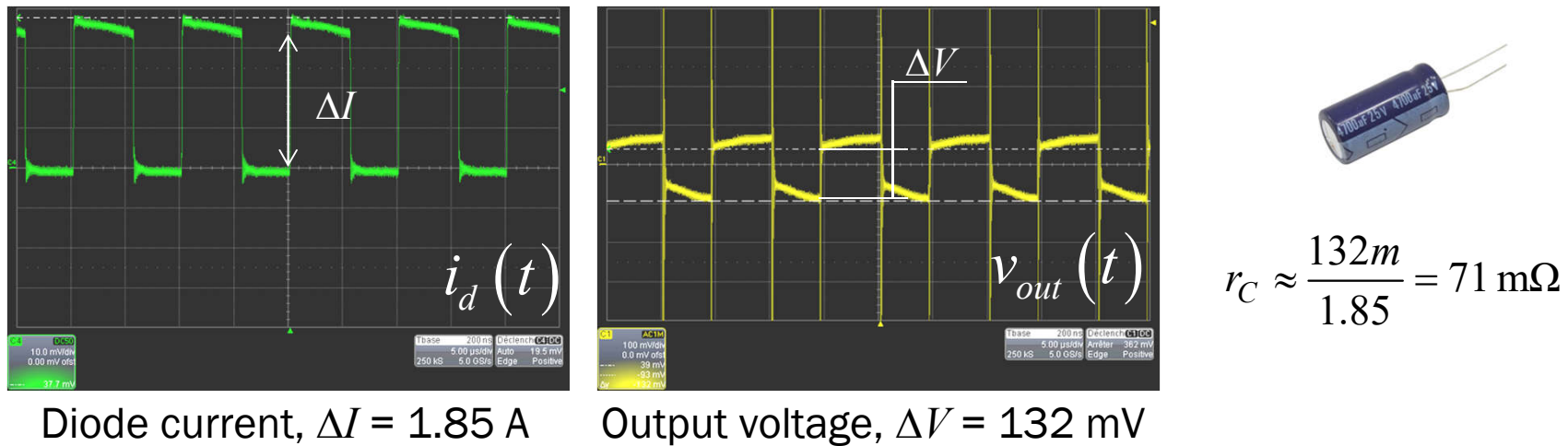- Display the diode current and output voltage in open loop




Build a Model for the Boost Converter

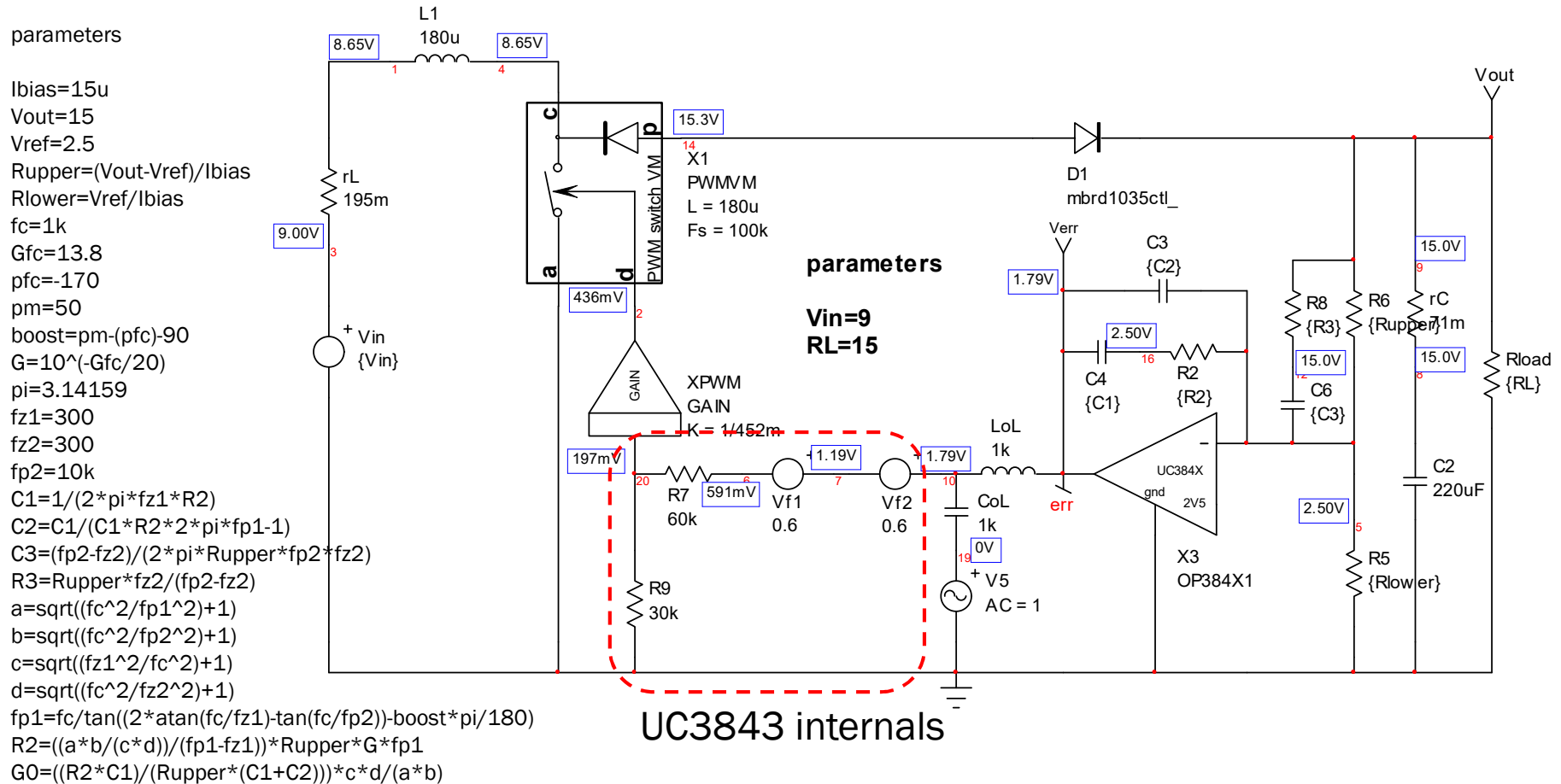□ Analyze the dynamic response with SPICE and compensate



Check the Model Reflects Reality

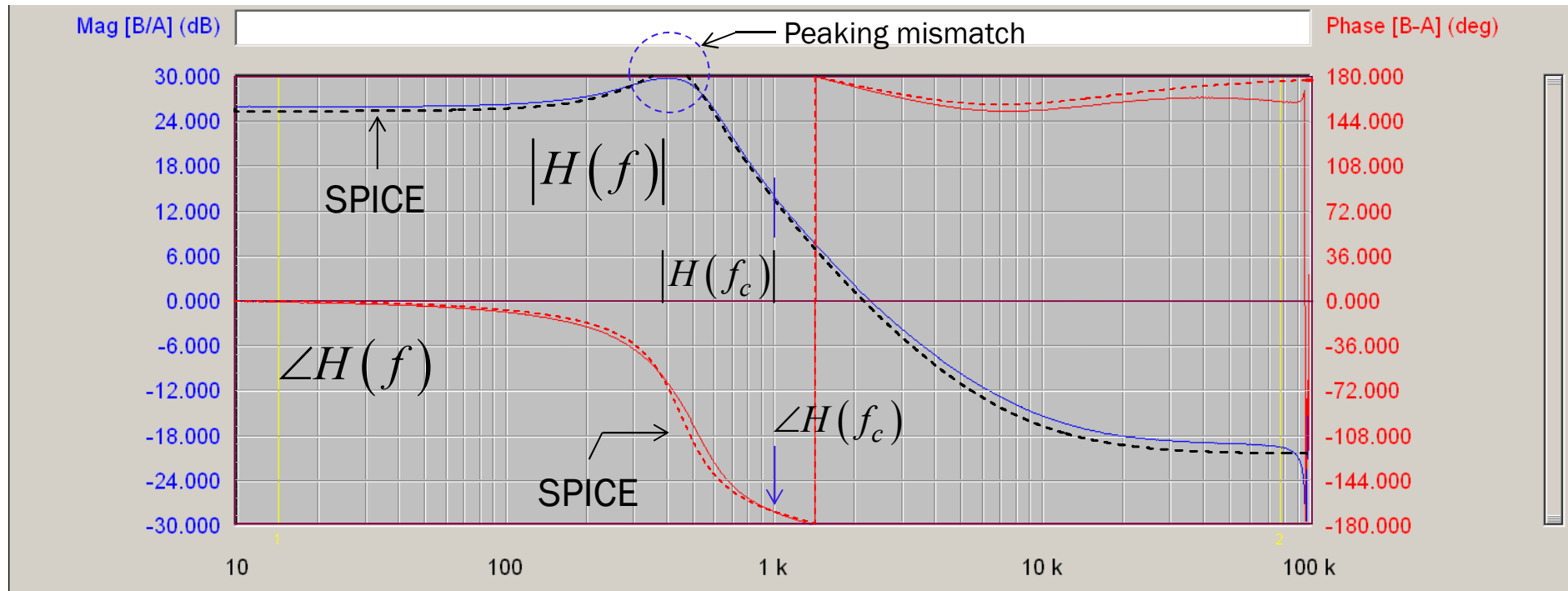- Scale then superimpose SPICE and analyzer responses




- Extract gain and phase values for a 1-kHz crossover goal

$$|H(f_c)| = 13.8 \text{ dB} \quad \angle H(f_c) = -170^\circ$$

Close the Loop and Check Margins


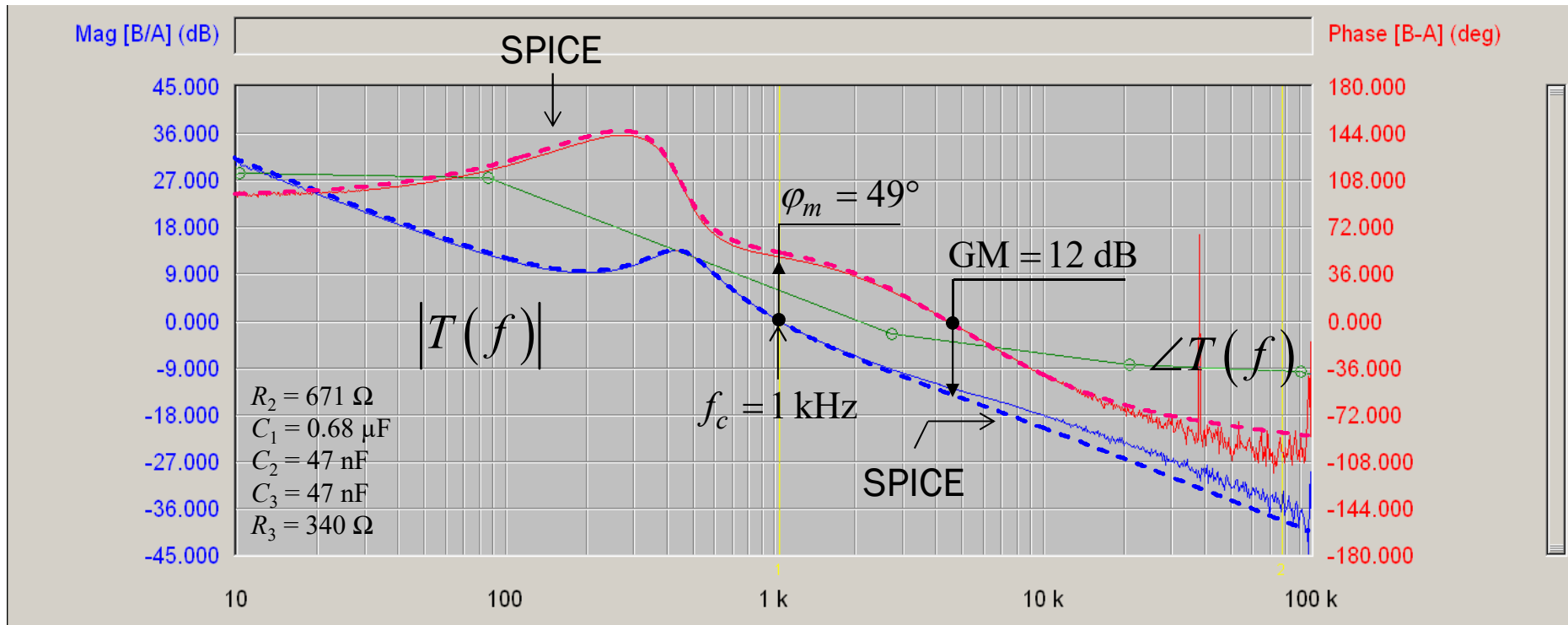
- Apply compensation strategy and plot/measure open-loop gain




$$f_{z_1} = f_{z_2} = 300 \text{ Hz} \quad f_{p_1} = 5.2 \text{ kHz} \quad f_{p_2} = 10 \text{ kHz}$$

Check Response to a Load Step

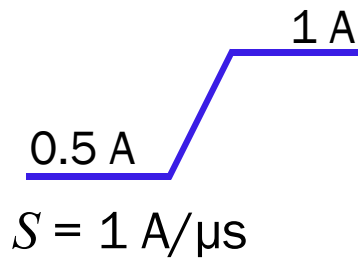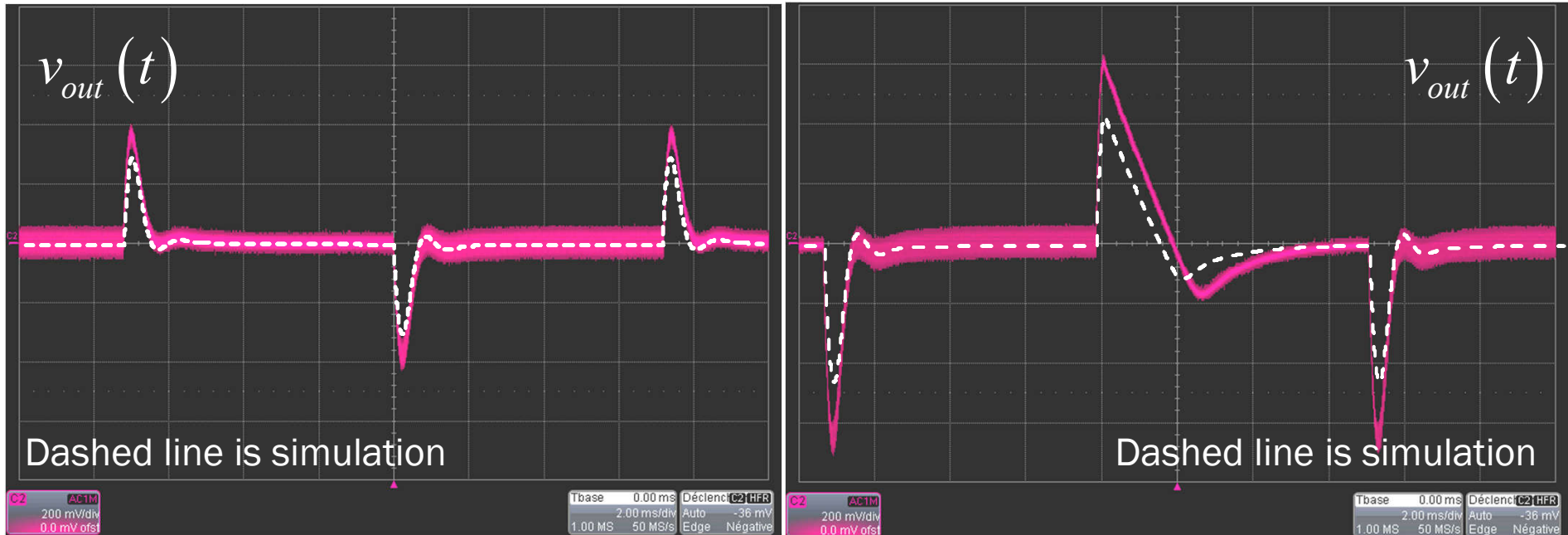- Step the output at different load current spans




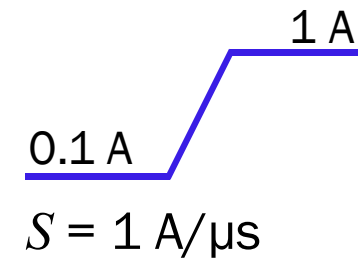SPICE predicts a deviation within acceptable limits even in a highly non-linear mode



Check the Dynamic Response Amplitude

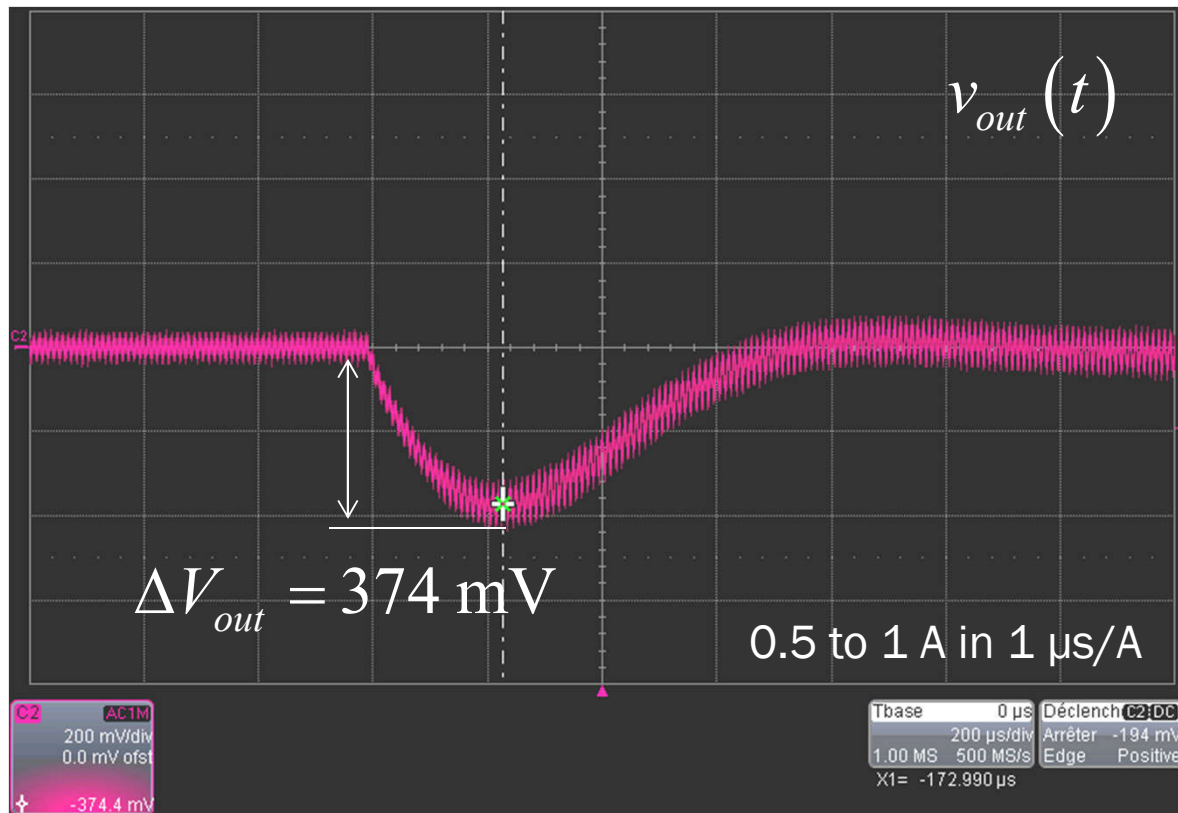- Verify simplified output voltage deviation formula



$$C_{out} = 220 \mu\text{F}$$

$$r_C = 77 \text{ m}\Omega$$

$$\begin{aligned} \Delta I_{out} &= 0.5 \text{ A} \\ f_c &= 1 \text{ kHz} \\ C_{out} &= 220 \mu\text{F} \end{aligned}$$


$$\Delta V_{out} \approx \frac{\Delta I_{out}}{2\pi f_c C_{out}} = 362 \text{ mV}$$

- ❖ The approximated formula works well in this case



A Boost Converter in Current Mode

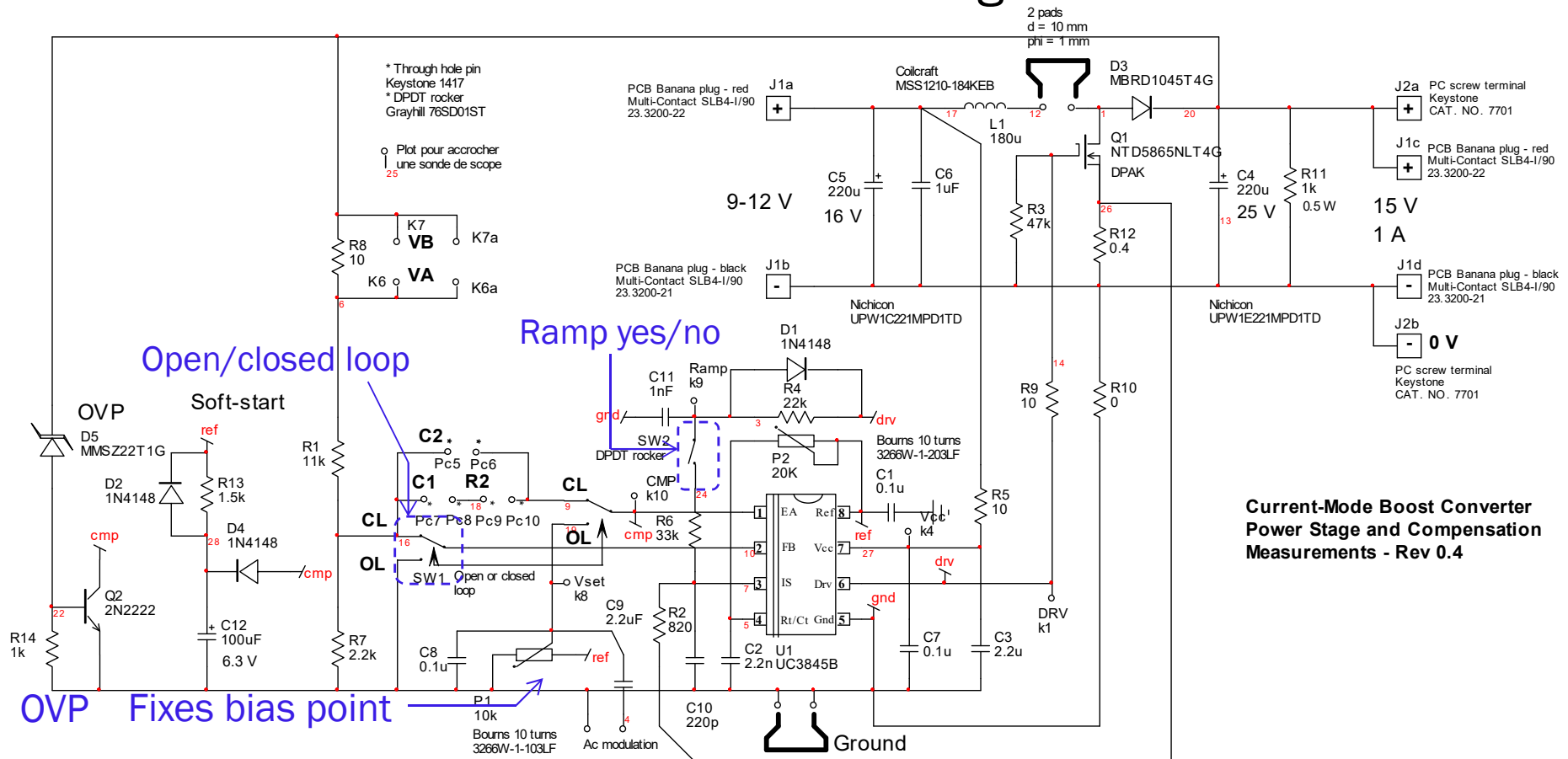
□ The converter still uses a UC3843 configured in current mode



❖ Similar protections as in the voltage-mode case

A Convenient CM Board to Test

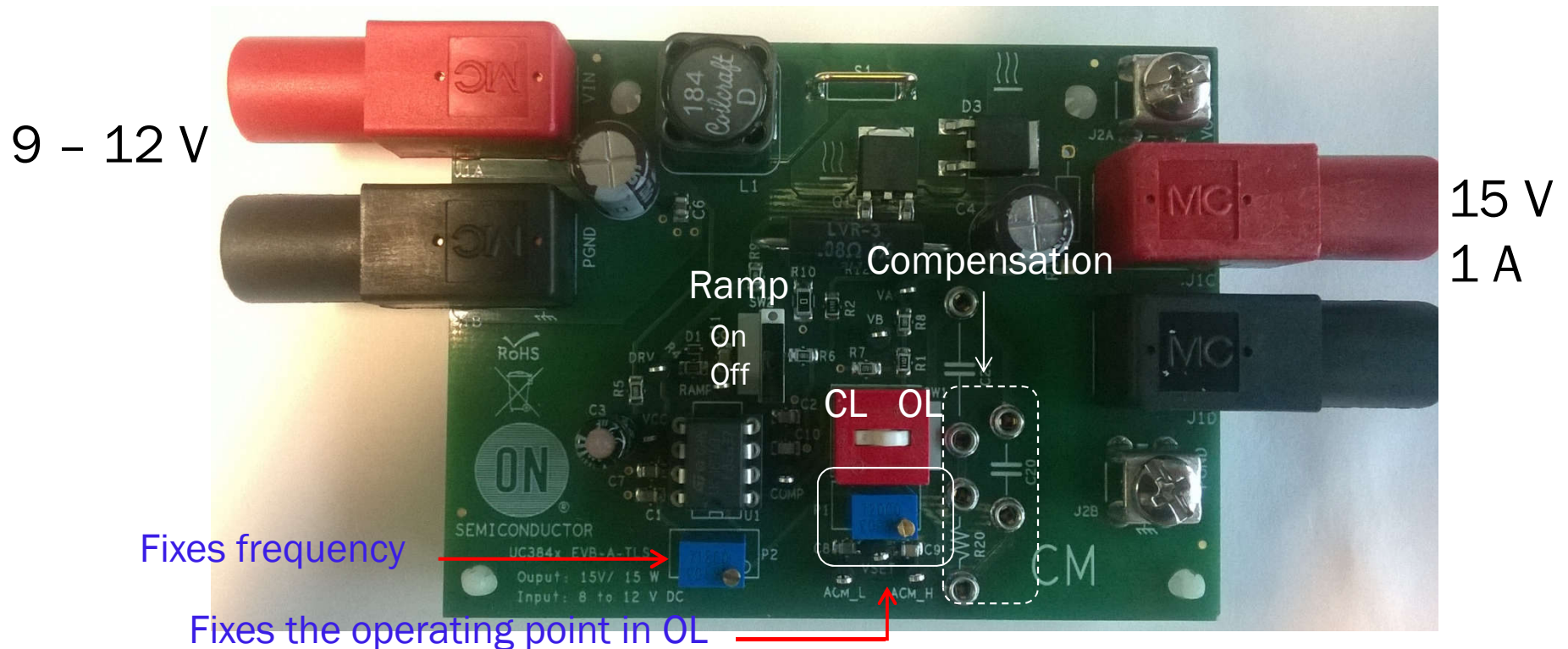
- ❑ The board includes switches to measure open and closed loops



- ❑ The compensation ramp can be turned on and off

Check the Amount of External Ramp

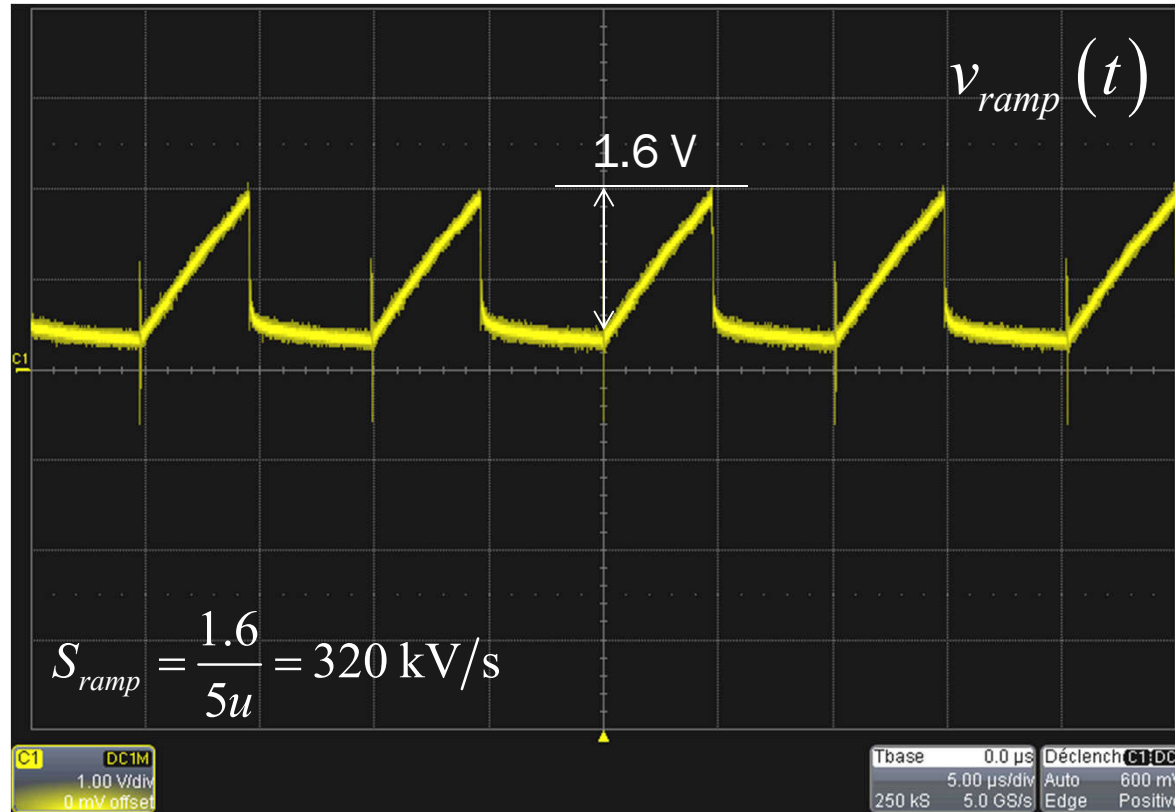
- The ramp level can be reflected in the SPICE model



- With 33 k Ω for R_{ramp} and 820 Ω for R_{CS} : $S_e = \frac{R_{CS}}{R_{ramp}} S_{ramp} \approx 8 \text{ kV/s}$


Use a Model which Includes Losses

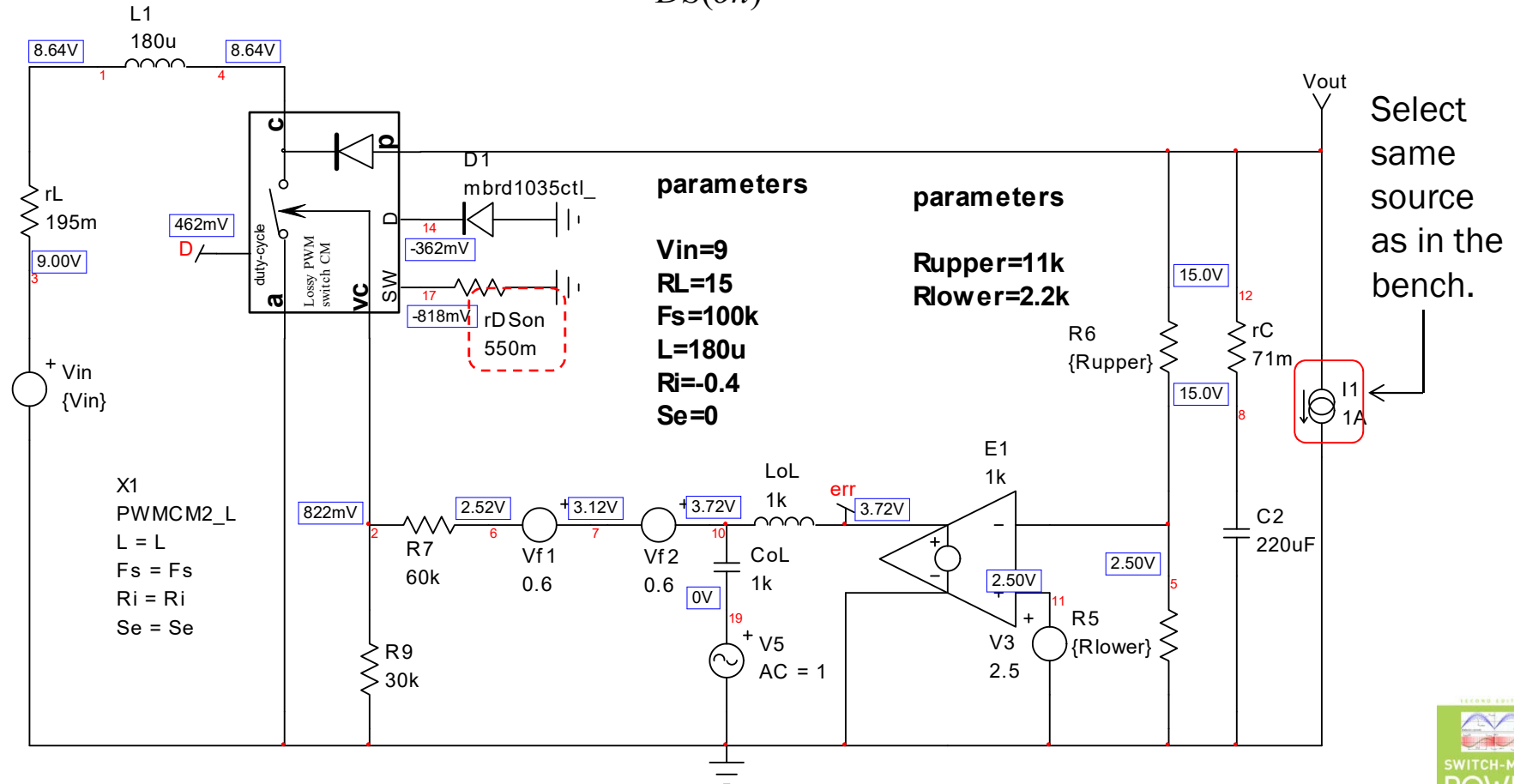- Characterize the MOSFET $r_{DS(on)}$ and all dc paths



- For a low V_{in} , use the lossy current mode model

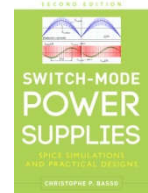C. Basso, Switch-Mode Power Supplies: SPICE Simulations and Practical Designs, 2nd ed., McGraw-Hill 2014



Watch for the Electronic Load



- The dc gain of the CM CCM boost converter depends on R

$$H_0 = \frac{R}{R_i} \frac{1}{2M + \frac{RT_{sw}}{LM^2} \left(\frac{1}{2} + \frac{S_e}{S_n} \right)} \quad R = 15 \Omega \quad \Rightarrow \quad \begin{array}{l} H_0 = 11 \text{ dB} \quad \text{with } S_e = 0 \text{ kV/s} \\ H_0 = 10.7 \text{ dB} \quad \text{with } S_e = 8 \text{ kV/s} \end{array}$$



- Make sure the load in SPICE matches the bench setup



Constant current

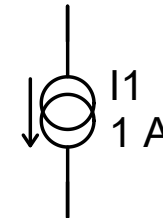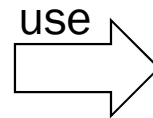


Constant resistance

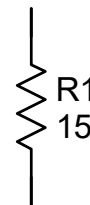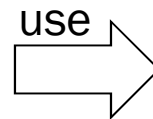

- ❖ H_0 is 14.5 dB with a 1-A source and 11 dB with a 15- Ω resistance

Extract the Power Stage Response

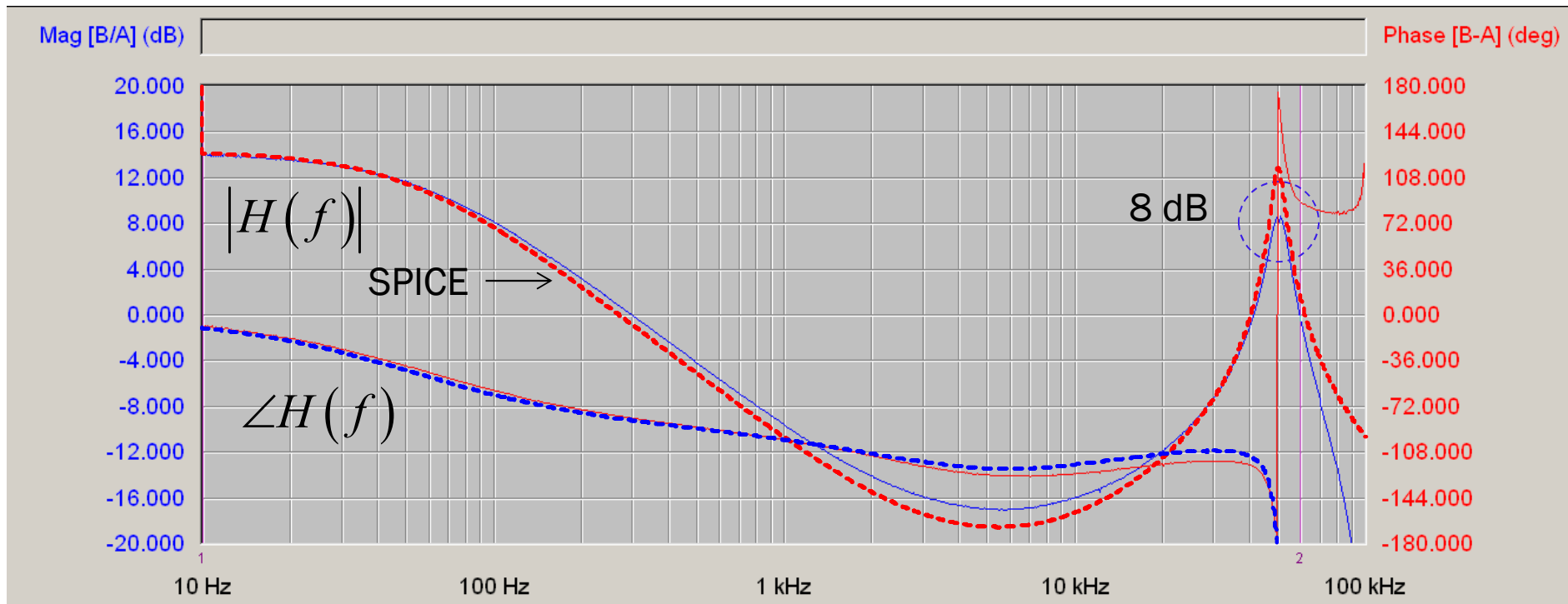
- The power stage shows peaking as expected at $F_{sw}/2$



- The measurement was carried with $V_{in} = 9\text{ V}$ and $I_{out} = 1\text{ A}$
- ❖ Load is in constant-current mode
- ❖ Watch modulation amplitude as you approach $F_{sw}/2$

Turn the Compensation Ramp On

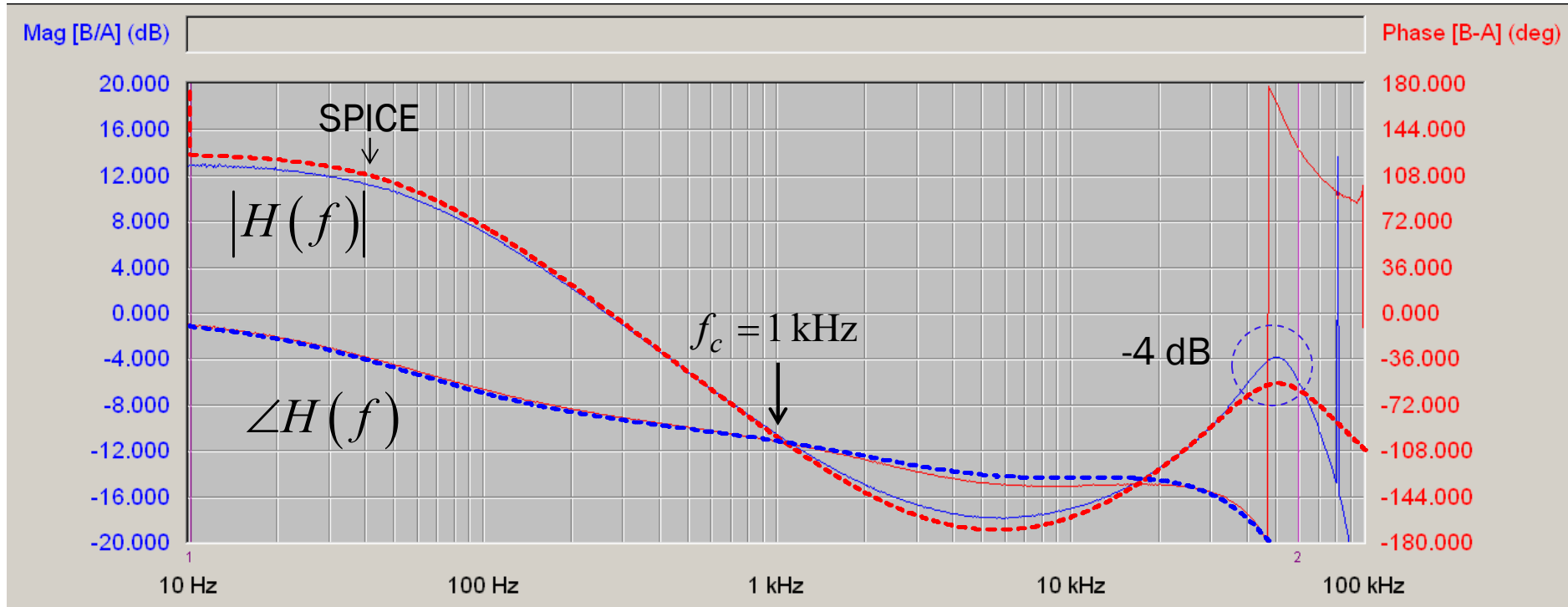- The power stage shows reduced peaking at $F_{sw}/2$



- Extract the data at the selected 1-kHz crossover frequency

$$|H(f_c)| = -11 \text{ dB} \quad \angle H(f_c) = -100^\circ$$

Use the Automated SPICE Sheet

□ Paste these data into the automated simulation sheet

parameters

Vref=2.5
 Vout=15
 Rupper=11k
 $I_b=(V_{out}-V_{ref})/R_{upper}$
 $R_{lower}=V_{ref}/I_b$



fc=1k
 Gfc=-11
 pfc=-100
 pm=70

boost=pm-(pfc)-90

$G=10^{-(G_{fc}/20)}$
 $\pi=3.14159$

$G=10^{-(G_{fc}/20)}$
 boost=pm-(pfc)-90
 $\pi=3.14159$
 $K=\tan((\text{boost}/2+45)*\pi/180)$
 $C_2=1/(2*\pi*fc*G*k*R_{upper})$
 $C_1=C_2*(K^2-1)$
 $R_2=k/(2*\pi*fc*C_1)$

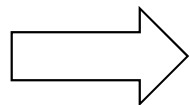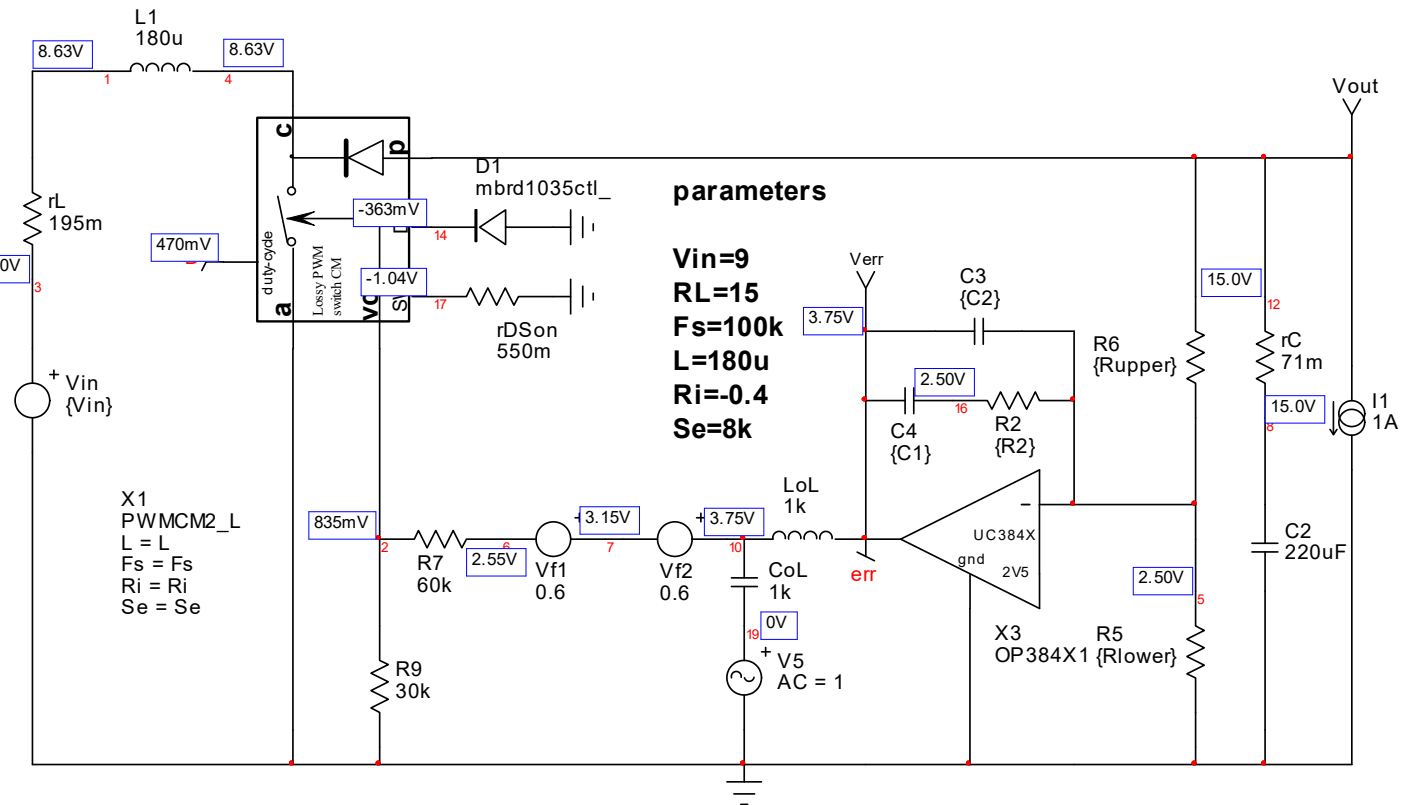$f_{p1}=1/(2*\pi*R_2*C_2)$
 $f_{z1}=1/(2*\pi*R_2*C_1)$




$$C_1 = 47 \text{ nF} - C_2 = 360 \text{ pF} - R_2 = 39 \text{ k}\Omega$$



Verify Loop Gain with the Analyzer

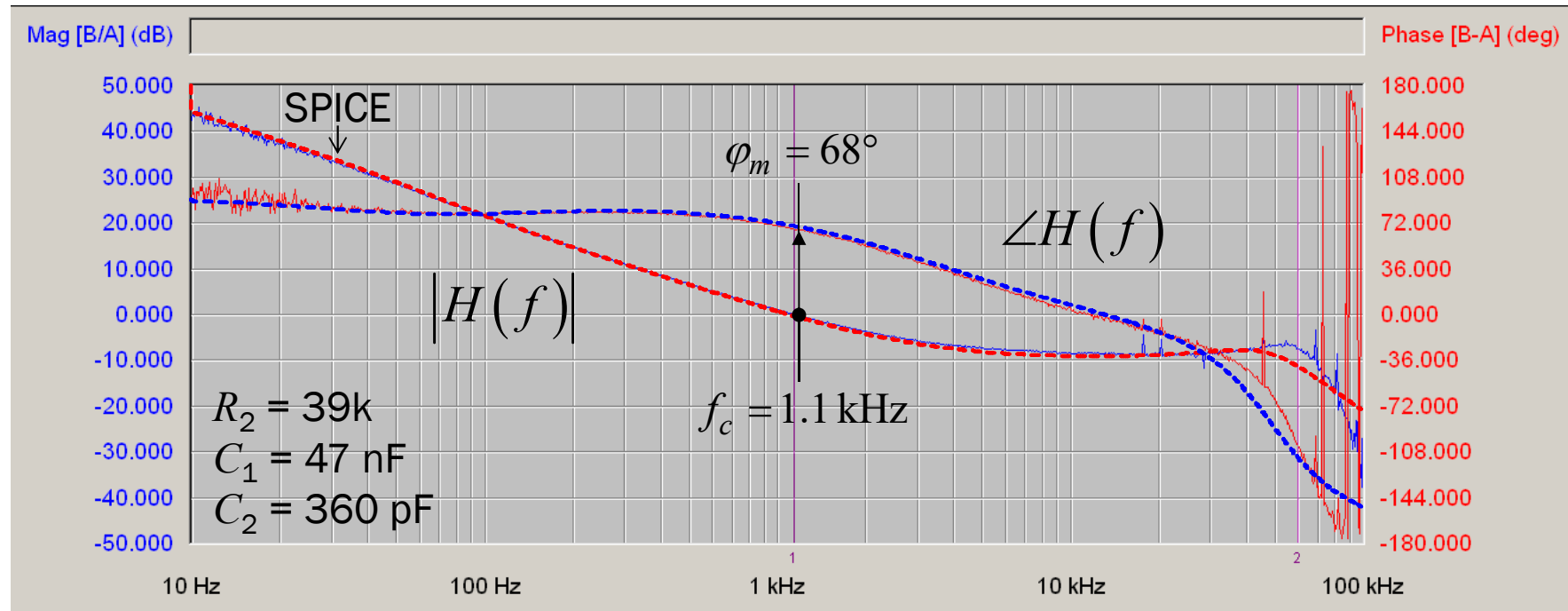
- The loop gain measurement agrees with the simulation



- The phase margin is 68° while crossover is 1.1 kHz
- ❖ The model is accurate and can be used for further analyses

Reduced Phase Margin for Experiments

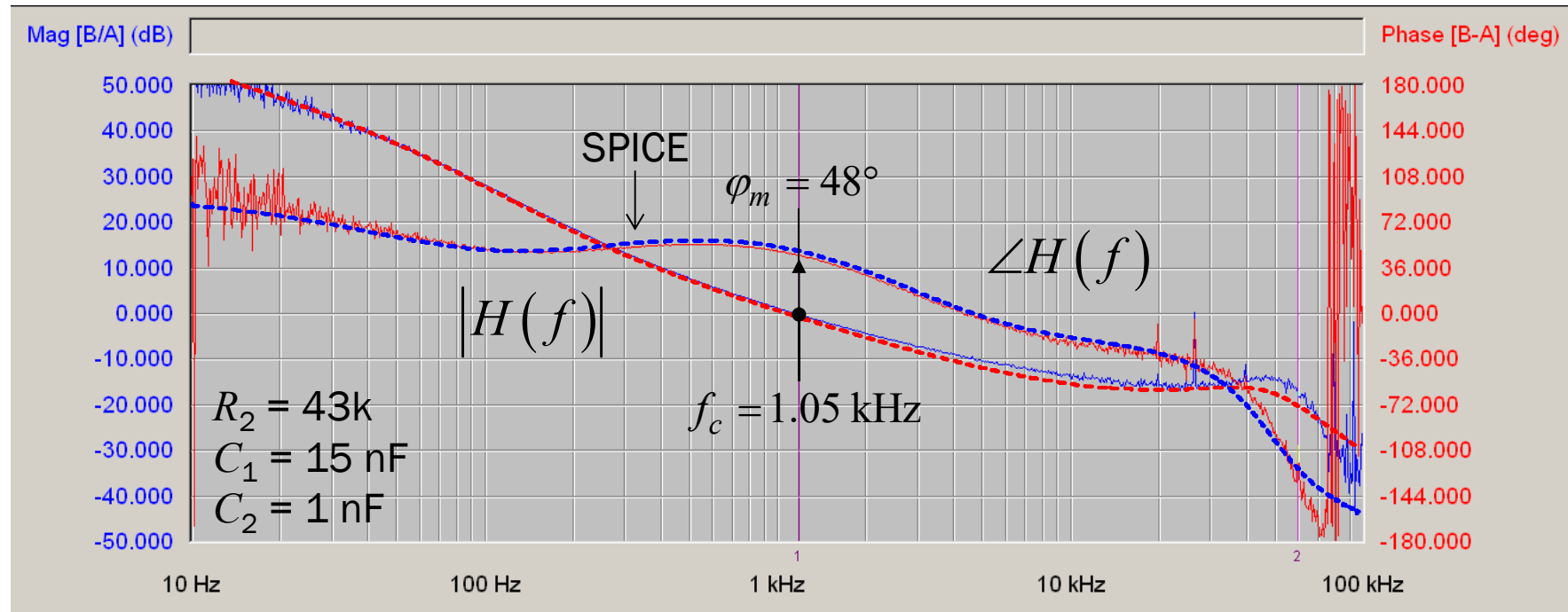
- A different compensation strategy, reducing the phase margin



- Phase margin is purposely reduced to 48° while f_c is constant

Comparing the two Responses


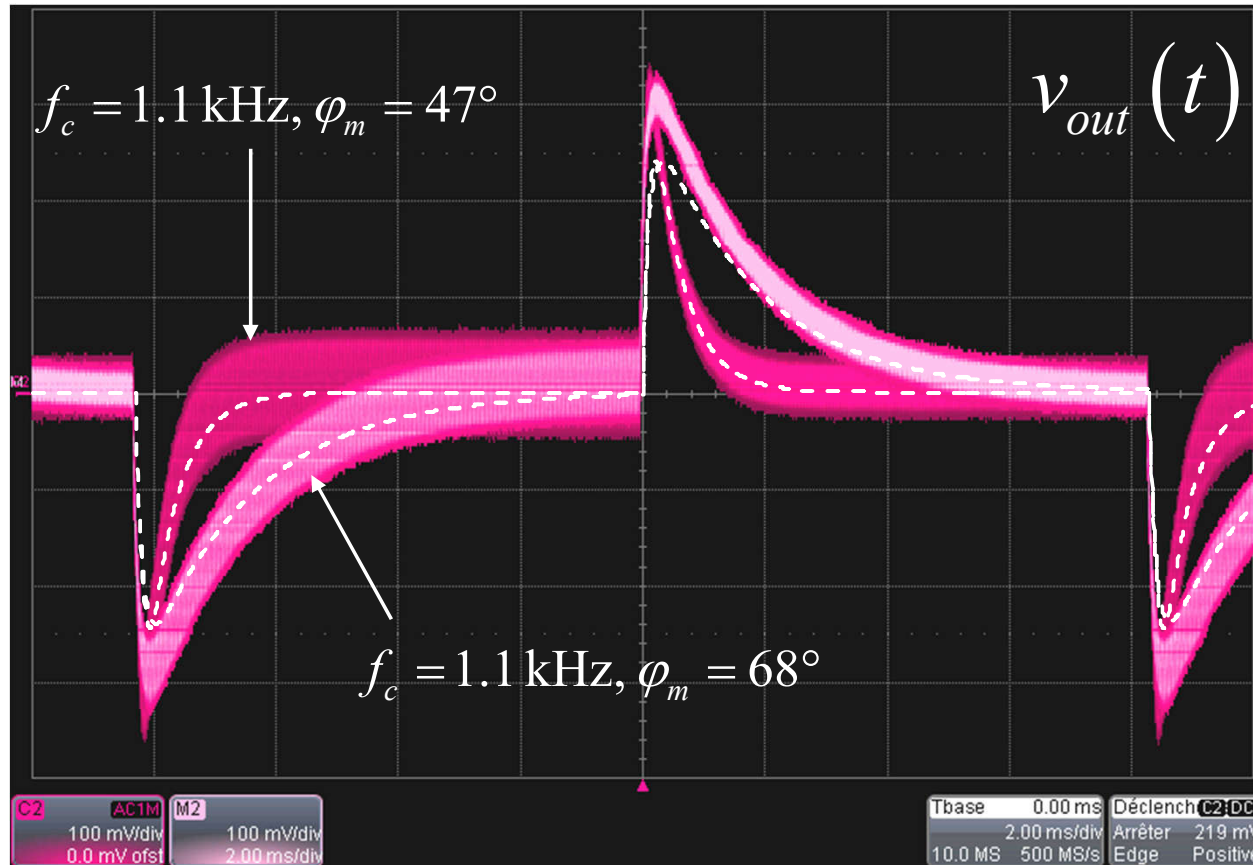
- The higher phase margin slows the recovery as expected



- Simulation in dash agrees quite well with bench results

Transient Response and Ext. Ramp

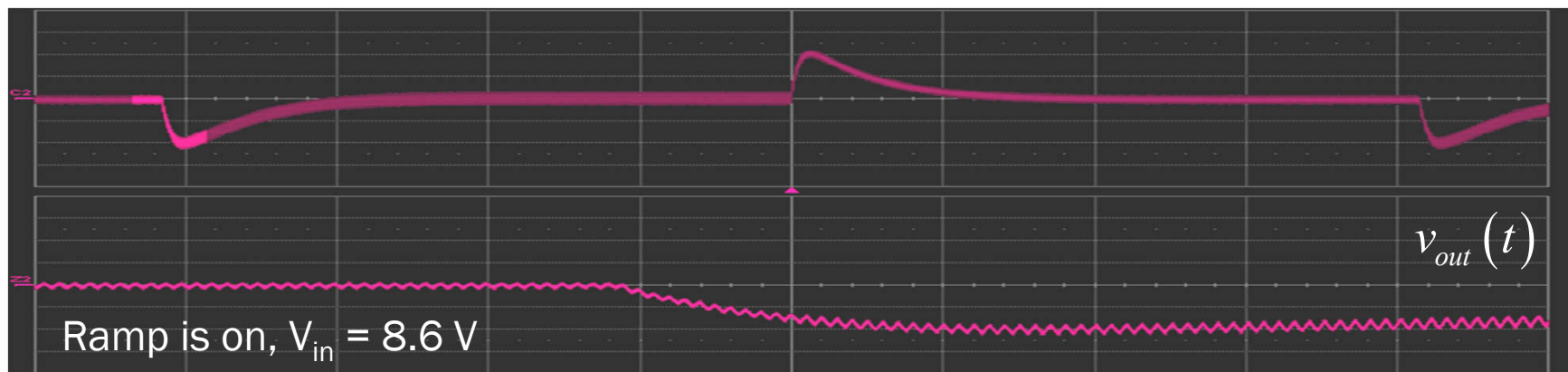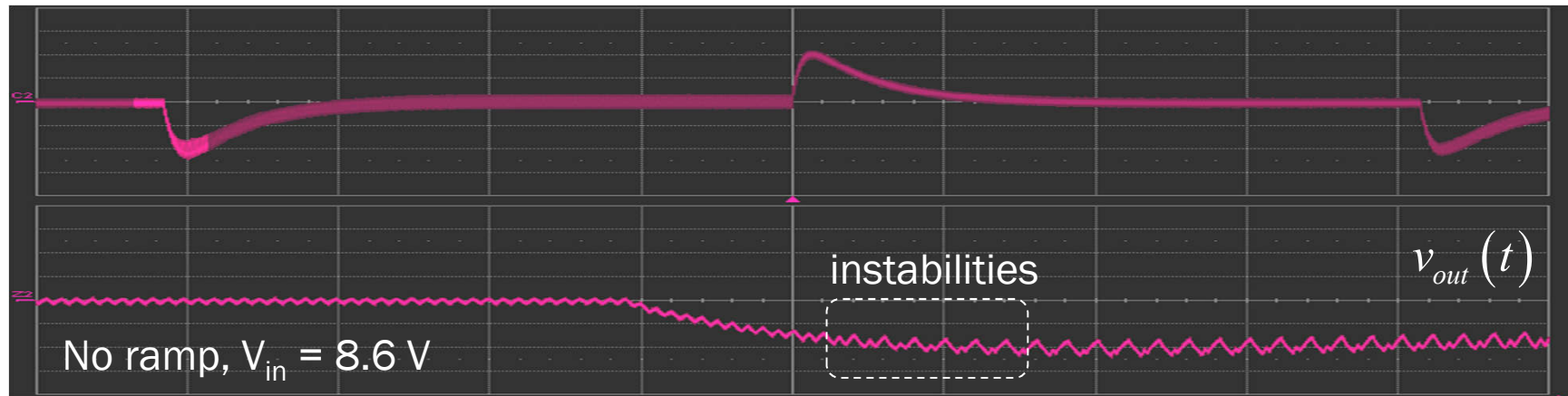
- Added compensation ramp brings stability at the lowest input



Closed loop, 0.5 A to 1 A in 1 $\mu\text{s}/\text{A}$

Comparing VM versus CM

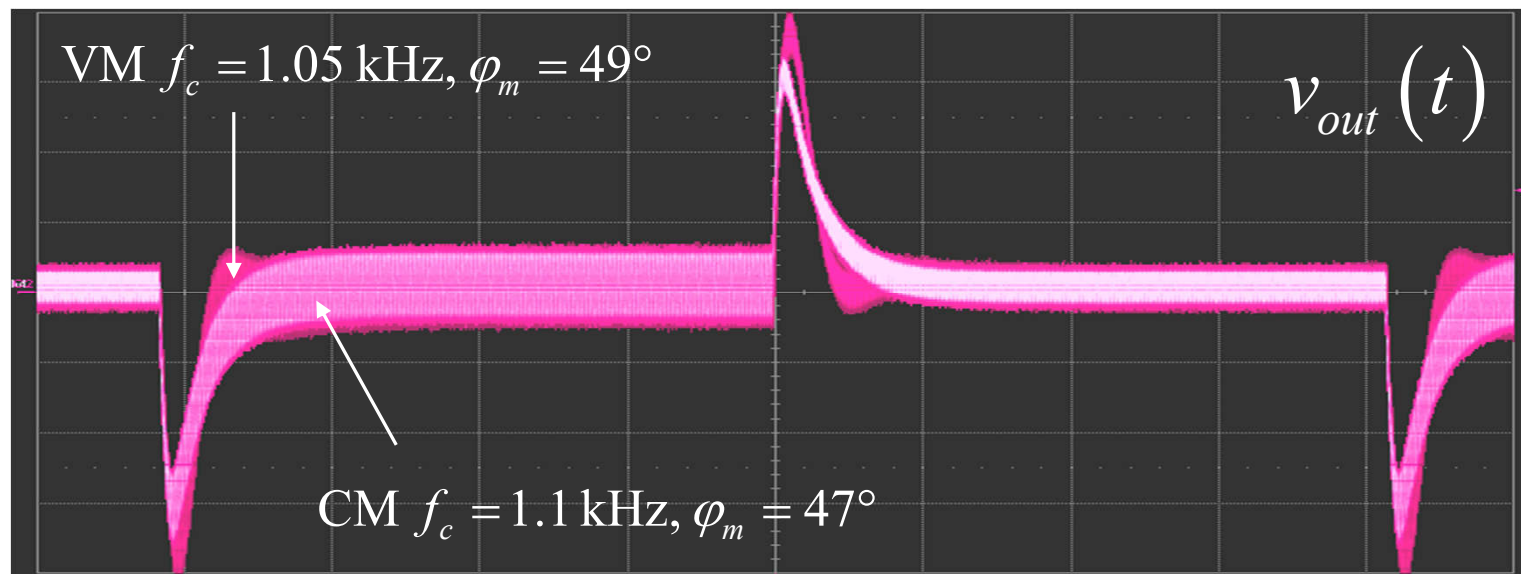- This board was purposely designed for a deep CCM operation
- ❖ In VM, the crossover is too close to the resonant frequency
- ❖ The gain is limited at f_0 and LC dominates the response



- Design rules would ask to lower L : RHPZ goes away from f_c
- Increase the distance between f_0 and crossover
- ❖ Make output capacitor bigger to reduce resonant frequency

Conclusion

- ❑ Several blocks shape the converter ac response
- ❑ The power stage dynamic response is what you need first
- ❑ You have four ways to obtain it:
 - ❖ Use small-signal analysis
 - ❖ Build an average model and simulate it
 - ❖ Simulate cycle by cycle with a PWL engine
 - ❖ Build a hardware prototype and measure
- ❑ The best is to combine these approaches together:
 - ❖ Analytical analysis gets you the insight on who does what?
 - ❖ Simulation lets you explore various compensation strategies
 - ❖ Hardware measurements confirms you did a good job!



Merci !
Thank you!
Xiè-xie!

